

MMIC Design and Technology

Passive Elements 2


Instructor Dr. Ali Medi

Topics

- Inductance Calculations
- Lumped Element Lines
- Impedance Matching

Inductance


$$L = \frac{1}{I} \iint B \cdot dS$$

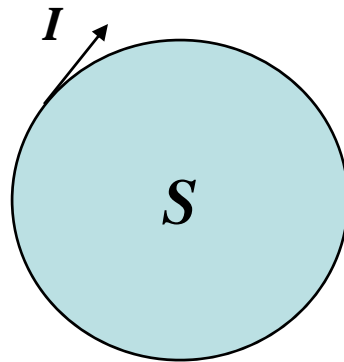


Single Loop

$$L = \mu R \left[\ln \left(\frac{R}{w+t} \right) + 0.078 \right] K_g$$
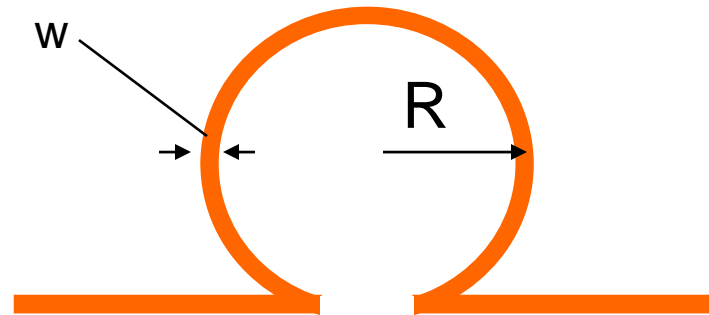
$$K_g = 0.57 - 0.145 \ln \left(\frac{w}{h} \right)$$




Inductance of Single Loop

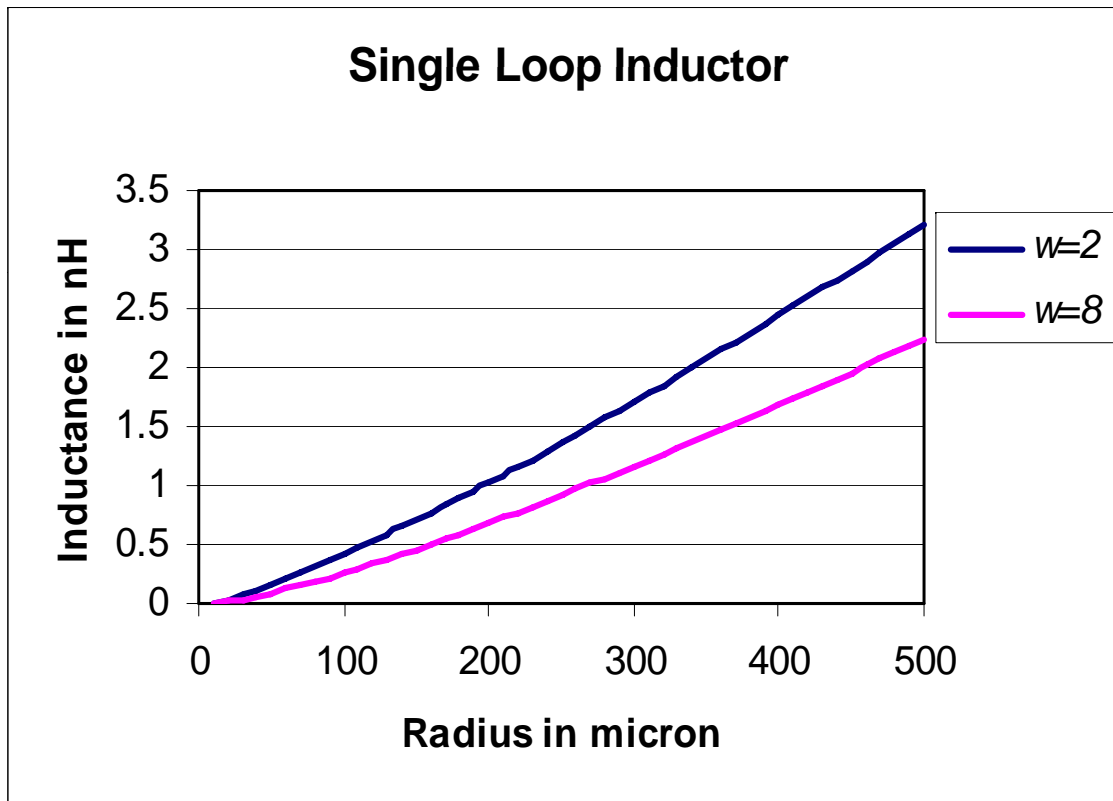

$h=0.1\text{mm}$

Spiral Inductor

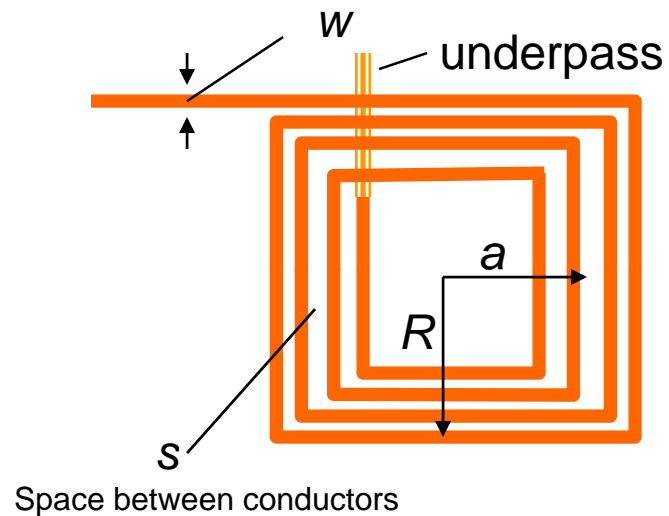


Square Spiral Inductor
Overall radius R
Mean radius a
Number of turns N
Conductor width w
Substrate thickness h
Conductor thickness t

Zero order estimate $L_{est} = \mu N^2 R$


$L = 3 \text{ nH}$ for $N=4$ and $R=.15\text{mm}$

Inductance of Spiral

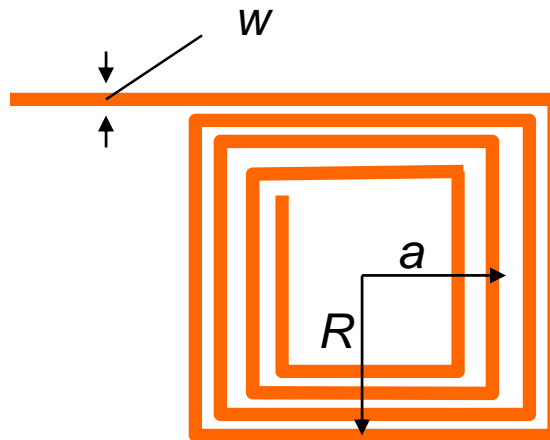- Positive inductance produced by mutual inductance of windings with current flowing in same direction
 - Minimize spacing to produce large inductance
- Windings with current flowing in opposite directions have negative mutual inductance and reduce total inductance
 - Increase open space in center to reduce negative mutual inductance



Calculation

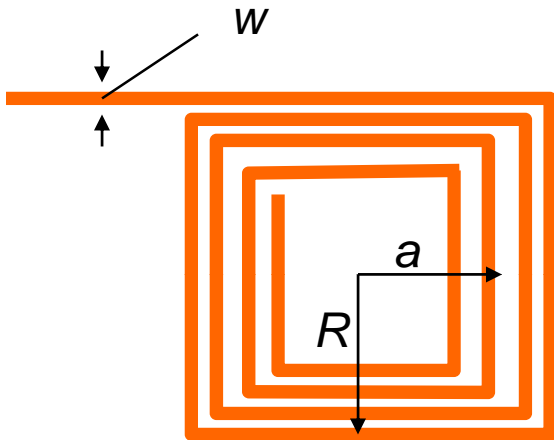

Detailed calculations of spiral inductors is found at:

H.M. Greenhouse, "Design of Planar Rectangular Microelectronic Inductor," IEEE Transactions on Parts, Hybrids, and Packaging, VPHP-10, no.2, June, 1974, pp 101-9.

$$L = \frac{37.5 \mu N^2 a^2}{22R + 14a}$$

Here is an approximation


Estimate good to about 5%

Inductance of Spiral

$$L = \frac{37.5 \mu N^2 a^2}{22R + 14a} K_g$$

$$K_g = 0.57 - 0.145 \ln\left(\frac{w}{h}\right)$$

Account for ground plane

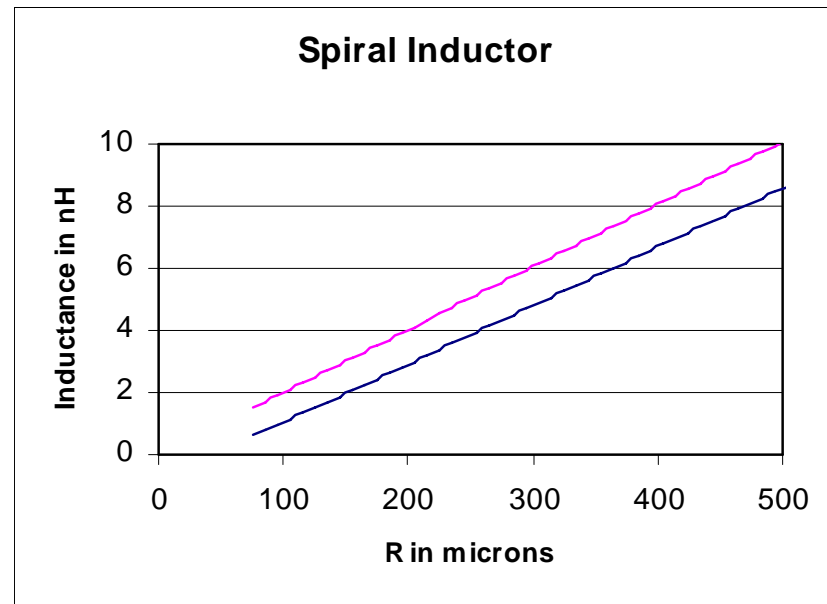


$N=4$, $w=10\mu\text{m}$


$H=100\mu\text{m}$

$s=10\mu\text{m}$

Layout Guidelines

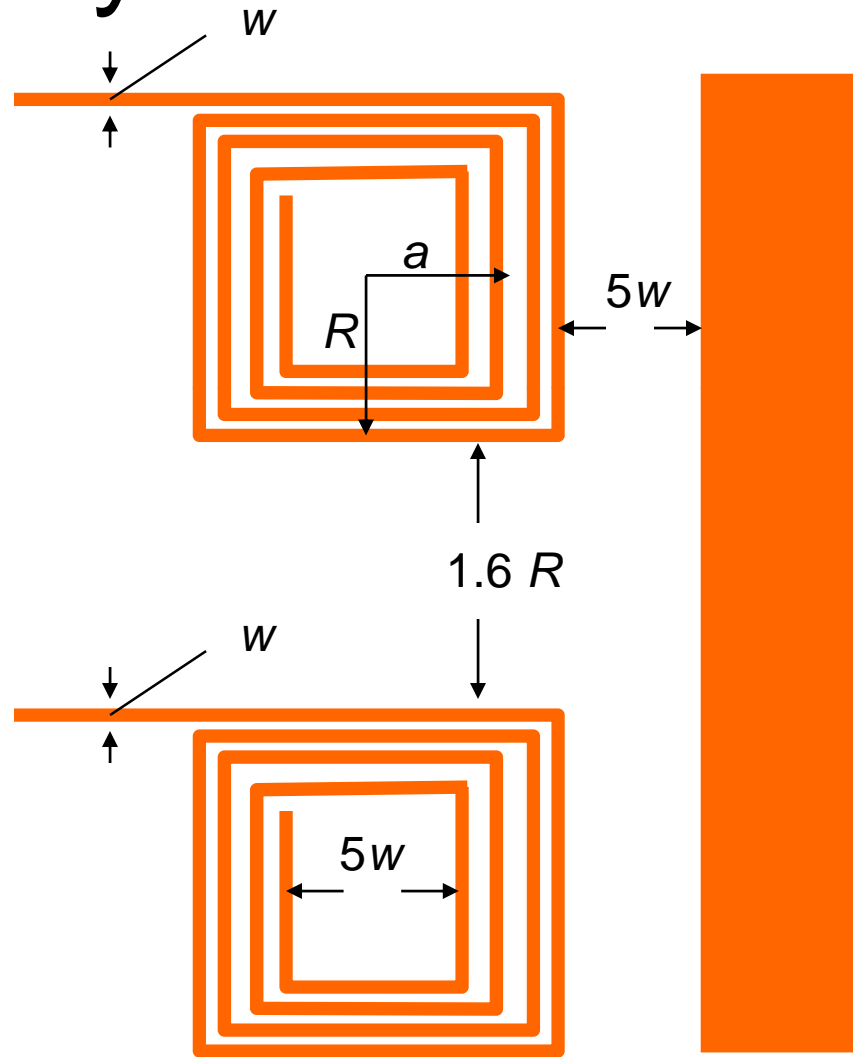

Spiral Inductor Equivalent Circuit

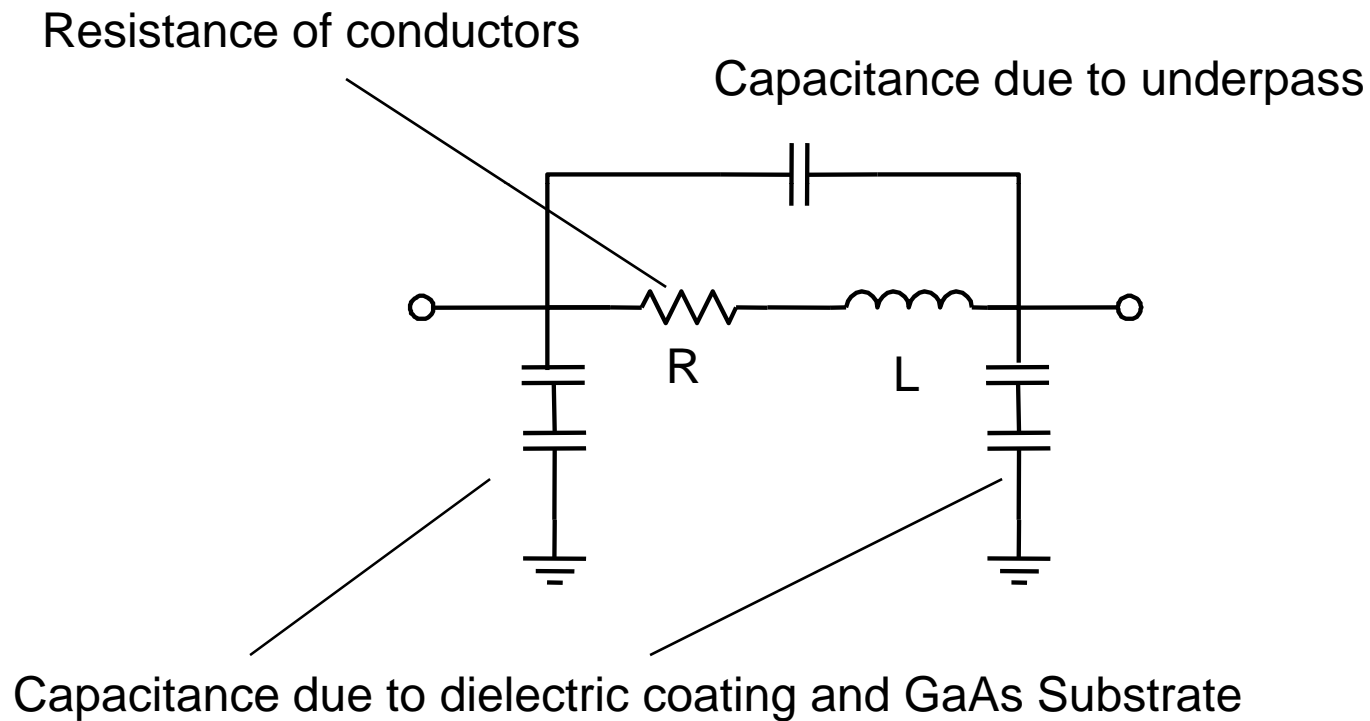

Best Practices

- Use top layer metal (thickest)
 - lowest resistive losses
- Minimize space between windings s
 - *Largest coupling between windings*
- Keep center open
 - Inner turns contribute little to L but still add to R and C


Lumped Element Transmission Lines

Replaces a $\frac{1}{4}$ wave length line with characteristic impedance Z_0


When:

$$L = \frac{Z_0}{2\pi f}$$

$$C = \frac{1}{2\pi f Z_0}$$

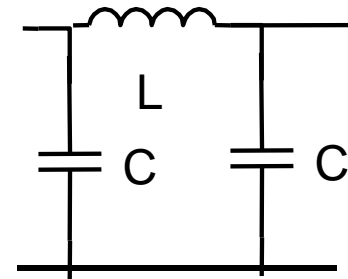

Lumped – Distributed Transmission Line

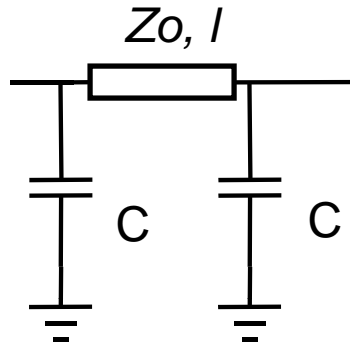

Replaces a $\frac{1}{4}$ wavelength line of $Z_{\lambda/4}$


With a reduced line length = l

And impedance Z_0

$$Z_0 = \frac{Z_{\lambda/4}}{\sin\left(\frac{2\pi l}{\lambda}\right)}$$

$$C = \frac{\cos\left(\frac{2\pi l}{\lambda}\right)}{2\pi f Z_{\lambda/4}}$$

Impedance Matching

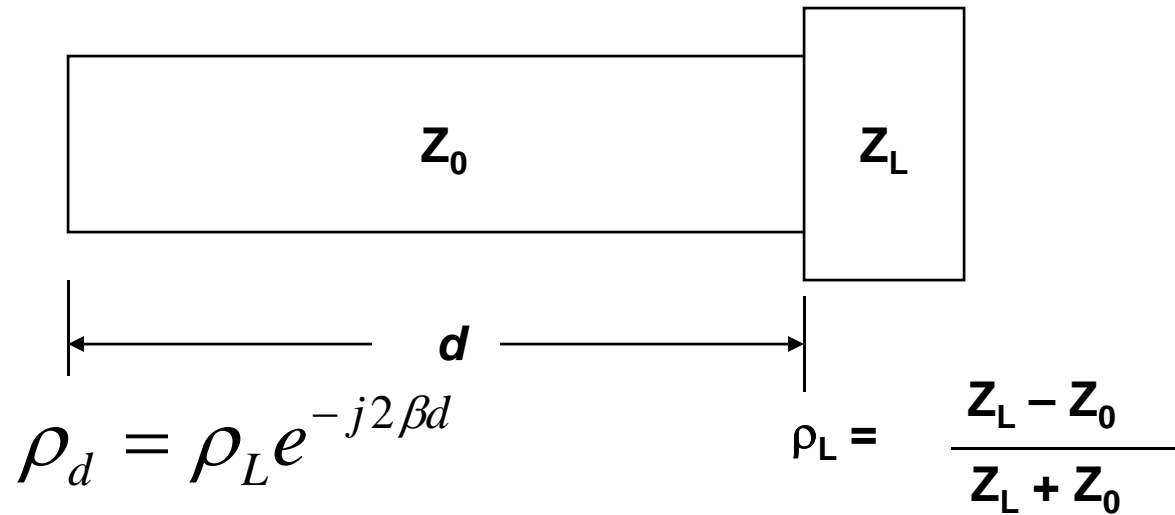

For lossless line $\beta = \frac{2\pi}{\lambda_g}$

$$Z_{in}(d) = Z_0 \left[\frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)} \right]$$

Special Cases

$$Z_{in}(d) = Z_0 \left[\frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)} \right]$$

$$d = \frac{\lambda_g}{4}$$

$$\tan(\beta d) = \tan\left(\frac{\pi}{2}\right) = \infty$$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

$$d = \frac{\lambda_g}{2}$$

$$\tan(\beta d) = \tan(\pi) = 0$$

$$Z_{in} = Z_L$$

Examples

- Match 50Ω source to 100Ω load
 - Design in micro-strip at 10GHz
 - What is the length
 - Design in lumped line at 10GHz
 - What are the values of L and C
 - What are the physical dimensions of L and C
 - Design in distributed-lumped line at 10GHz
 - What is the reduced line length and impedance
 - What is the value of C
 - What are the physical dimensions