






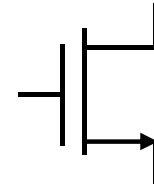
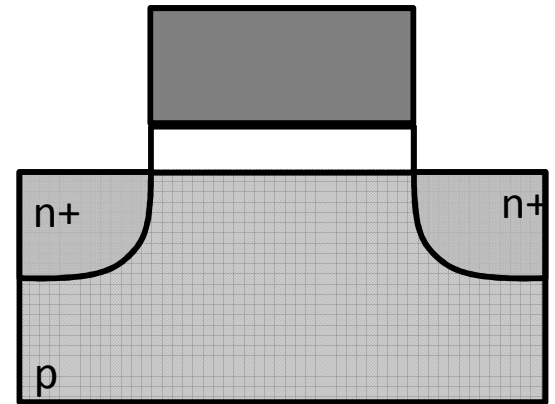
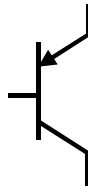
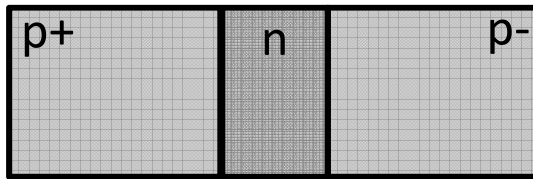
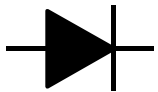
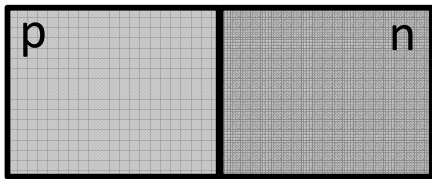
Session 0:
Principles of Electronics
Review of Solid State Devices

From Atom to Transistor






Objective


1. 
2. 
3. 
4. 
5. 

To Understand: how “Diodes,” and “Transistors” operate!



21 Century Alchemy!

1. 
2. 
3. 
4. 
5. 

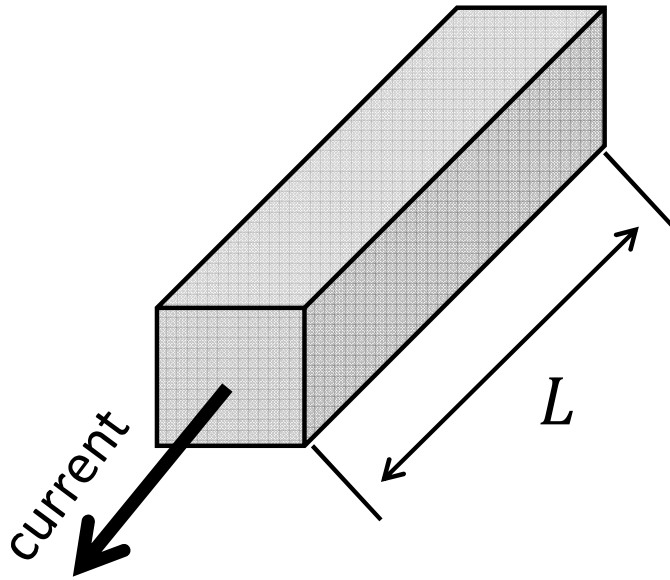

Ohm's law






$$R = \frac{V}{I} \rightarrow \rho = R \frac{A}{L} \quad \text{resistivity}$$


Resistivity is characteristic of the material

Art of VLSI design is:
to put together materials with different resistivity's next to each other to perform a certain task.



Periodic Table of Elements

1. 
2. 
3. 
4. 
5. 

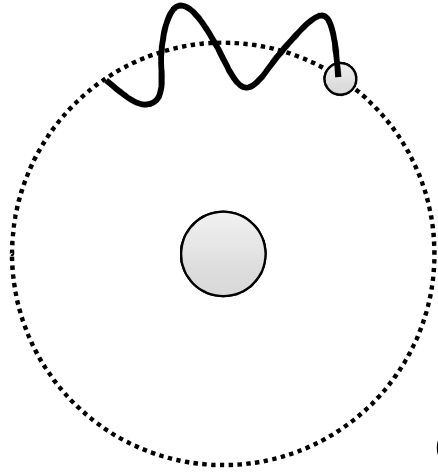

Bohr Atomic Model


wave-particle duality

$$\lambda = h/p$$

$$mvr = n\hbar$$

de Broglie standing wave



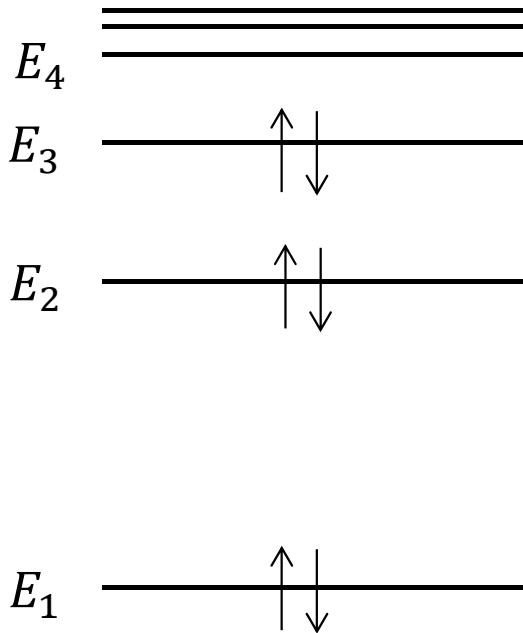


Energy Bands:





Abbreviated Periodic Table

II	III	IV	V	VI
4 Be	5 B	6 C	7 N	8 O
12 Mg	13 Al	14 Si	15 P	16 S
30 Zn	31 Ga	32 Ge	33 As	34 Se
48 Cd	49 In	50 Sn	51 Sb	52 Te
80 Hg	81 Tl	82 Pb	83 Bi	84 Po



Bohr Atomic Model

1. 
2. 
3. 
4. 
5. 



Single atom:

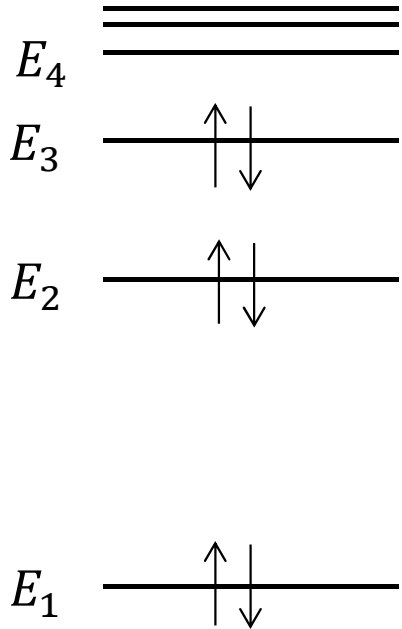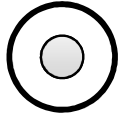

2 atoms:

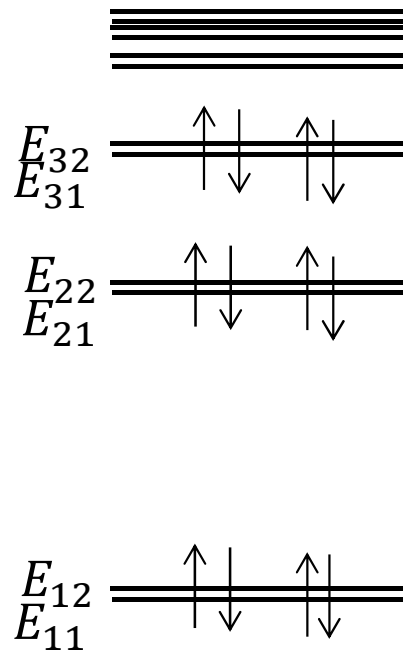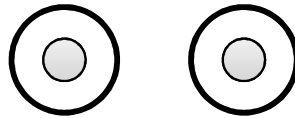



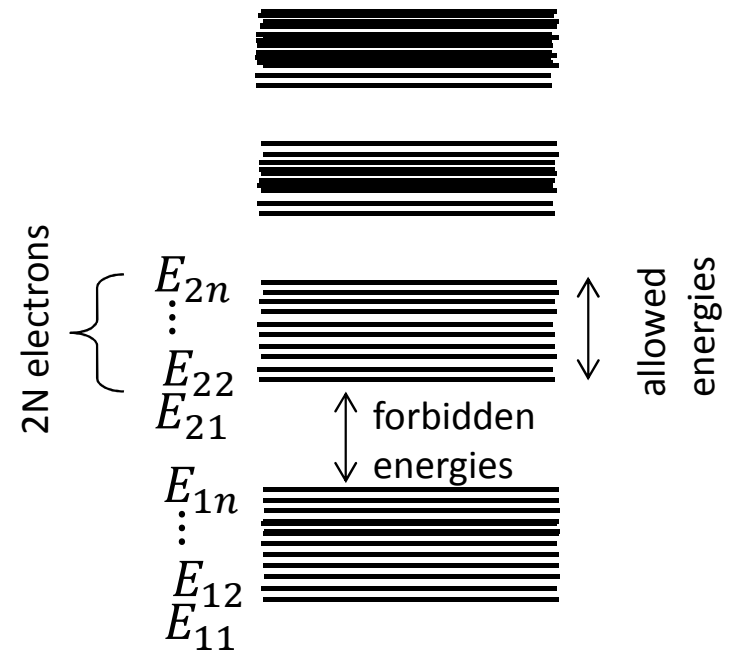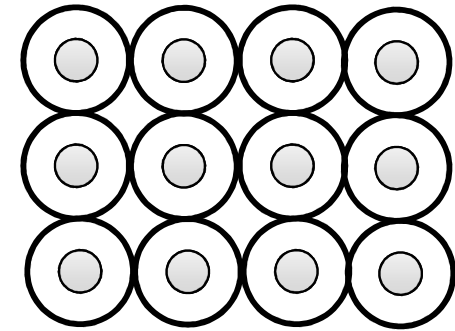


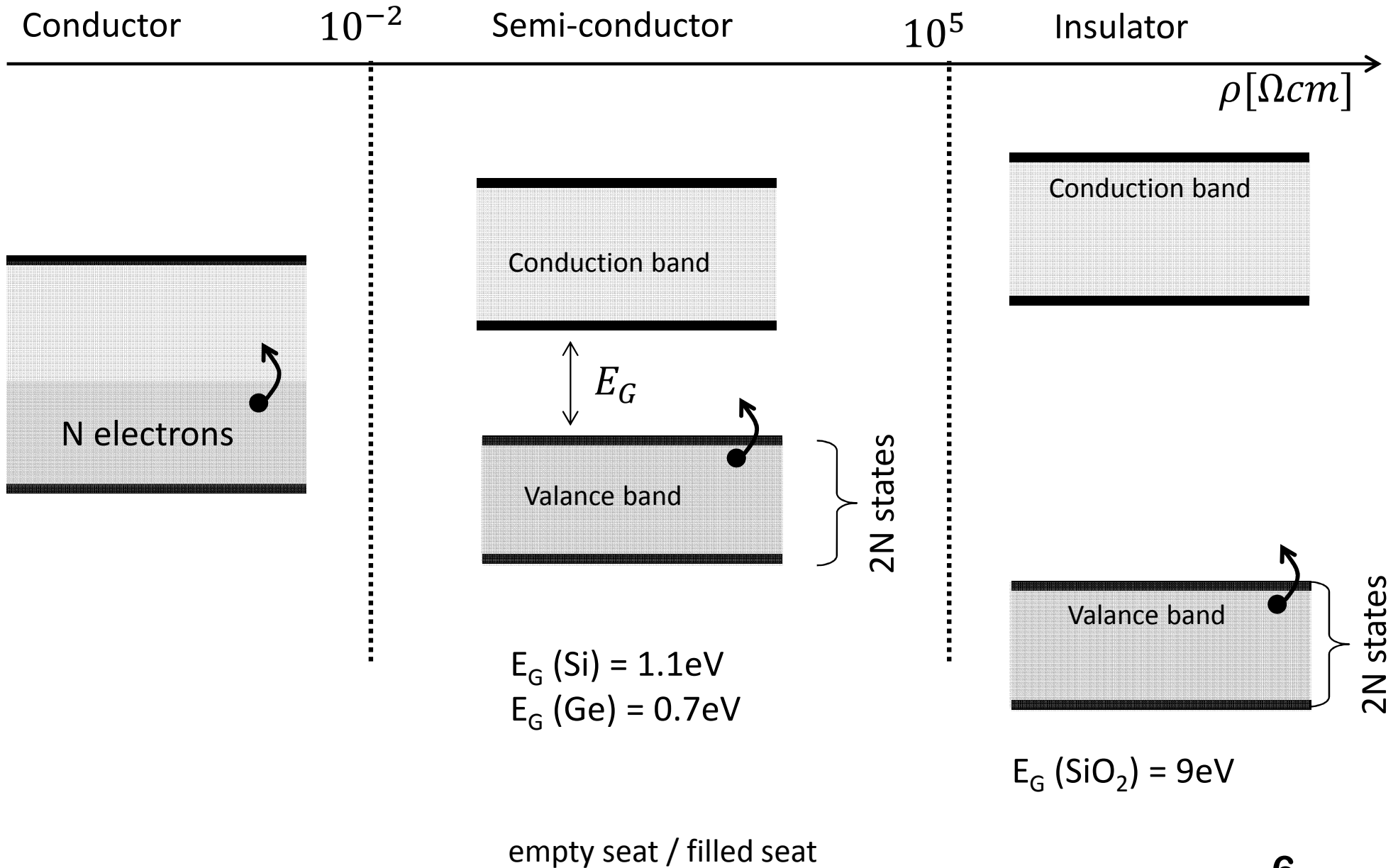
N atoms:








Pauli exclusion principle


Materials

1. 
2. 
3. 
4. 
5. 





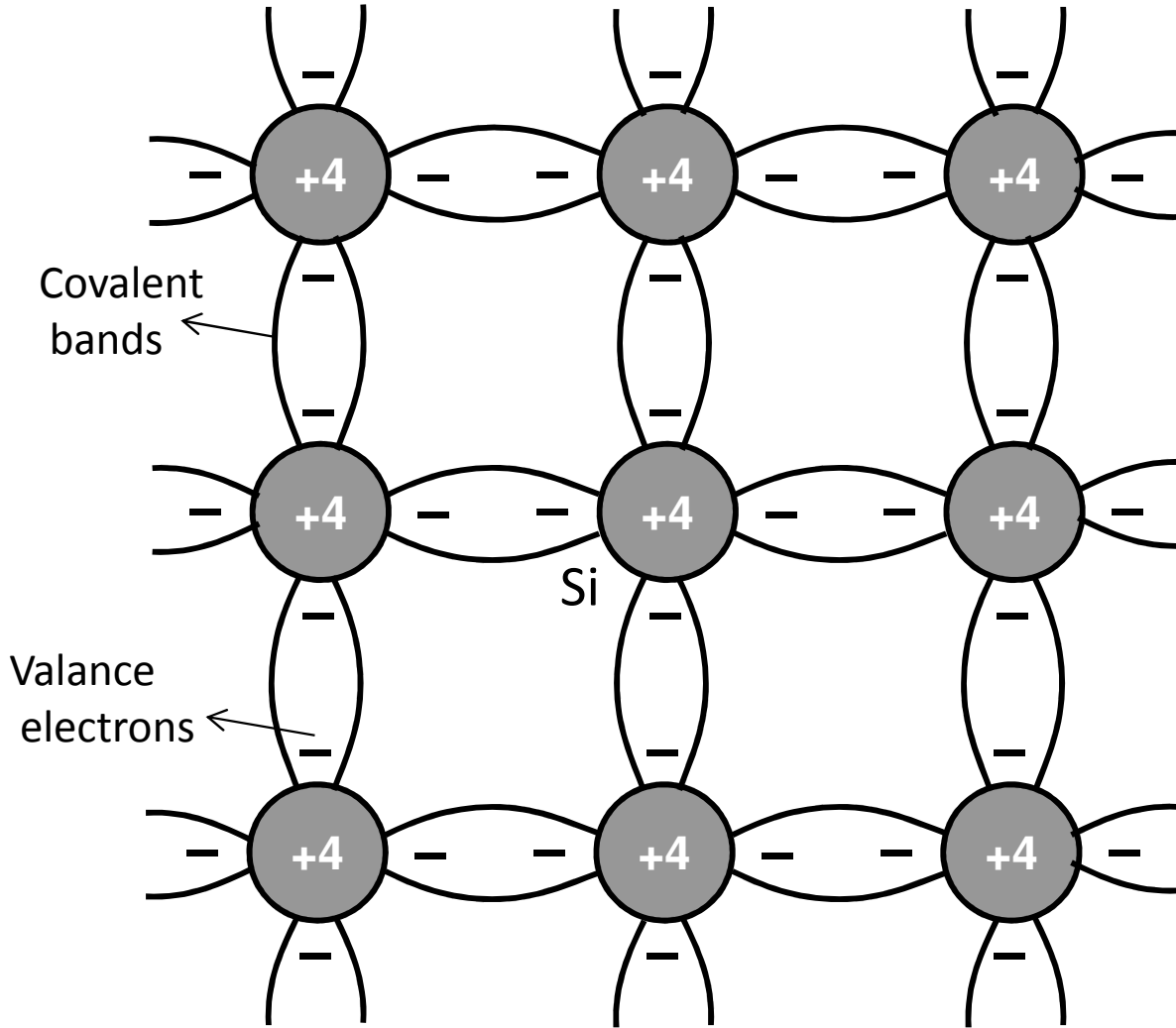


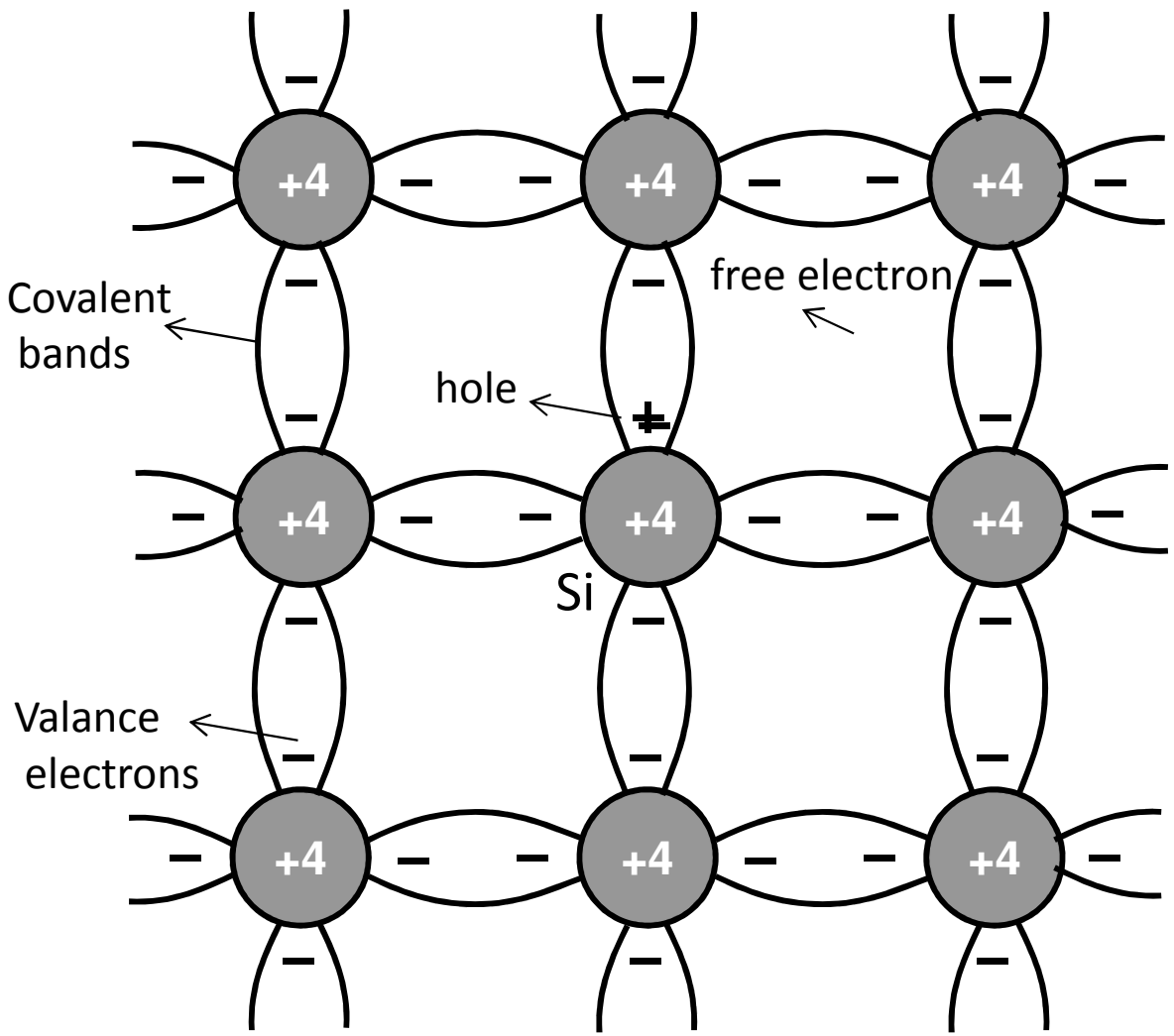
Intrinsic Semiconductor

1. 
2. 
3. 
4. 
5. 



Intrinsic Semiconductor

- 1. 
- 2. 
- 3. 
- 4. 
- 5. 



n_0 electron density






p_0 hole density


$$n_0 = p_0 = n_i$$

 useless!!

$$n_i \Big|_{T=300K} = 10^{10} \text{ cm}^{-3} \ll n(\text{Si}) = 2 \times 10^{23} \text{ cm}^{-3}$$

n-type Semiconductor

1. 
2. 
3. 
4. 
5. 

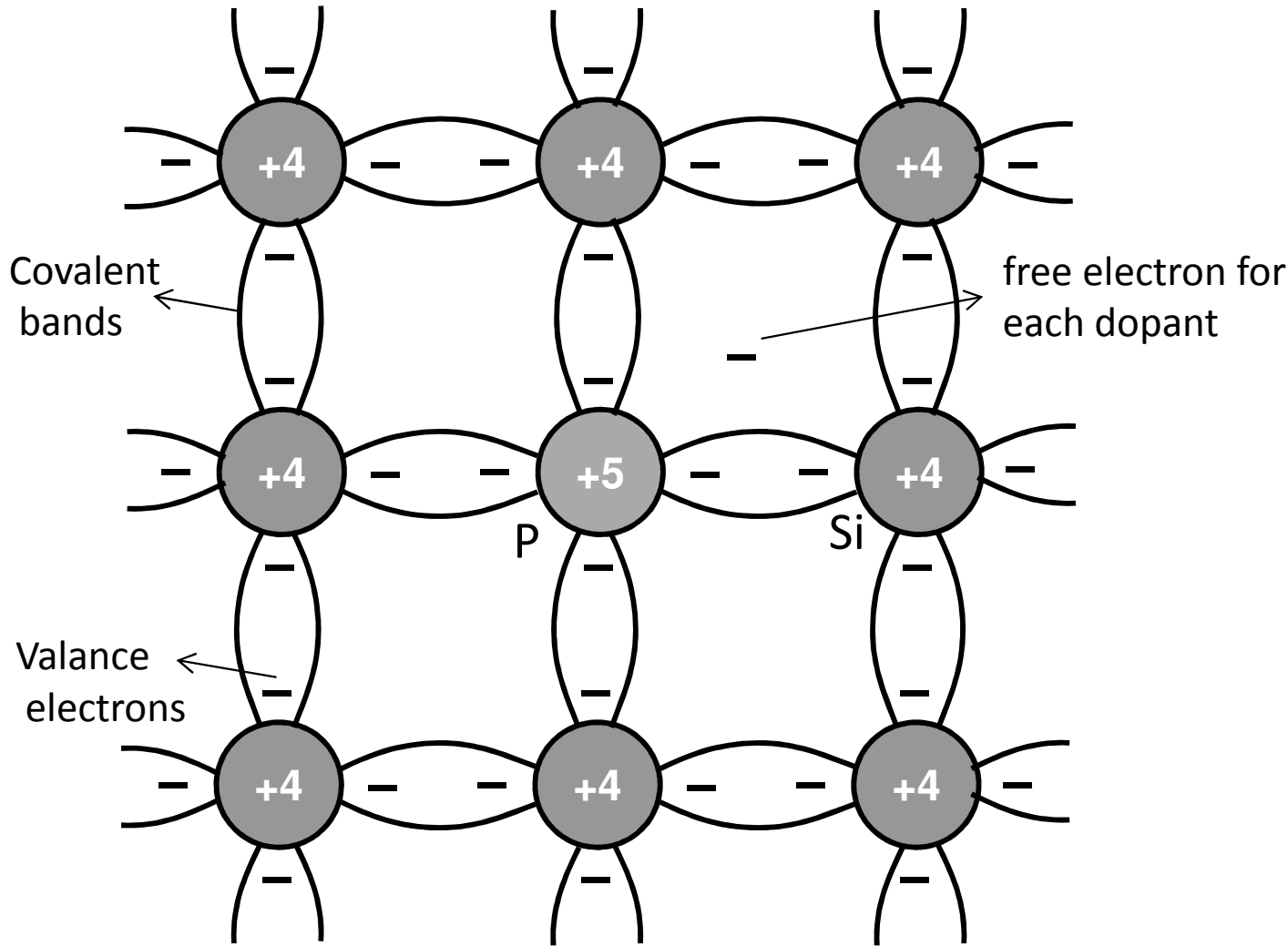

Donor: P , As , Sb

n_0 electron density

p_0 hole density

$$n_0 = N_D$$


$$n_0 p_0 = n_i^2$$

N_D up to 10^{19} cm^{-3}

☺ $n(\text{Si}) = 2 \times 10^{23} \text{ cm}^{-3}$

p-type Semiconductor

- 1.
- 2.
- 3.
- 4.
- 5.

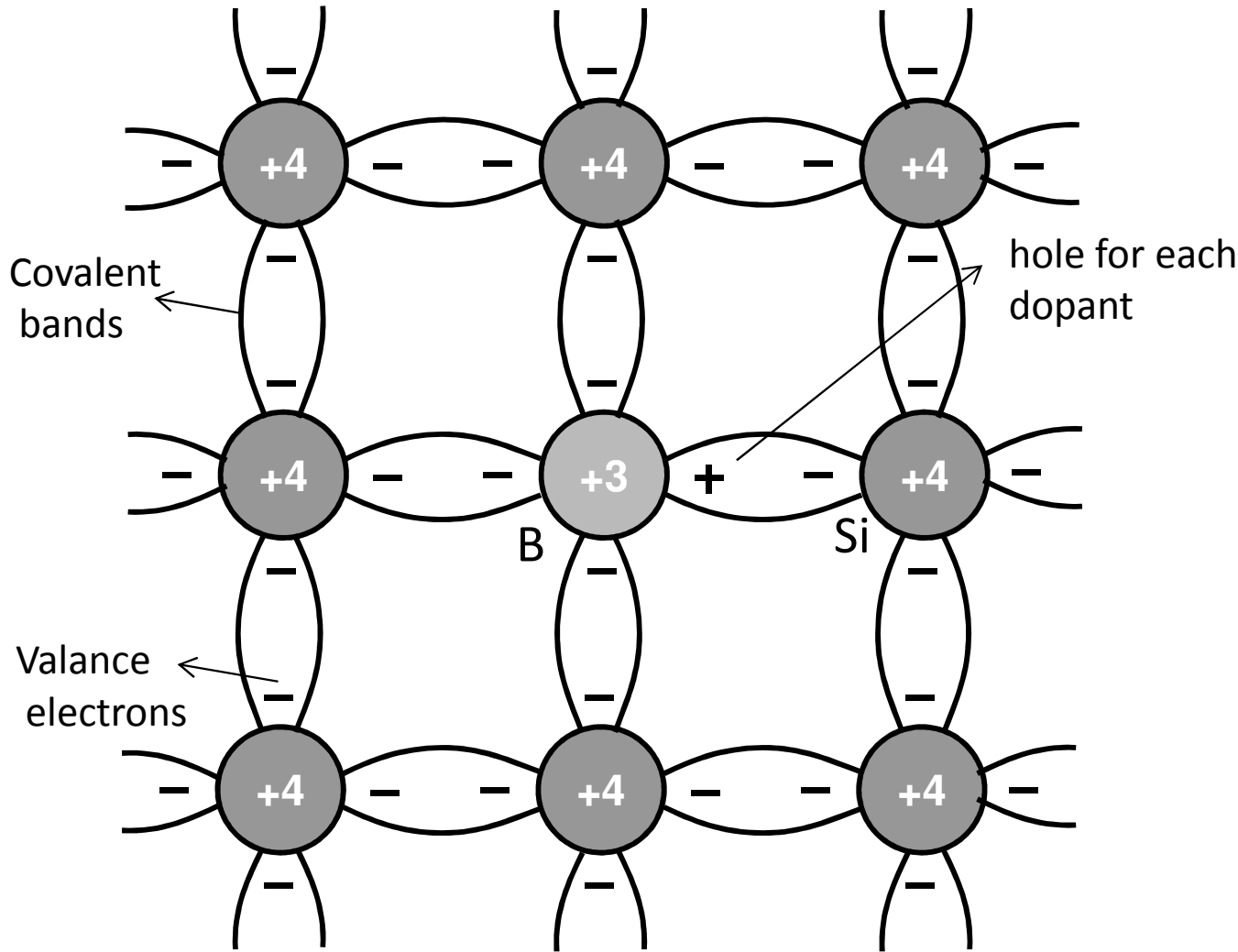

Acceptor: B , Ga , In

n_0 electron density

p_0 hole density






$$n_0 = N_A$$


$$n_0 p_0 = n_i^2$$

$$N_A \text{ up to } 10^{19} \text{ cm}^{-3}$$






$$\text{☺ } n(\text{Si}) = 2 \times 10^{23} \text{ cm}^{-3}$$

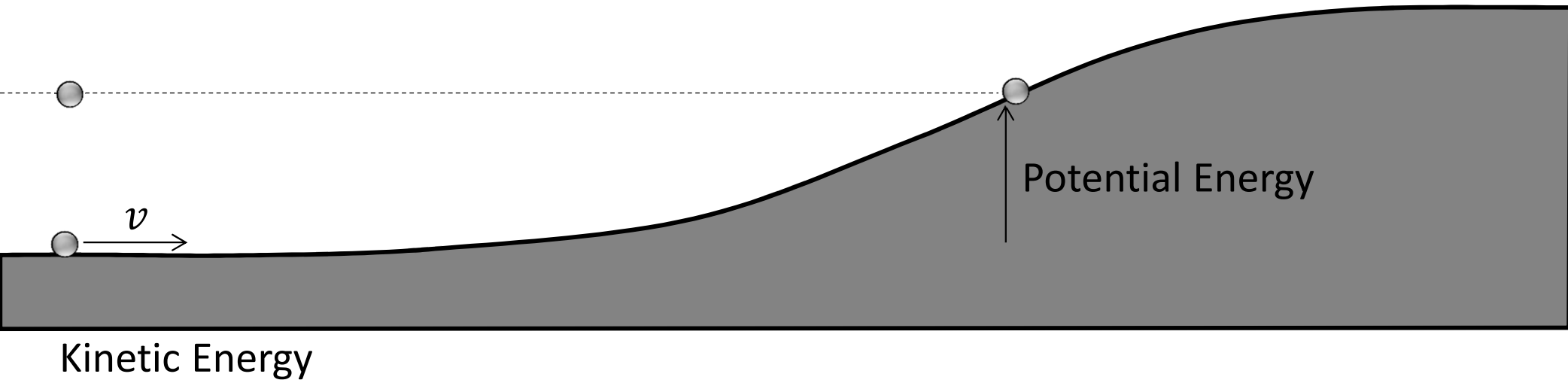
Energy Diagrams

1. 
2. 
3. 
4. 
5. 





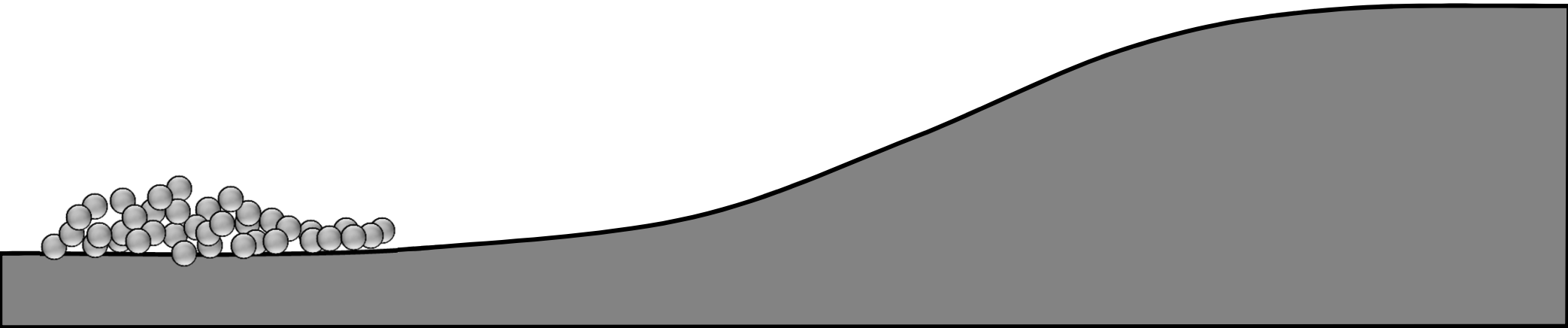


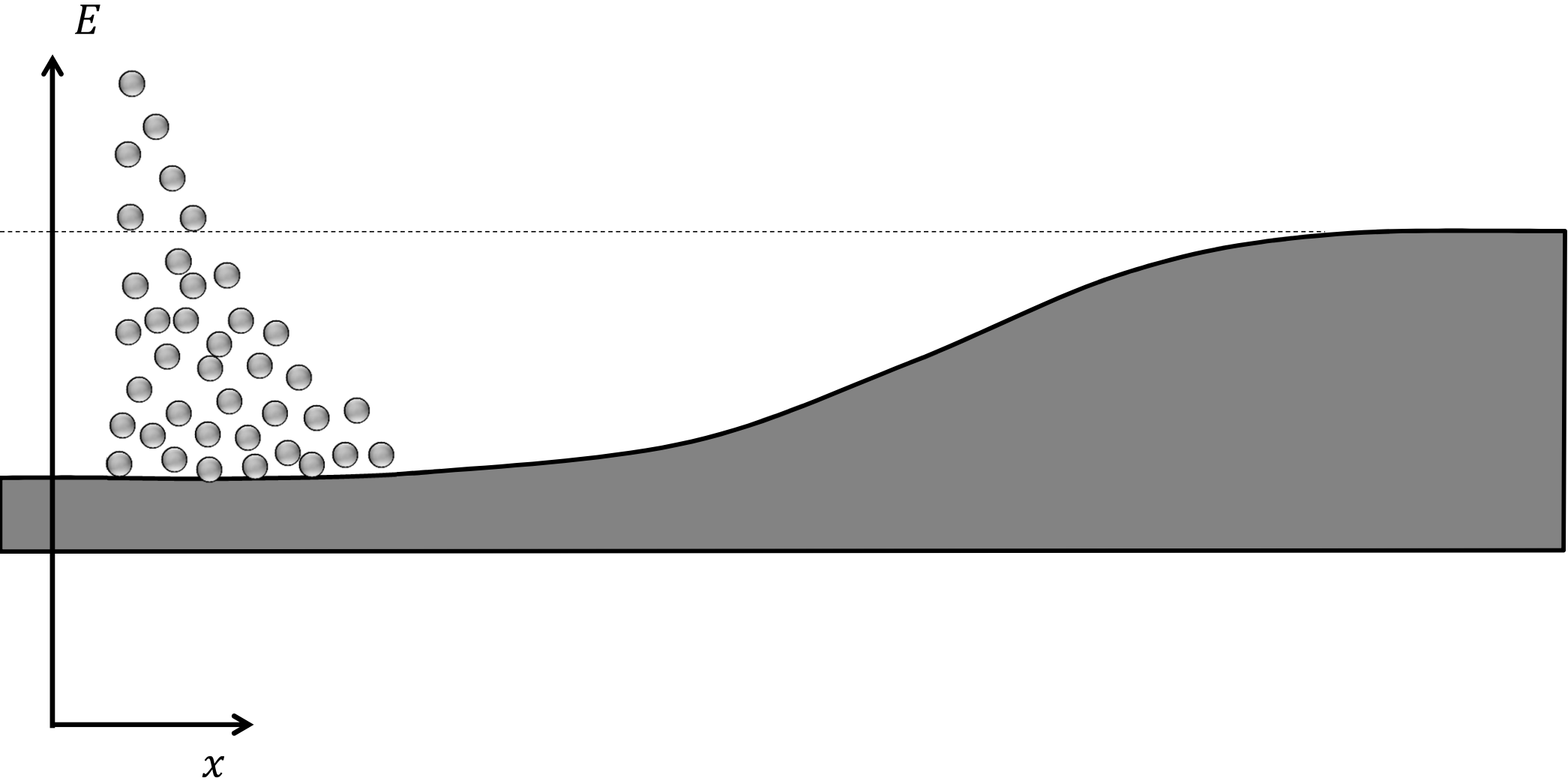
Energy Diagrams

1. 
2. 
3. 
4. 
5. 








Energy Diagrams

- 1. 
- 2. 
- 3. 
- 4. 
- 5. 



Density of States

1. 
2. 
3. 
4. 
5. 

Azadi stadium



Boxing stadium




In Stadium: Number of available seats could be a function of distance from the center so

N : number of available states for the electrons could be function of "Energy" : $N(E)$

Seats are not the same for fans so empty states for electrons!

Fermi Function

Probability of Electron Distribution

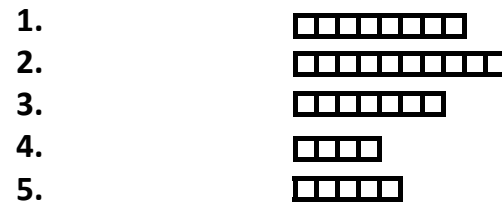


$$f(E) = \frac{1}{1 + e^{(E-E_F)/kT}}$$

E_f is called the Fermi energy or the Fermi level.

If we are $3kT$ away from the Fermi energy then we might use Boltzmann approximation:
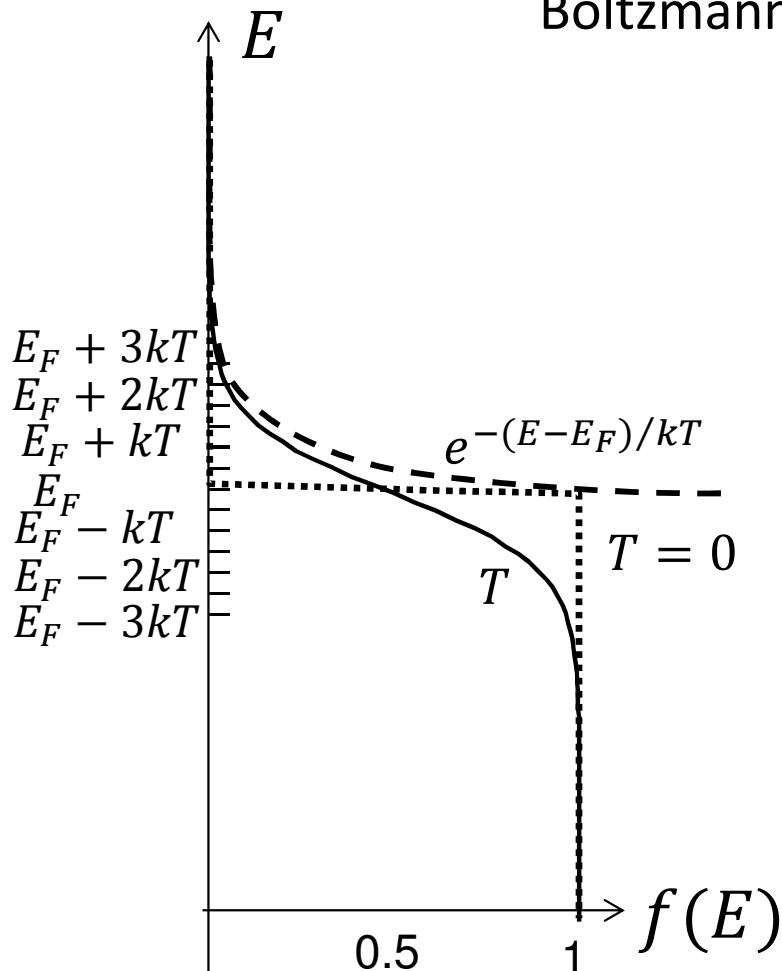
$$f(E) \approx e^{-(E-E_F)/kT} \quad \text{if} \quad E - E_F \gg kT$$






$$f(E) \approx 1 - e^{-(E_f-E)/kT} \quad \text{if} \quad E - E_F \ll -kT$$




$$N(E) f(E) = \text{\# of electrons at energy } E$$
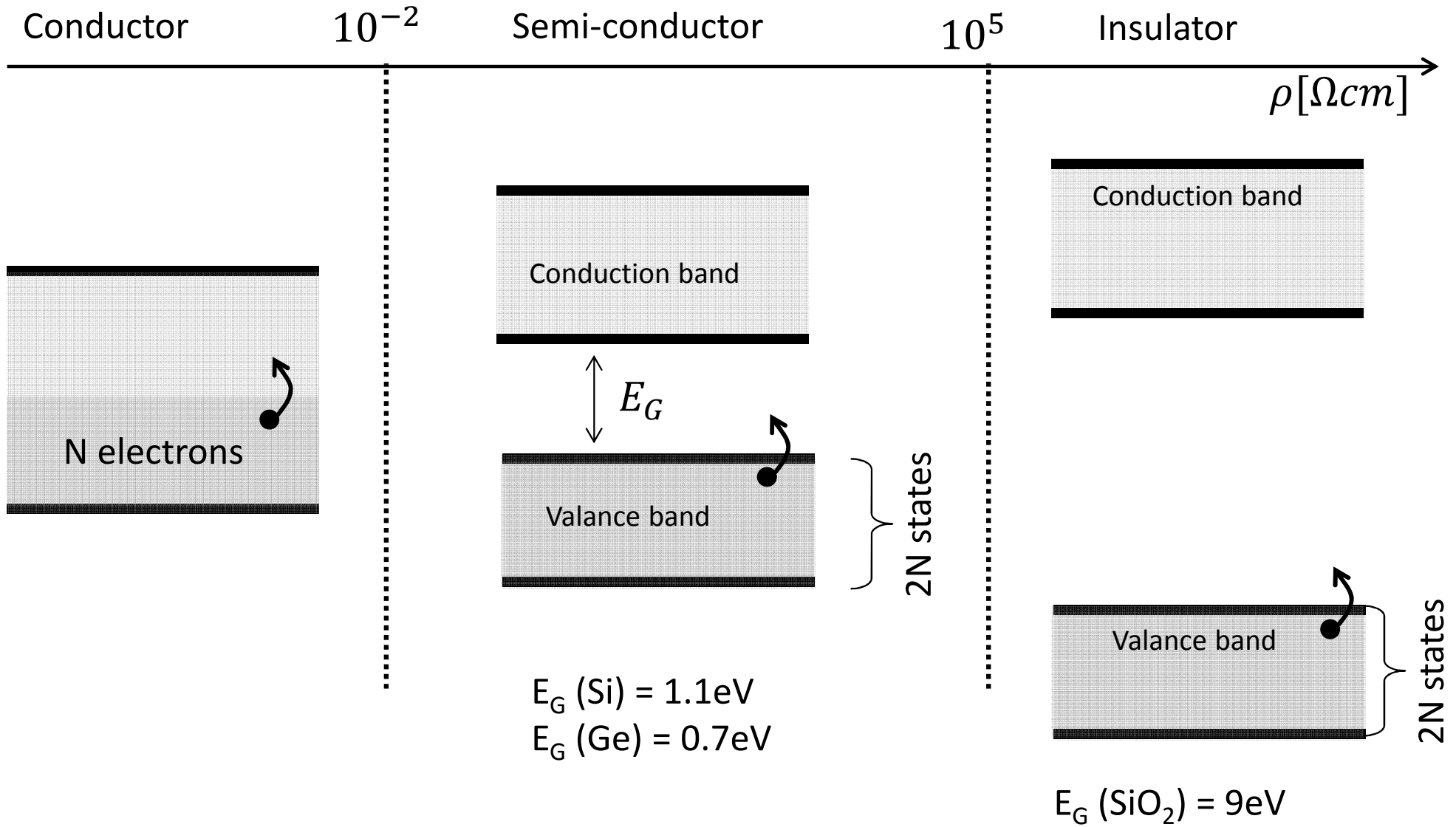
$$N(E)(1 - f(E)) = \text{\# of holes at energy } E$$






Materials

1. 
2. 
3. 
4. 
5. 



empty seat / filled seat


Electron / Holes : Intrinsic

1. 
2. 
3. 
4. 
5. 






intrinsic

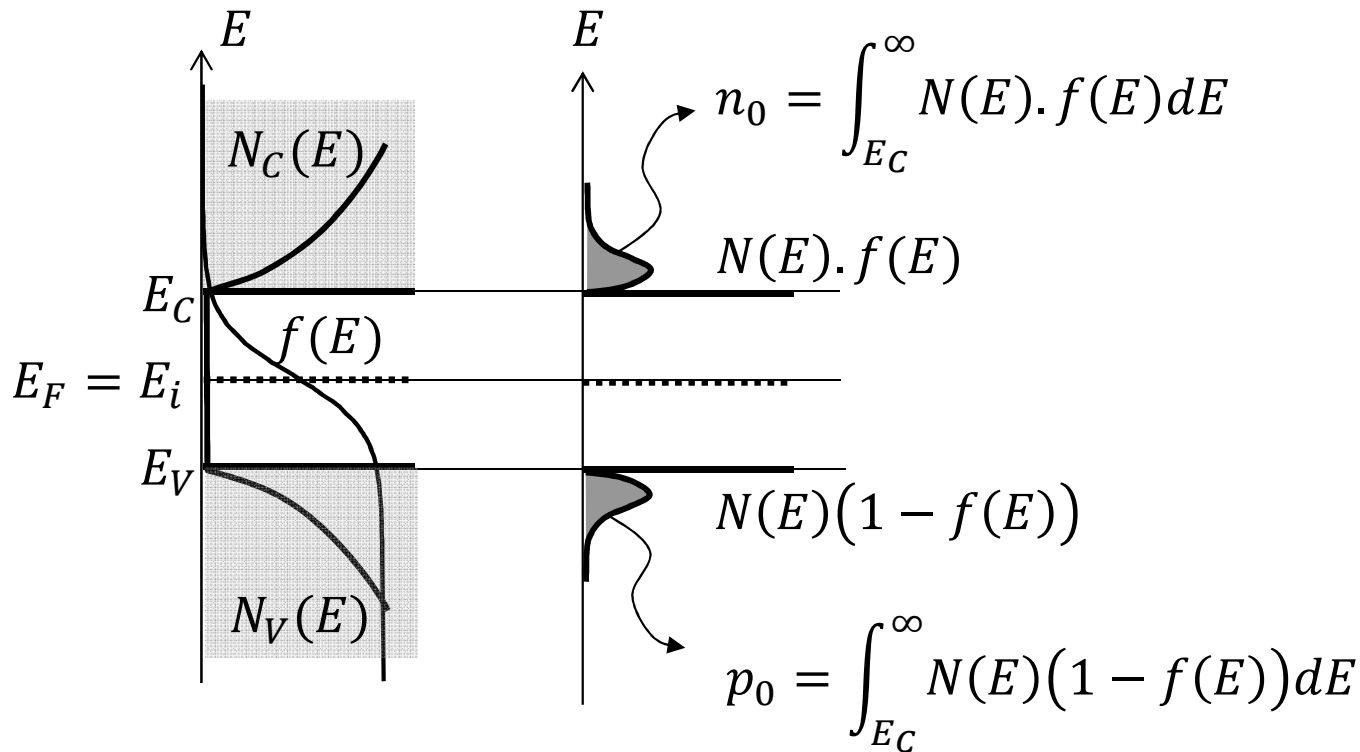$N(E) f(E) =$ # of electrons at energy E

$N(E)(1 - f(E)) =$ # of holes at energy E




Electron / Holes : n-type

1. 
2. 
3. 
4. 
5. 

n-type



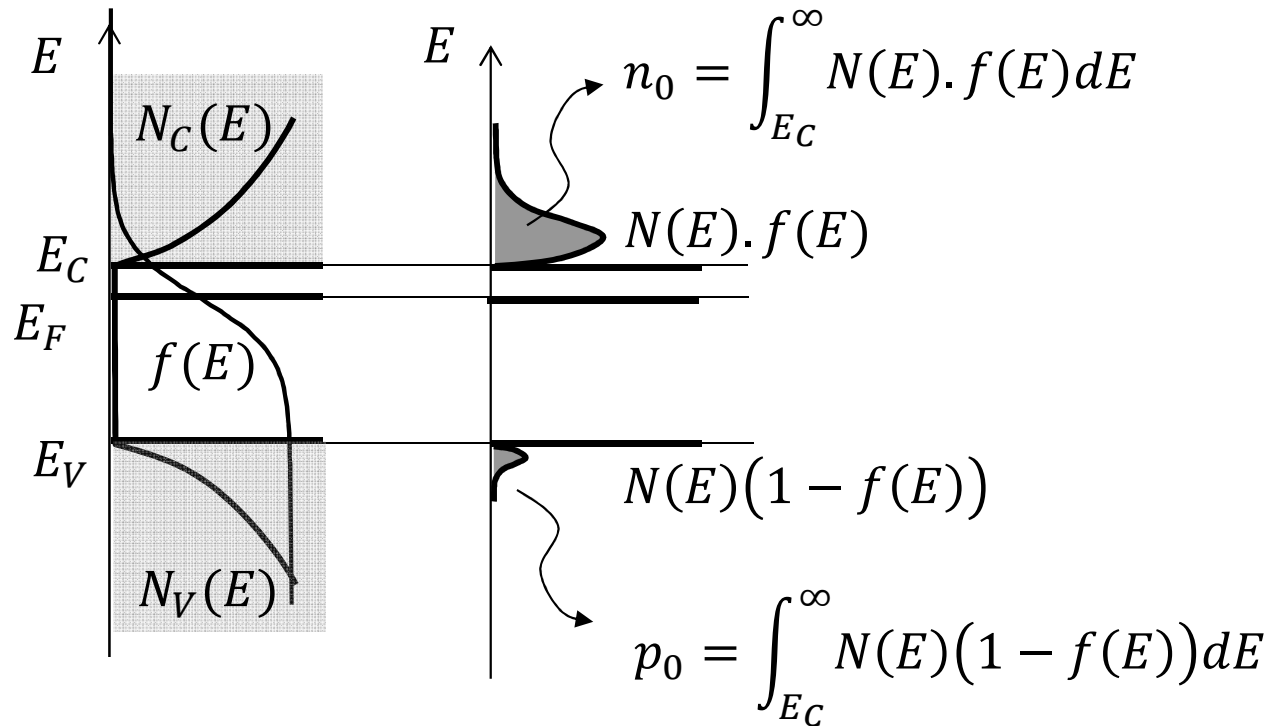


$N(E) f(E) =$ # of electrons at energy E

$N(E)(1 - f(E)) =$ # of holes at energy E



$n_0 \gg p_0$


Electron / Holes : p-type

1. 
2. 
3. 
4. 
5. 






p-type

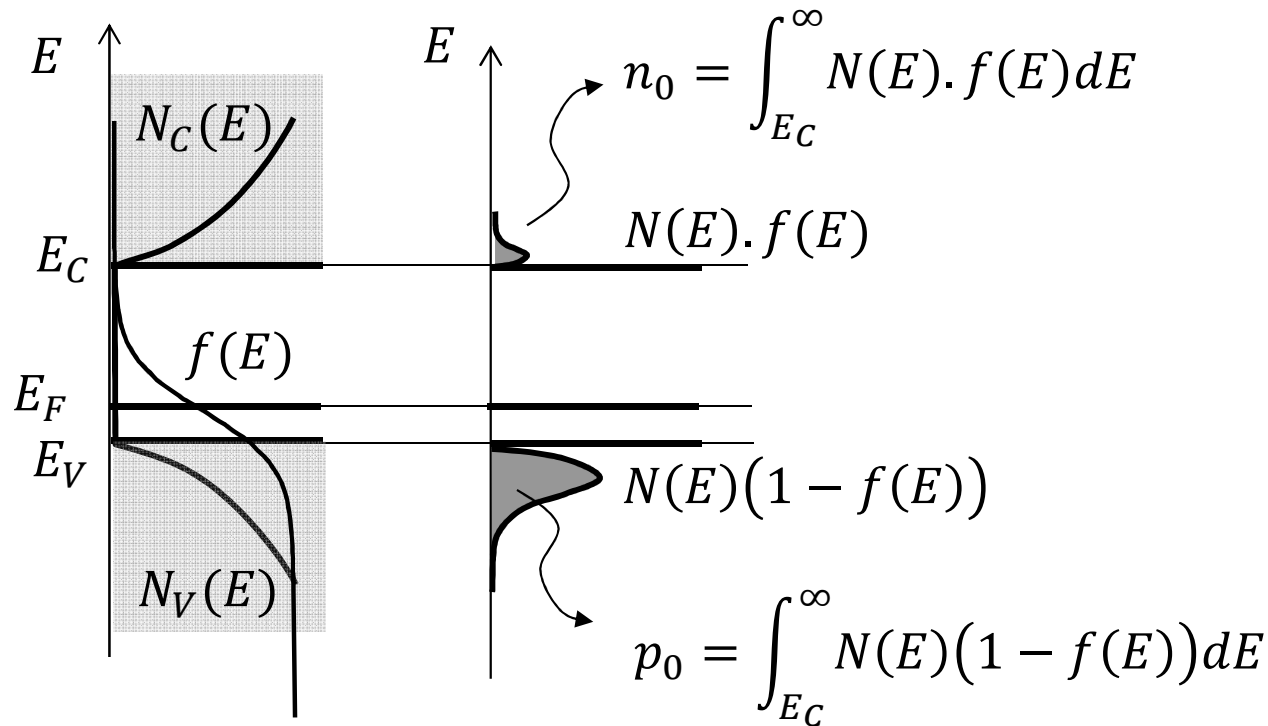
$N(E) f(E) =$ # of electrons at energy E

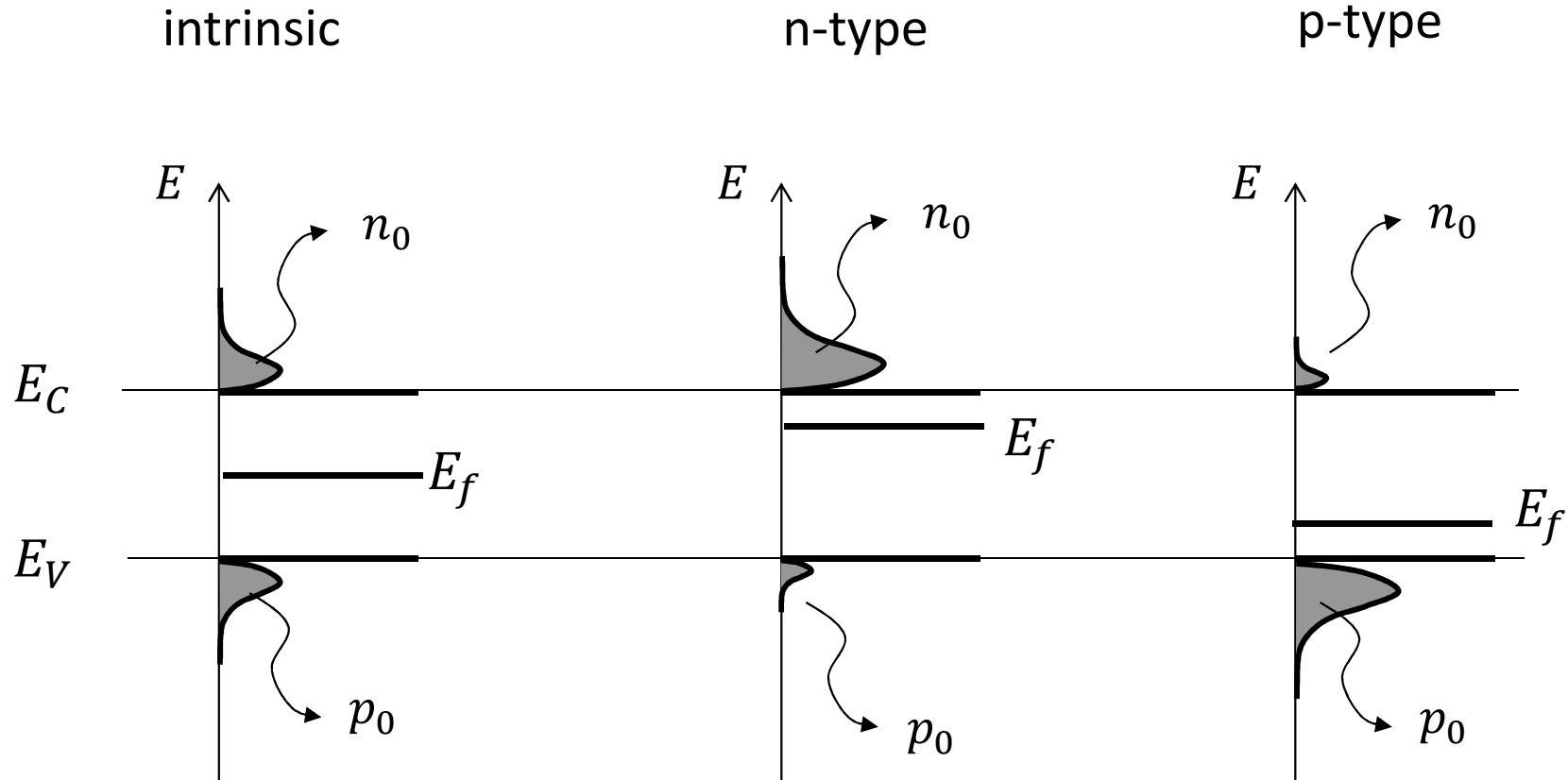$N(E)(1 - f(E)) =$ # of holes at energy E








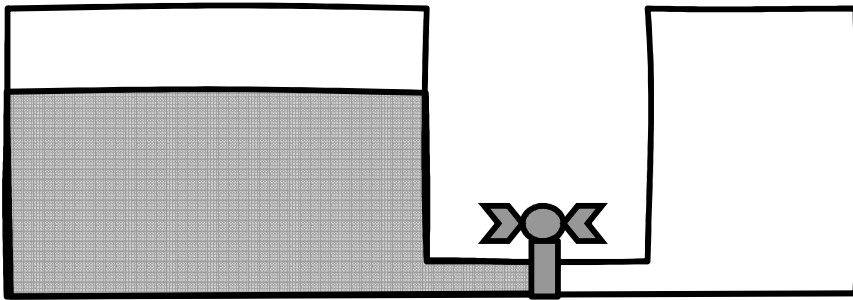
Fermi Energy

1. 
2. 
3. 
4. 
5. 




Fermi Energy



1. 
2. 
3. 
4. 
5. 



p-type

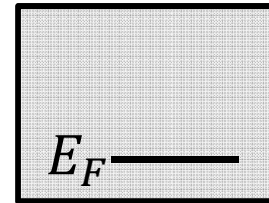


n-type

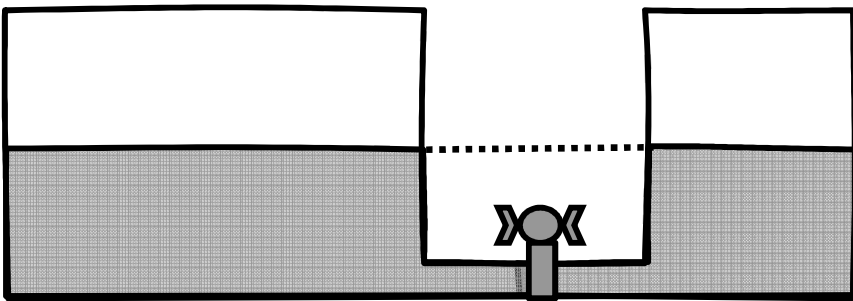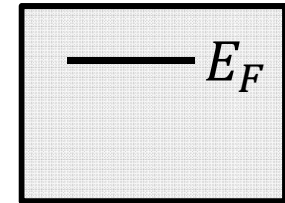



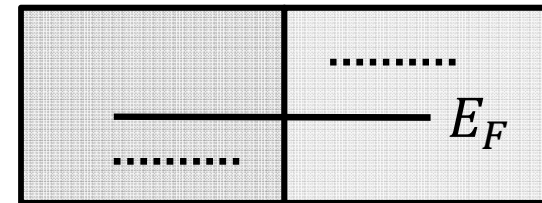


p-type


n-type





Flow of Charge

1. 
2. 
3. 
4. 
5. 

Drift Electric field

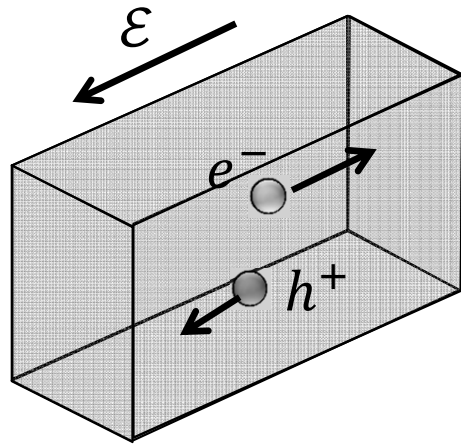


gravitational field

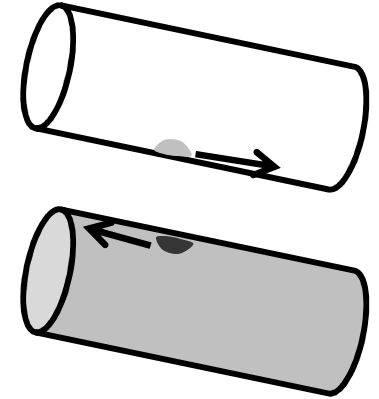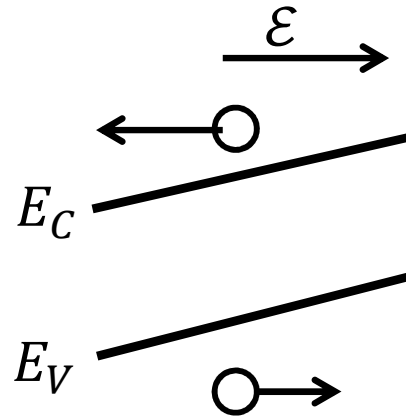

$$J_n = qn\mu\mathcal{E}$$

Diffusion

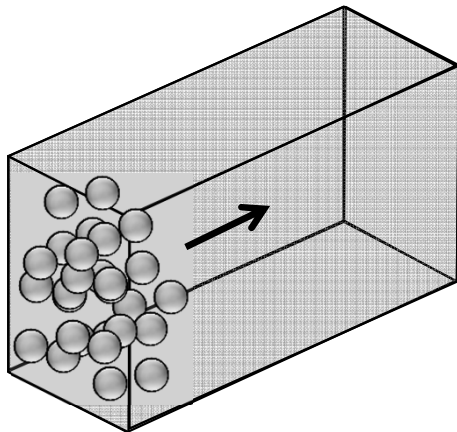






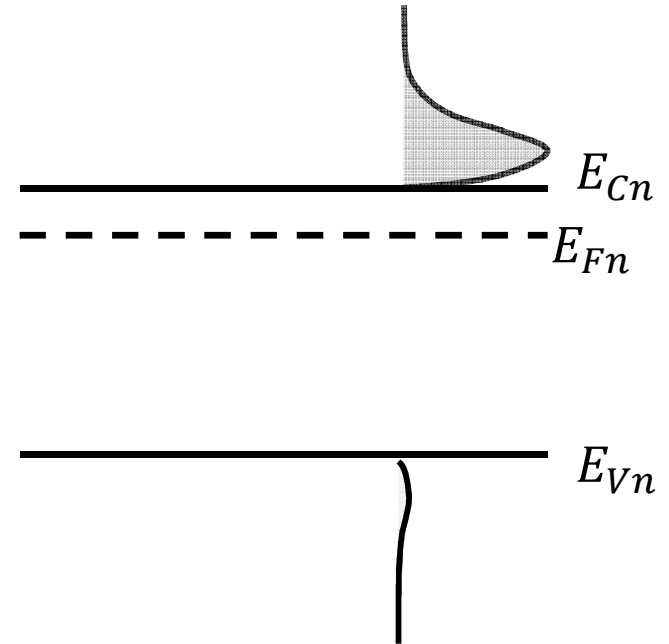
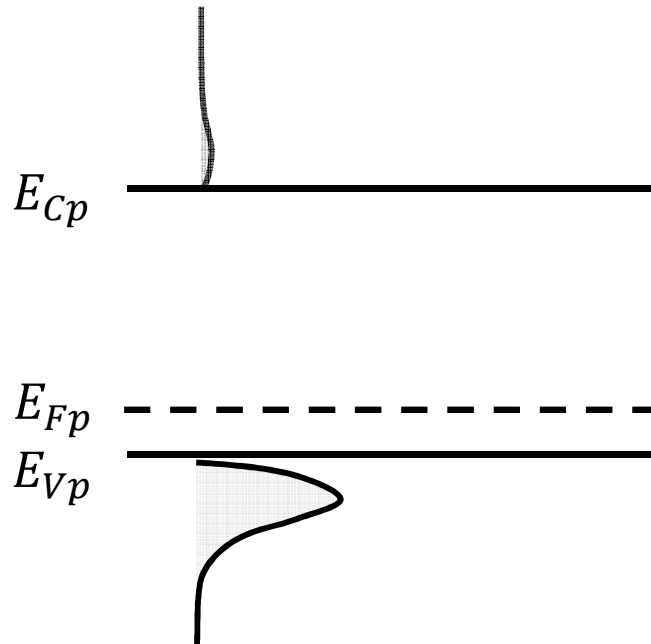
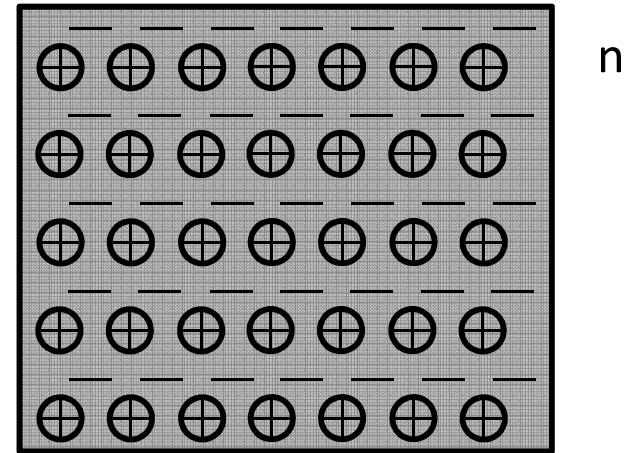
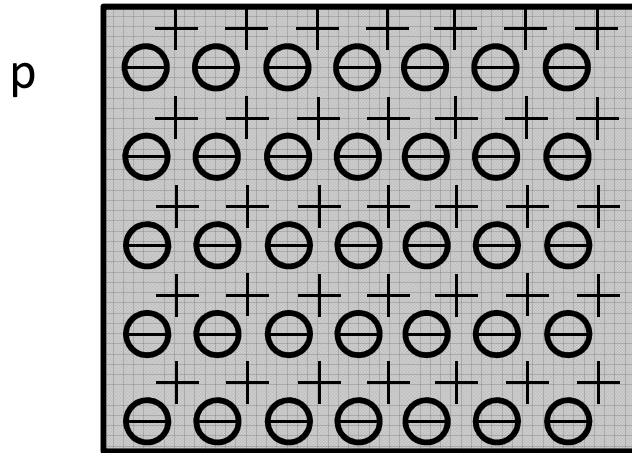
Charges move to be evenly distributed throughout space. Similar to perfume in room or heat in a solid

$$J_n = qD_n \frac{dn}{dx}$$






$$J_p = -qD_p \frac{dp}{dx}$$


PN Junction

1. 
2. 
3. 
4. 
5. 





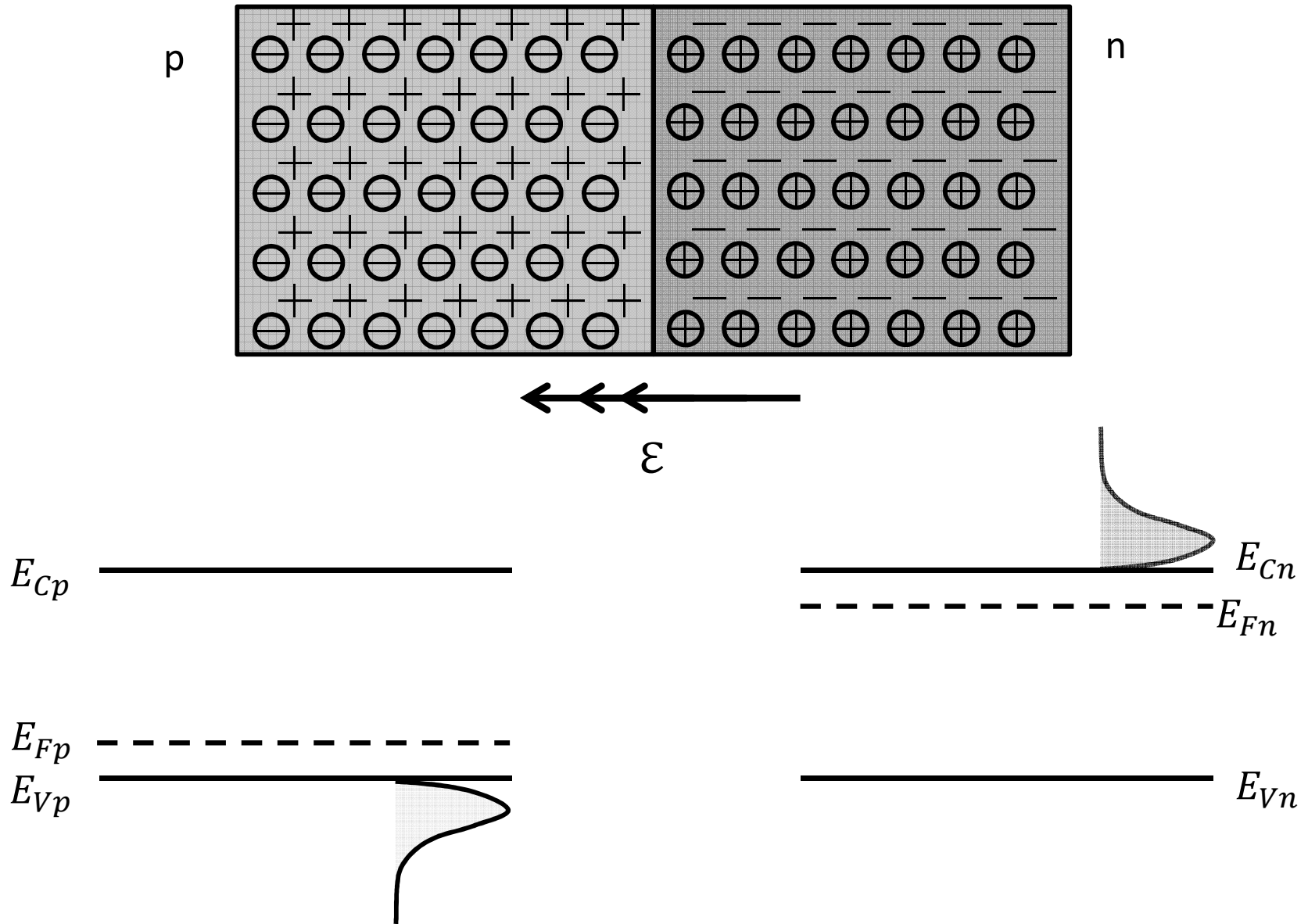


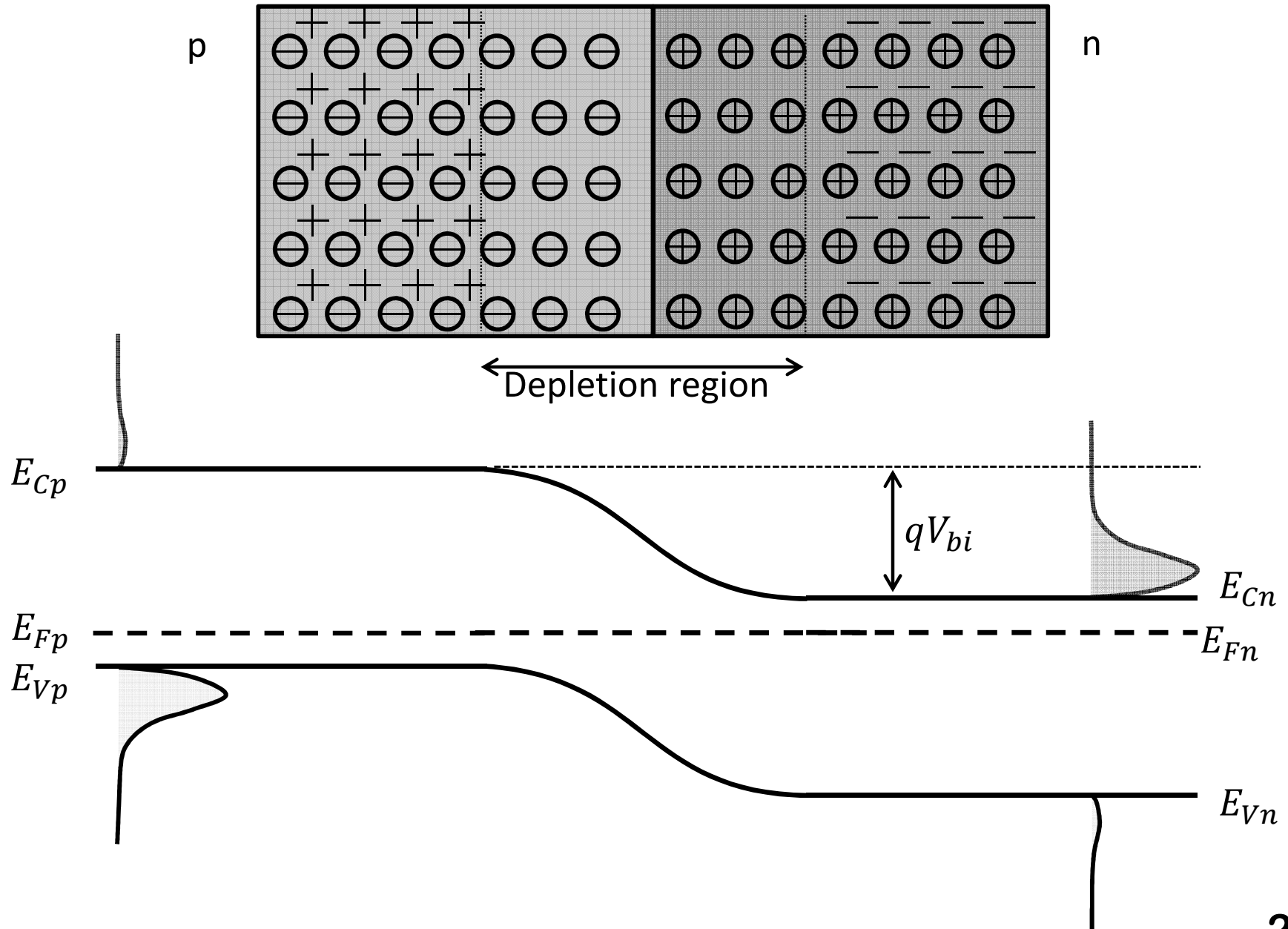
PN junctions

1. 
2. 
3. 
4. 
5. 








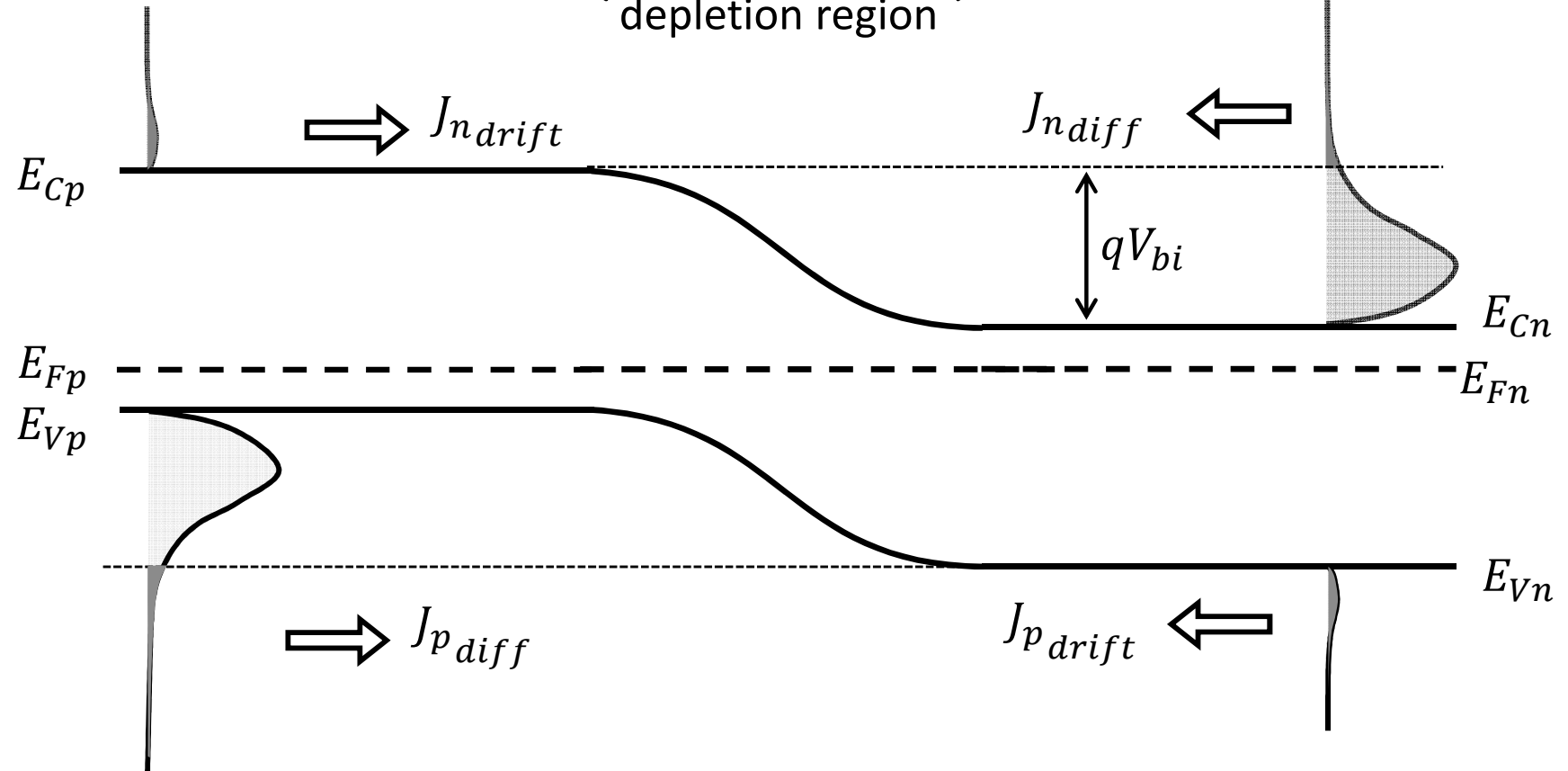
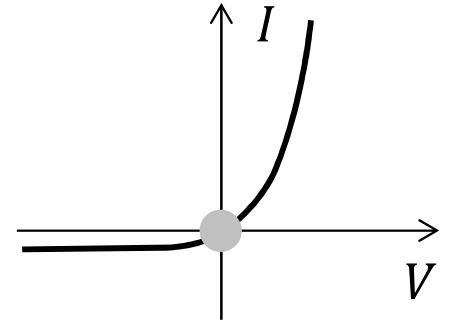
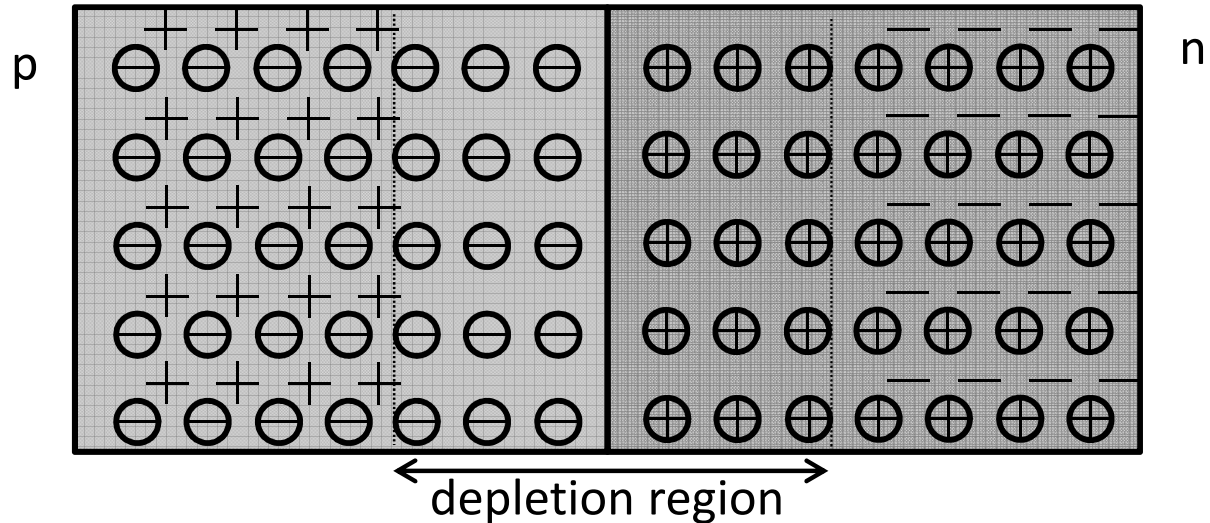
PN junctions

1. 
2. 
3. 
4. 
5. 








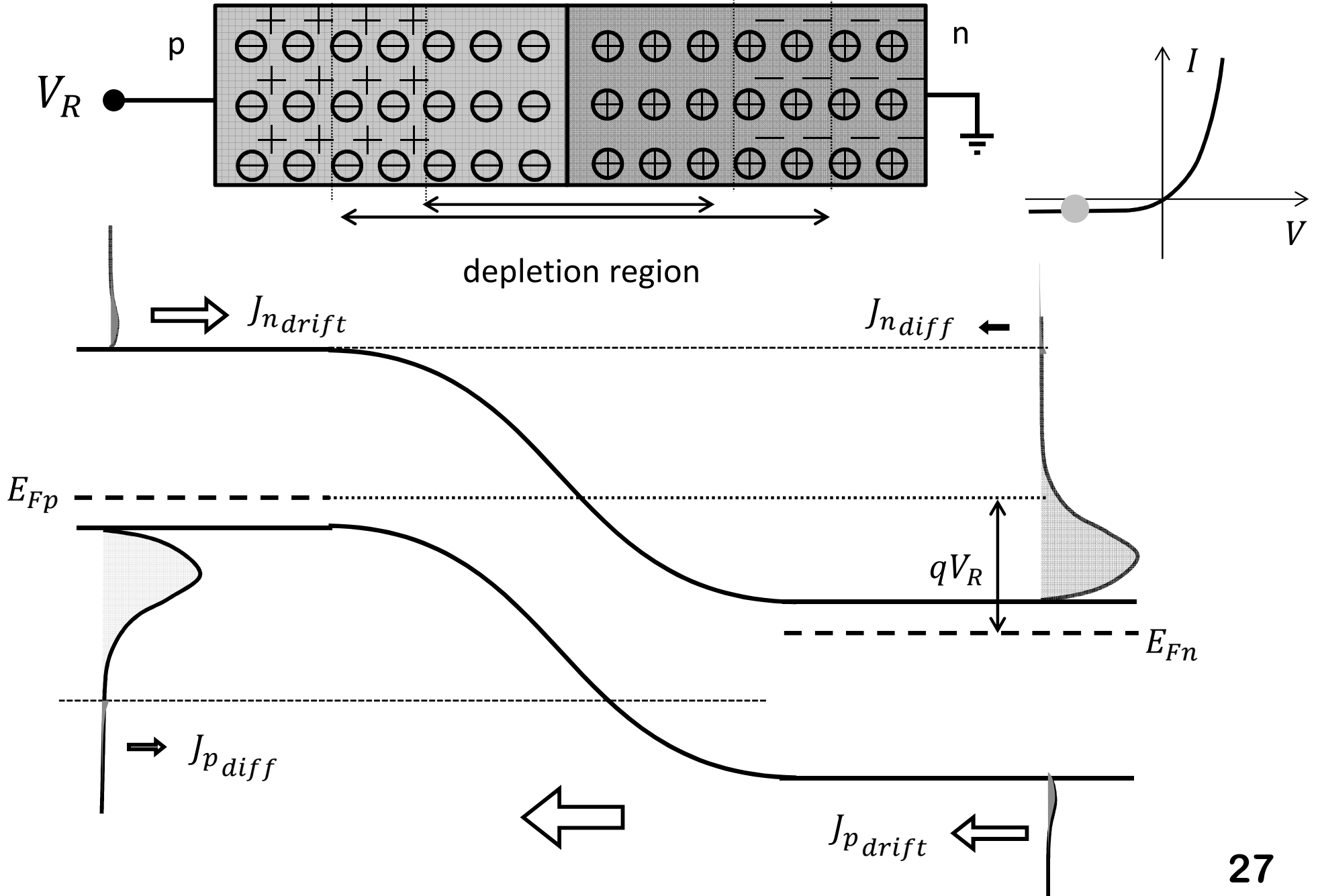
PN junctions

1. 
2. 
3. 
4. 
5. 








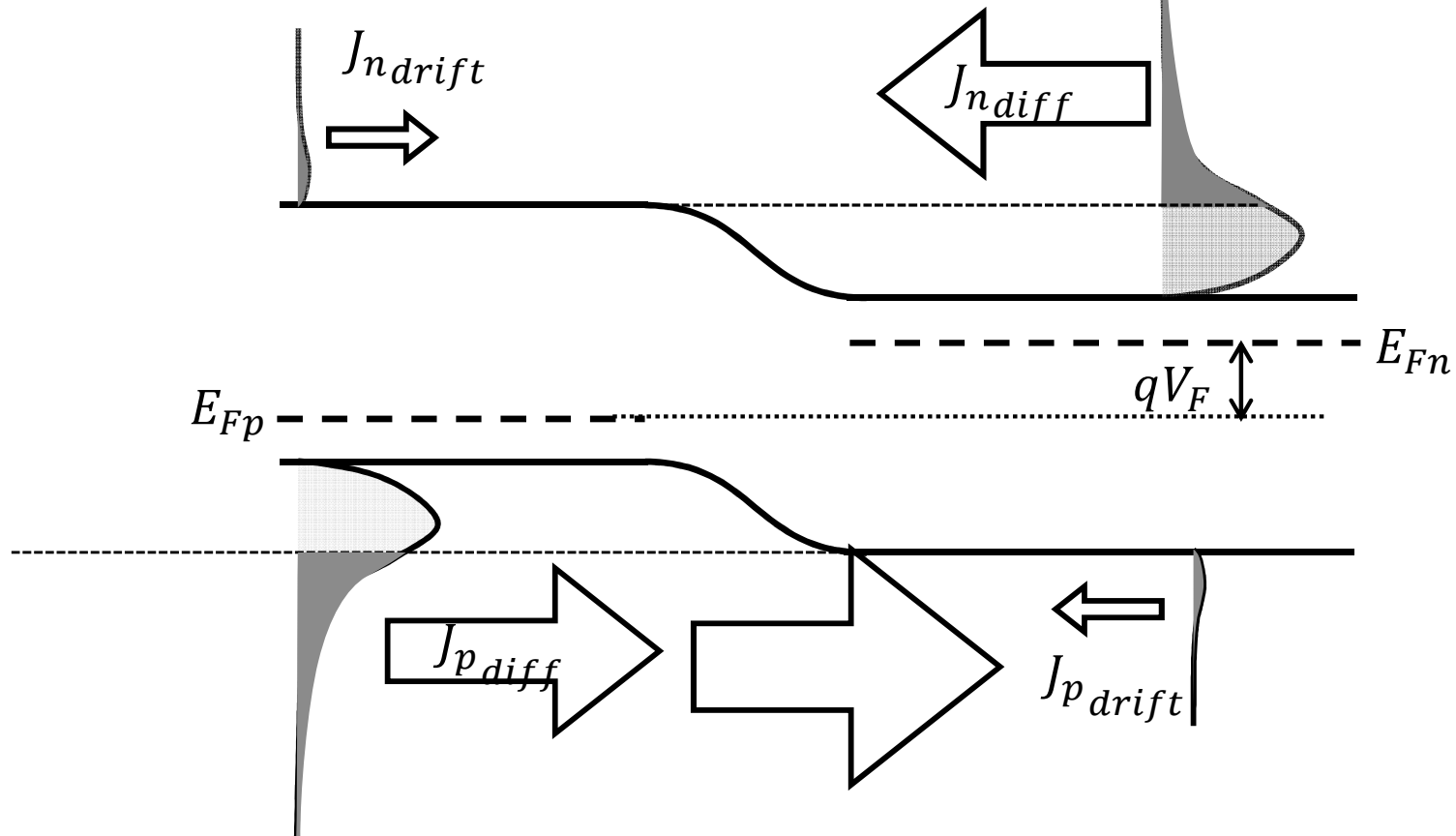
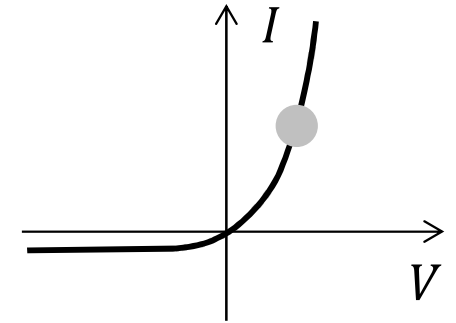
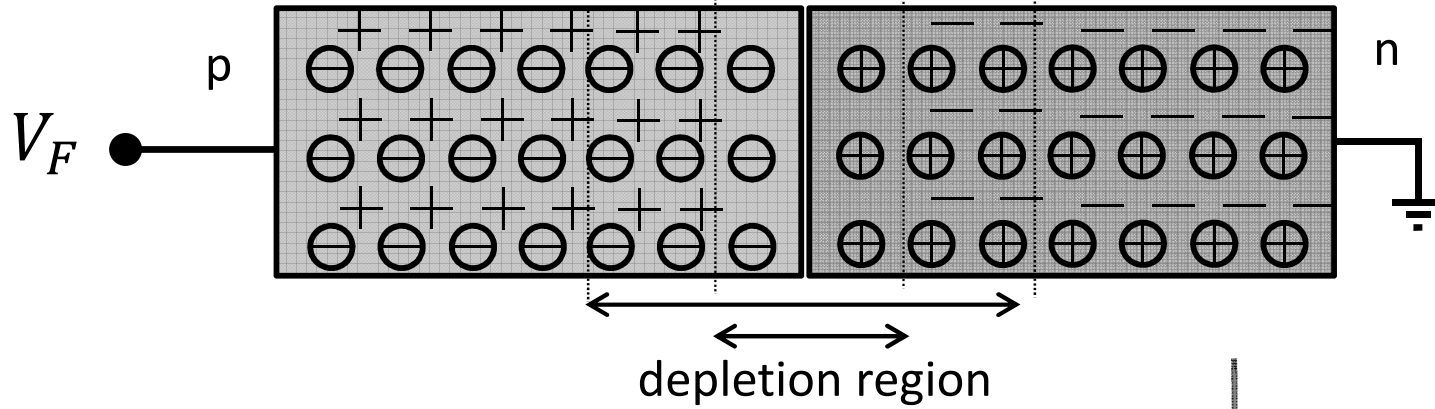
PN junctions , Reverse Biased

1. 
2. 
3. 
4. 
5. 








PN junctions , Forward Biased


1. 
2. 
3. 
4. 
5. 



BJT Electrostatics

1. 
2. 
3. 
4. 
5. 

*pn*p

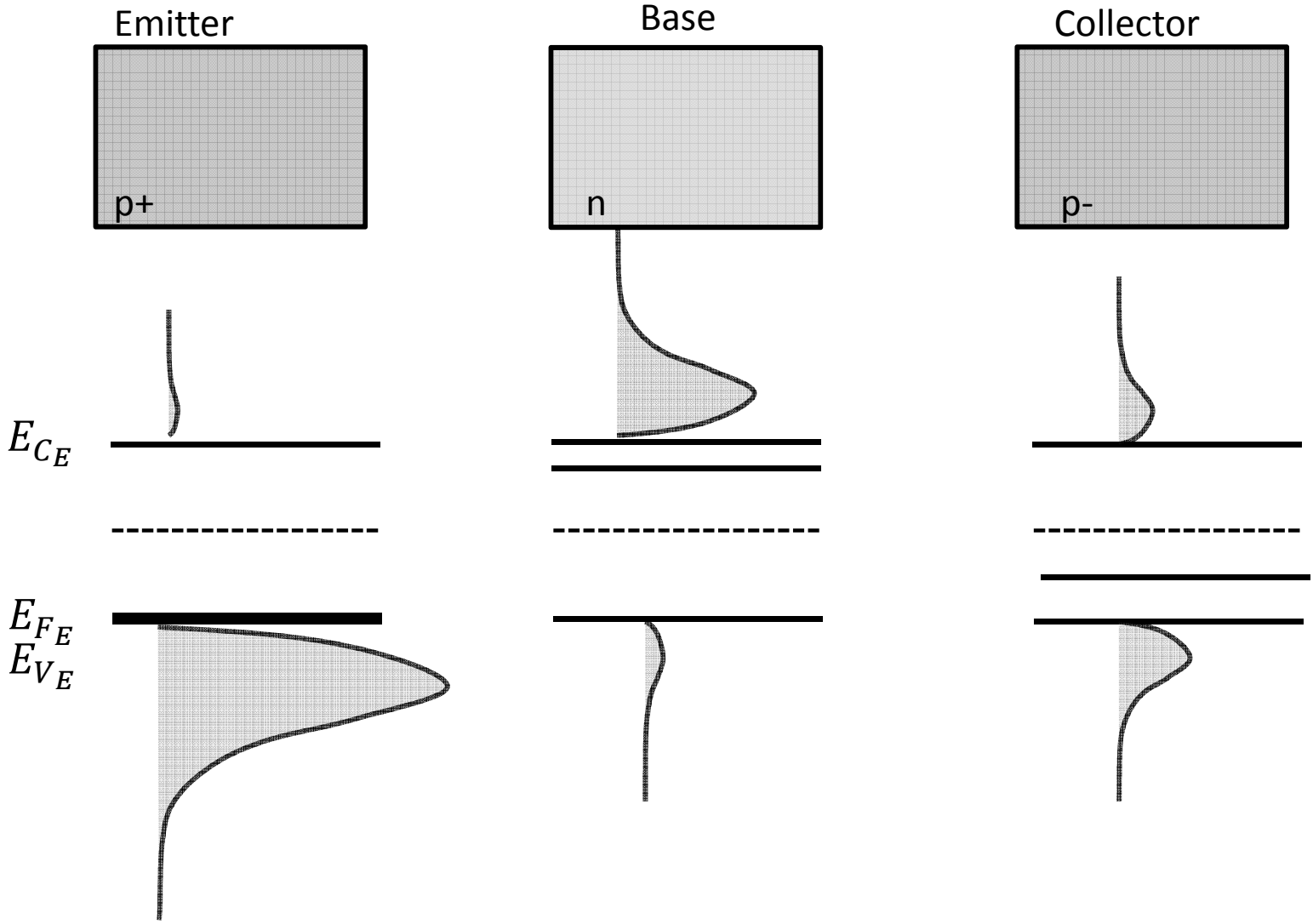


Under normal operating conditions, the BJT may be viewed electrostatically as two independent pn junctions

BJT Electrostatics



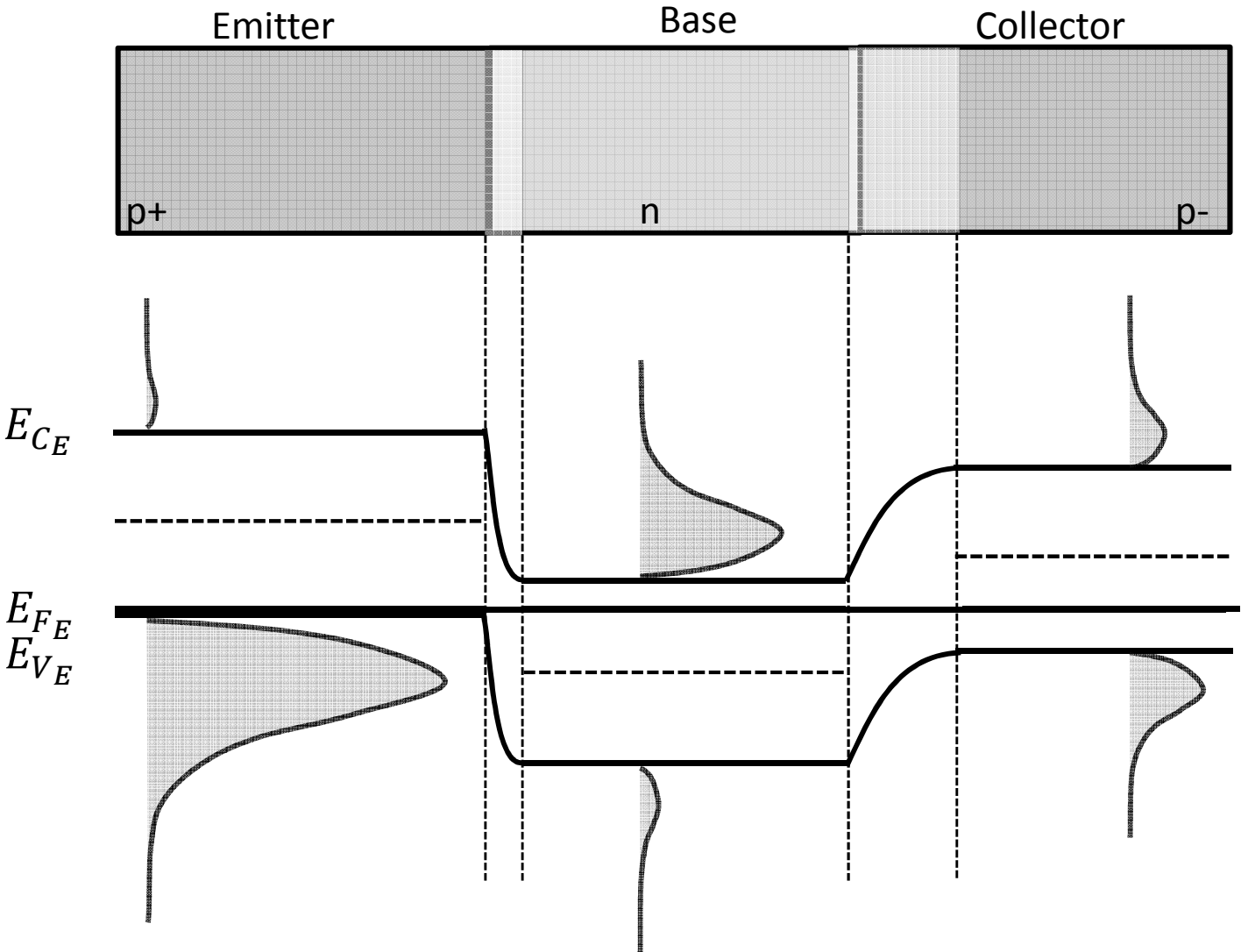


- 1.
- 2.
- 3.
- 4.
- 5.


*pn*p








Under normal operating conditions, the BJT may be viewed electrostatically as two independent pn junctions

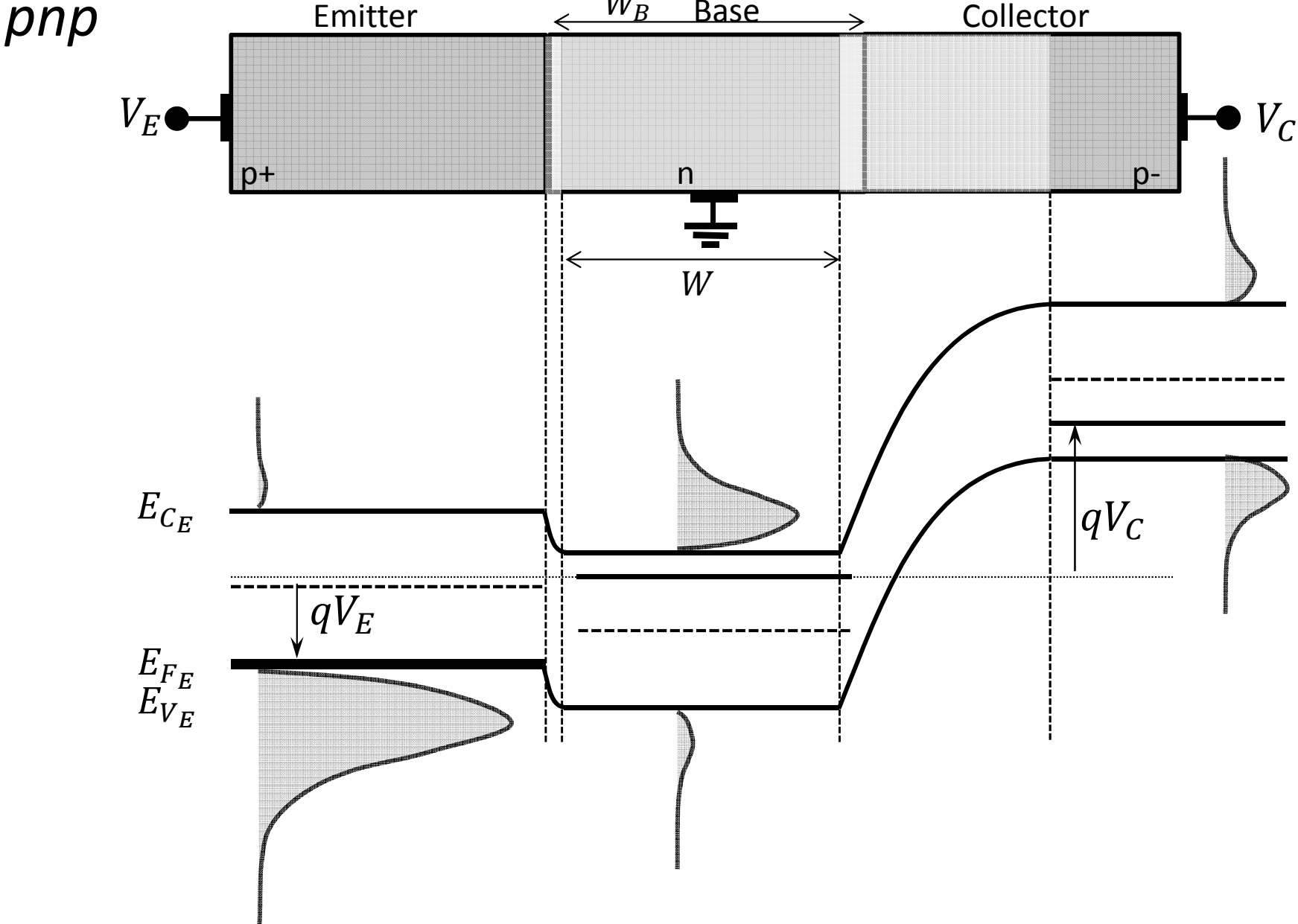BJT Electrostatics


- 1. 
- 2. 
- 3. 
- 4. 
- 5. 








JFET

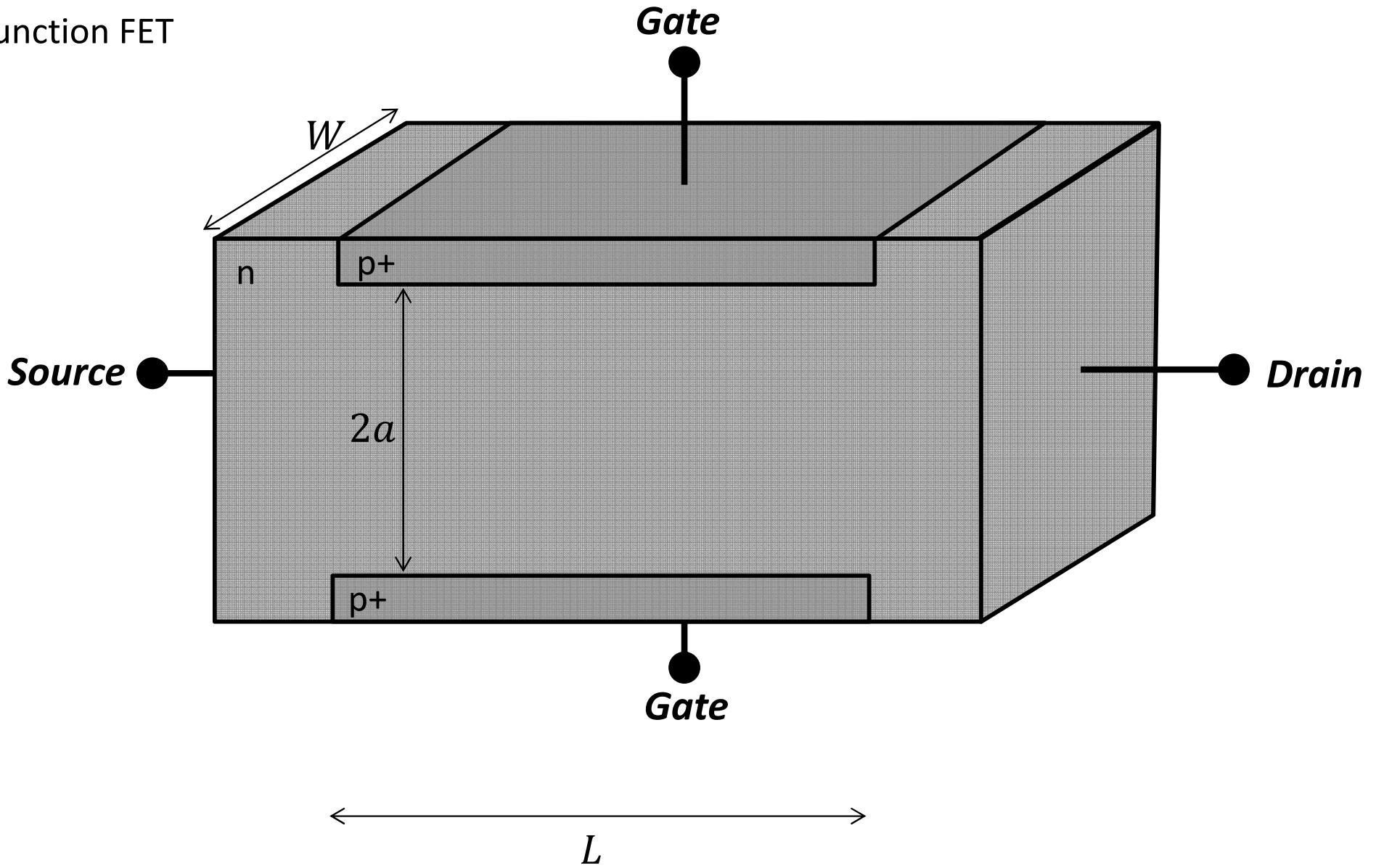
- 1. 
- 2. 
- 3. 
- 4. 
- 5. 

Junction FET




JFET



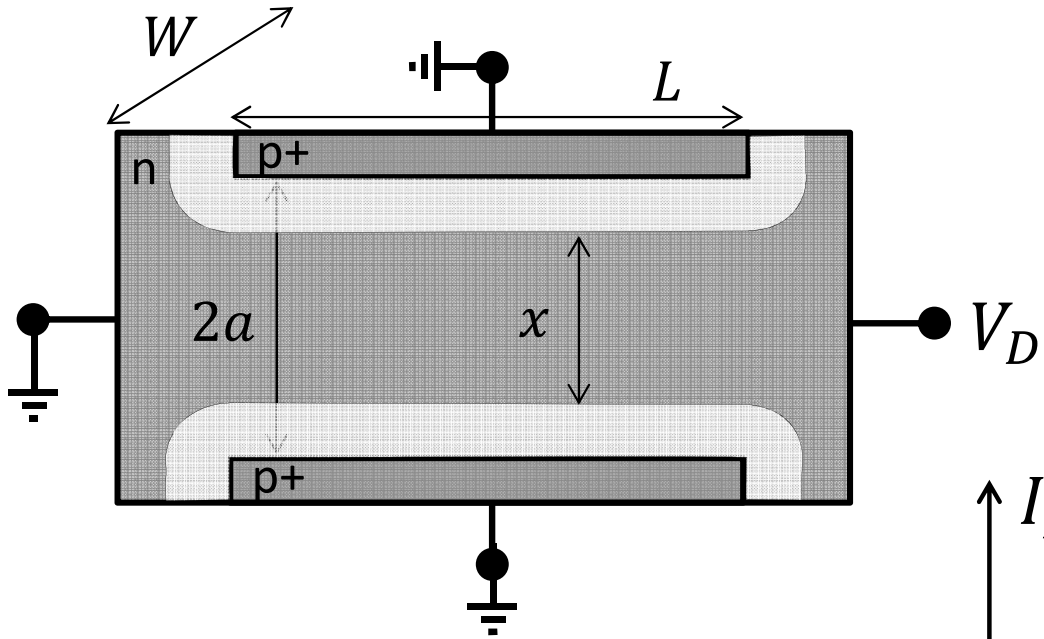


1. 
2. 
3. 
4. 
5. 

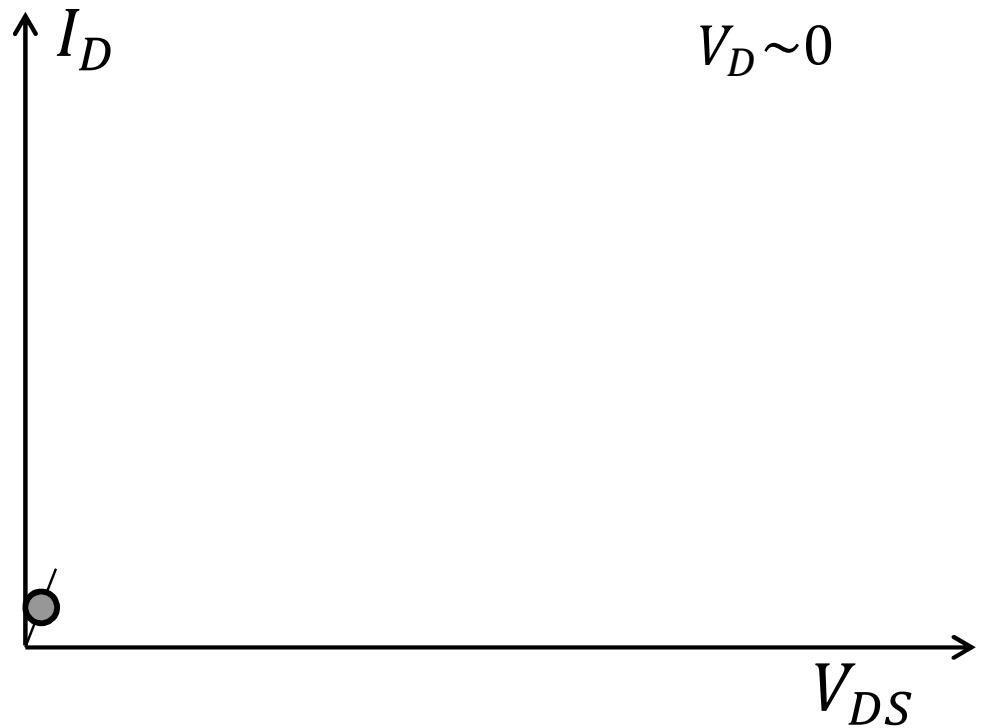


$$R = \rho \frac{L}{Wx}$$




JFET



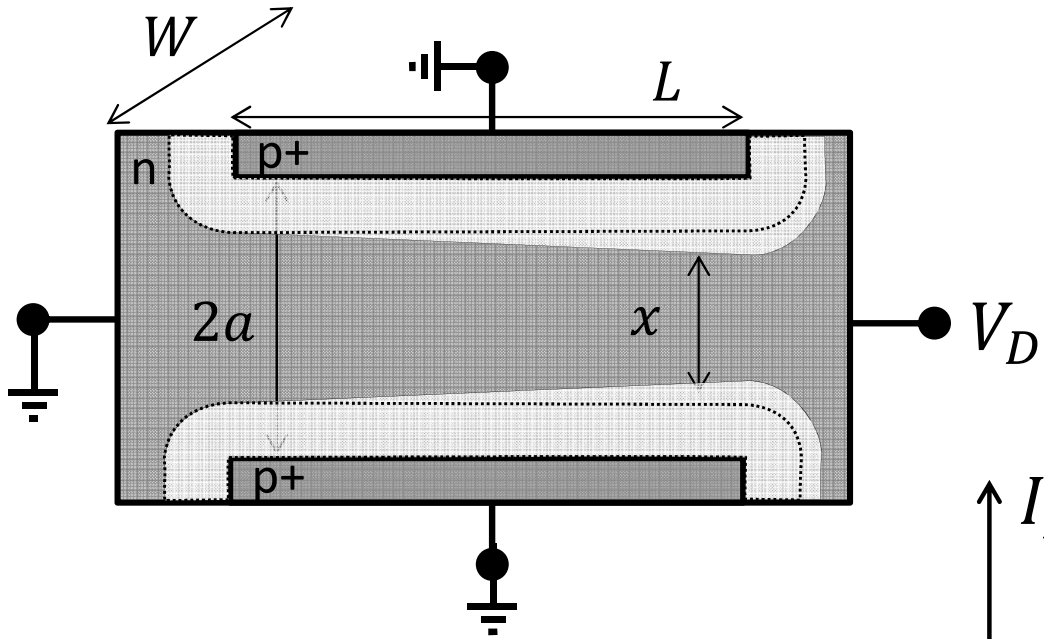


1. 
2. 
3. 
4. 
5. 

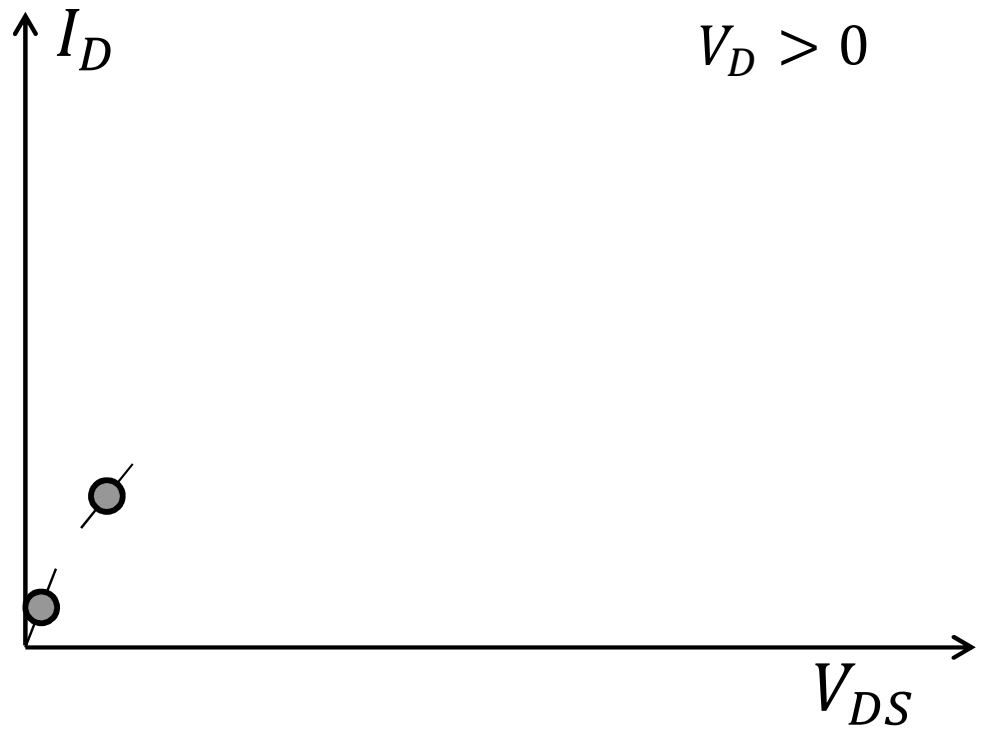


$$R = \rho \frac{L}{Wx}$$




JFET



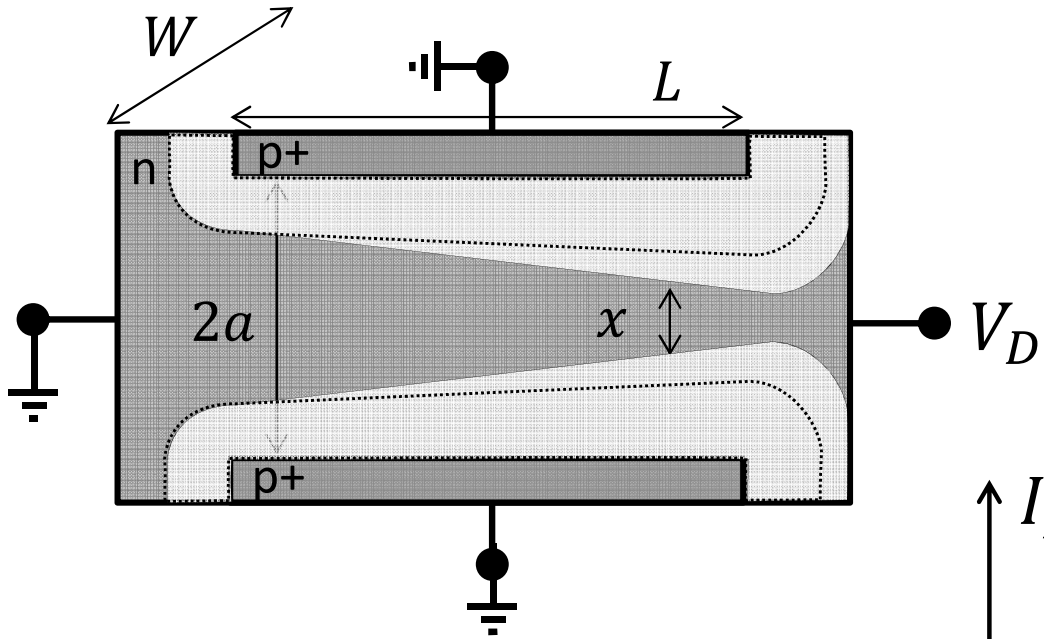


1. 
2. 
3. 
4. 
5. 

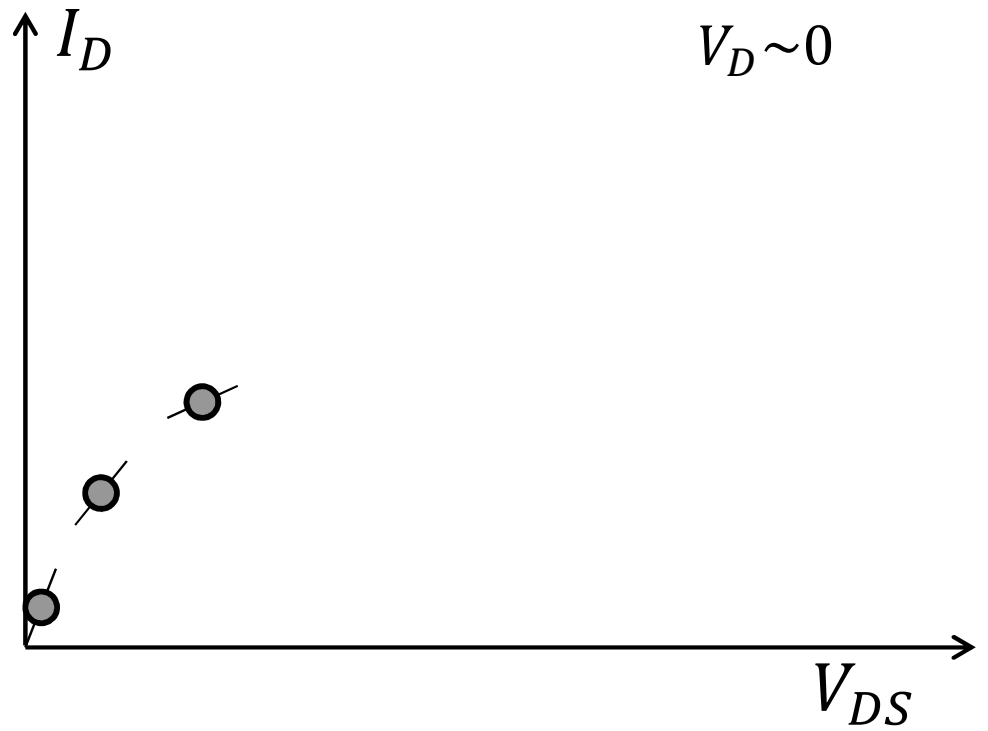


$$R = \rho \frac{L}{Wx}$$




JFET



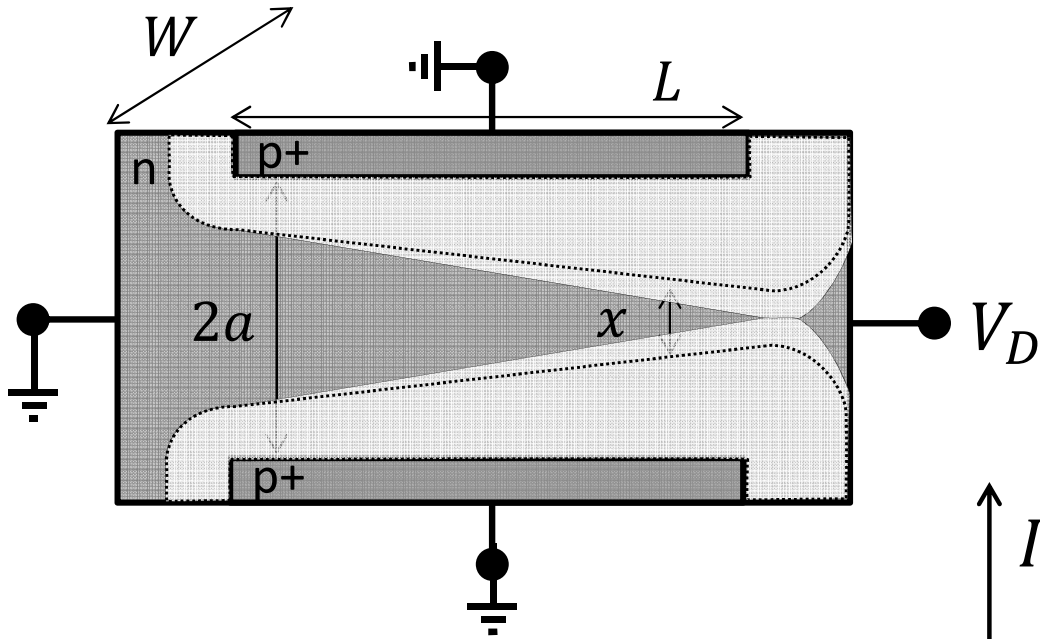


1. 
2. 
3. 
4. 
5. 

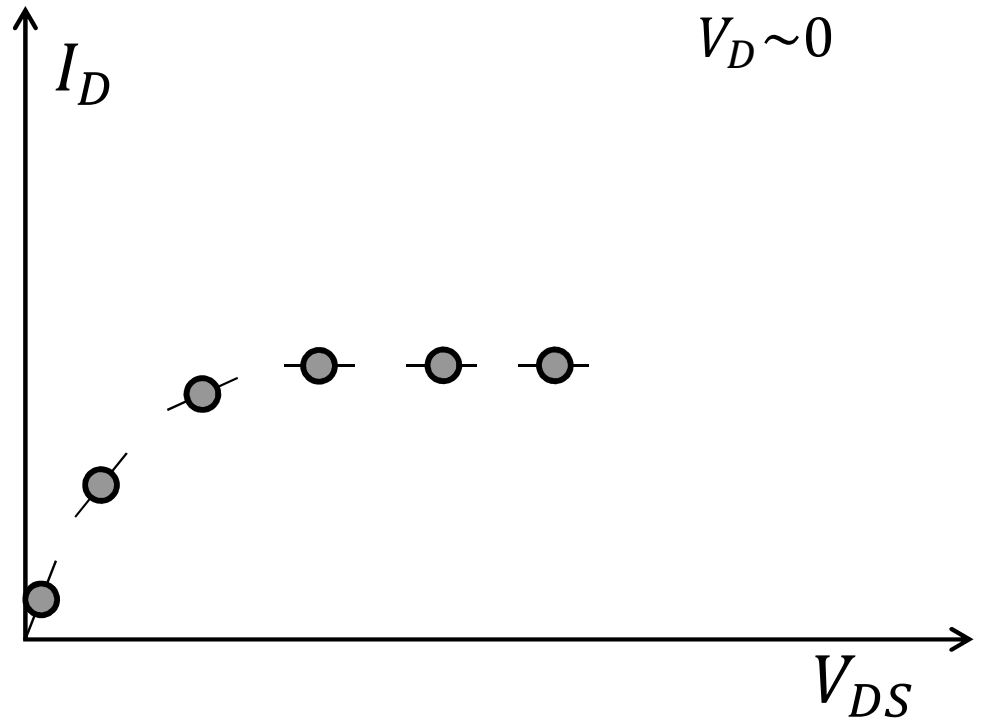


$$R = \rho \frac{L}{Wx}$$




JFET



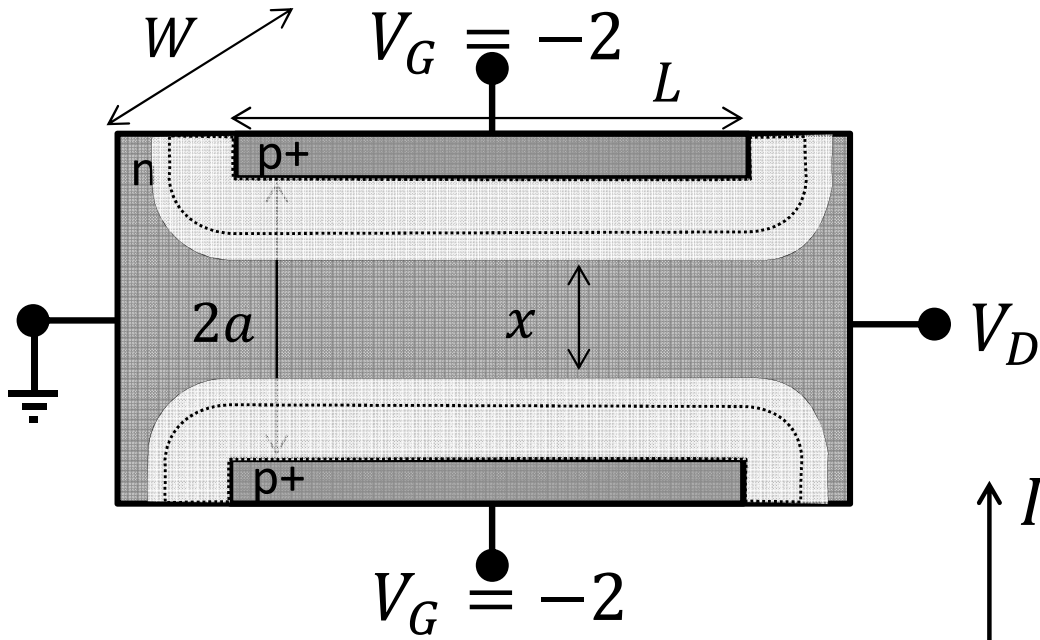


1. 
2. 
3. 
4. 
5. 


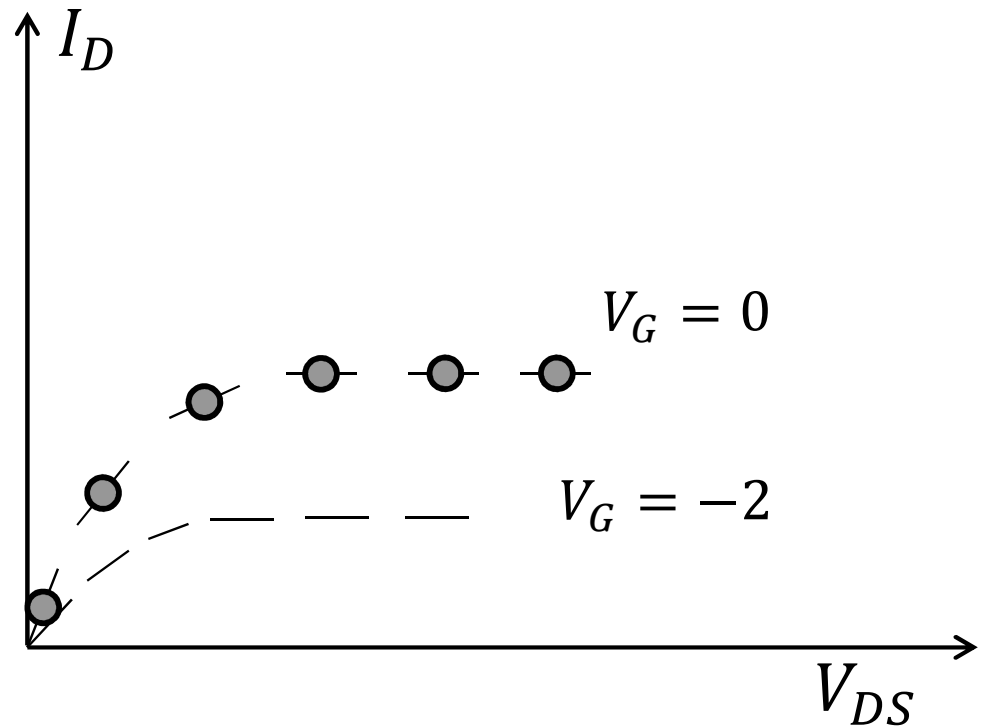


$$R = \rho \frac{L}{Wx}$$





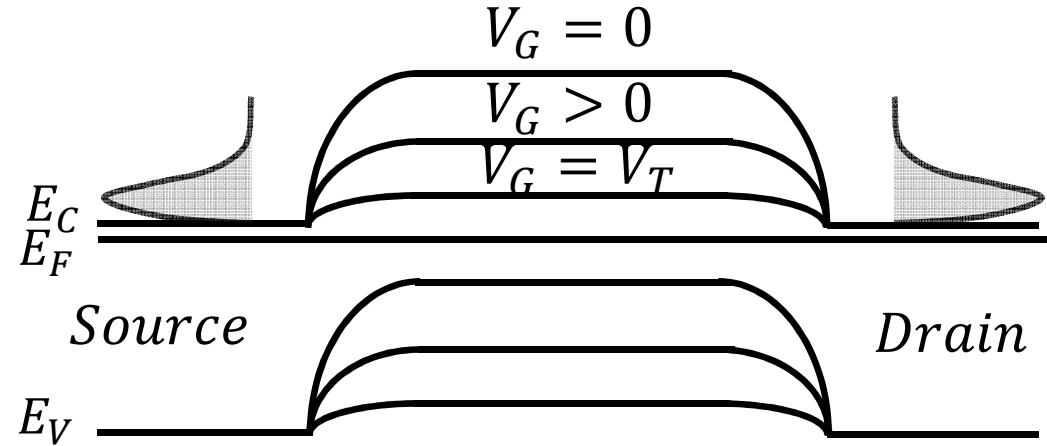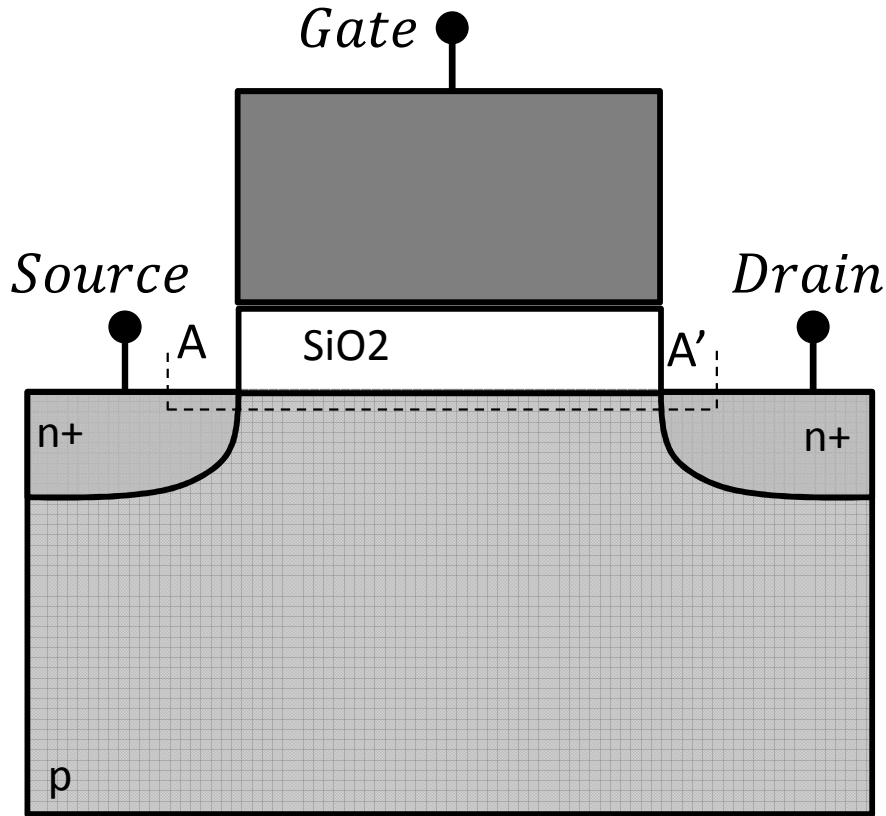


Qualitative Theory of the NMOSFET





1. 
2. 
3. 
4. 
5. 








The potential barrier to electron flow from the source into the channel region is lowered by applying $V_{GS} > V_T$

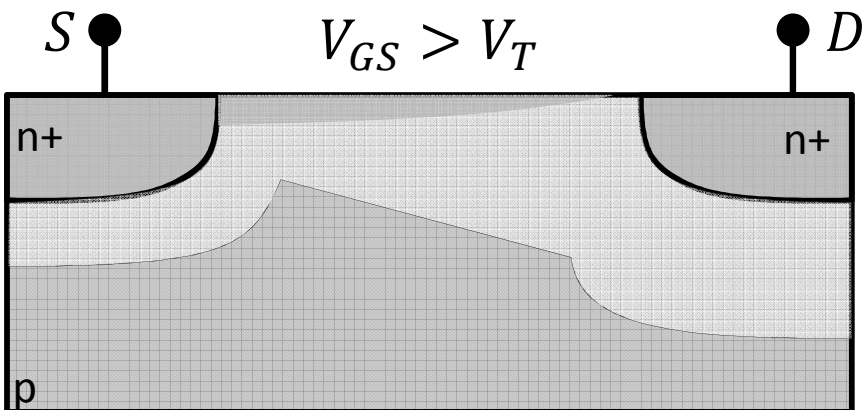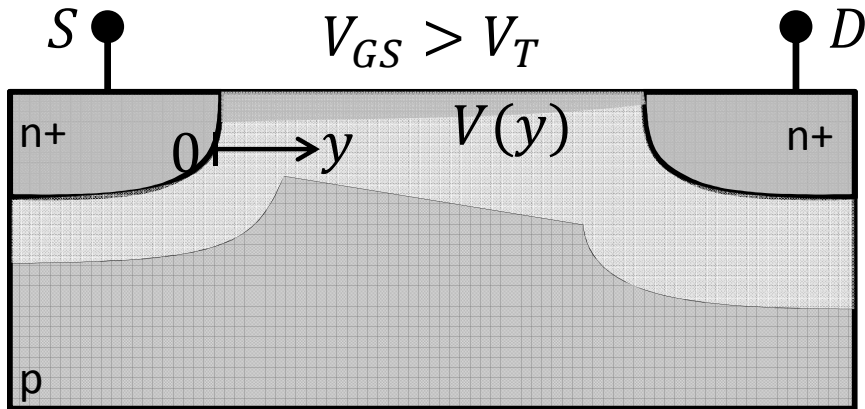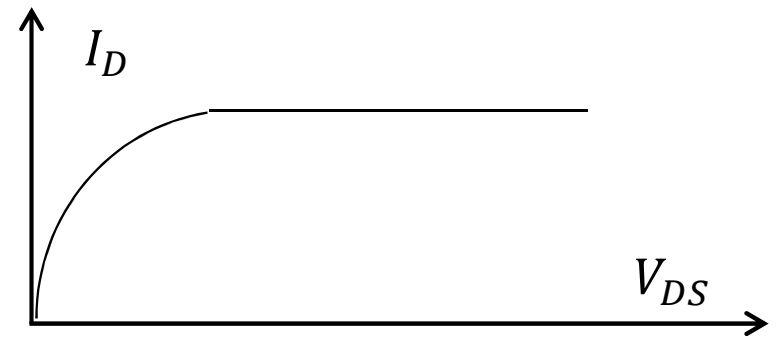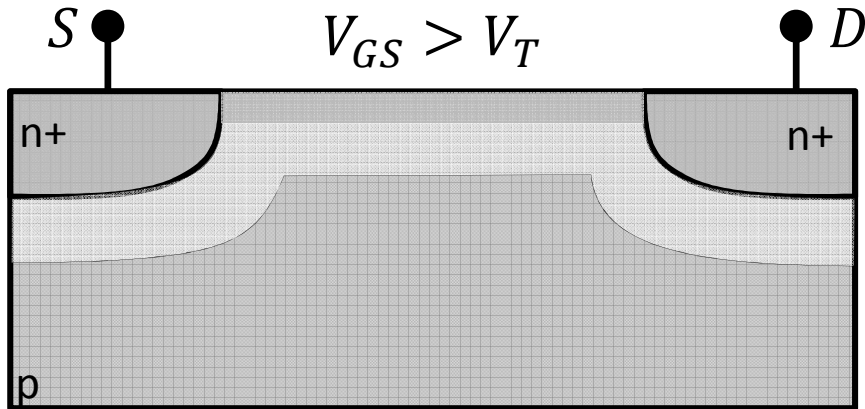
Qualitative Theory of the NMOSFET

1. 
2. 
3. 
4. 
5. 



Fermi Energy

1. 
2. 
3. 
4. 
5. 

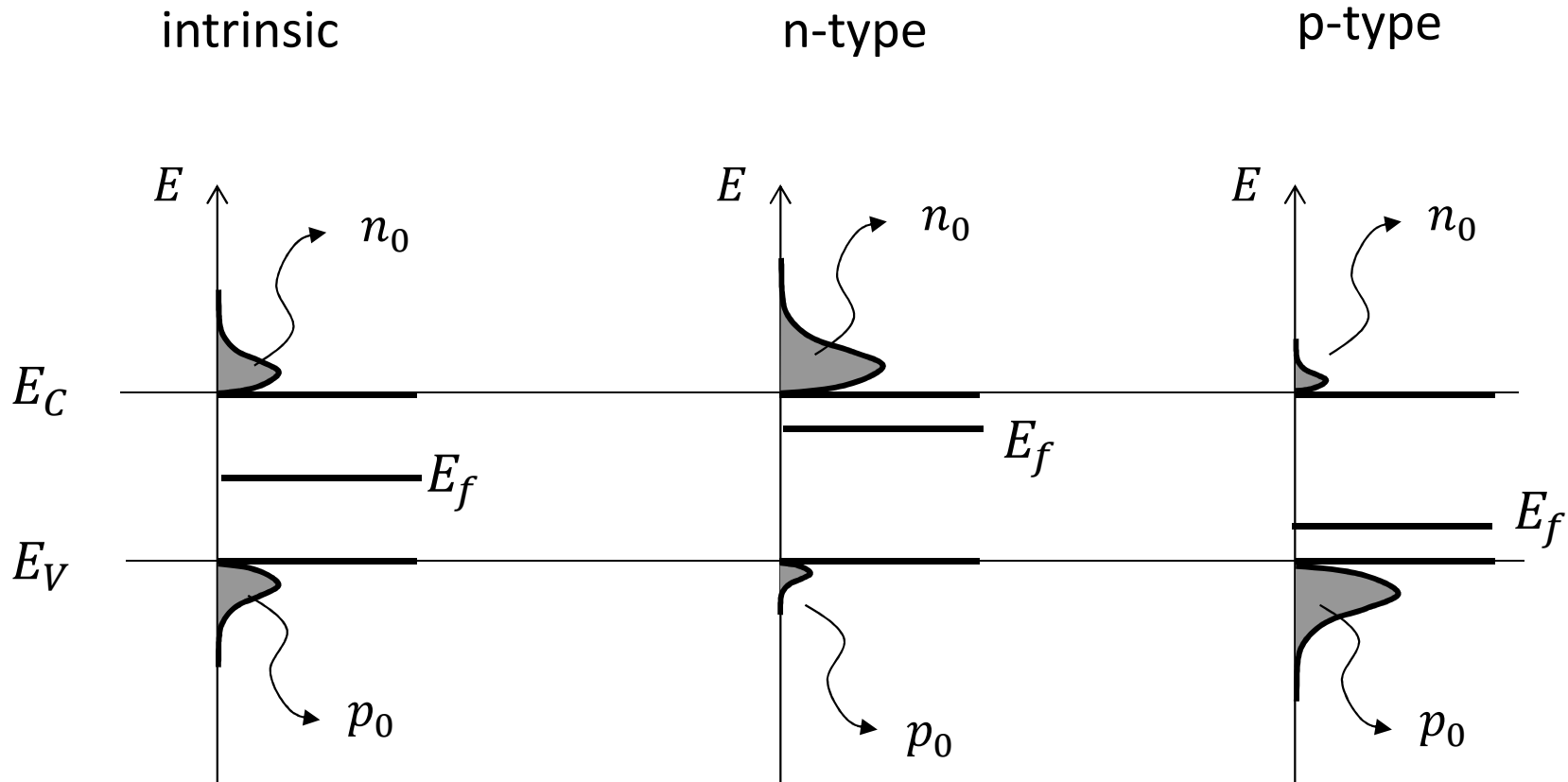






$$n_0 p_0 = n_i^2$$

$$n_{i_Si} = 5.2 \times 10^{15} T^{3/2} e^{-E_G/2kT}$$


$$n_{i_Si}(T = 300K) = 1.08 \times 10^{10} \text{ cm}^{-3}$$

$$n_{i_Si}(T = 600K) = 1.54 \times 10^{15} \text{ cm}^{-3}$$

Drift

- 1. 
- 2. 
- 3. 
- 4. 
- 5. 

Electric field


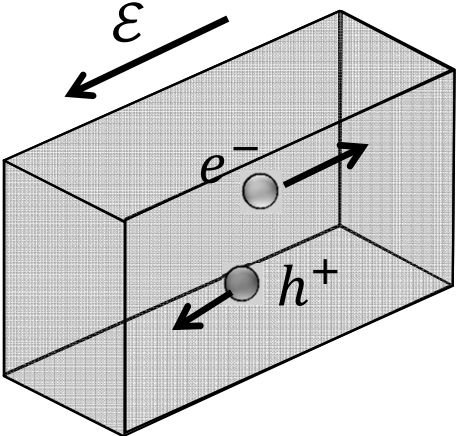


$$v_e = -\mu_n \mathcal{E}$$

$$v_h = \mu_p \mathcal{E}$$

→

gravitational field

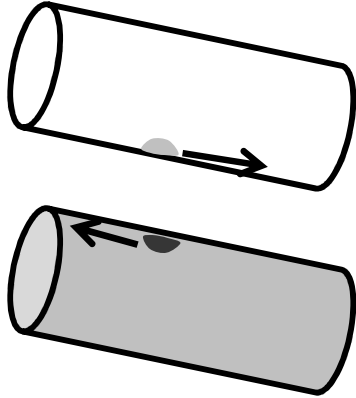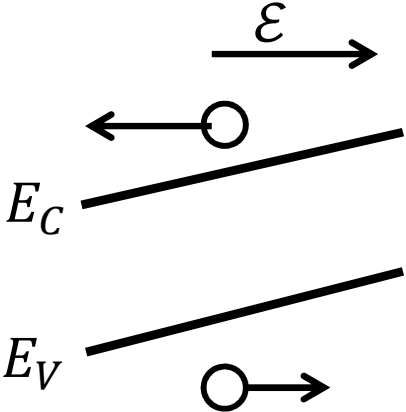






$$J = qn\mu_n \mathcal{E} + qp\mu_p \mathcal{E}$$


$$\mu_n = 1350 \text{ cm}^2/\text{Vs}$$

$$\mu_p = 480 \text{ cm}^2/\text{Vs}$$

Velocity Saturation at high fields!

Diffusion

1. 
2. 
3. 
4. 
5. 

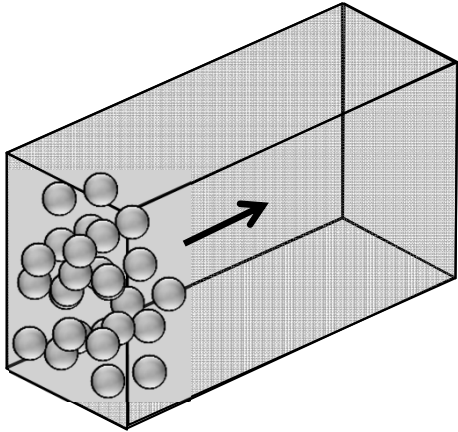

Charges move to be evenly distributed throughout space. Similar to perfume in room or heat in a solid






$$J_n = qD_n \frac{dn}{dx}$$


$$J_p = -qD_p \frac{dp}{dx}$$

Einstein Relation






$$\frac{D}{\mu} = \frac{kT}{q}$$



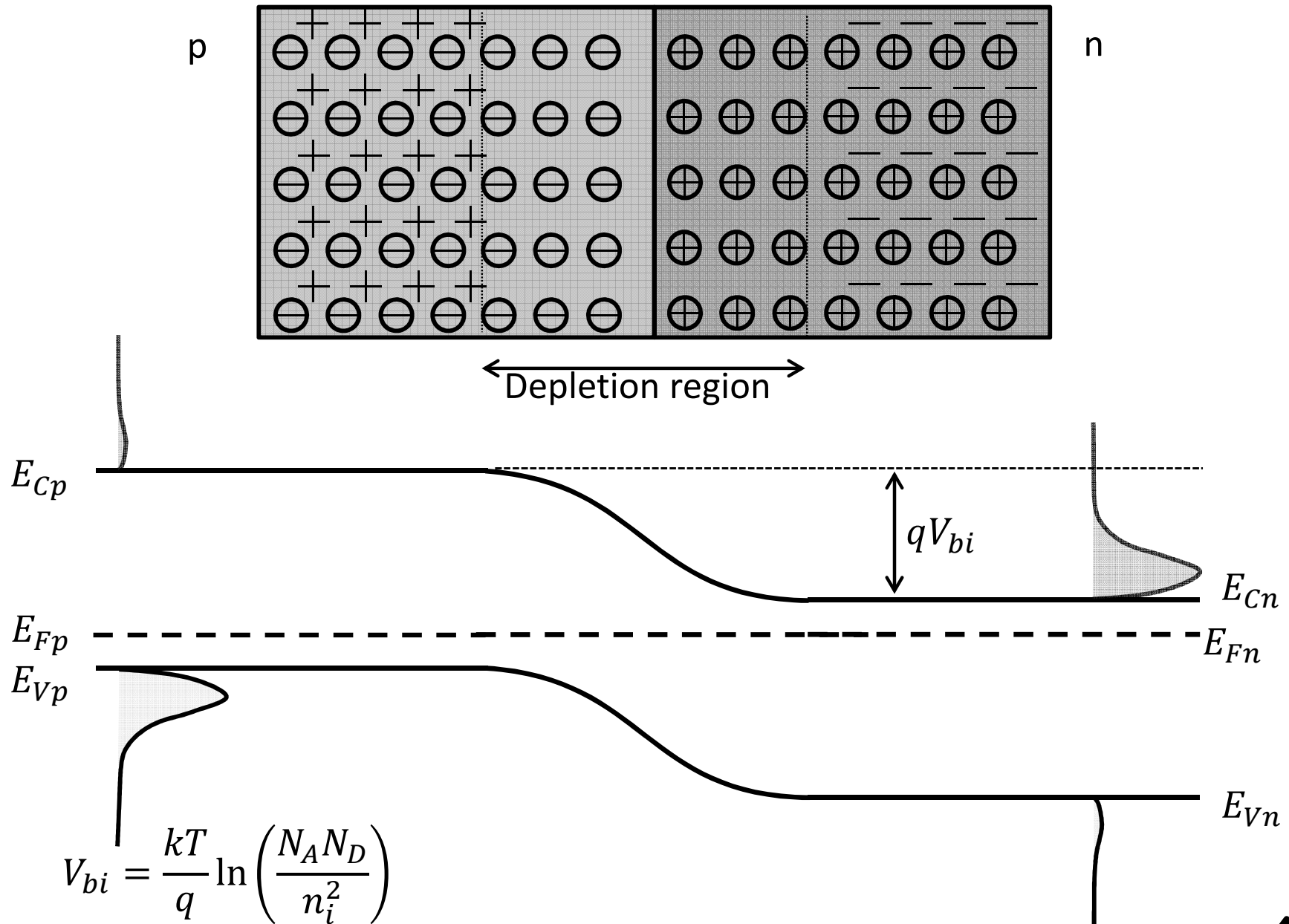
PN junctions

1. 
2. 
3. 
4. 
5. 




PN junctions

1. 
2. 
3. 
4. 
5. 

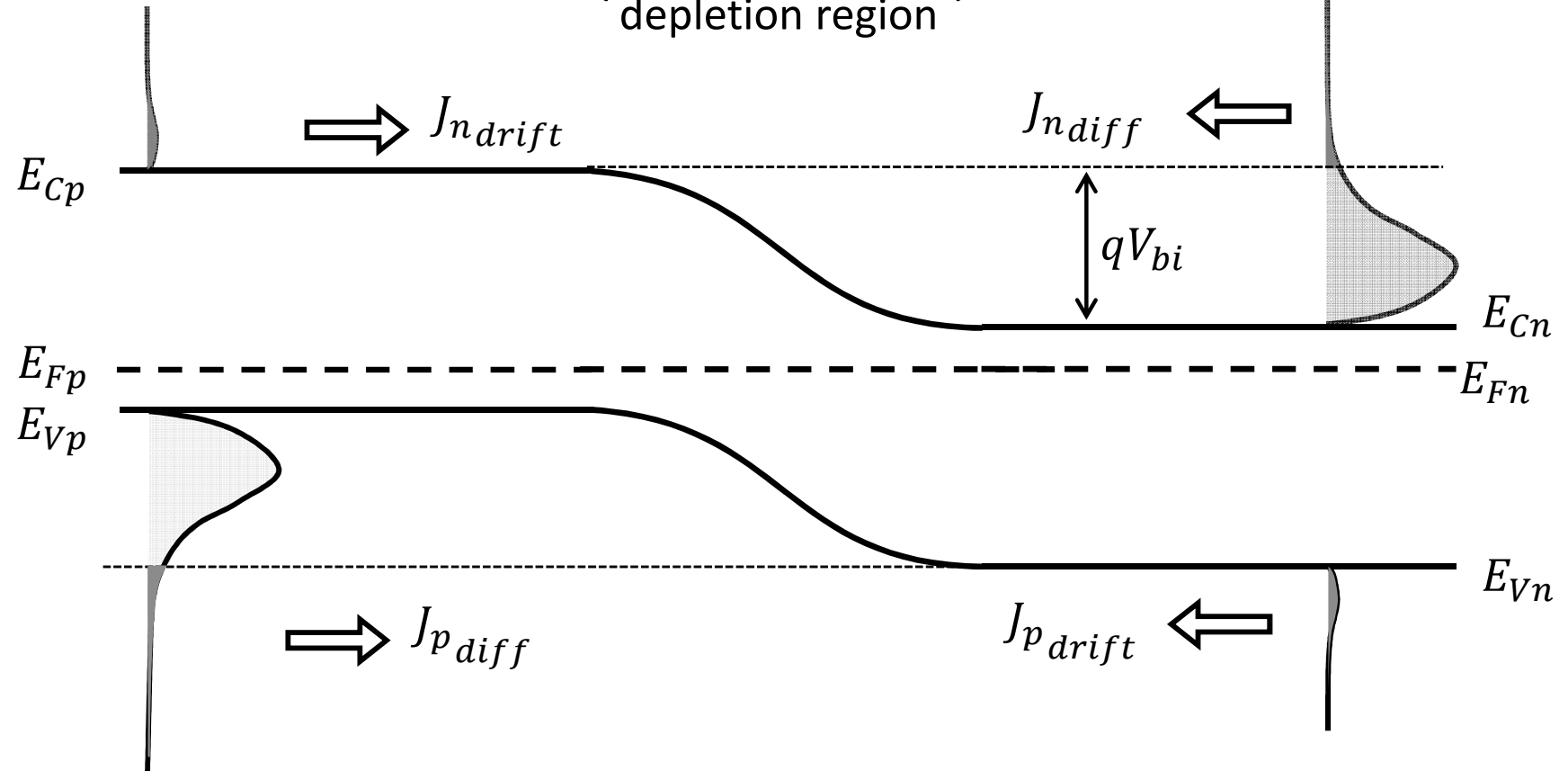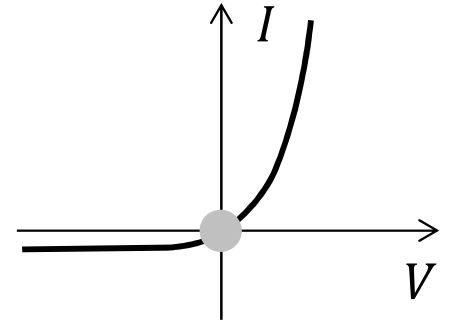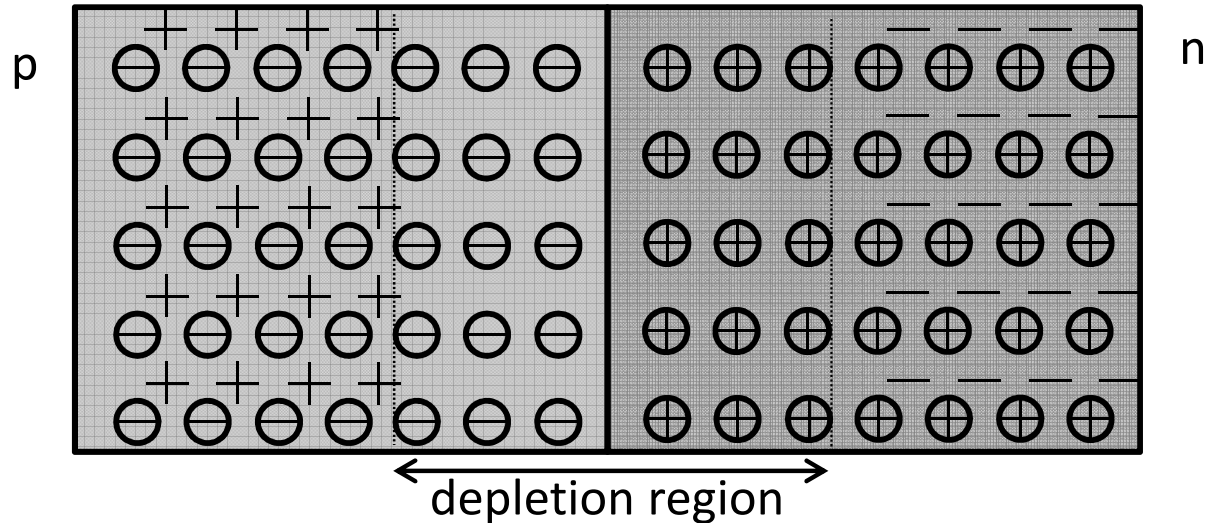



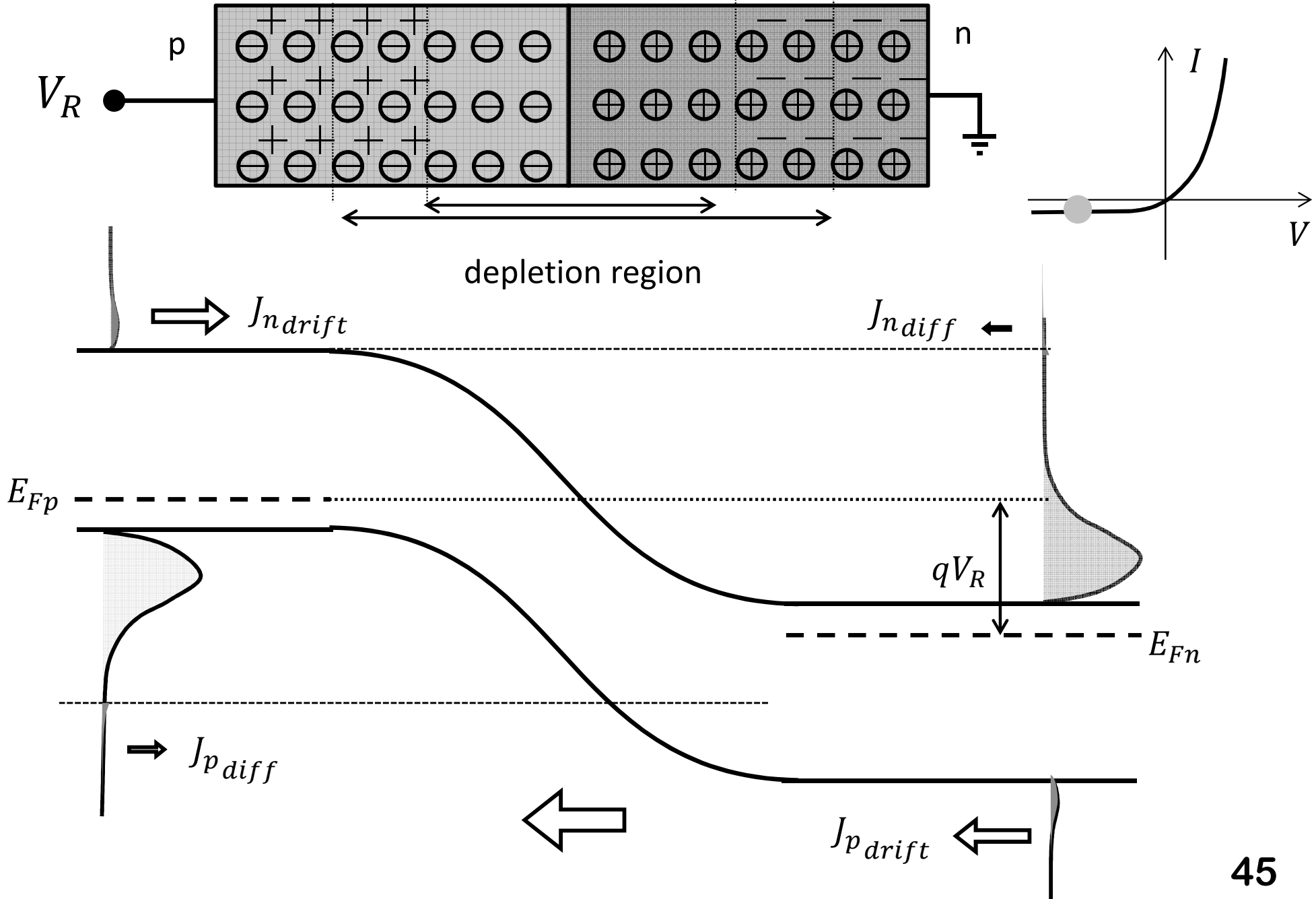


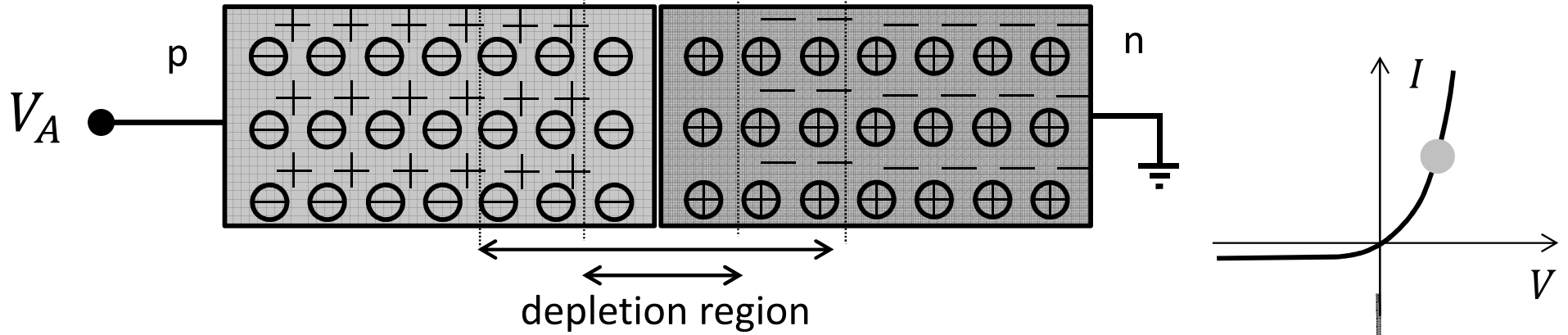
PN junctions , Reverse Biased

- 1.
- 2.
- 3.
- 4.
- 5.




PN junctions , Forward Biased

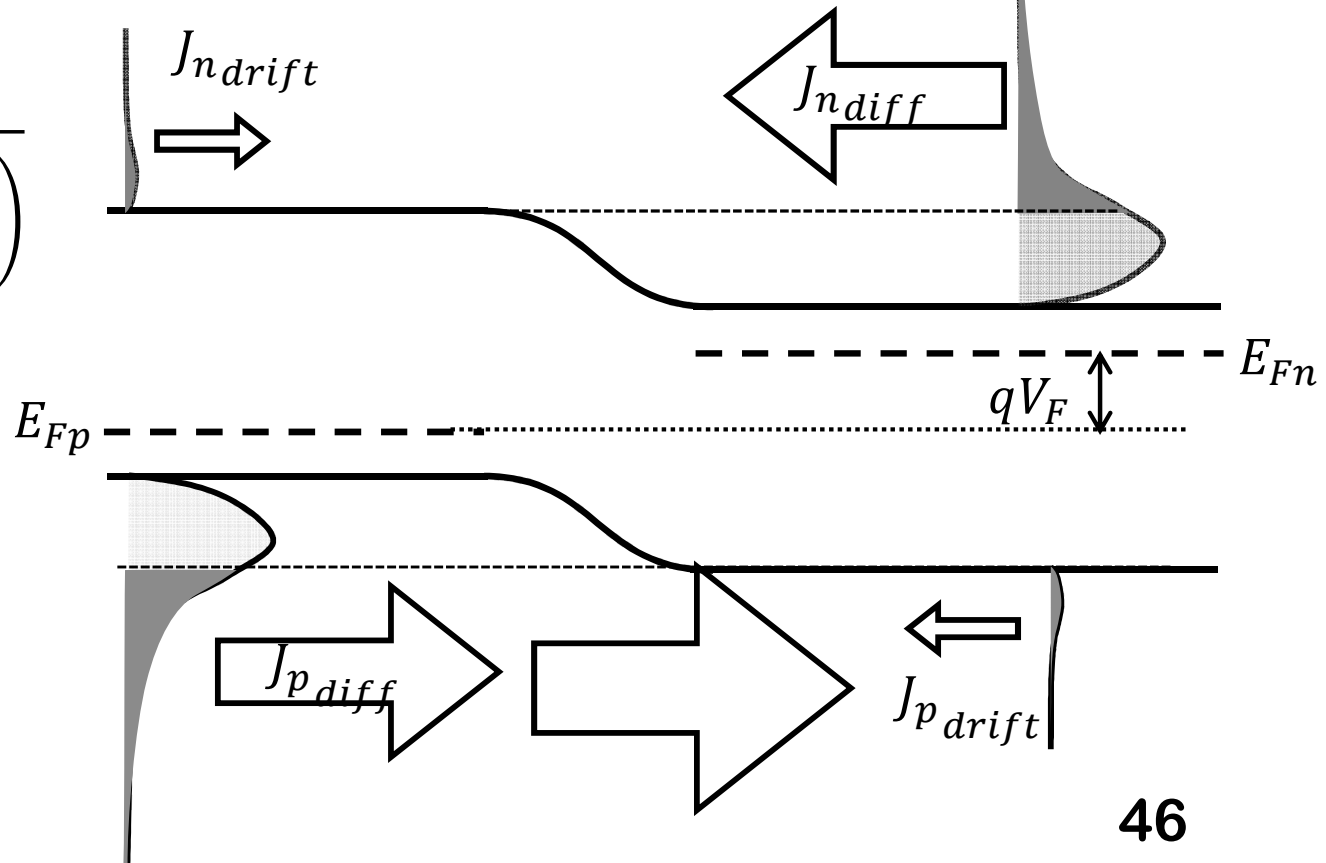
1. 
2. 
3. 
4. 
5. 




$$W = \sqrt{\frac{2\epsilon_s(V_{bi} - V_A)}{q} \left(\frac{1}{N_D} + \frac{1}{N_A} \right)}$$




W vs. Va

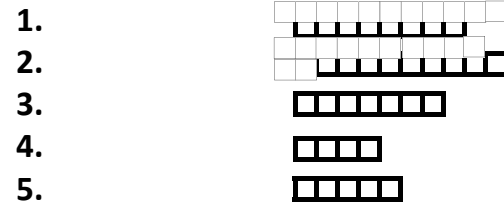

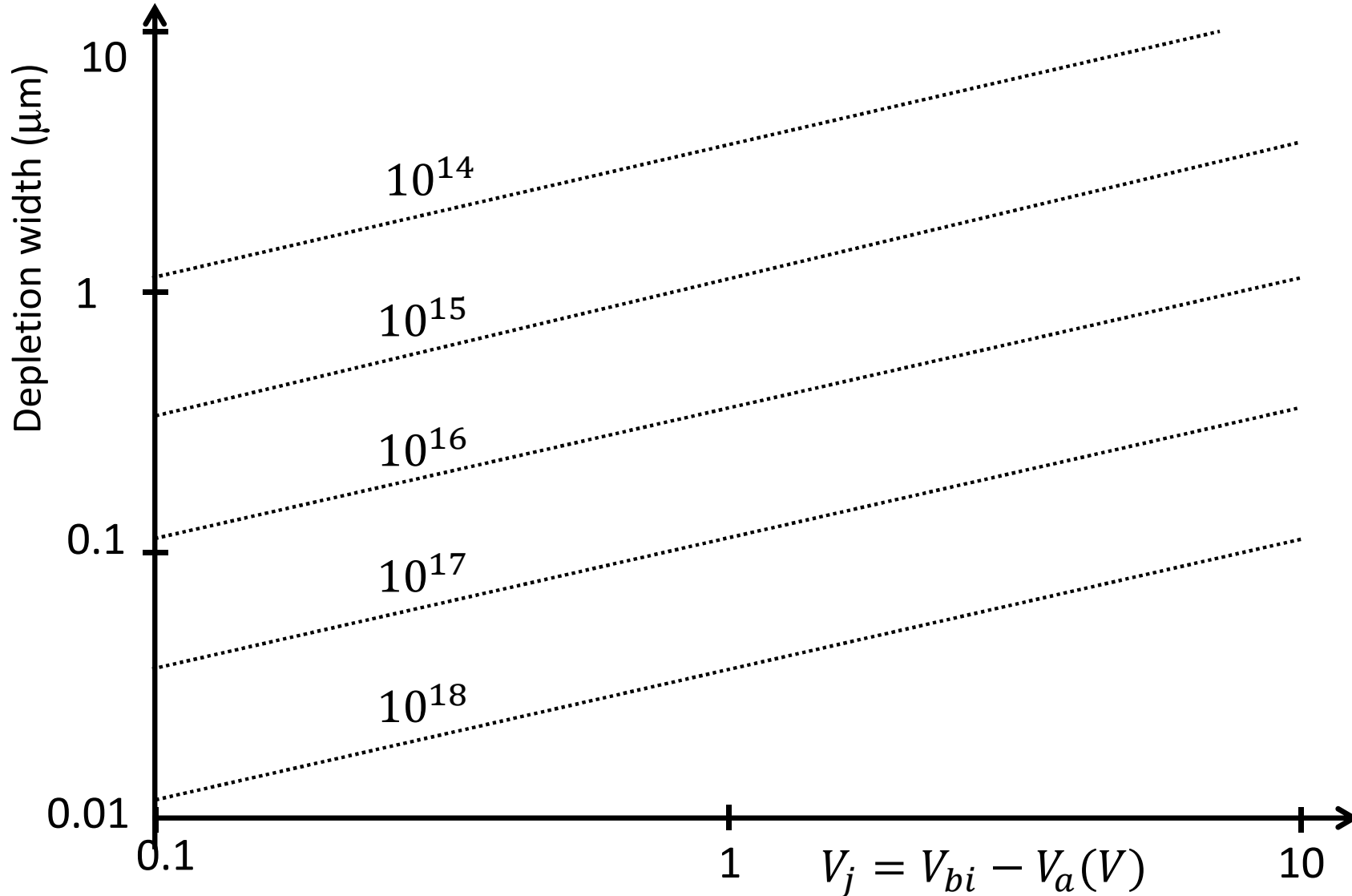
The junction width for one-sided step junctions in silicon as a function of junction voltage with the doping on the lightly doped side as a parameter.





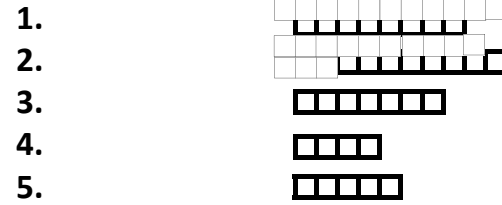


W vs. Na

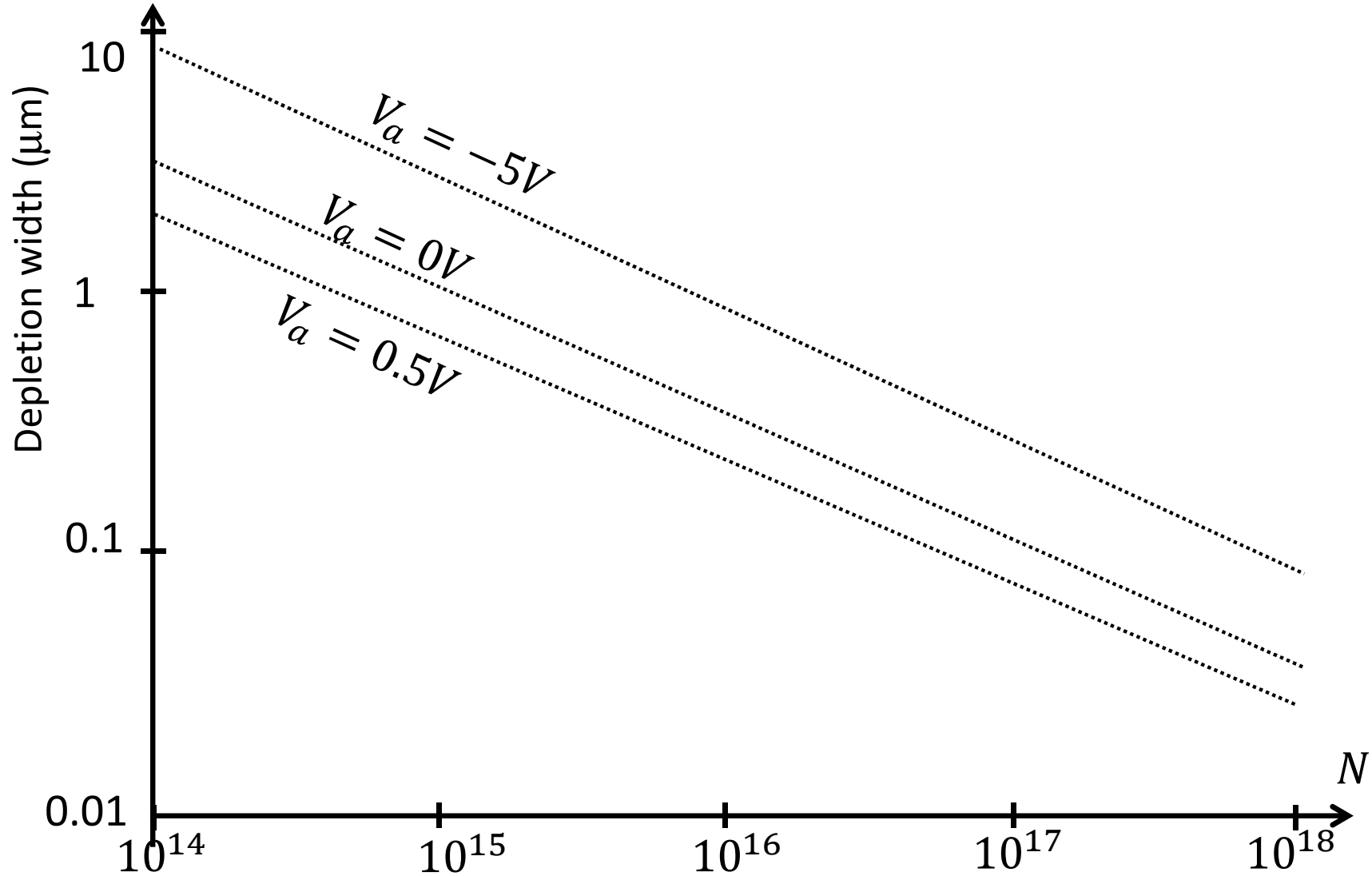


Junction width for a one-sided junction is plotted as a function of doping on the lightly doped side for three different operating voltages.



pn Junction: I-V Characteristic

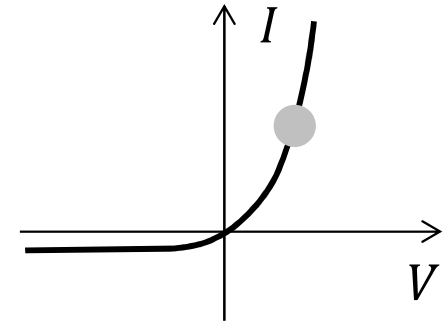1. 
2. 
3. 
4. 
5. 



$$I = qA \left(\frac{D_n n_i^2}{L_n N_A} + \frac{D_p n_i^2}{L_p N_D} \right) (e^{qV/kT} - 1)$$
$$= I_S (e^{qV/kT} - 1)$$



$$\left. \begin{array}{l} T = 300K \\ A = 100 \mu m^2 \\ L_p = 30 \mu m, L_n \\ = 20 \mu m, \end{array} \right\} I_S = 1.77 \times 10^{-17} A$$

Small signal model

1.
2.
3.
4.
5.

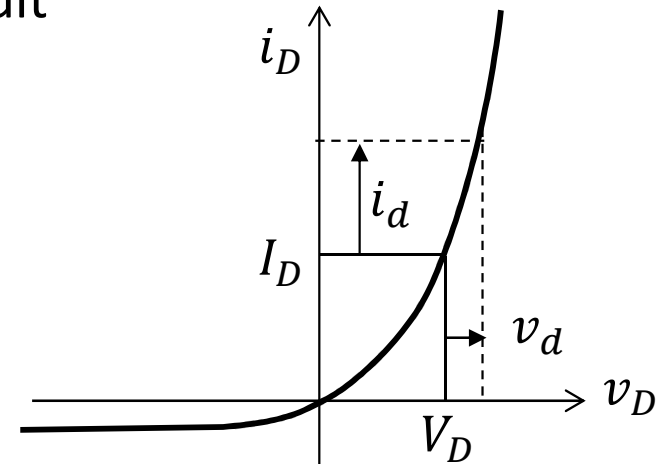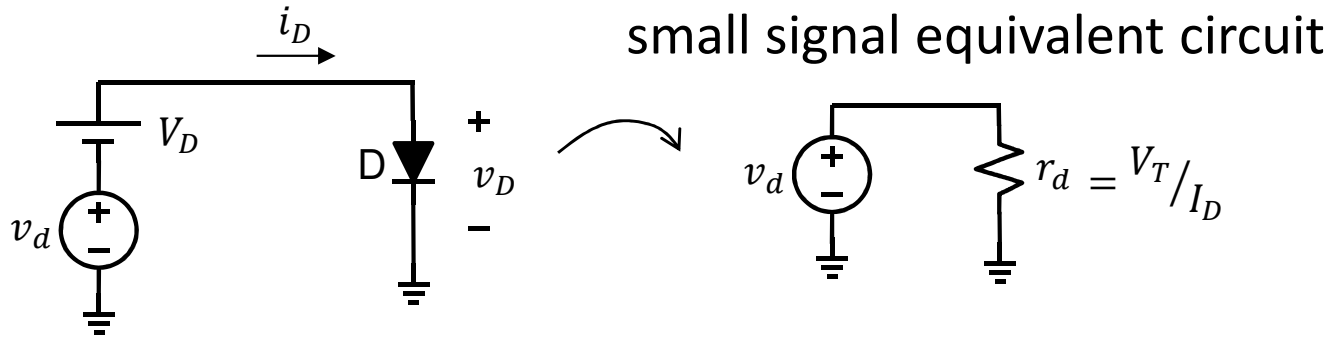

$$i_D = I_s (e^{qv_D/kT} - 1)$$

$$\cong I_s e^{v_D/V_T}$$

$$= I_s e^{v_D/V_T} e^{\hat{v}_i \sin \omega t / V_T}$$

$$= I_s e^{v_D/V_T} \left(1 + \frac{\hat{v}_i \sin \omega t}{V_T} + \dots \right)$$

$$\cong I_s e^{v_D/V_T} \left(1 + \frac{\hat{v}_i \sin \omega t}{V_T} \right)$$

$$I_D + i_d = I_s e^{v_D/V_T} \left(1 + \frac{v_d}{V_T} \right)$$

$$i_d = I_D \frac{v_d}{V_T}$$

$$kT/q = V_T$$

$$i_D = I_D + i_d$$

$$v_D = V_D + v_d = V_D + \hat{v}_i \sin \omega t$$



BIG IFFFF!

$$\hat{v}_i \ll V_T$$



BJT Types and Definitions

1.
2.
3.
4.
5.



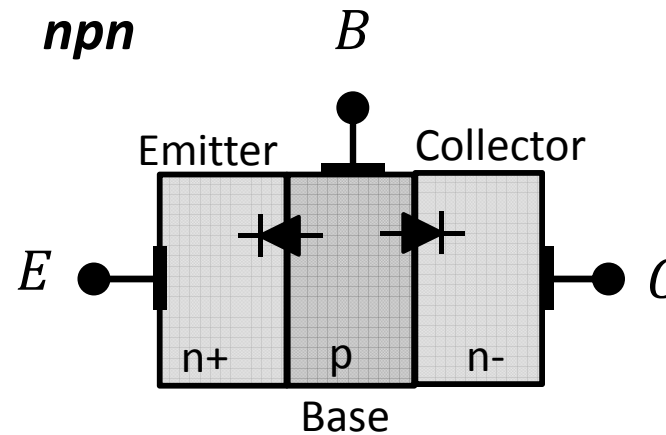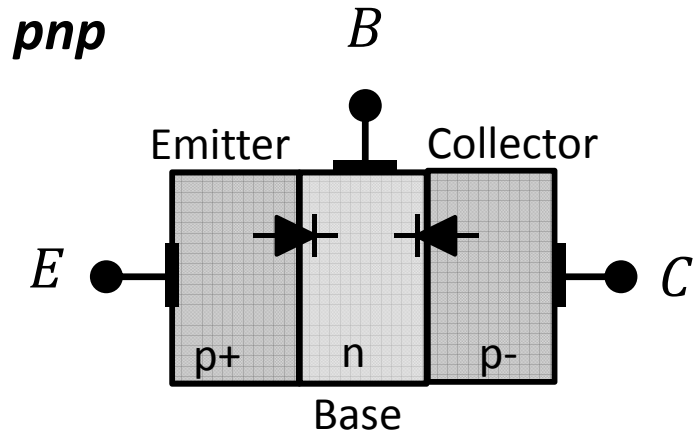

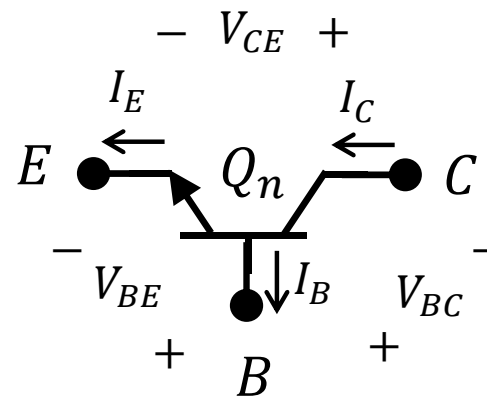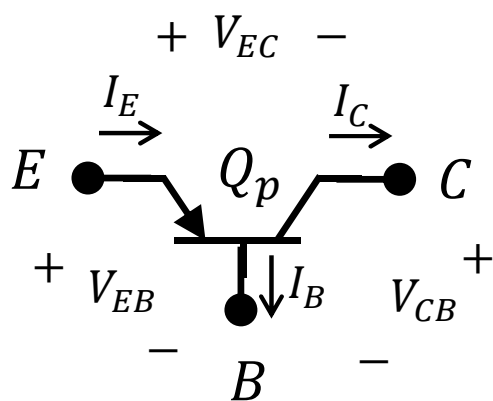
The BJT is a 3-terminal device, with two types: PNP and NPN










Asymmetric!





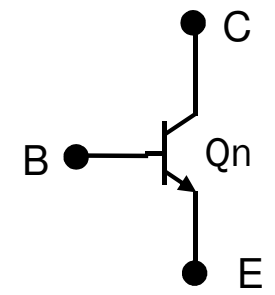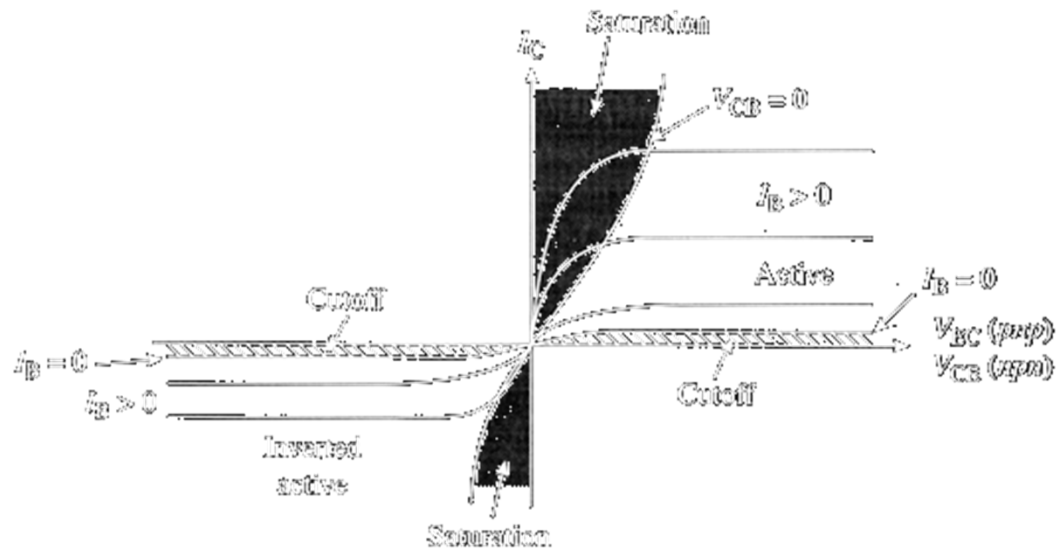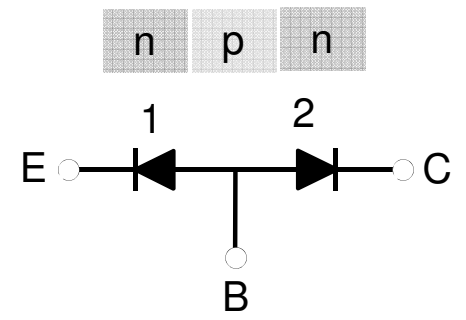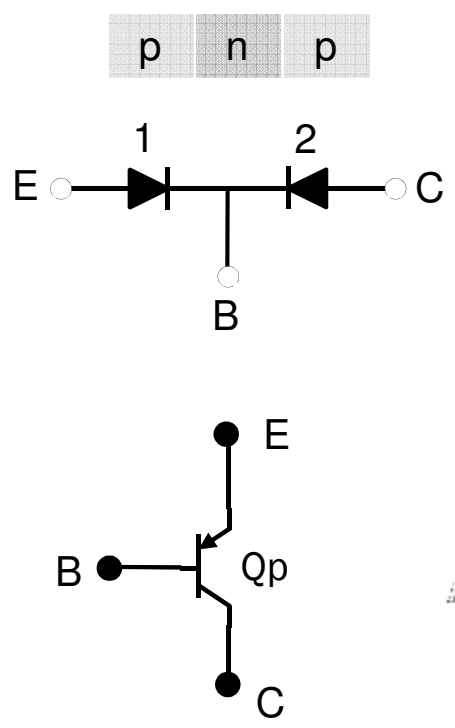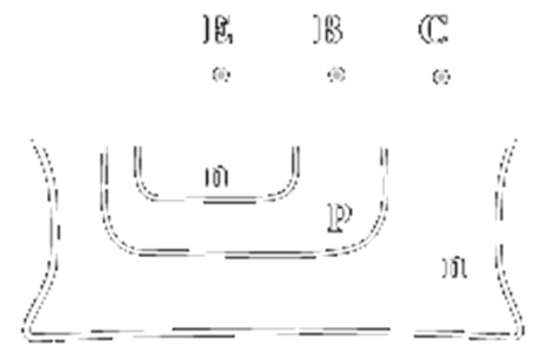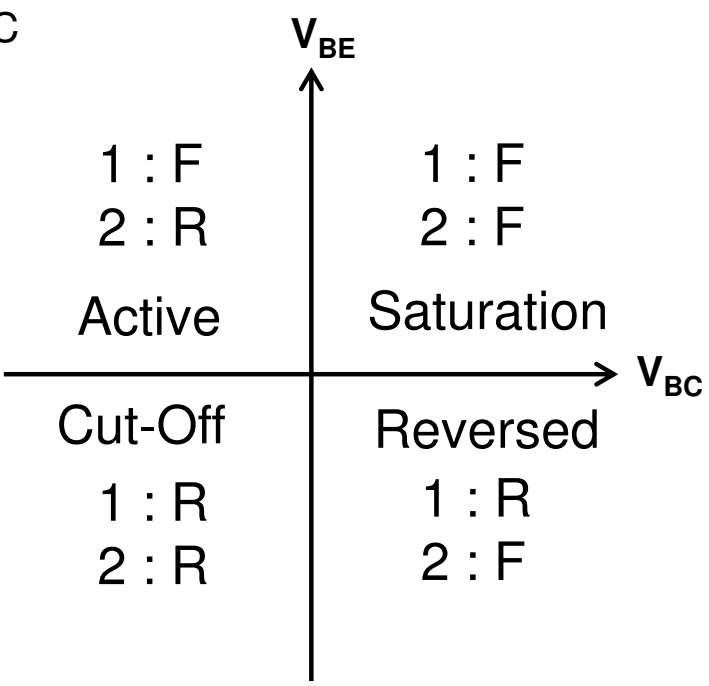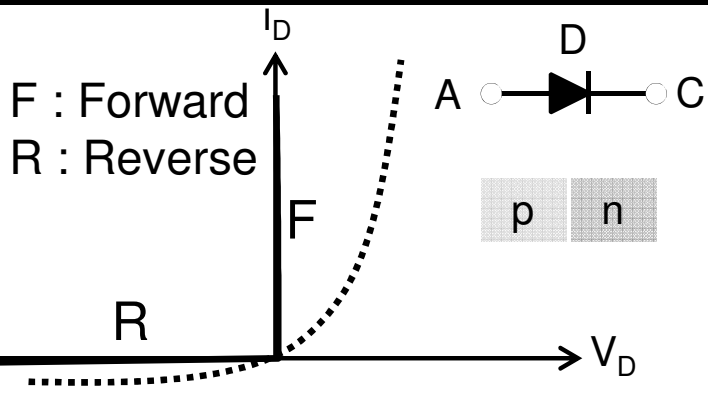


BJT: Bipolar Junction Transistor


1. 
2. 
3. 
4. 
5. 



BJT Electrostatics

- 1. 
- 2. 
- 3. 
- 4. 
- 5. 

pnp

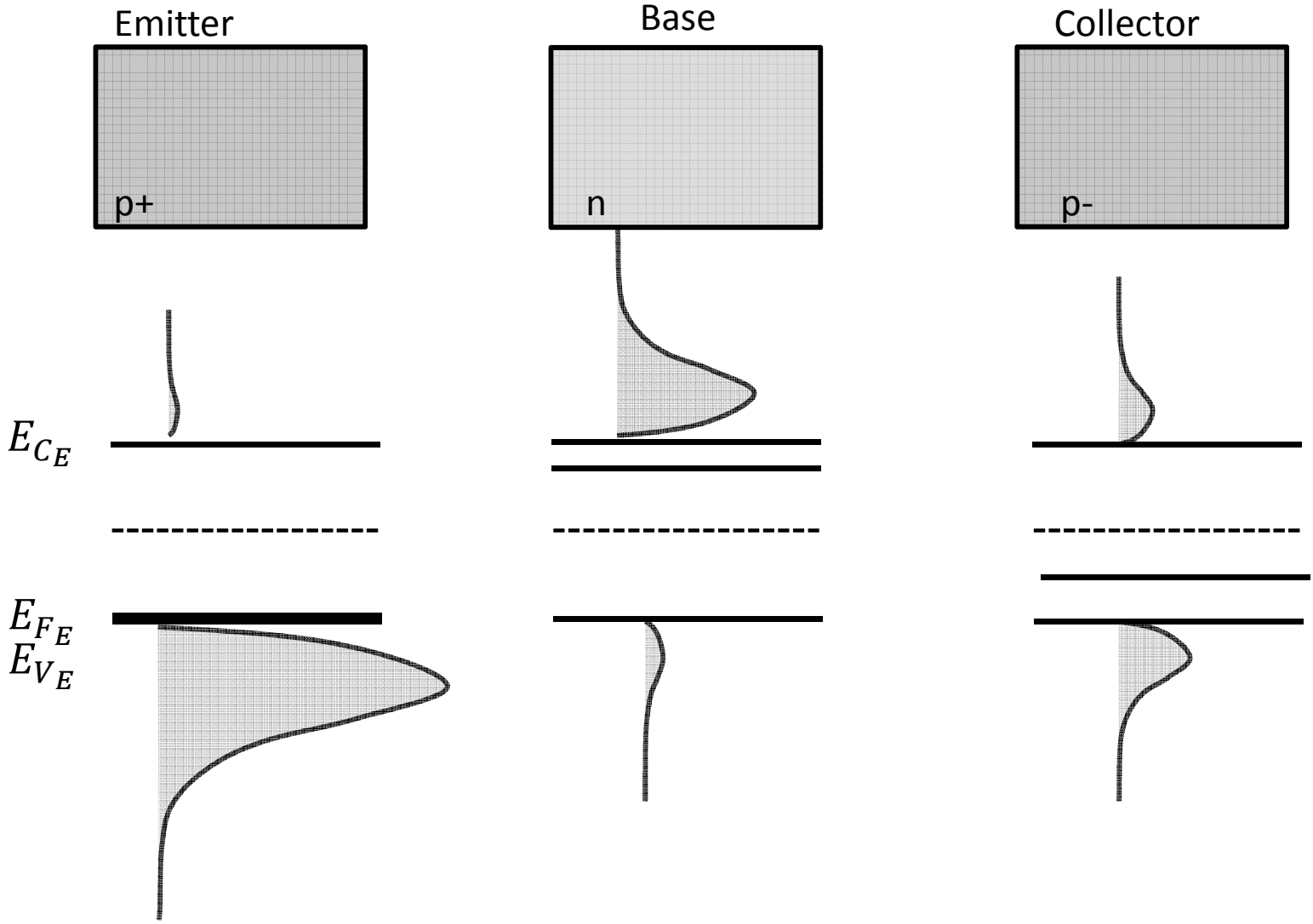


Under normal operating conditions, the BJT may be viewed electrostatically as two independent pn junctions

BJT Electrostatics



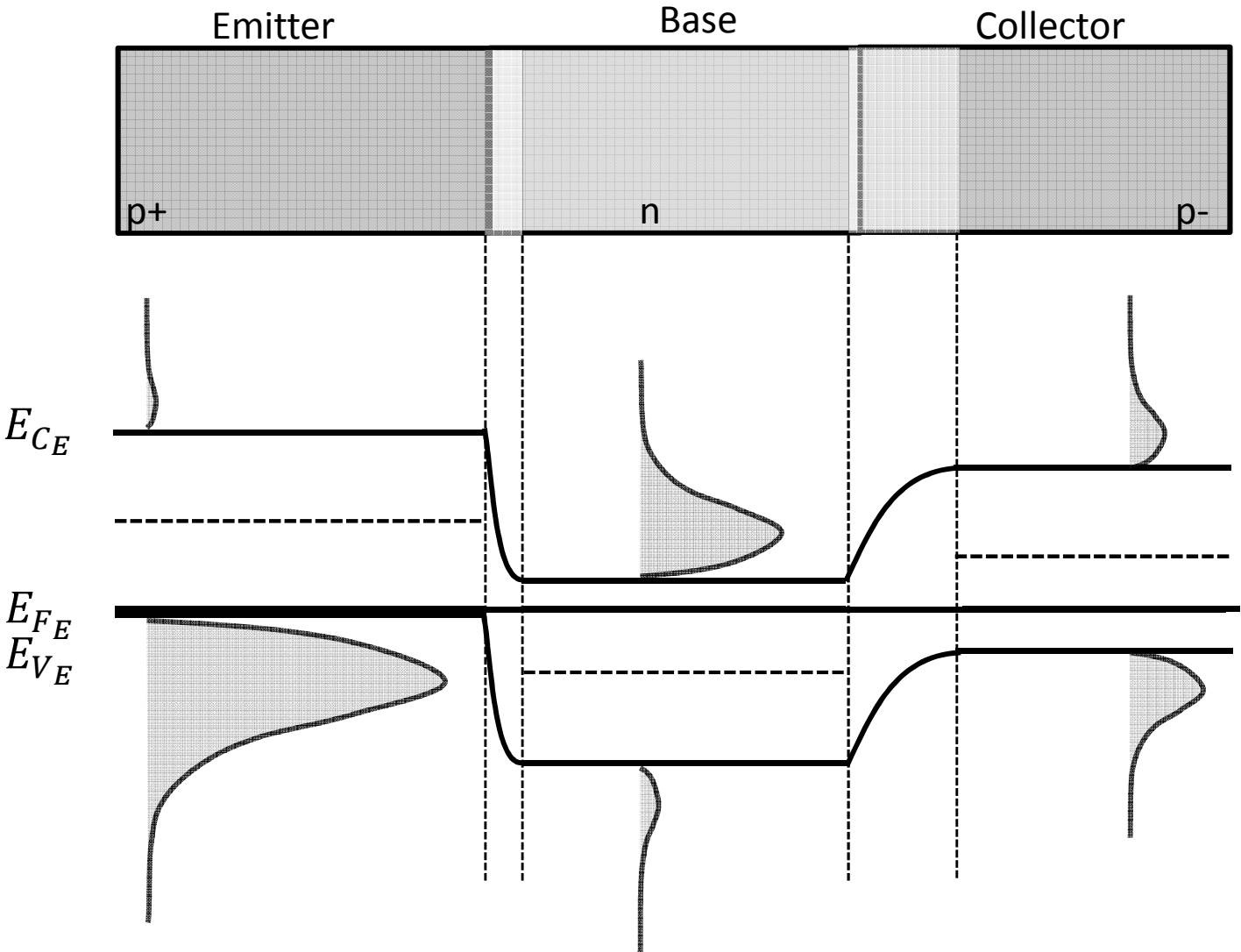


- 1.
- 2.
- 3.
- 4.
- 5.


*pn*p








Under normal operating conditions, the BJT may be viewed electrostatically as two independent pn junctions

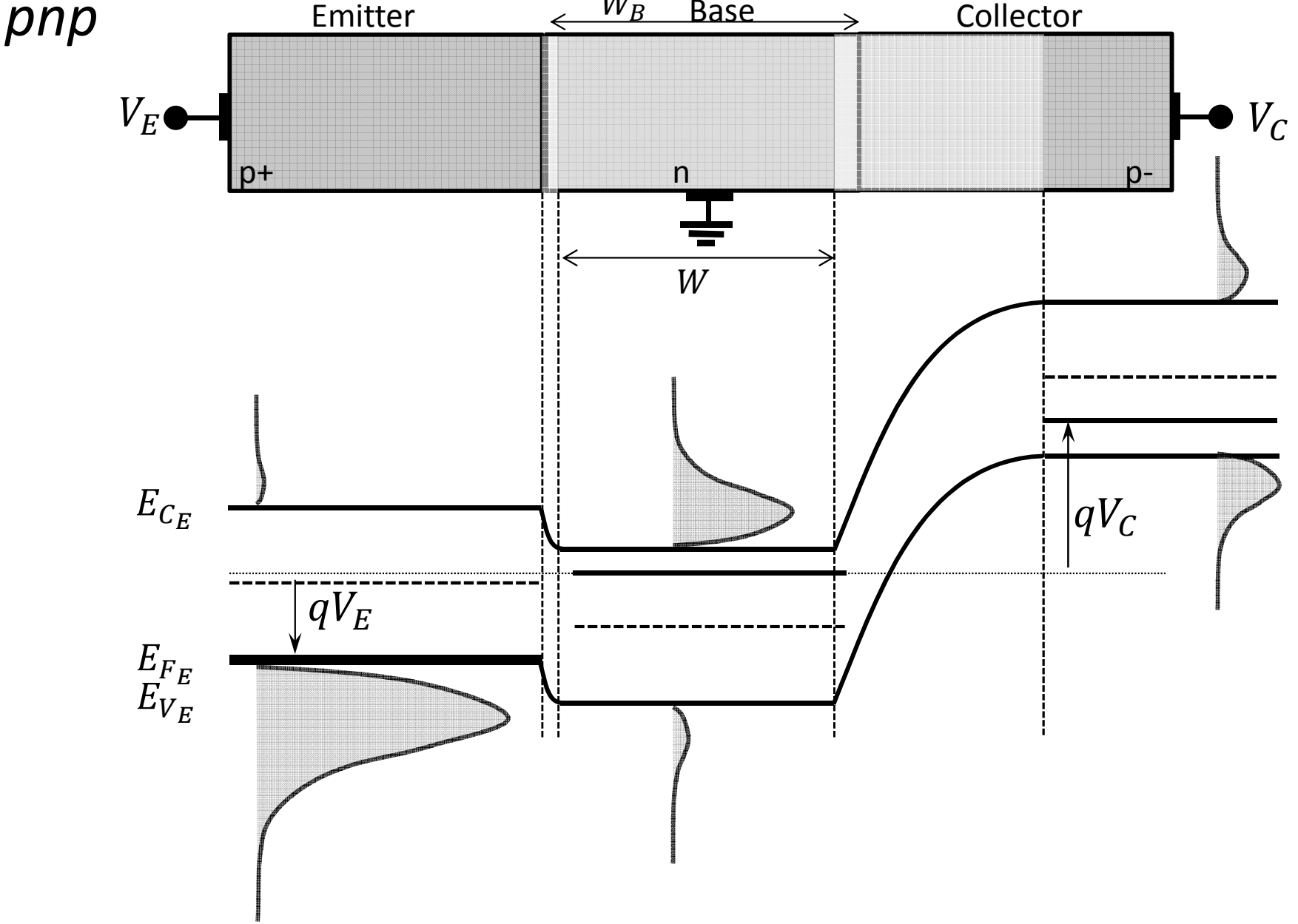
BJT Electrostatics

- 1. 
- 2. 
- 3. 
- 4. 
- 5. 




BJT Electrostatics

- 1. 
- 2. 
- 3. 
- 4. 
- 5. 

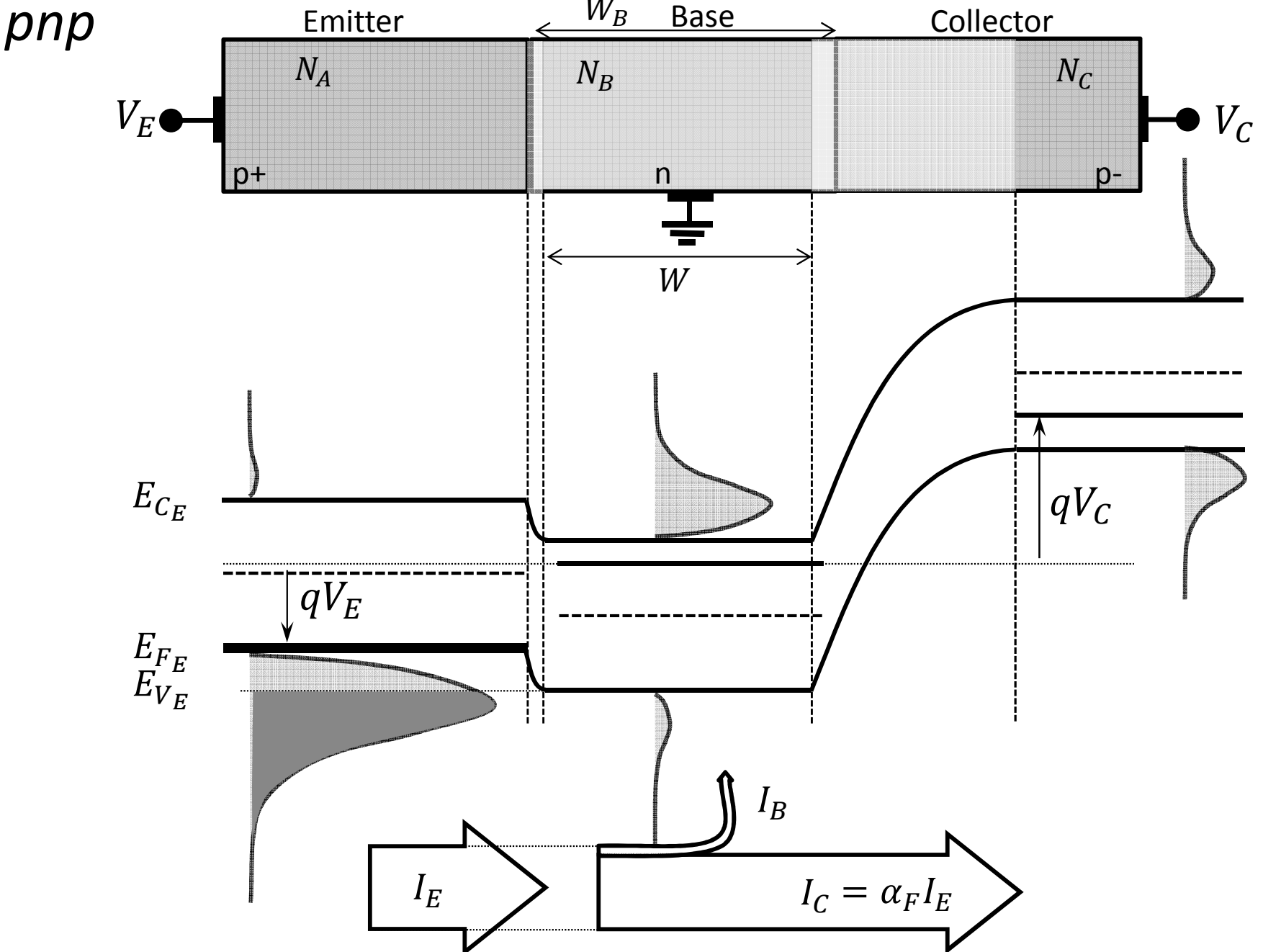

Collector Current (PNP)

1.
2.
3.
4.
5.

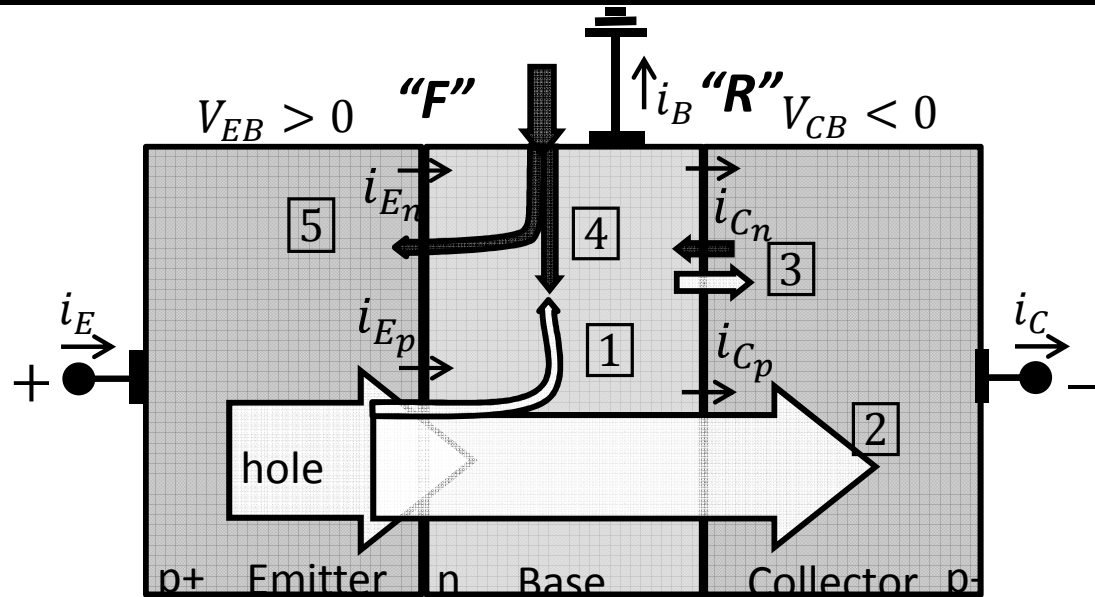

The collector current is comprised of:

- 2 Holes injected from emitter, which do not recombine in the base
- 3 Reverse saturation current of collector junction


$$I_C = \alpha_{dc} I_E + I_{CBO}$$

where I_{CBO} is the collector current which flows when $I_E = 0$






$$I_C = \alpha_{dc} (I_C + I_B) + I_{CBO}$$

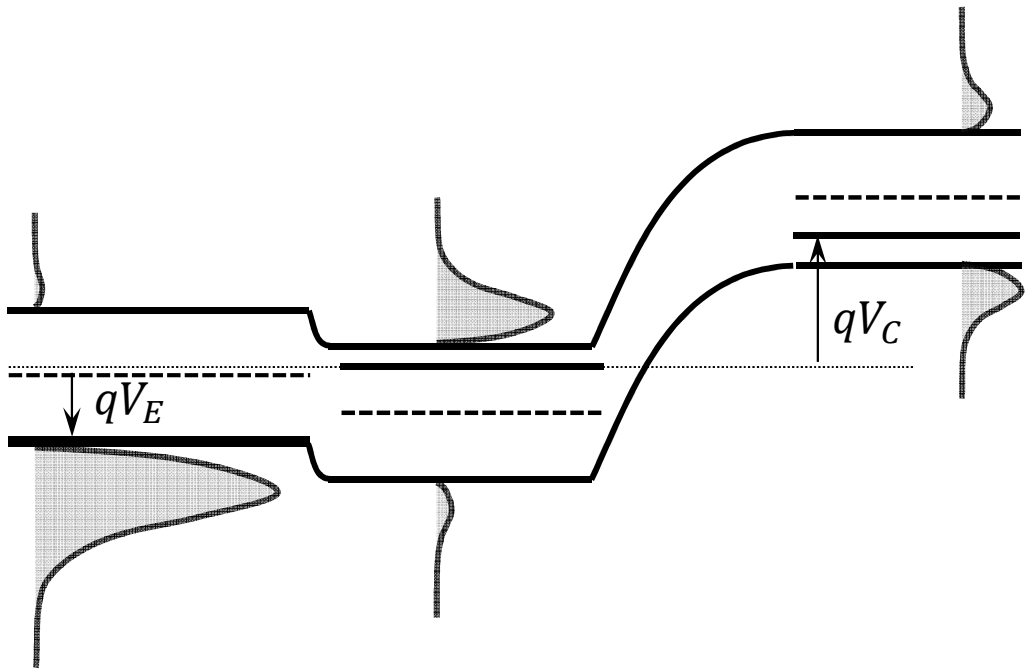
$$I_C = \frac{\alpha_{dc}}{1 - \alpha_{dc}} I_B + \frac{I_{CBO}}{1 - \alpha_{dc}}$$

$$= \beta I_B + I_{CEO}$$



BJT: Bipolar Junction Transistor



1. 
2. 
3. 
4. 
5. 

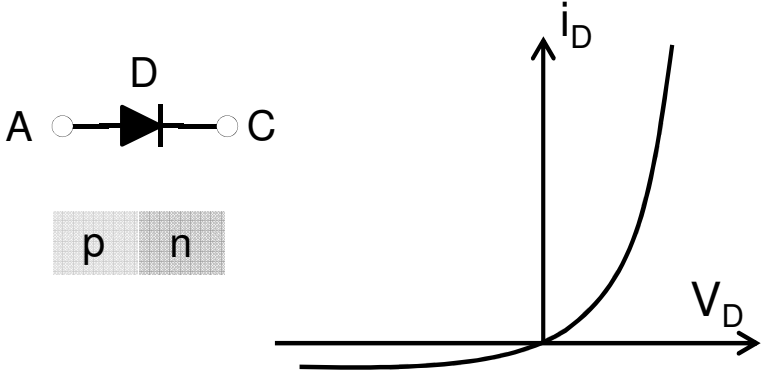

$$i_D \propto e^{v_D/nV_T}$$

$$\frac{\Delta v_D}{\Delta T} \approx -2 \frac{mV}{K} \Big|_{i_D=cte}$$
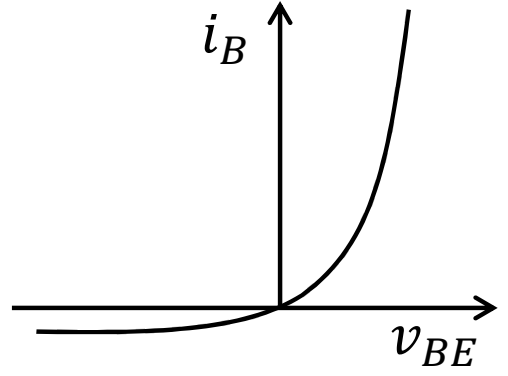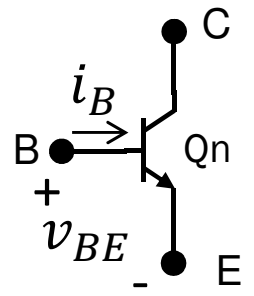
$$\frac{i_D(T_2)}{i_D(T_1)} \approx 2^{(T_2-T_1)/10K}$$




$$i_B \propto e^{v_{BE}/nV_T}$$

$$\frac{\Delta v_{BE}}{\Delta T} \approx -2 \frac{mV}{K} \Big|_{i_E=cte}$$


$$\frac{i_C(T_2)}{i_C(T_1)} \approx 2^{(T_2-T_1)/10K}$$

BJT Circuit Configurations


1.
2.
3.
4.
5.

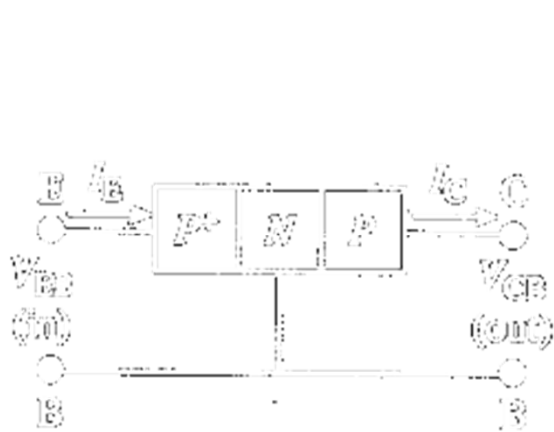

CB: Common Base

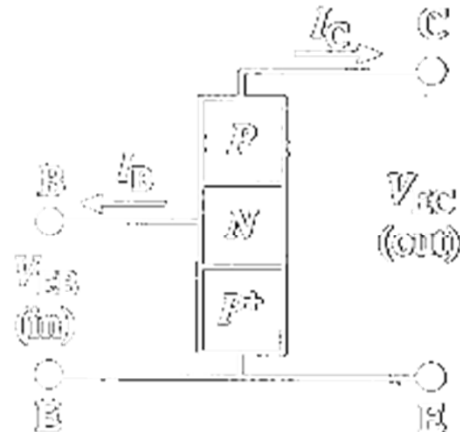


CE: Common Emitter

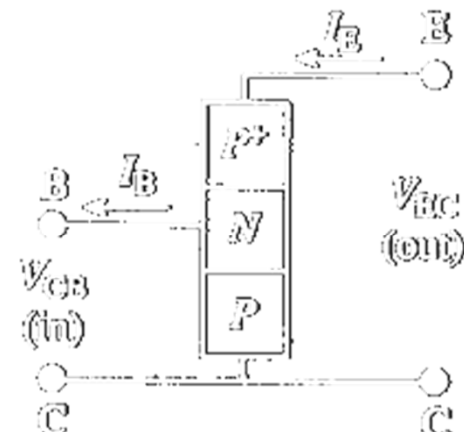





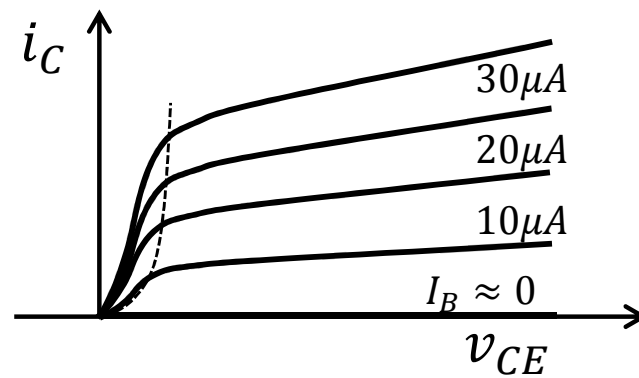

CC: Common Collector


Output Characteristics for Common-Emitter Configuration




BJT Configurations

1.  
2. 
3. 
4. 
5. 


CE: Common Emitter

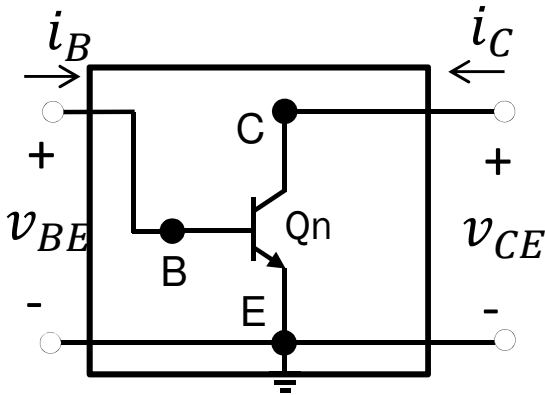

CB: Common Base

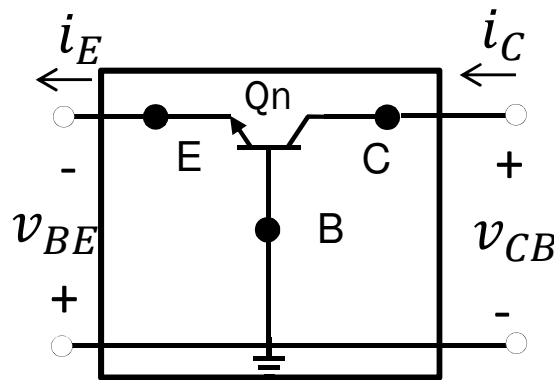

CC: Common Collector

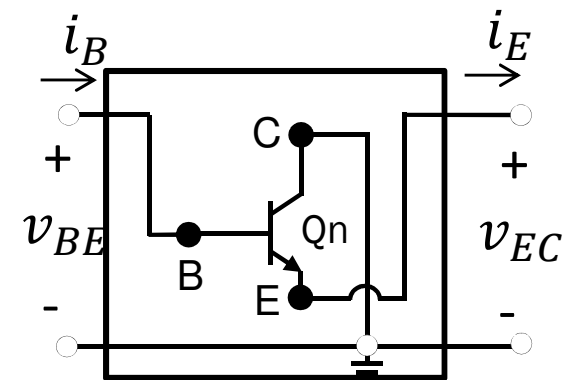

Input Characteristic

i_B vs. v_{BE} for different V_{CE}






Output Characteristic


i_C vs. v_{CE} for different V_{BE} or i_B

Transfer Characteristic


i_C vs. v_{BE} or i_B for different V_{CE}

CE: Common Emitter


1. 
2. 
3. 
4. 
5. 

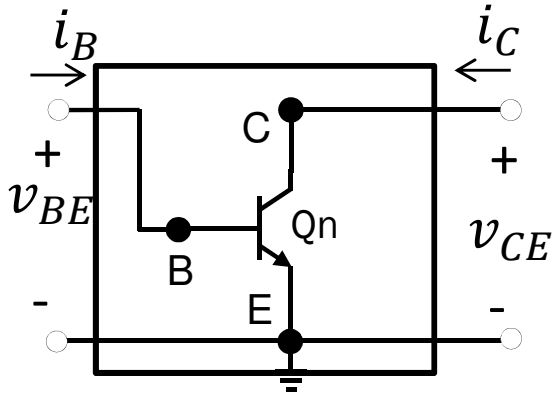

Input Characteristic

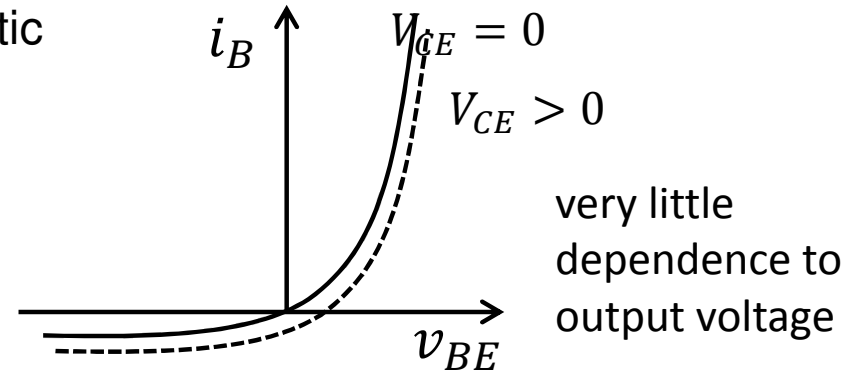


Output Characteristic

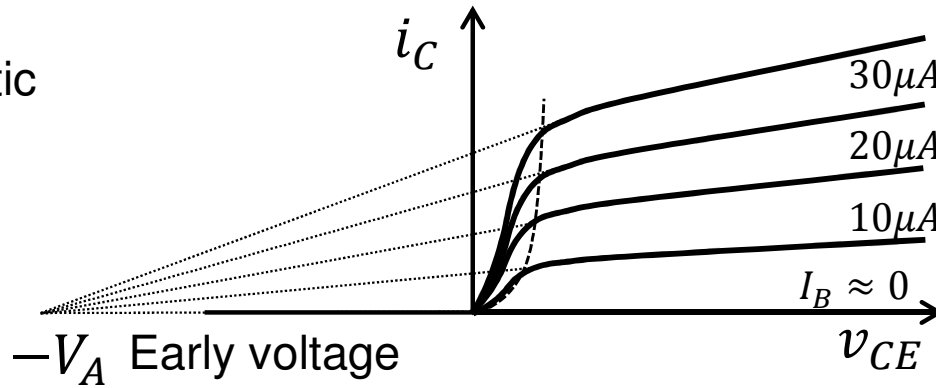

Active:
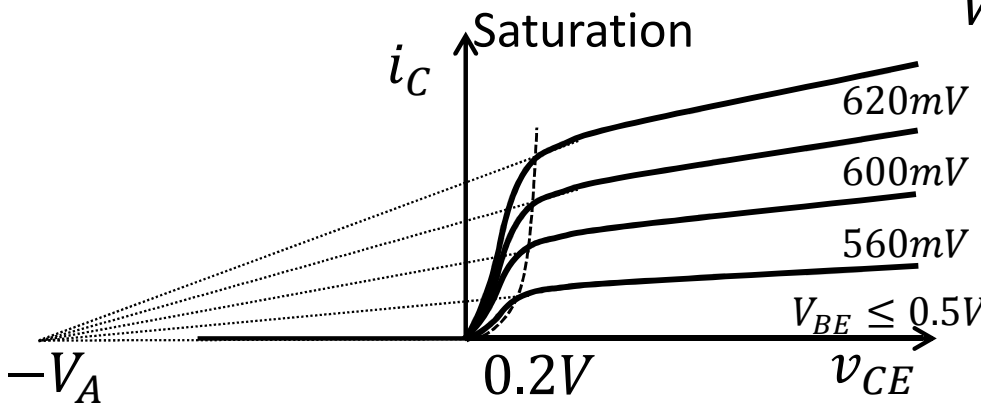
$$i_C = I_S e^{\frac{v_{BE}}{nV_T}} \left(1 + \frac{v_{CE}}{V_A}\right)$$






$V_{CE} \uparrow \rightarrow W \uparrow \rightarrow \beta \uparrow \rightarrow I_C \uparrow$





Active


Cut-Off

CE: Transistor Model



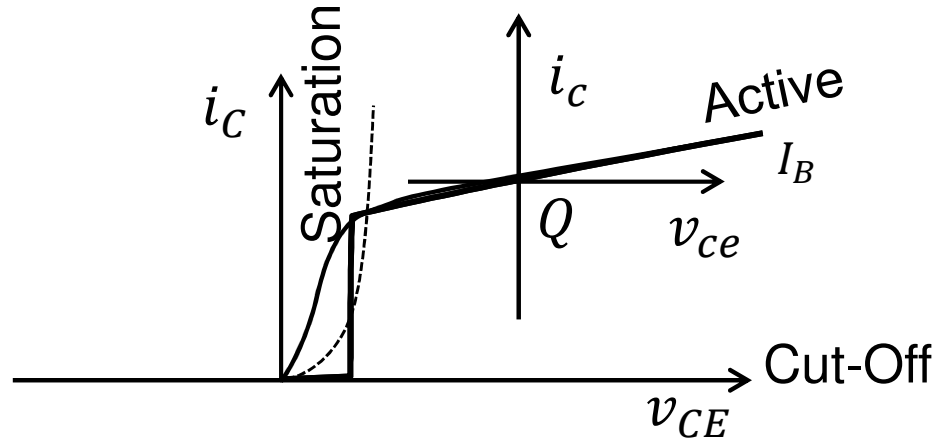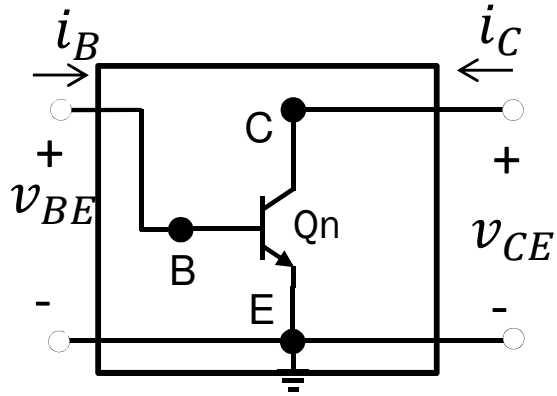


1. 
2. 
3. 
4. 
5. 


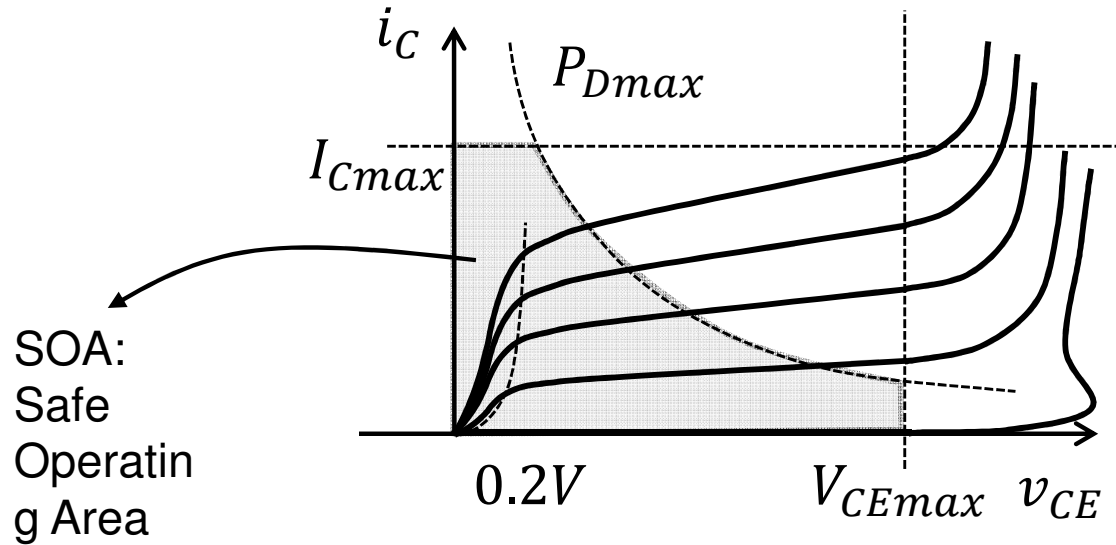


Output Characteristic



CE: Output Characteristic

1. 
2. 
3. 
4. 
5. 

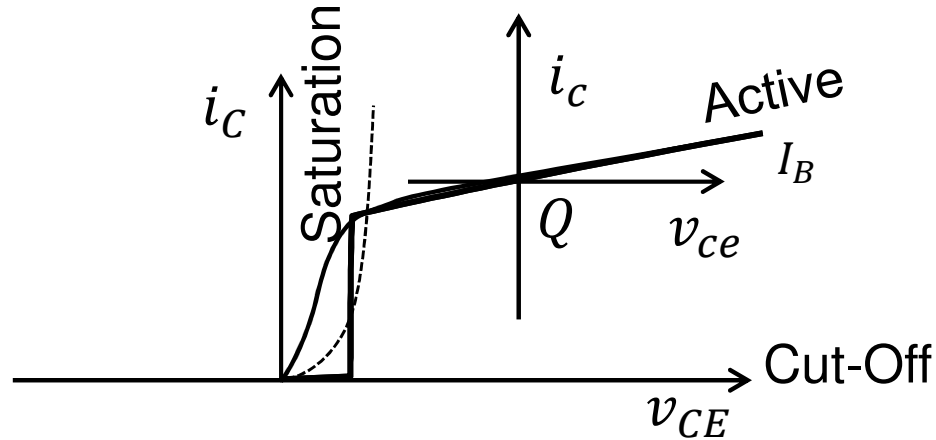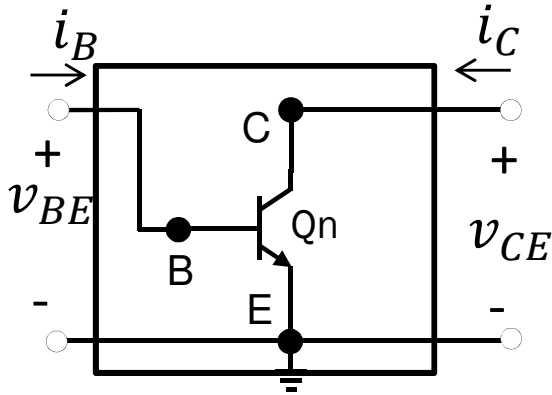

$$i_B = I'_S e^{\frac{v_{BE}}{nV_T}} \left(1 + \frac{v_{CE}}{V_A}\right)$$

$$i_C \approx I_S e^{\frac{v_{BE}}{nV_T}} \left(1 + \frac{v_{CE}}{V_A}\right)$$

$$i_B = \frac{I_S}{\beta} e^{\frac{v_{BE}}{nV_T}} \left(1 + \frac{v_{CE}}{V_A}\right)$$

Ideally linear:

$$\beta = \frac{i_C}{i_B} = \frac{I_C}{I_B} = \frac{i_c}{i_b}$$

$$BDC = \beta_{DC} = \left. \frac{i_C}{i_B} \right|_{I_C=I_Q} = \beta_F \left(1 + \frac{v_{CE}}{V_A}\right)$$



SPICE

$$BF = \beta_F = \left. \frac{i_C}{i_B} \right|_{V_{CB}=0}$$

$$BAC = \left. \frac{\partial i_C}{\partial i_B} \right|_{I_C=I_Q} = \frac{i_c}{i_b}$$


CE: Common Emitter

1.
2.
3.
4.
5.

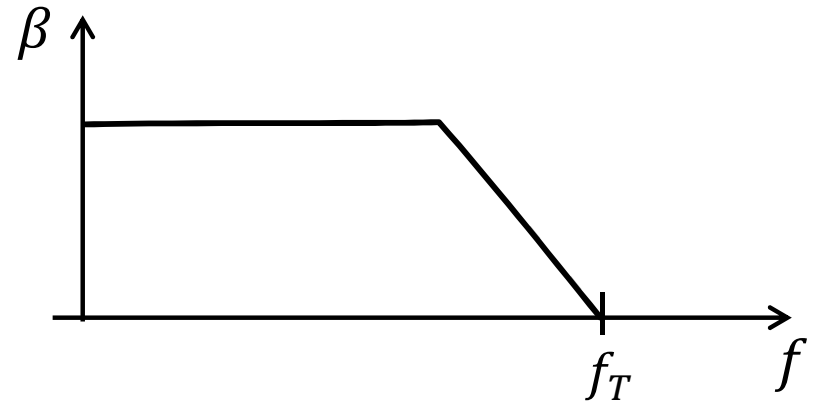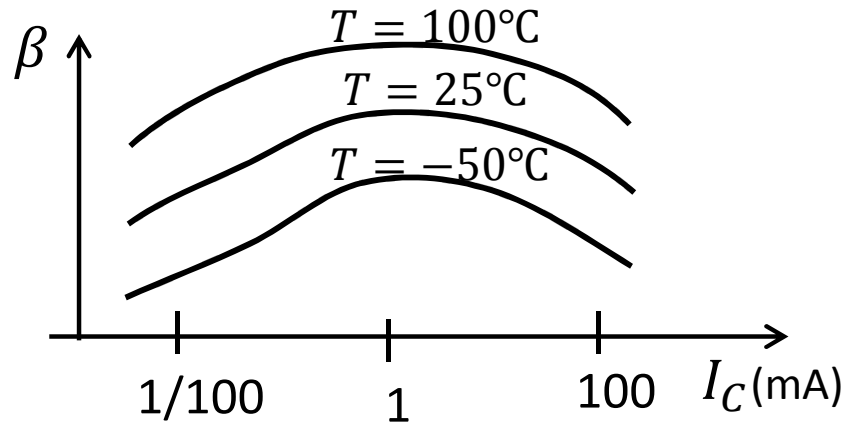


CB: Common Base


1.
2.
3.
4.
5.

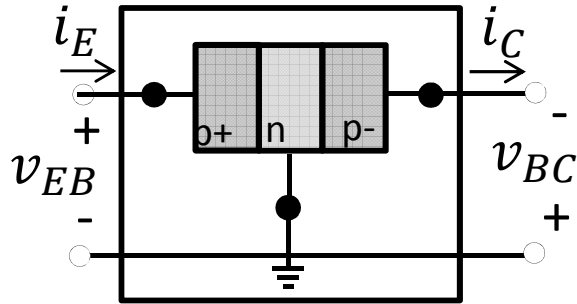

Input Characteristic

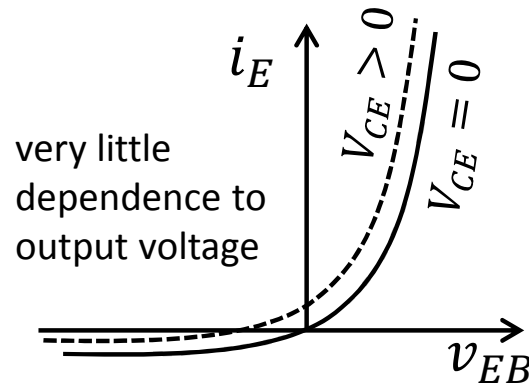


Output Characteristic

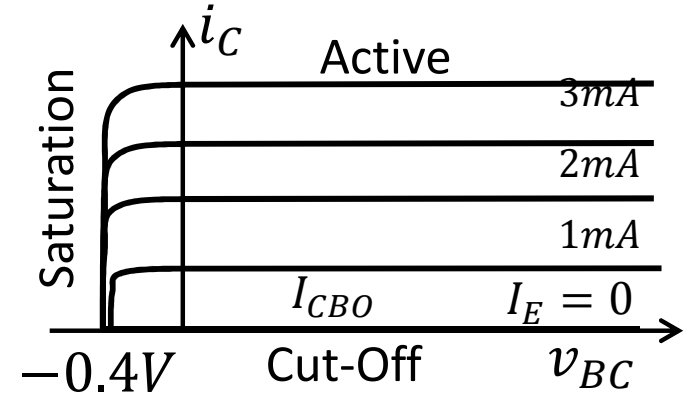

Active:

$$i_C = \alpha i_E$$

$$\alpha = \frac{\beta}{\beta + 1}$$

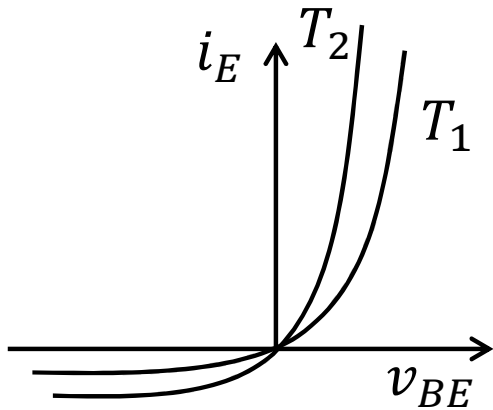


$$T_2 > T_1$$






$$\frac{\Delta v_{BE}}{\Delta T} \approx -2 \frac{mV}{K} \Big|_{i_E = cte}$$








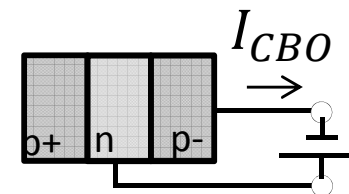
I_{CBO} Leakage current of BC diode

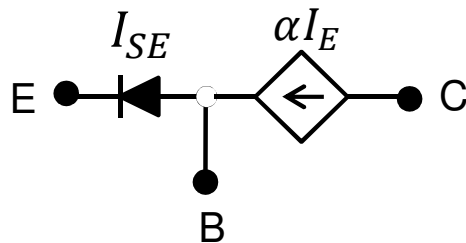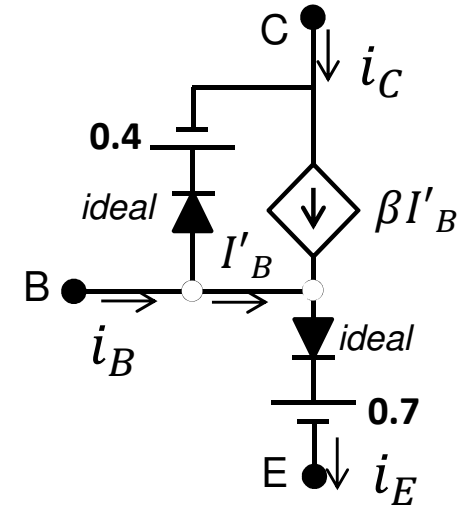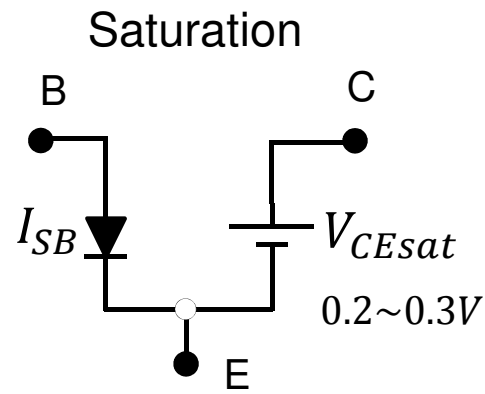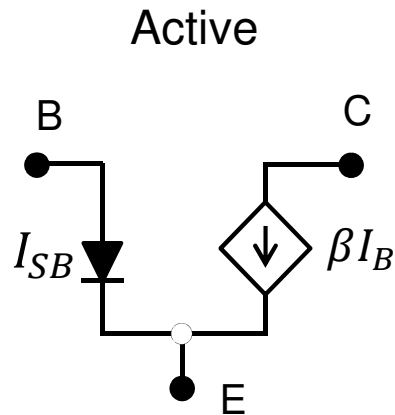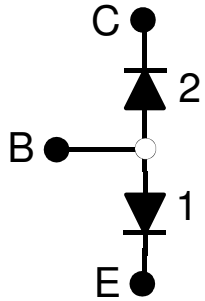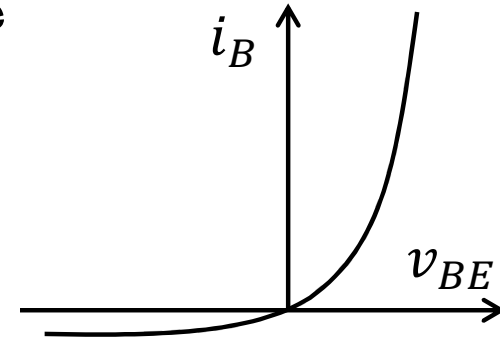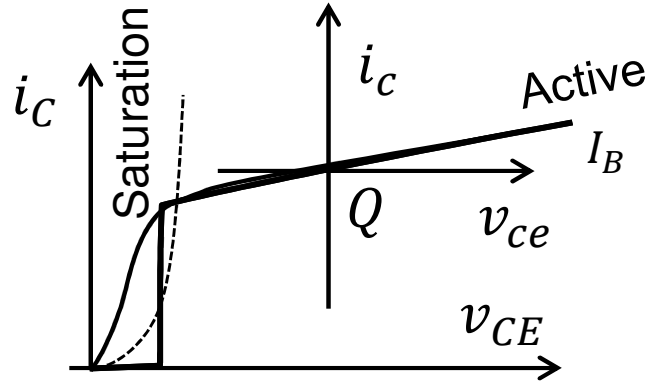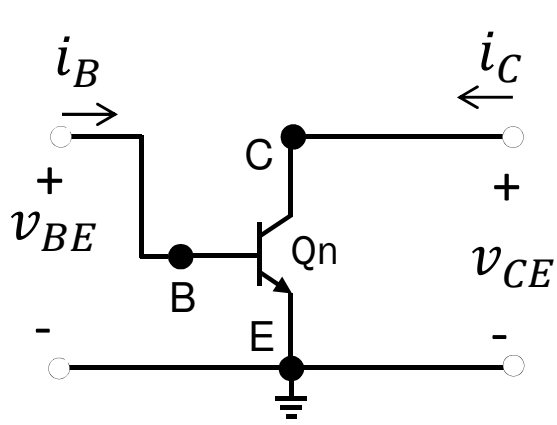Determined by n_{C0} as $n_{C0} \gg p_{B0}$








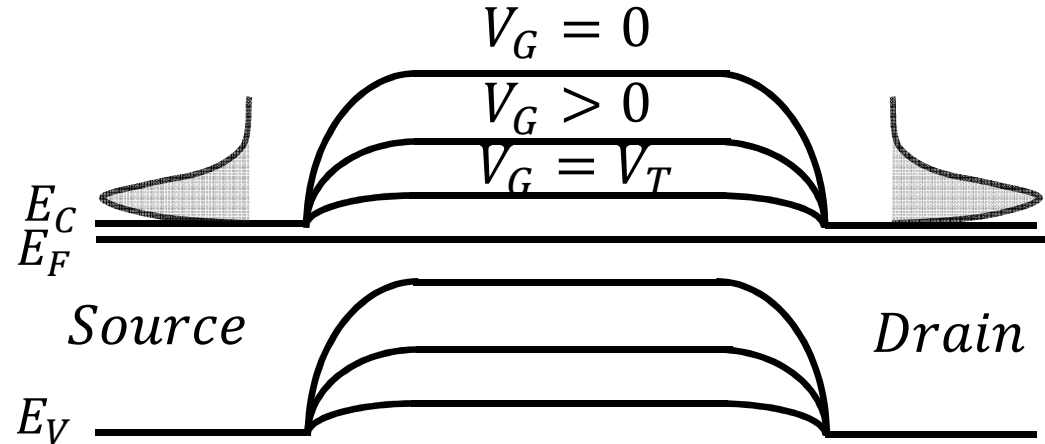
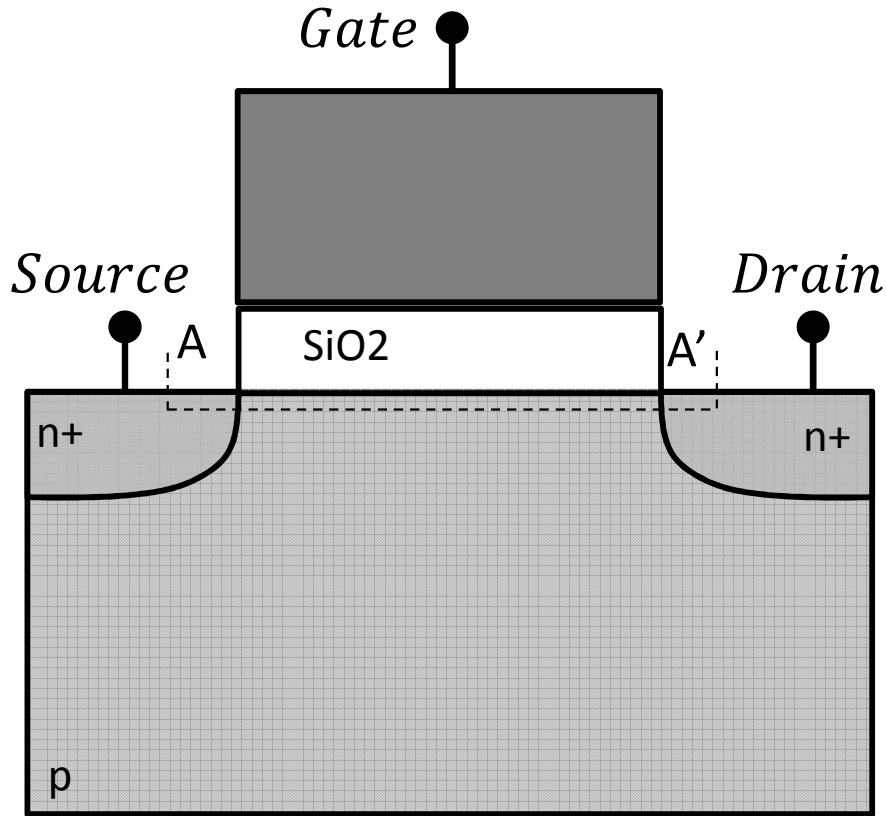
Large Signal Model

1. 
2. 
3. 
4. 
5. 








Qualitative Theory of the NMOSFET





1. 
2. 
3. 
4. 
5. 








The potential barrier to electron flow from the source into the channel region is lowered by applying $V_{GS} > V_T$

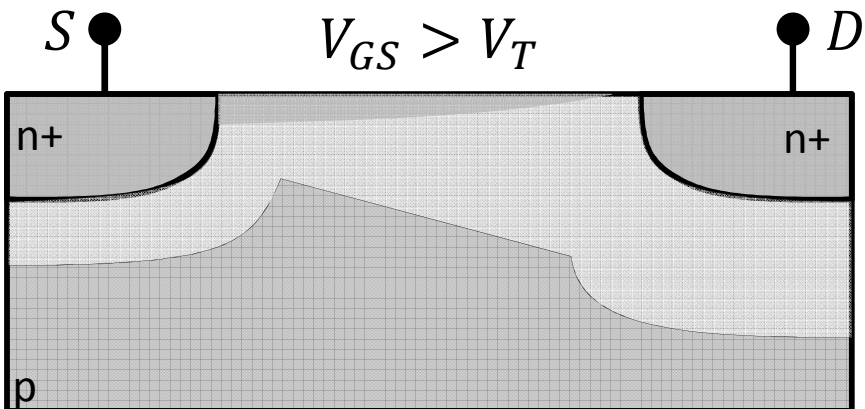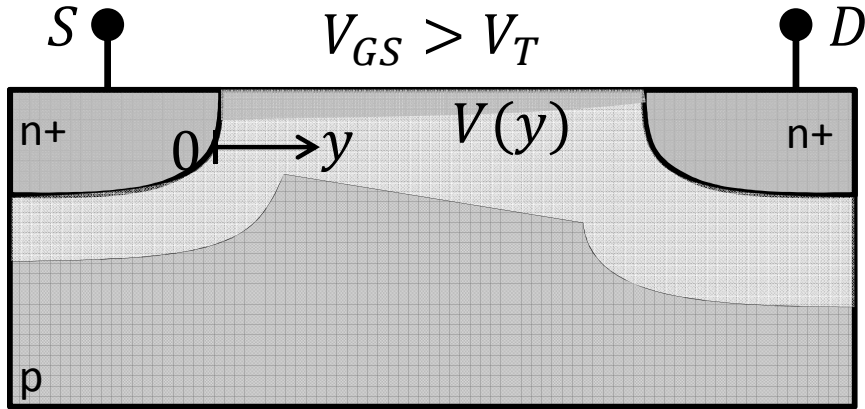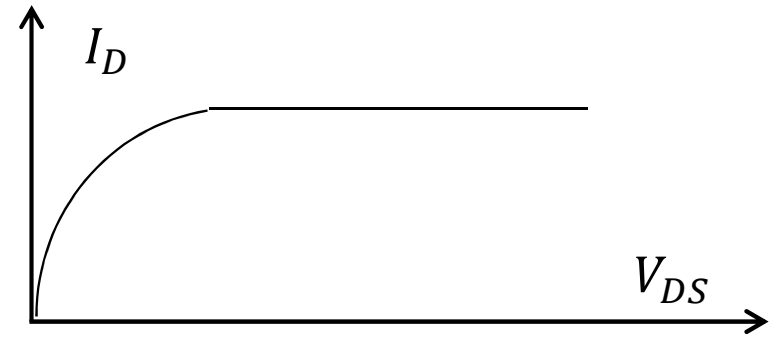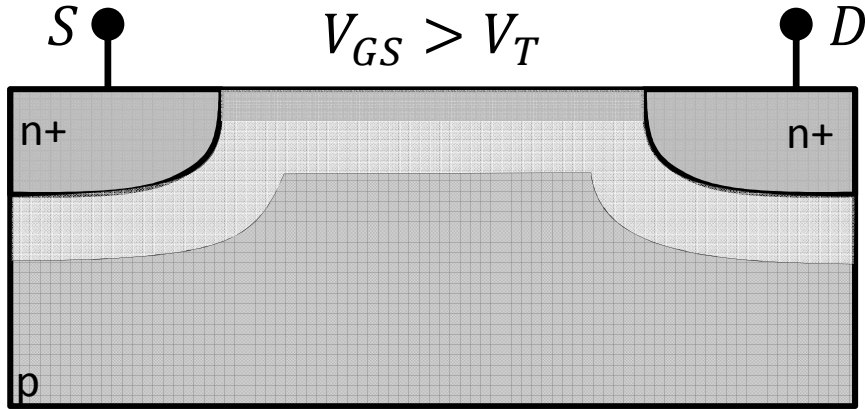
Qualitative Theory of the NMOSFET

1. 
2. 
3. 
4. 
5. 




MOSFET I-V Curve

1. 
2. 
3. 
4. 
5. 

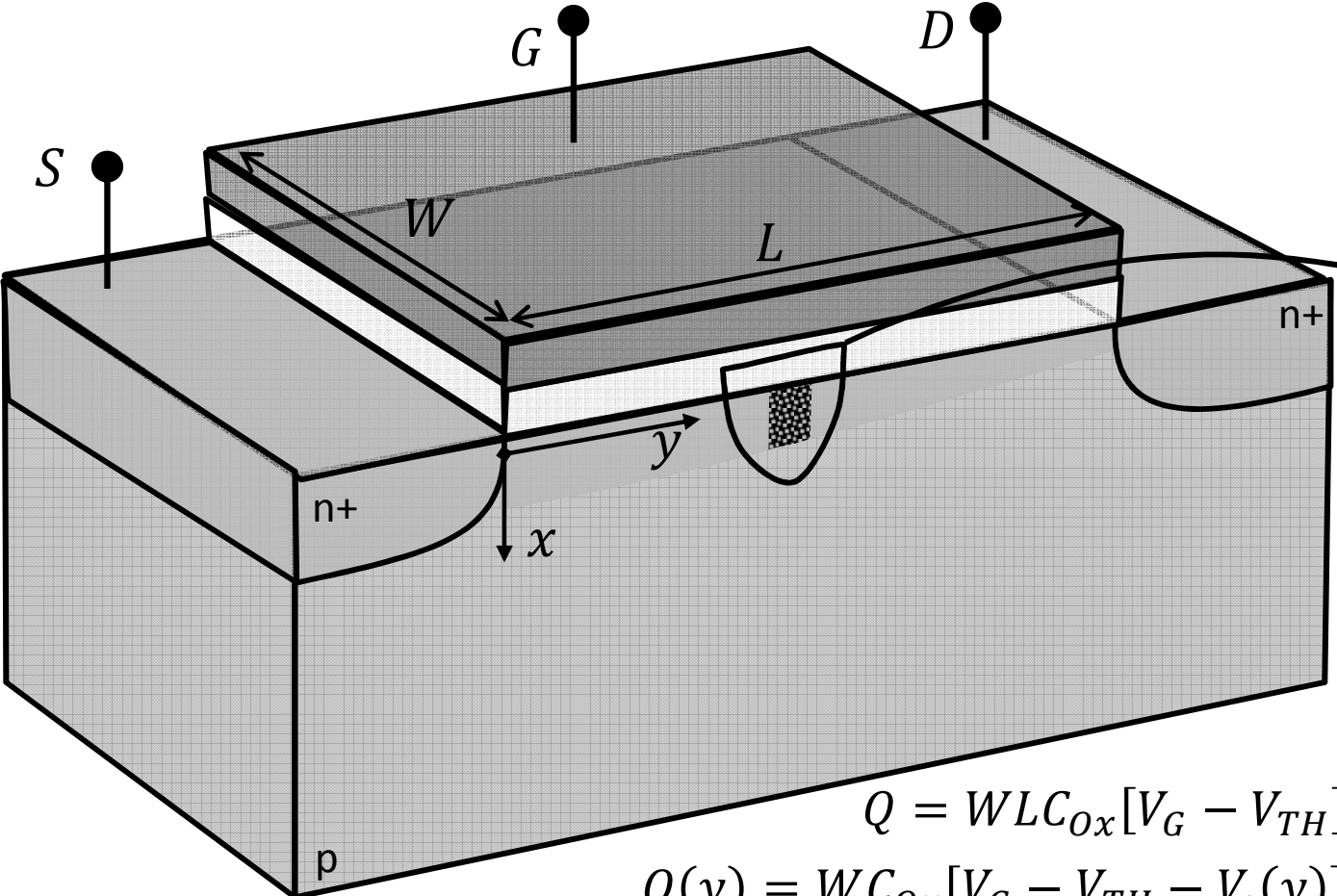

$$V_c(y)$$
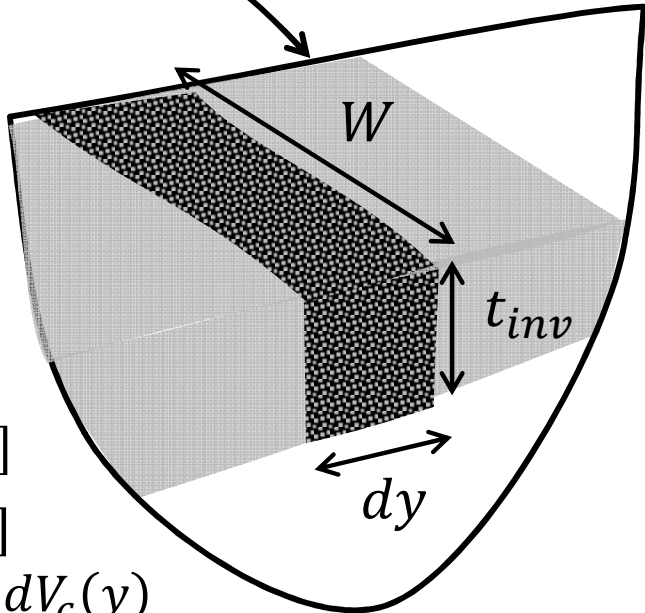
$$\begin{cases} V_c(0) = V_S \\ V_c(L) = V_D \end{cases}$$



$$Q = WLC_{ox}[V_G - V_{TH}]$$

$$Q(y) = WC_{ox}[V_G - V_{TH} - V_c(y)]$$






$$I = Q \cdot v$$

$$v = -\mu_n \mathcal{E} = \mu_n \frac{dV_c(y)}{dy}$$

$$I_D = WC_{ox}[V_G - V_{TH} - V_c(y)]\mu_n \frac{dV_c(y)}{dy}$$


$$\int_{y=0}^{y=L} I_D dy = \int_{V_c=0}^{V_c=V_{DS}} W\mu_n C_{ox}[V_G - V_{TH} - V_c(y)] dV_c(y)$$

MOSFET I-V Curve

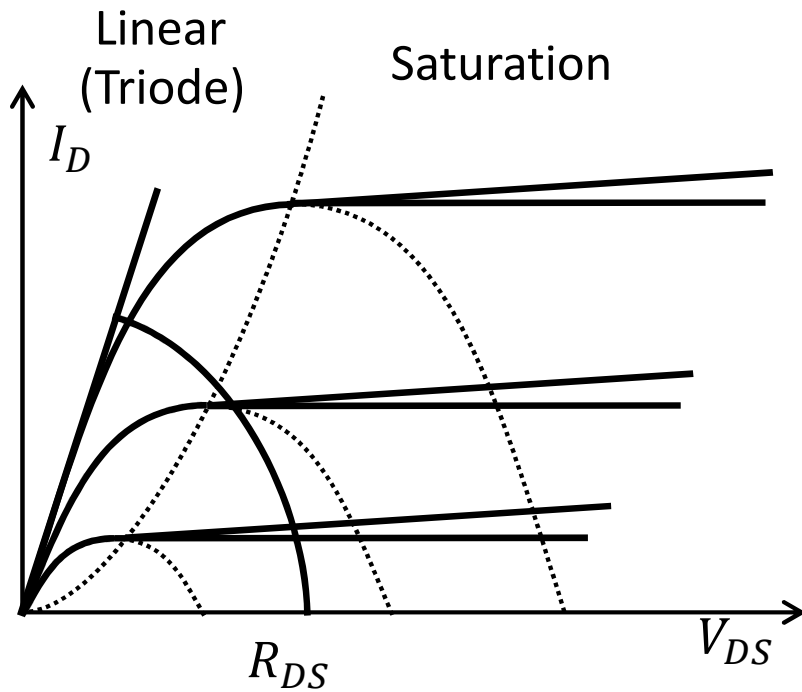
1. 
2. 
3. 
4. 
5. 

$$I_{DS} = \frac{1}{2} \frac{W}{L} \mu_{eff} C_{Ox} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2]$$

$$I_{DS} = \begin{cases} \frac{1}{2} \frac{W}{L} \mu_{eff} C_{Ox} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2] & V_{DS} < V_{DSsat} \text{ Linear} \\ \frac{1}{2} \frac{W}{L} \mu_{eff} C_{Ox} (V_{GS} - V_T)^2 & V_{DS} > V_{DSsat} = V_{GS} - V_T \text{ Saturation} \end{cases}$$





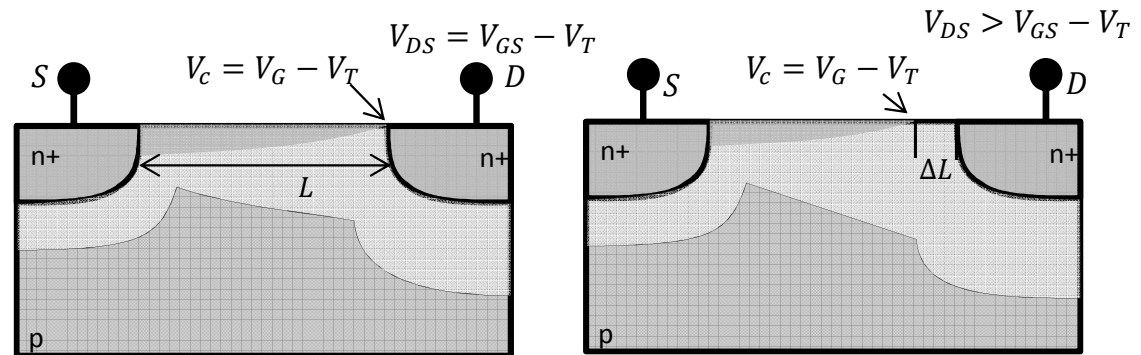


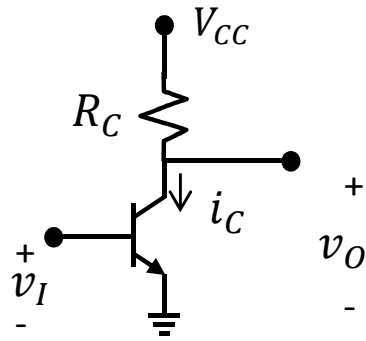
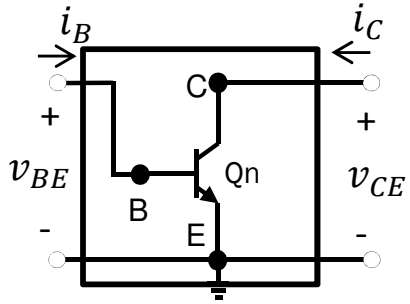
$$R_{DS} = \left(\frac{\partial I_{DS}}{\partial V_{DS}} \Big|_{V_{DS}=0} \right)^{-1} = \left(\frac{W}{L} \mu_{eff} C_{Ox} (V_{GS} - V_T) \right)^{-1}$$



“channel-length modulation”




Voltage Amplifier

1. 
2. 
3. 
4. 
5. 





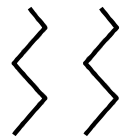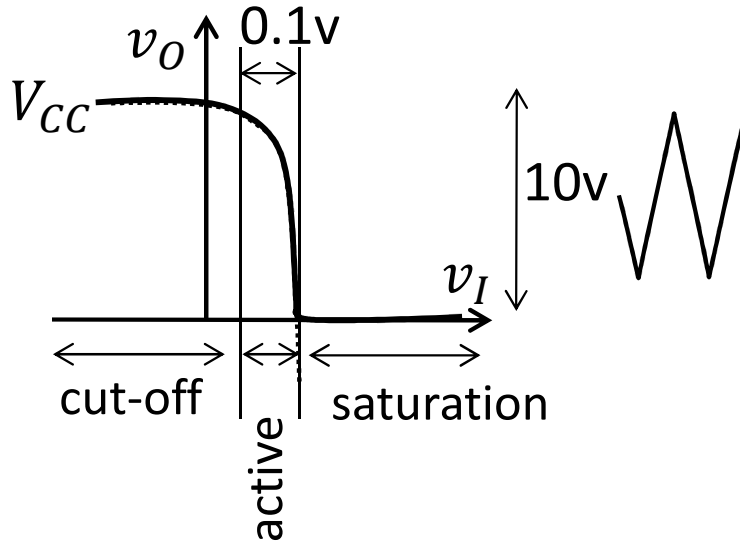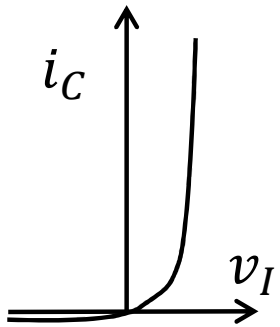


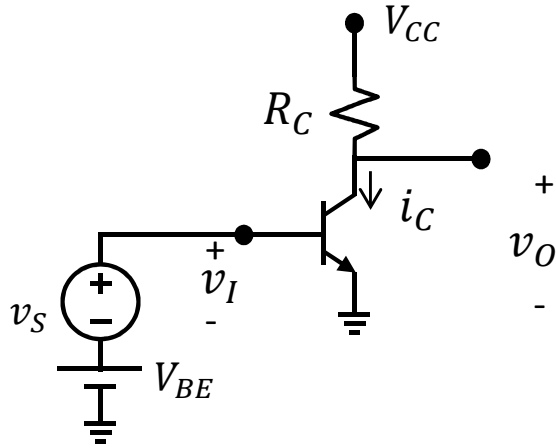
$$v_O = V_{CC} - R_C i_C$$

$$i_C = \beta i_B = I_S (e^{\frac{v_I}{V_T}} - 1)$$






Biasing: $V_{BE} = \text{cte}$






1. 
2. 
3. 
4. 
5. 

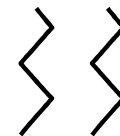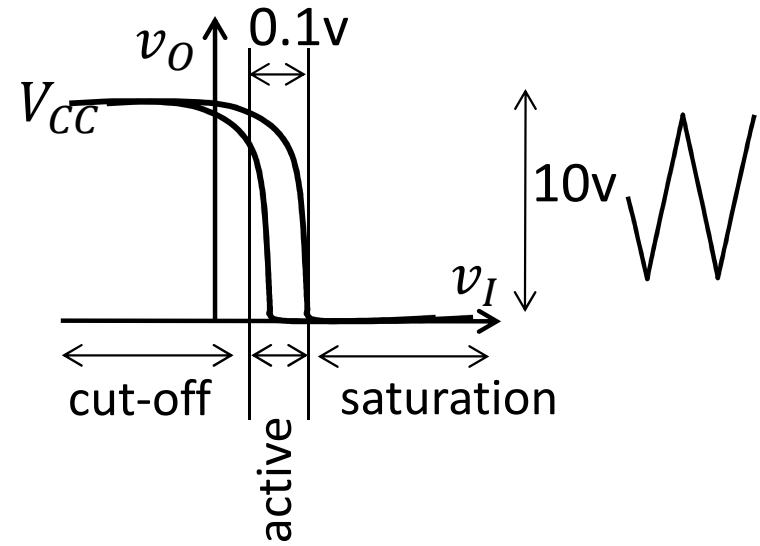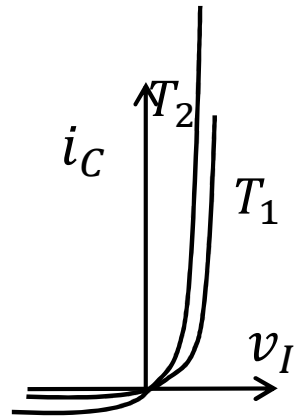


✓ DC-coupled



Biasing: $I_B = \text{cte}$

1. 
2. 
3. 
4. 
5. 

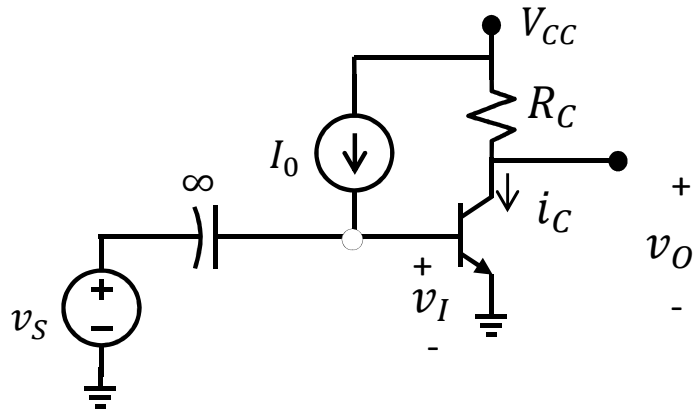

$$I_B = I_0$$

$$I_C = \beta I_B$$

$$V_{CC} = 10V$$

$$I_C = 1mA \quad \beta = 100$$


$$I_0 = 10\mu A$$

For max swing:

$$V_C \sim 5V \quad \rightarrow R_C \sim 5k\Omega$$

For max gain:
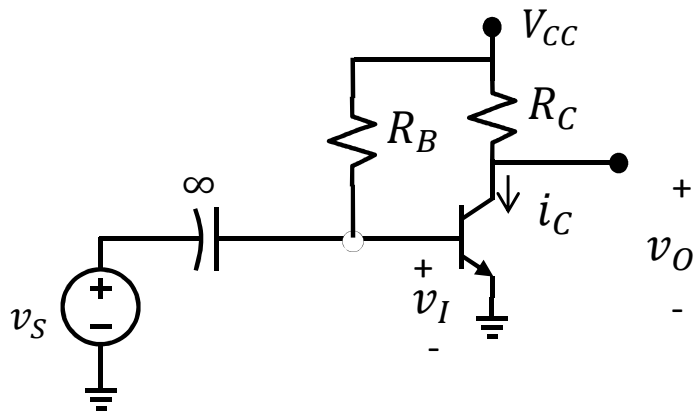
$$V_C \sim 0.3V \quad \rightarrow R_C \sim 9.7k\Omega$$



$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$V_{CC} = 10V$$

$$I_C = 1mA$$


$$\rightarrow R_B = 930k\Omega$$

Replace it with transistor with $\beta = 250$






$$I_C = 2.5mA$$

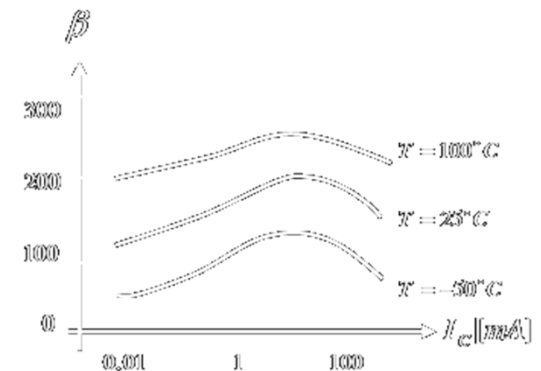
$$V_{CE} = 10 - 5 \times 2.5 = -2.5 < V_{CEsat}$$

What is the problem?



Biasing: $I_B = \text{cte}$

1. 
2. 
3. 
4. 
5. 

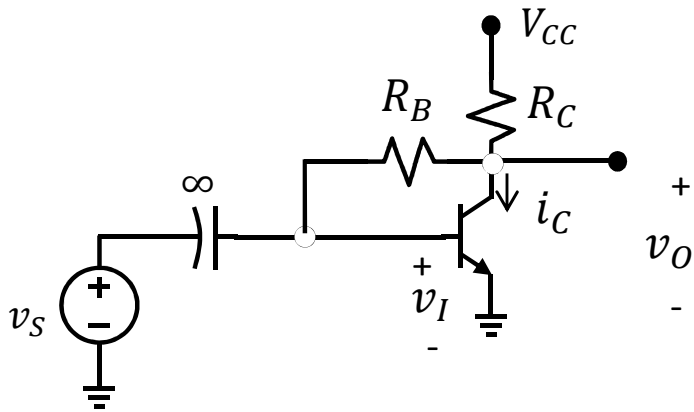


$$V_{CC} = 10V \quad I_C = 1mA \quad \beta = 100$$

For max swing: $V_C \sim 5V$



$$R_B = \frac{V_C - V_{BE}}{I_B} = \beta \frac{V_C - V_{BE}}{I_C}$$

$$\rightarrow R_B = 430k\Omega$$

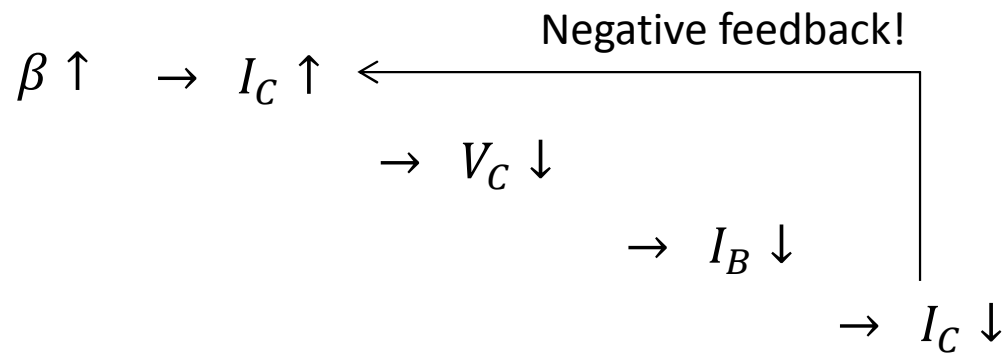

Biasing: $I_E = \text{cte}$

- 1.
- 2.
- 3.
- 4.
- 5.

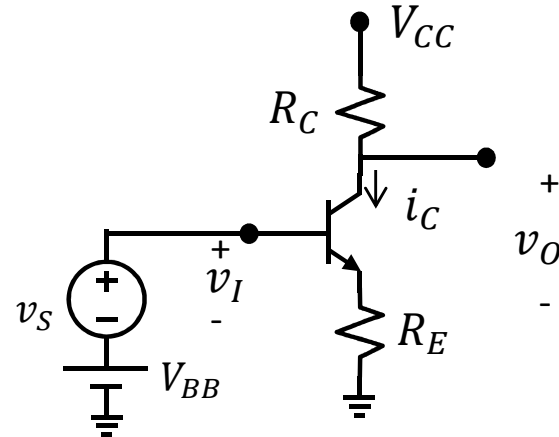
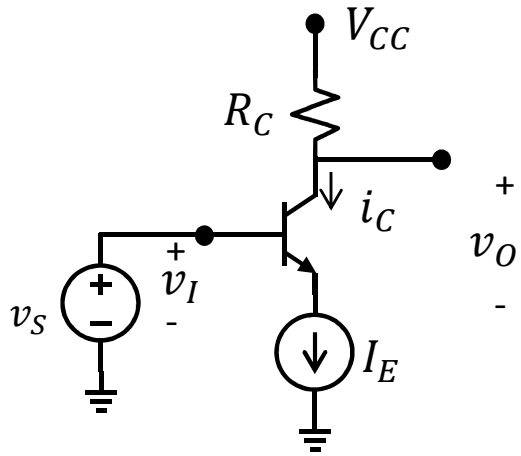


$$I_E = \frac{V_{BB} - V_{BE}}{R_E}$$


I_E independent of V_{BE}

$$V_{BB} \gg V_{BE}$$



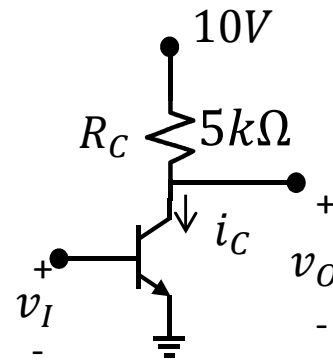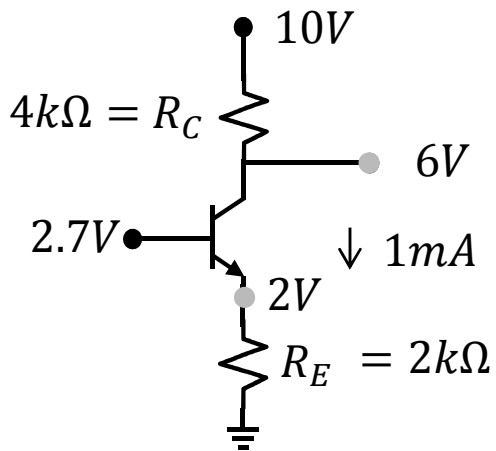


$$V_{BB} \sim 2.7V$$

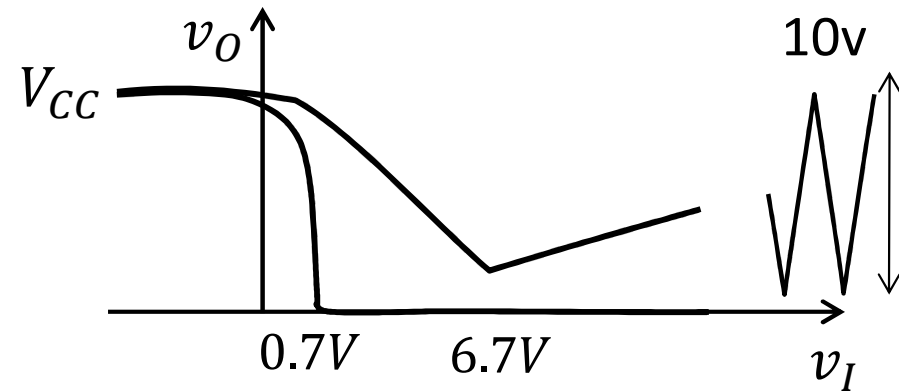


Where is the trade-off?



Biasing: $I_E = \text{cte}$



1. 
2. 
3. 
4. 
5. 

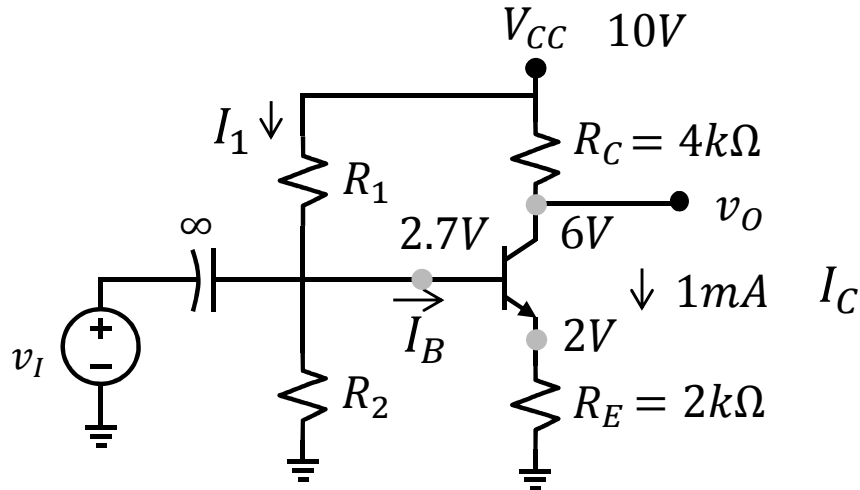

$$I_B = \frac{I_C}{\beta}$$

Assume: $I_1 \gg I_B$

$$V_B = \frac{R_2}{R_2 + R_1} V_{CC}$$

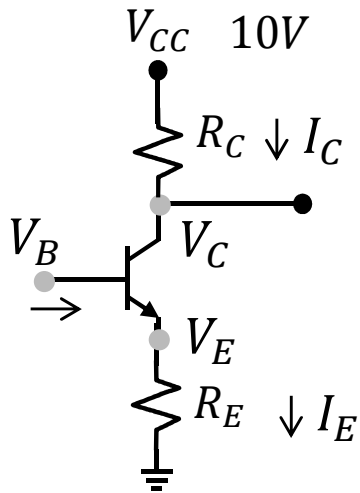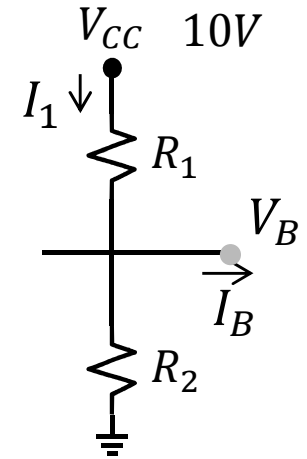


$$V_E = V_B - V_{BEon}$$

$$I_E = \frac{V_E}{R_E}$$

$$I_C = \alpha I_E \approx I_E$$

$$V_C = V_{CC} - I_C R_C$$

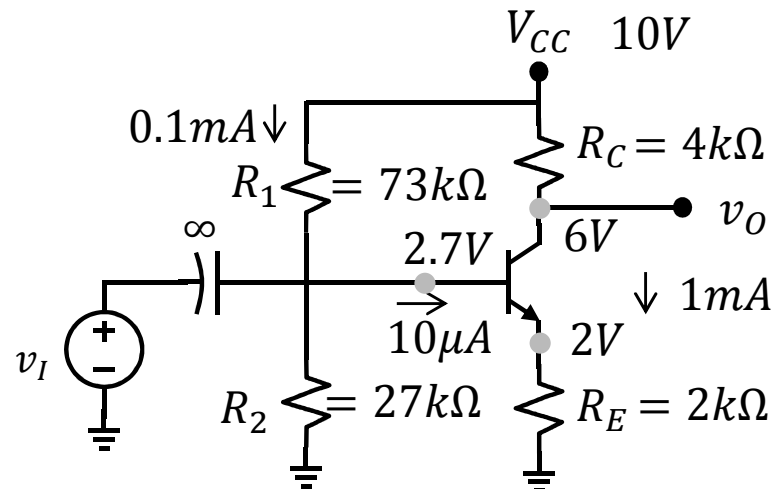


?

This is for design
how about analysis

Biasing: $I_E = \text{cte}$

- 1.
- 2.
- 3.
- 4.
- 5.



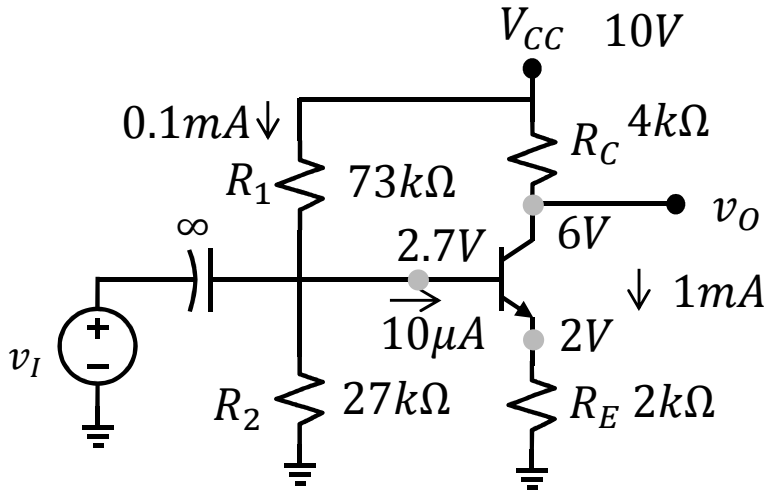


Assume: $I_1 \gg I_B$ $I_1 = 0.1\text{mA}$

$V_B = 2.7\text{V}$ $V_E = 2\text{V}$

$I_E = 1\text{mA}$ $I_B = 0.01\text{mA}$



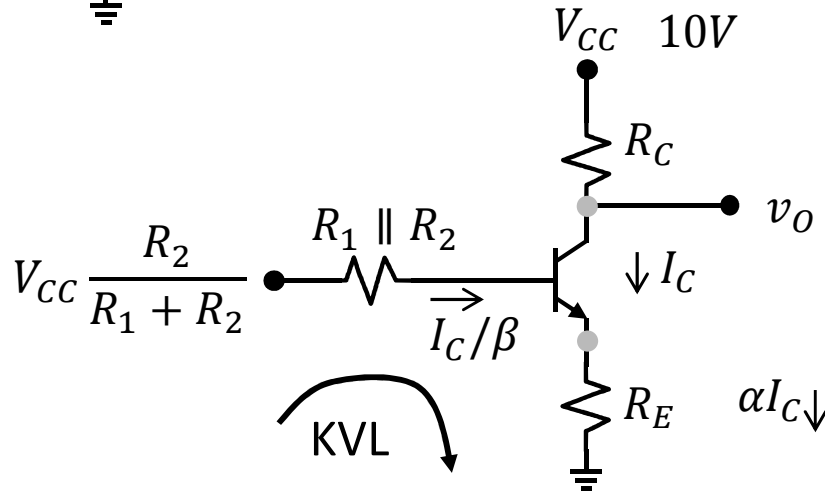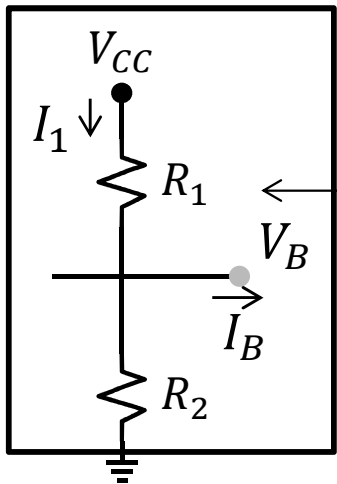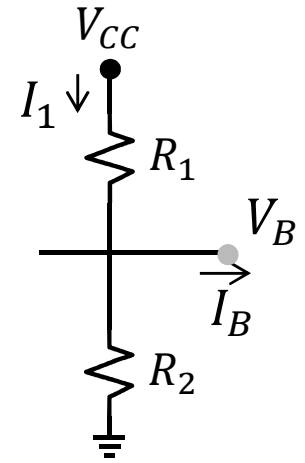


What if β was 10!




$$\frac{R_2}{R_1 + R_2} V_{CC} = I_C \frac{R_1 \parallel R_2}{\beta} + V_{BEon} + \alpha R_E I_C \quad \rightarrow I_C = \dots$$

For the above numbers: $I_C = \frac{2}{0.99 \times 2k + 0.01 \times 19.7k} = 0.92\text{mA}$


Biasing: $I_E = \text{cte}$

1. 
2. 
3. 
4. 
5. 

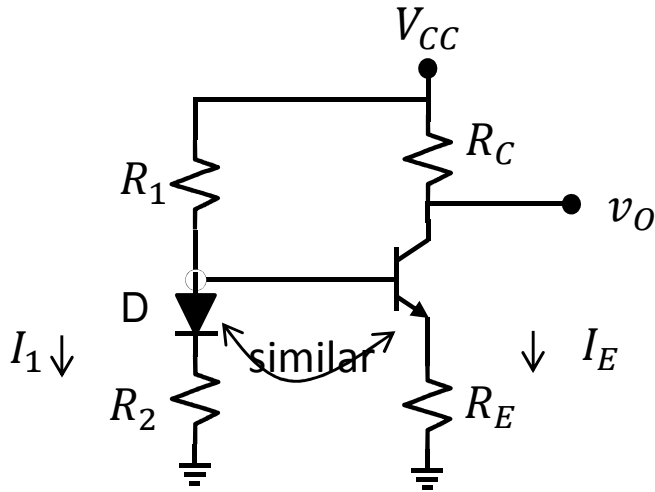

$$I_1 R_2 + V_D = V_{BEon} + I_E R_E$$

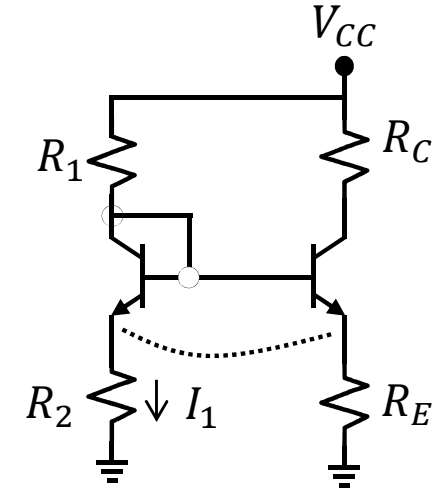
$$I_1 \approx \frac{V_{CC}}{R_1 + R_2} \quad I_E = \frac{R_E}{R_2} I_1$$



$$I_1 R_2 = I_E R_E$$

$$I_1 = \frac{V_{CC} - V_{BEon}}{R_1 + R_2}$$

Only in Integrated Circuits!

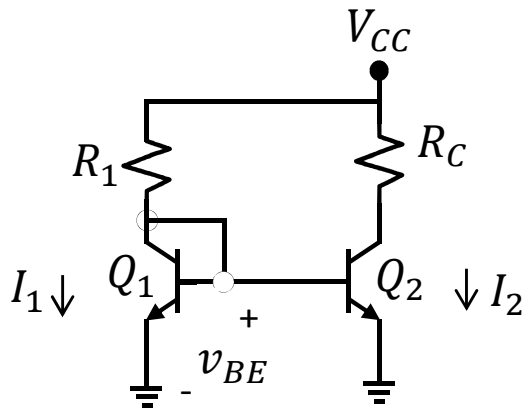

$$I_1 = \frac{V_{CC} - V_{BEon}}{R_1}$$

$$I_1 = I_{S1} (e^{v_{BE}/V_T} - 1)$$


$$I_2 = I_{S2} (e^{v_{BE}/V_T} - 1)$$

$$\frac{I_2}{I_1} = \frac{I_{S2}}{I_{S1}} = \frac{A_{Q2}}{A_{Q1}}$$

area


Biasing: Example 01

- 1.
- 2.
- 3.
- 4.
- 5.

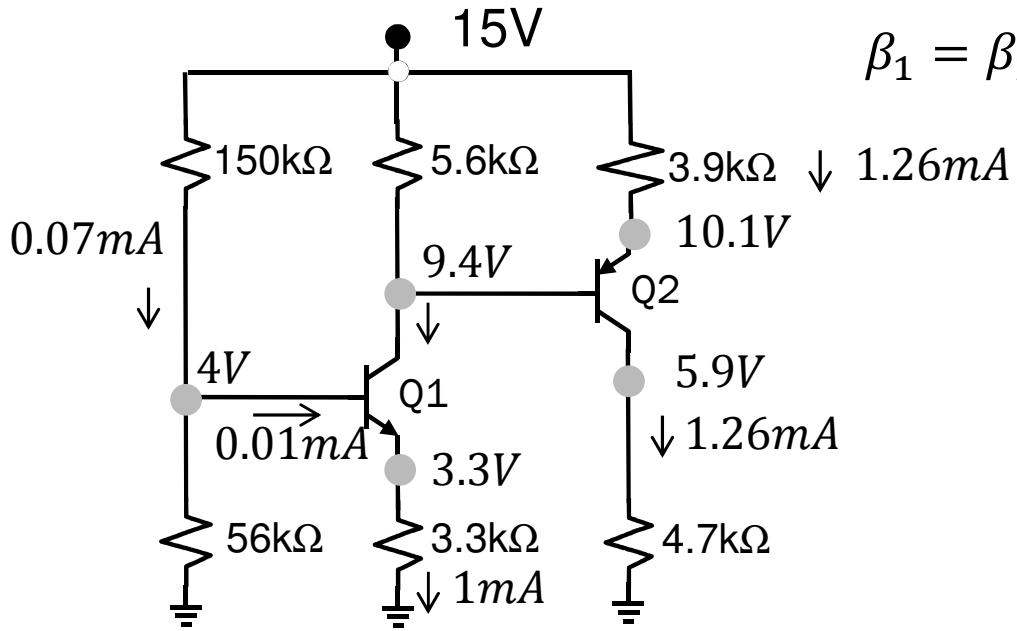

$$\beta_1 = \beta_2 = 100 \quad V_{BE_{on}} = 0.7$$

	Q_1	Q_2
I_C [mA]	1	1.26
V_{CE} [V]	6.1	-4.2

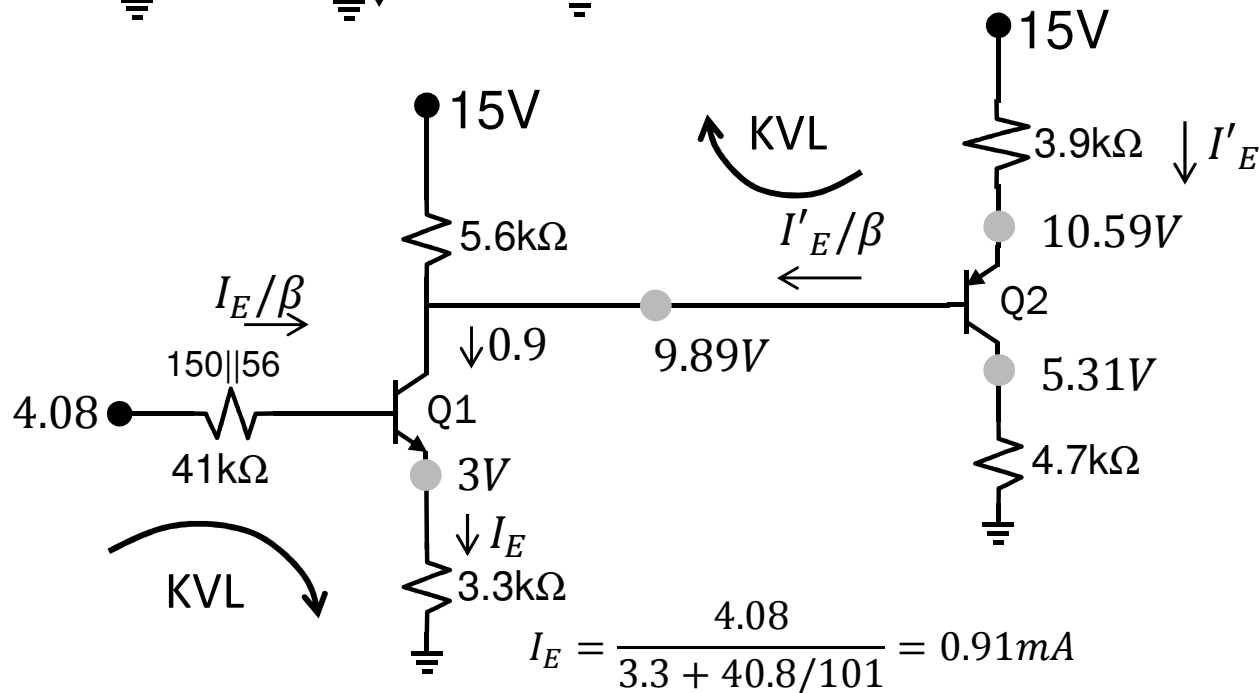


$$3.9I'_E + 0.7 = 5.6\left(0.9 - \frac{I'_E}{\beta}\right)$$

$$I'_E = 1.13mA$$

Biasing: Example 02


- 1.
- 2.
- 3.
- 4.
- 5.

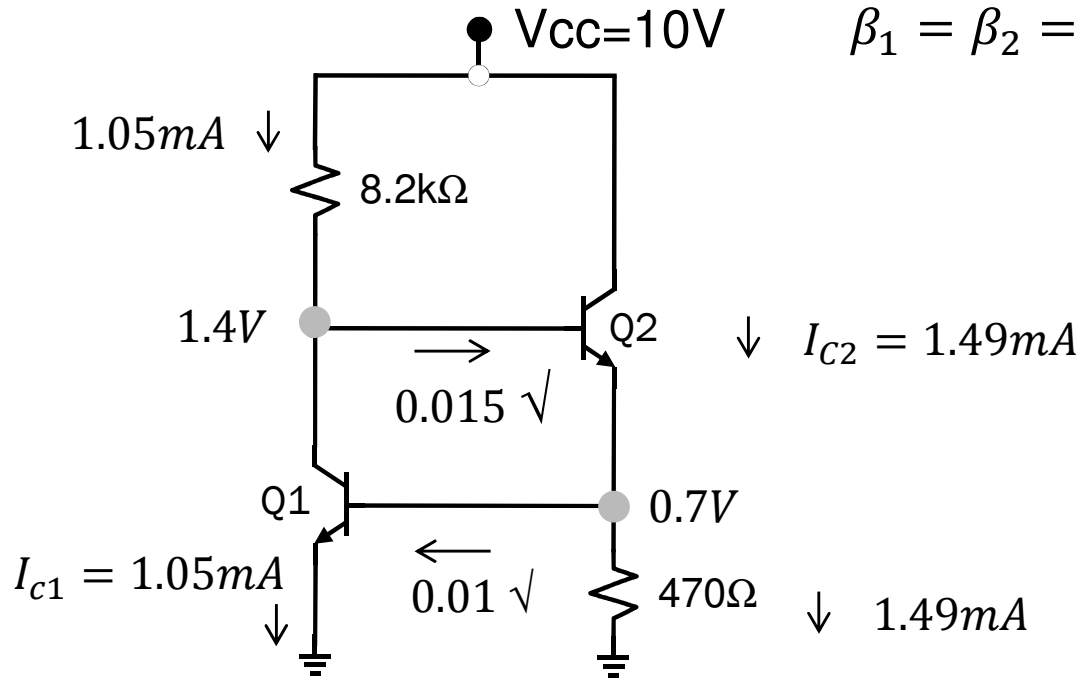


	Q_1	Q_2
$I_C [mA]$	1.05	1.49
$V_{CE} [V]$	1.4	9.3

Biasing: Example 03

- 1.
- 2.
- 3.
- 4.
- 5.

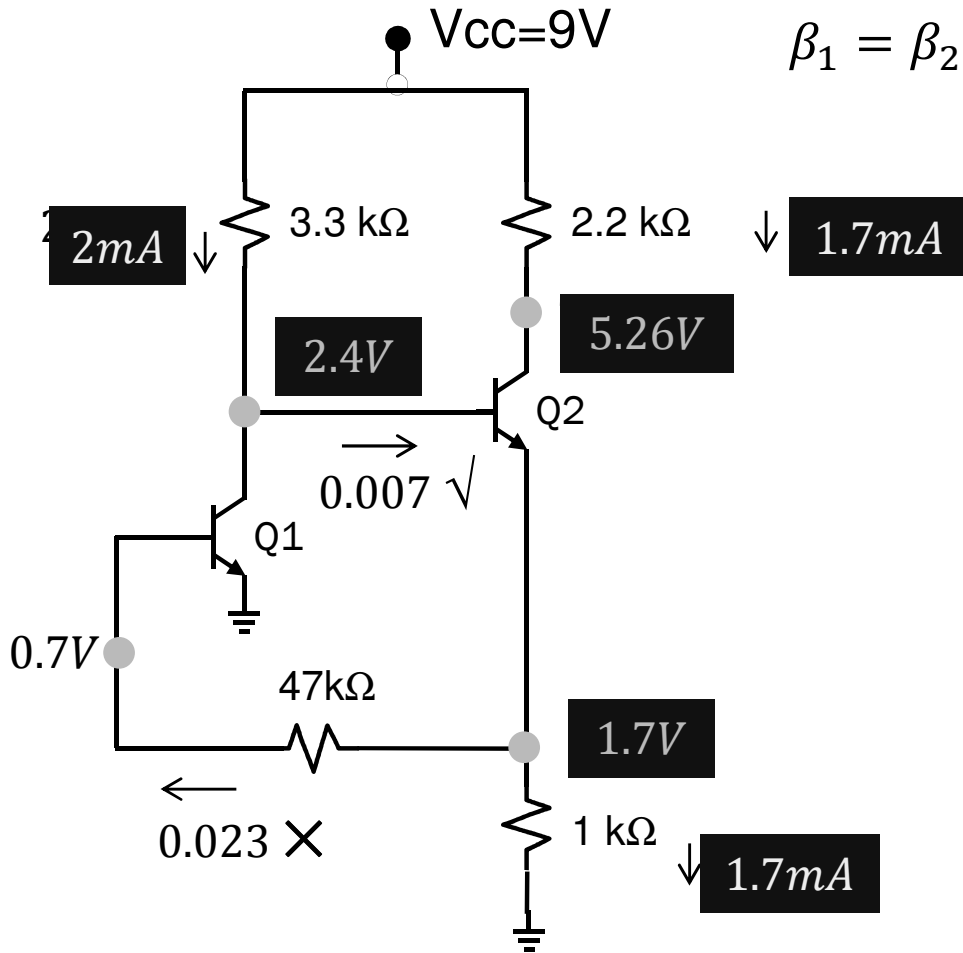



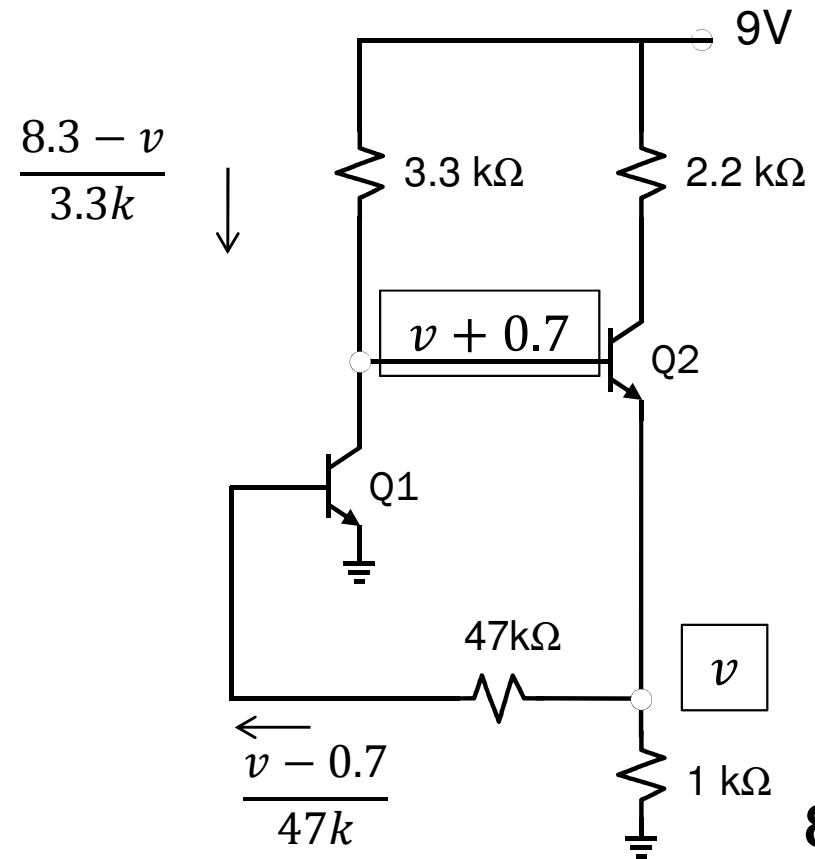


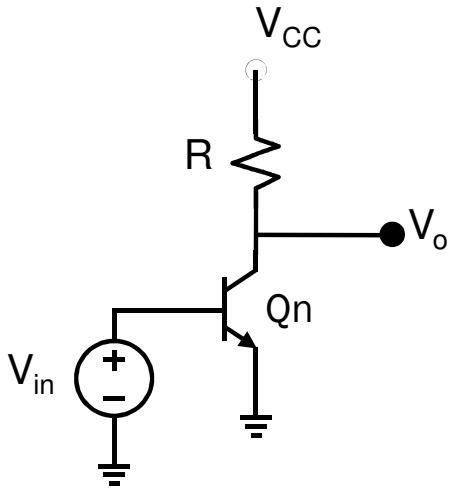
	Q_1	Q_2
I_C [mA]	2	1.7
V_{CE} [V]	2.4	3.56



$$\frac{8.3 - v}{330} = \frac{v - 0.7}{47} \Rightarrow v = 1.65$$

Linear BJT Amplifier

1. 
2. 
3. 
4. 
5. 



$$V_T = 26mV \quad V_A = 200V$$







$$i_C = I_S e^{\frac{v_{BE}}{nV_T}} \left(1 + \frac{v_{CE}}{V_A}\right) \approx I_S e^{\frac{v_{BE}}{nV_T}}$$

$$v_{BE} = V_B + \hat{v}_i \sin \omega t$$


$$\begin{aligned}
 v_o &= V_{CC} - R i_C = V_{CC} - R I_S e^{\frac{V_B}{V_T}} e^{\frac{\hat{v}_i \sin \omega t}{V_T}} \\
 &= V_{CC} - R I_C \left(1 + \frac{\hat{v}_i}{V_T} \sin \omega t + \frac{\hat{v}_i^2}{2V_T^2} \sin^2 \omega t + \dots \right) \\
 &\approx \underbrace{V_{CC} - R I_C}_{V_o} - \underbrace{R I_C \frac{\hat{v}_i}{V_T}}_{v_o} \sin \omega t
 \end{aligned}$$

$$A_V = \frac{v_o}{v_{in}} = \frac{-R_C I_C}{V_T} = -g_m R_C \quad g_m = \frac{I_C}{V_T}$$

Amplifiers

1.  
2. 
3. 
4. 
5. 

Voltage Amplifier

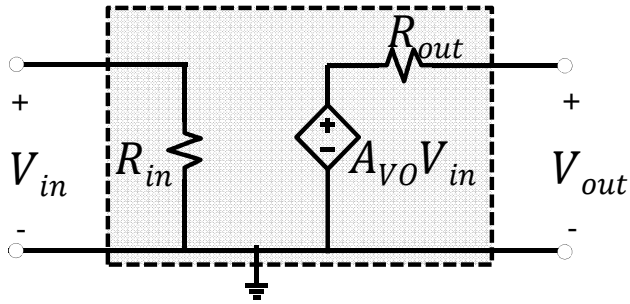

$$A_{VO} = \left. \frac{V_{out}}{V_{in}} \right|_{i_{out}=0}$$


open circuit voltage gain

Ideal:

$$R_{in} = \infty$$

$$R_{out} = 0$$

Current Amplifier

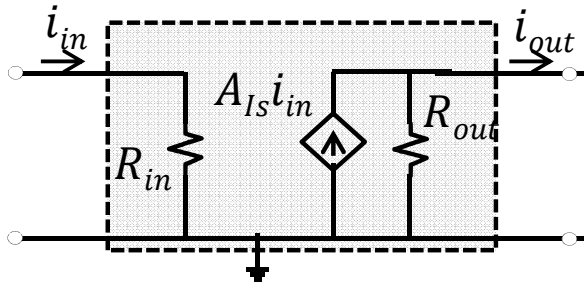


$$A_{IS} = \left. \frac{i_{out}}{i_{in}} \right|_{V_{out}=0}$$

short circuit current gain

$$R_{in} = 0$$

$$R_{out} = \infty$$

Trans-Conductance Amplifier

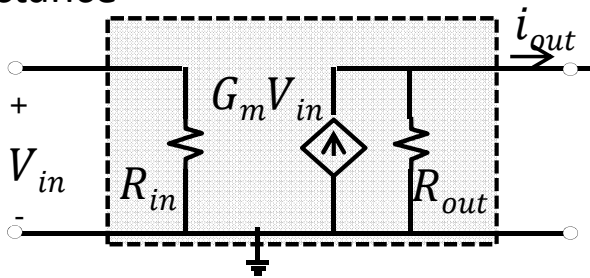


$$G_m = \left. \frac{i_{out}}{V_{in}} \right|_{V_{out}=0}$$

short circuit Trans-conductance

$$R_{in} = \infty$$

$$R_{out} = \infty$$

Trans-Resistance Amplifier

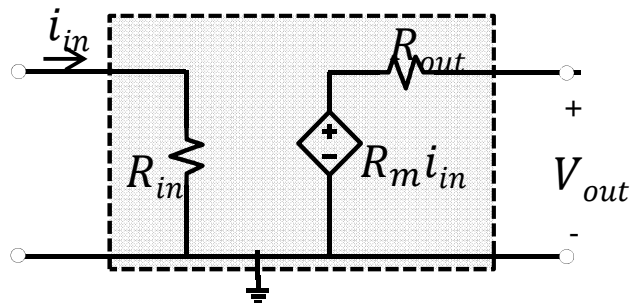






$$R_m = \left. \frac{V_{out}}{i_{in}} \right|_{i_{out}=0}$$


open circuit Trans-resistance

$$R_{in} = 0$$

$$R_{out} = 0$$


BJT Small Signal Model (h- π)

1. 
2. 
3. 
4. 
5. 

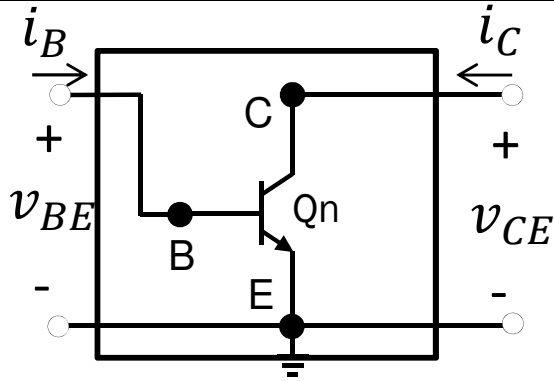

$$i_C = I_S \left(e^{\frac{v_{EB}}{V_T}} - 1 \right) \left(1 + \frac{v_{CE}}{V_A} \right)$$
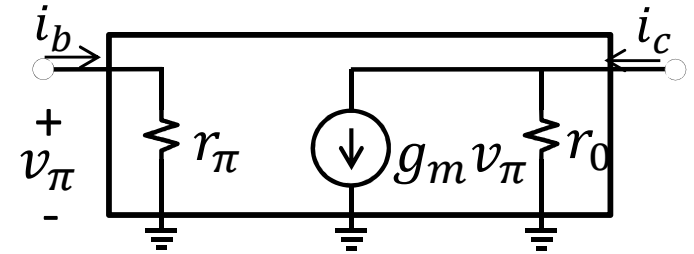
$$\cong \underbrace{I_S e^{\frac{v_{EB}}{V_T}}}_{I_C} \left(1 + \frac{v_{CE}}{V_A} \right)$$



Input resistance:

$$r_{\pi} \equiv \frac{\partial v_{BE}}{\partial i_B} = \left(\frac{\partial i_B}{\partial v_{BE}} \right)^{-1} = \beta \left(\frac{\partial i_C}{\partial v_{BE}} \right)^{-1} = \beta \left(\frac{I_S}{V_T} e^{\frac{v_{EB}}{V_T}} \right)^{-1} = \beta \frac{V_T}{I_C} = \frac{\beta}{g_m} = \beta r_m$$

Output resistance:


$$r_o \equiv \frac{\partial v_{CE}}{\partial i_C} = \left(\frac{\partial i_C}{\partial v_{CE}} \right)^{-1} = \left(\frac{I_C}{V_A} \right)^{-1} = \frac{V_A}{I_C}$$

Transconductance:

$$g_m \equiv \frac{\partial i_C}{\partial v_{BE}} = \frac{I_S}{V_T} e^{\frac{v_{EB}}{V_T}} = \frac{I_C}{V_T} = \frac{1}{r_m}$$

Example 01 - CE

- 1.
- 2.
- 3.
- 4.
- 5.


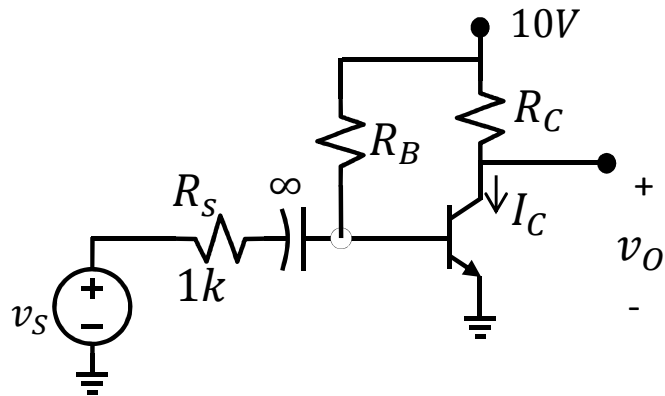


Assume $\beta = 100$ $V_A \sim \infty$

Design for $I_C = 1mA$ and maximum swing

Find A_v, R_{in}, R_{out}
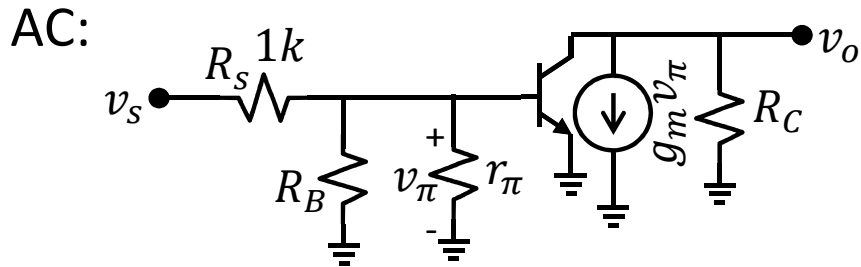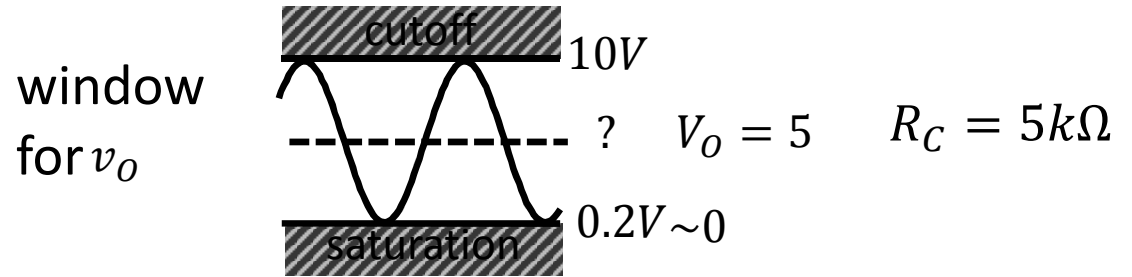
$$\text{DC: } R_B = \frac{10 - 0.7}{0.01mA} = 930k\Omega$$



$$v_\pi = v_s \frac{r_\pi \parallel R_B}{r_\pi \parallel R_B + R_s} \sim v_s \frac{r_\pi}{r_\pi + R_s}$$


$$v_o = -g_m v_\pi R_C$$

$$A_v = \frac{v_o}{v_s} = -g_m R_C \frac{r_\pi}{r_\pi + R_s} = \frac{-\beta R_C}{r_\pi + R_s} = \frac{-R_C}{r_m + R_s/\beta} = -\frac{\text{Collector resistance}}{\text{Emitter's circuit resistance}}$$

$$\text{if } R_s \rightarrow 0: \quad A_v = -g_m R_C$$



Example 02 - CE

1.
2.
3.
4.
5.

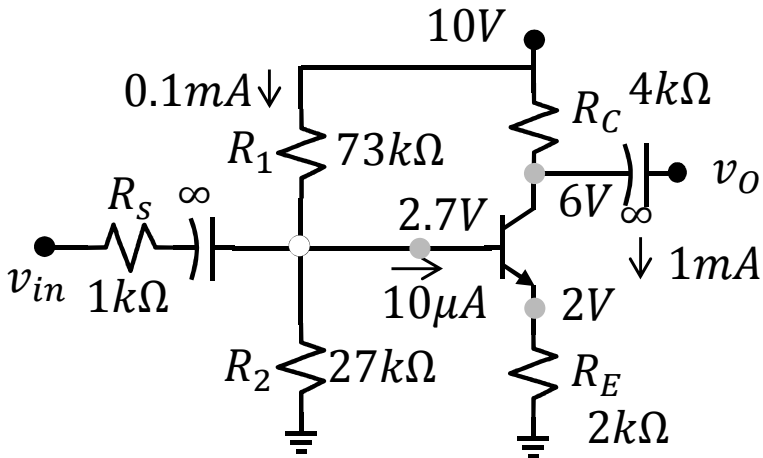

Assume $\beta = 100$ $V_A \sim \infty$ Find A_v, R_{in}, R_{out}

AC circuit

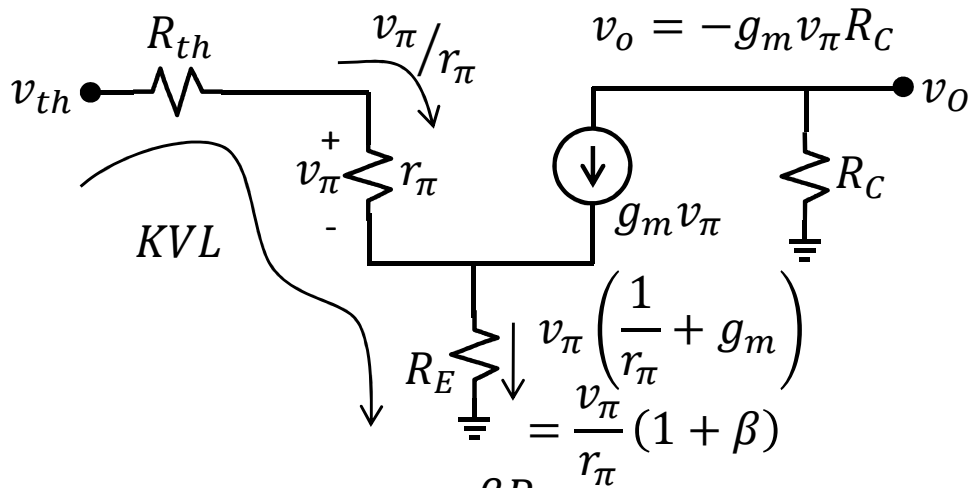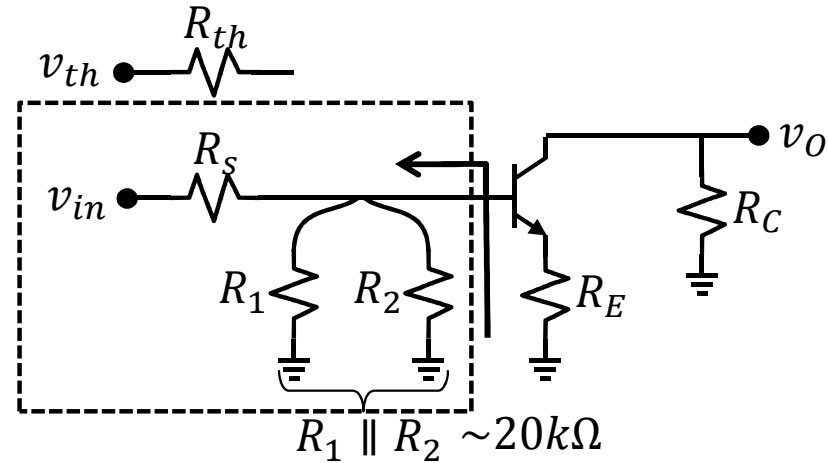

$$v_{th} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_s} v_{in} \quad R_{th} = R_1 \parallel R_2 \parallel R_s$$

$$\text{KVL: } -v_{th} + R_{th} \frac{v_{\pi}}{r_{\pi}} + v_{\pi} + R_E \frac{v_{\pi}}{r_{\pi}} (1 + \beta) = 0$$






$$v_{\pi} = v_{th} \frac{r_{\pi}}{R_{th} + r_{\pi} + R_E (1 + \beta)}$$


$$A'_v = \frac{v_o}{v_{th}} = \frac{-\beta R_C}{R_{th} + r_{\pi} + R_E (1 + \beta)}$$

$$= \frac{R_{th} + r_{\pi}}{\beta} + R_E \left(\frac{1 + \beta}{\beta} \right)$$


$$A_v = \frac{v_o}{v_s} = \frac{v_{th}}{v_s} \cdot \frac{v_o}{v_{th}} = -\frac{20}{21} \cdot \frac{4}{\frac{3.5}{100} + 2 \times \frac{101}{100}} = -1.8$$

Example 02 - CE


1. 
2. 
3. 
4. 
5. 

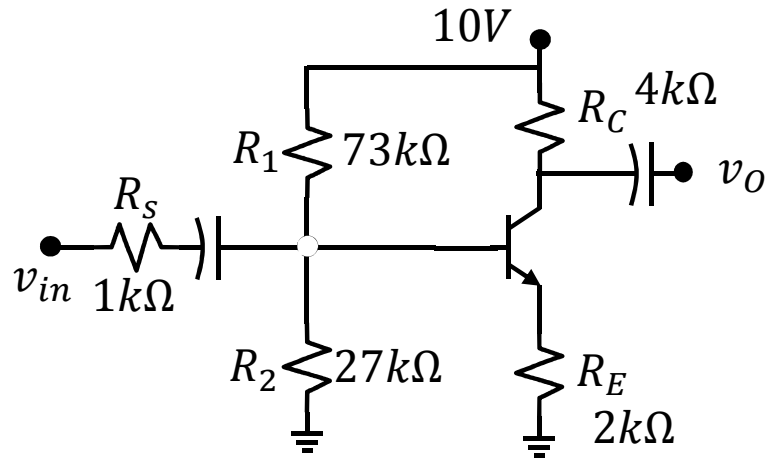

$$A_v = -1.8$$

 


How we can increase gain?

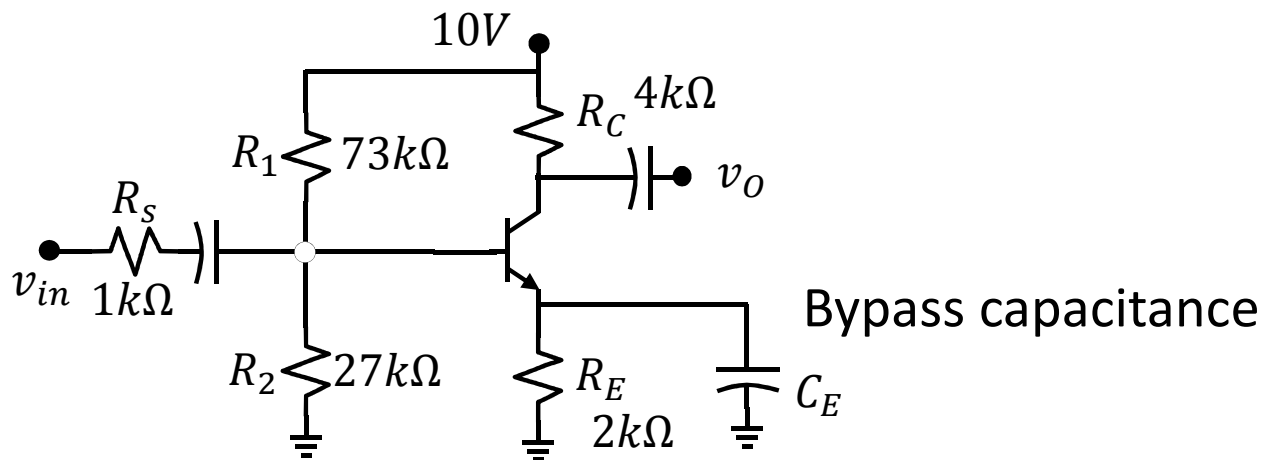


Example 03 - CC

- 1.
- 2.
- 3.
- 4.
- 5.

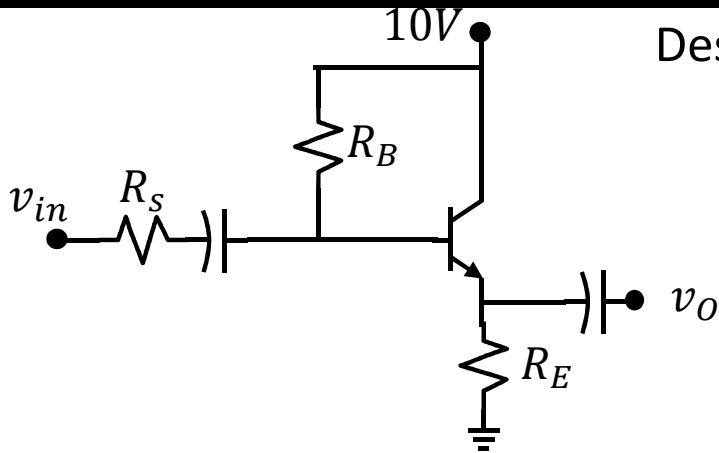


Design a buffer $I_C = 1mA$

AC circuit

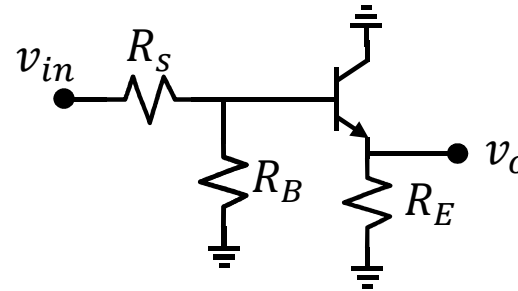


window for v_E

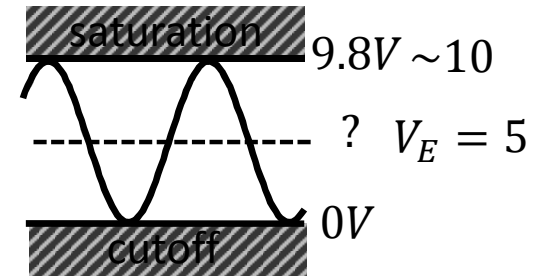

$$R_E = 5k\Omega$$
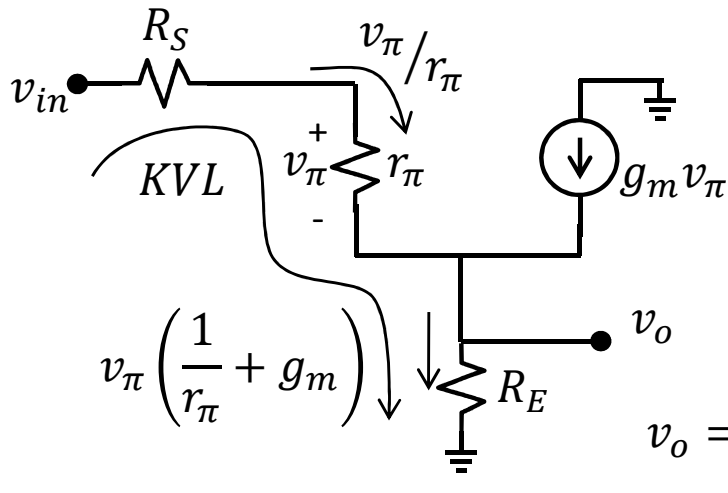
$$R_B = \frac{10 - 5.7}{0.01m} = 430k\Omega$$



KVL:






$$-v_{in} + R_S \frac{v_{\pi}}{r_{\pi}} + v_{\pi} + R_E \left(\frac{v_{\pi}}{r_{\pi}} + g_m v_{\pi} \right) = 0$$


$$v_{\pi} = \frac{v_{in}}{\frac{R_S}{r_{\pi}} + 1 + R_E \left(g_m + \frac{1}{r_{\pi}} \right)}$$

$$v_o = v_{\pi} \left(\frac{1}{r_{\pi}} + g_m \right) R_E$$


$$A_v = \frac{v_o}{v_{in}} = \frac{\left(\frac{1}{r_{\pi}} + g_m \right) R_E}{\frac{R_S}{r_{\pi}} + 1 + R_E \left(g_m + \frac{1}{r_{\pi}} \right)} = \frac{R_E}{\frac{R_S + r_{\pi}}{1 + \beta} + R_E} \sim 1$$

Example 03 - CC


1. 
2. 
3. 
4. 
5. 

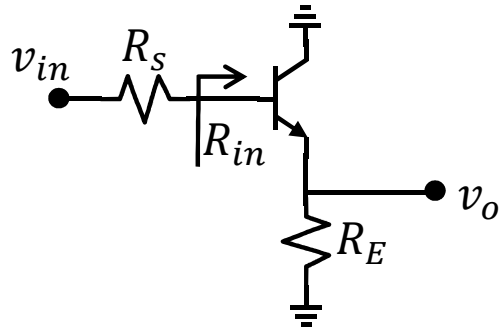
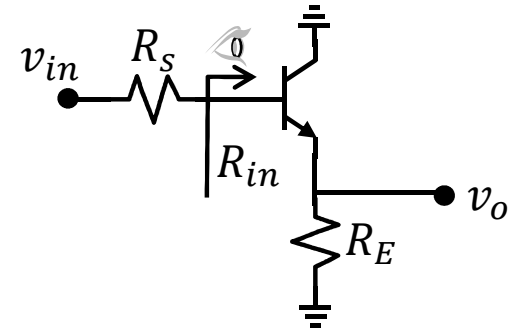
$$\frac{v_o}{v_{in}} = \frac{R_E}{\frac{R_S + r_\pi}{1 + \beta} + R_E}$$




$$R_{in} = r_\pi + R_E(1 + \beta)$$

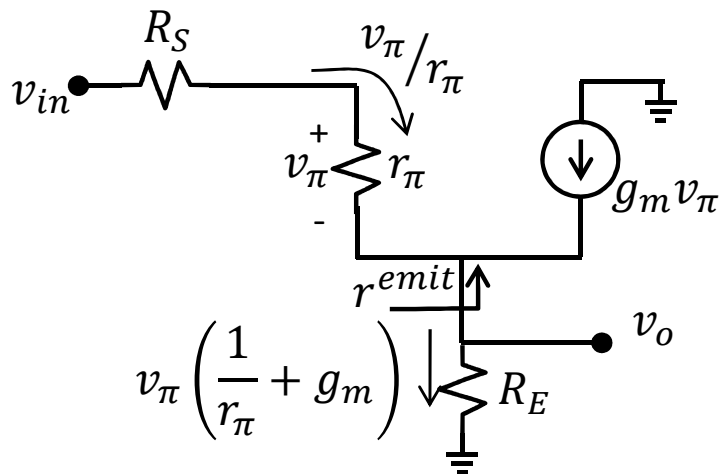

$$R_{in} = \frac{v_\pi + R_E \left(\frac{v_\pi}{r_\pi} + g_m v_\pi \right)}{\frac{v_\pi}{r_\pi}}$$

$$= r_\pi + R_E(1 + \beta)$$

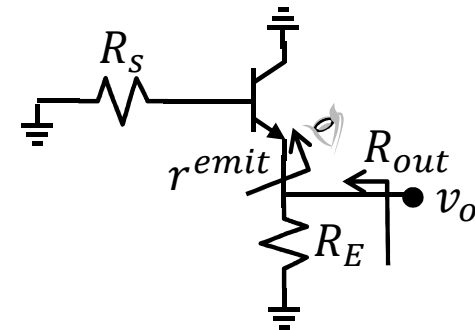


$$R_{out} = R_E \parallel r^{emit}$$

$$= R_E \parallel \frac{R_S + r_\pi}{1 + \beta}$$

Example 04 – Multi-stage Amplifier

- 1.
- 2.
- 3.
- 4.
- 5.

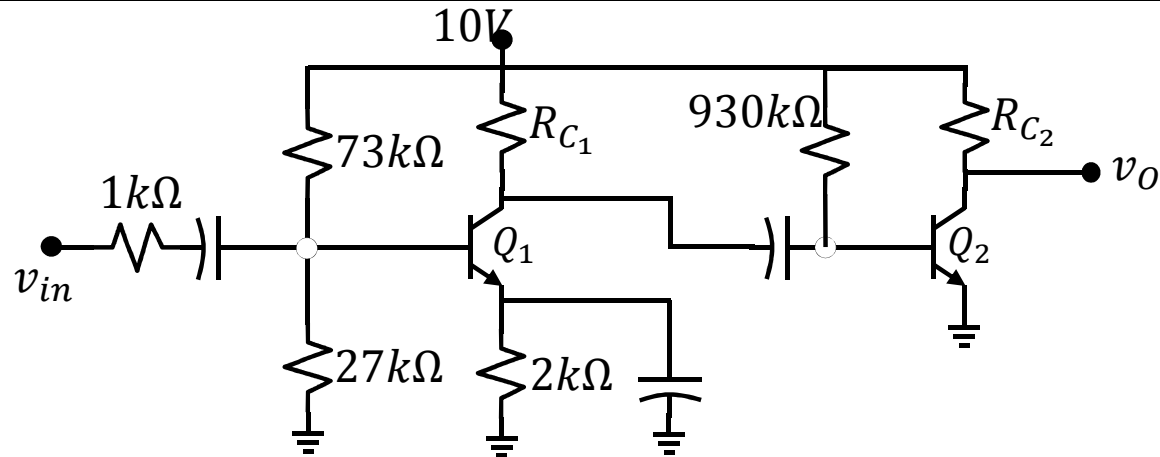


Design an amplifier:

- $I_C = 1mA$
- $\beta = 100$
- $A_v \geq 1000$
- $V_{CC} = 10V$
- $R_S = 1k\Omega$

$$R_{C1} = \frac{10 - 3}{1m} = 7k\Omega$$

$$R_{C2} = \frac{10 - 5}{1m} = 5k\Omega$$

AC circuit

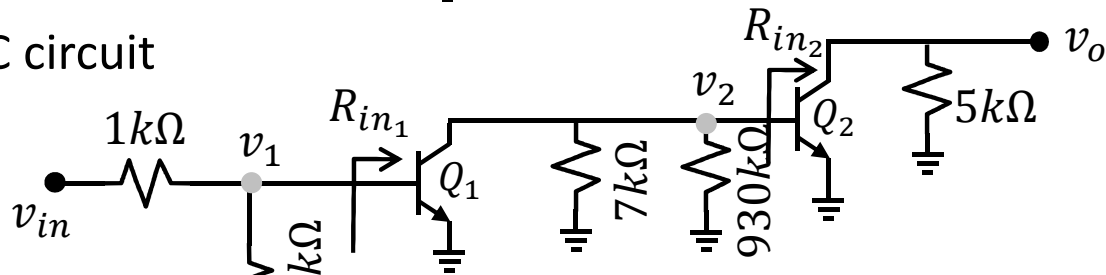


$$A_v = \frac{v_o}{v_i} = \frac{v_1}{v_i} \cdot \frac{v_2}{v_1} \cdot \frac{v_o}{v_2}$$

$$A_v = 10143$$

$$\frac{v_o}{v_2} = -g_{m2} 5^k = -200$$


$$\frac{v_2}{v_1} = -g_{m1} (7 \parallel 930 \parallel r_{\pi 2}) = -73$$

$$\frac{v_1}{v_i} = \frac{20^k \parallel r_{\pi 1}}{20^k \parallel r_{\pi 1} + 1^k} = 0.69$$

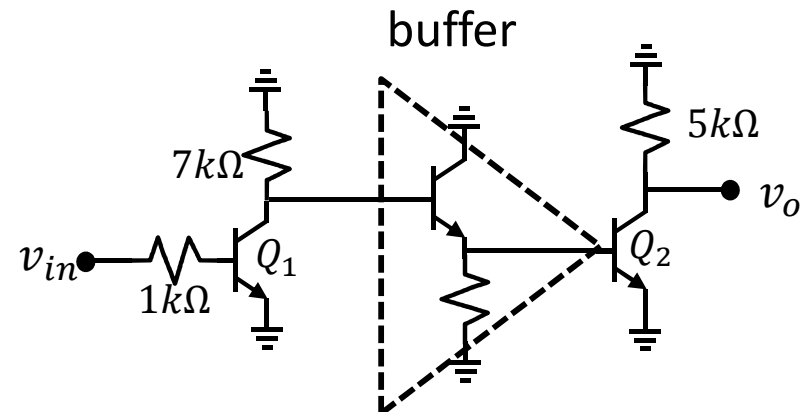


Example 05 – CE , CB, CC


- 1.
- 2.
- 3.
- 4.
- 5.

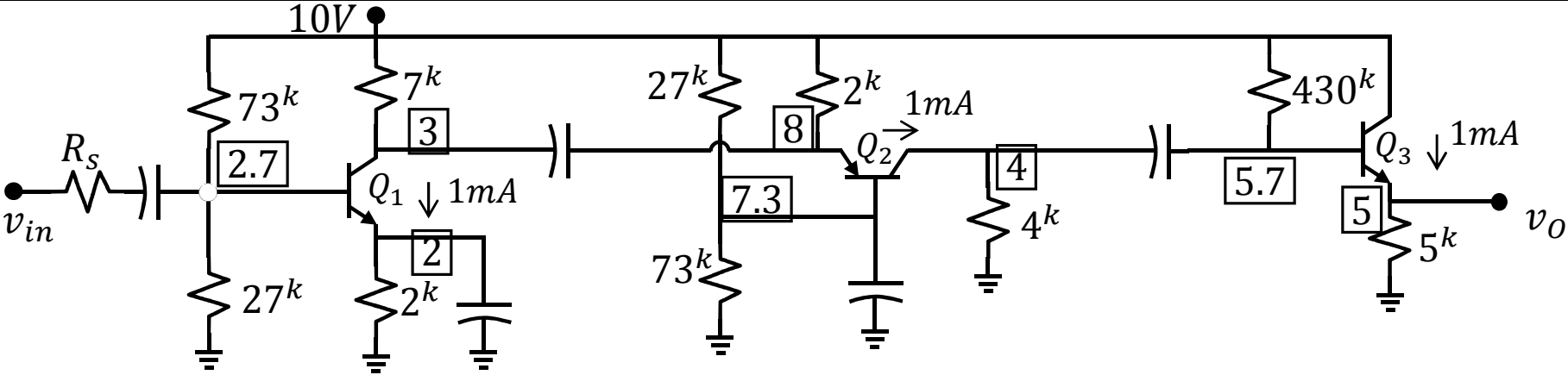



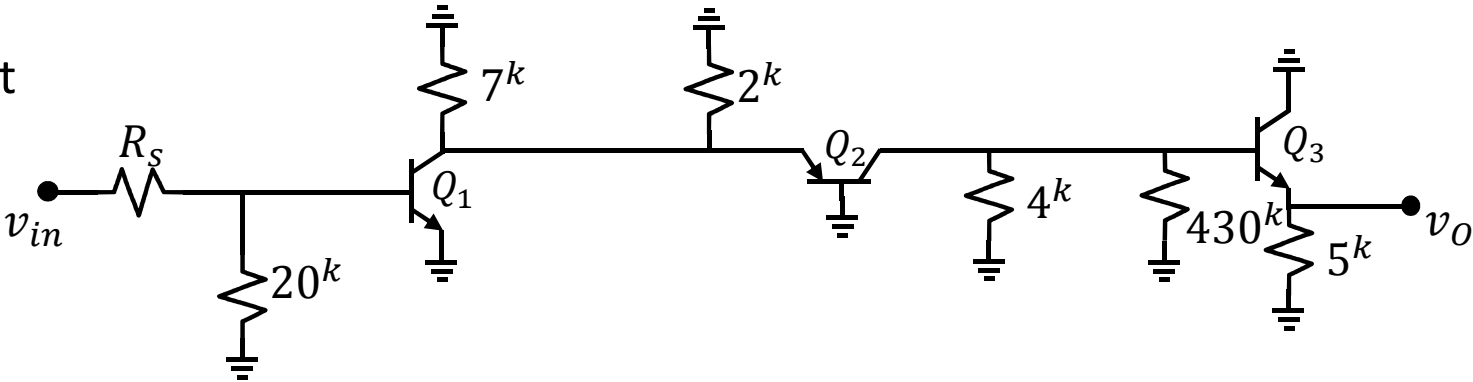


AC circuit









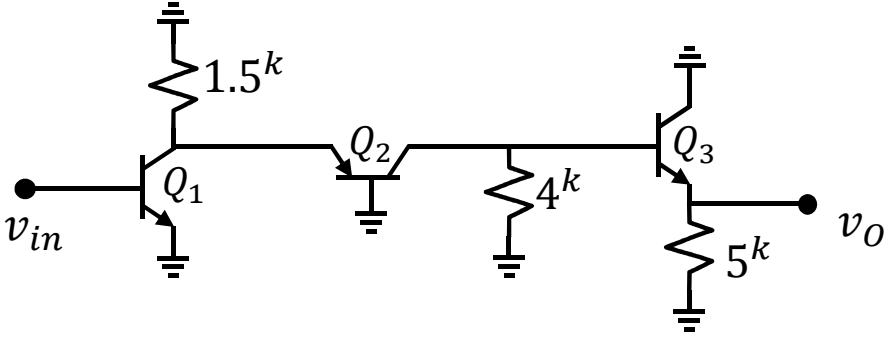


$R_s \ll ?$



Common Base


1. 
2. 
3. 
4. 
5. 

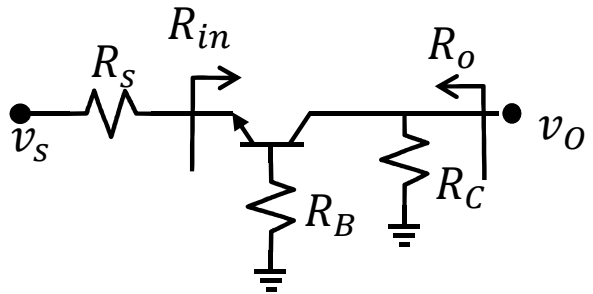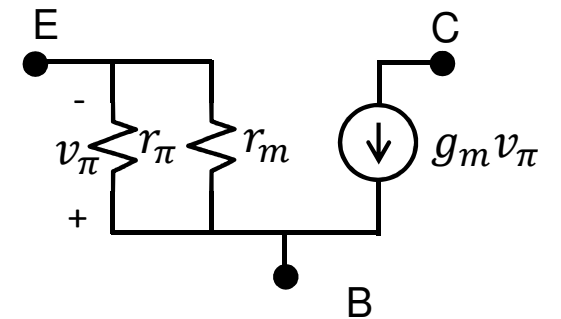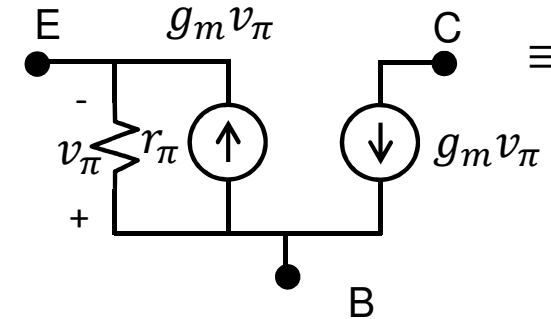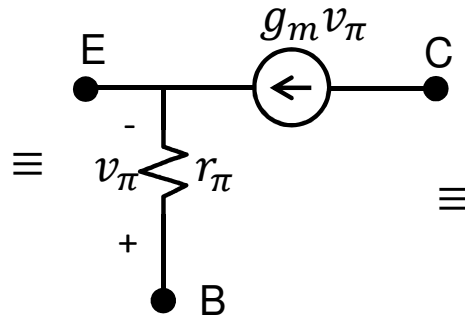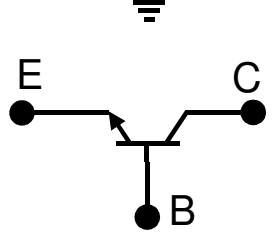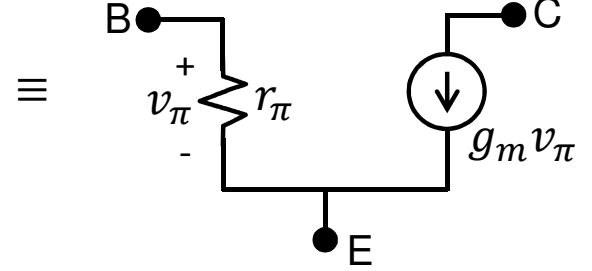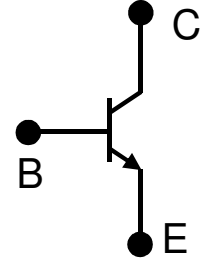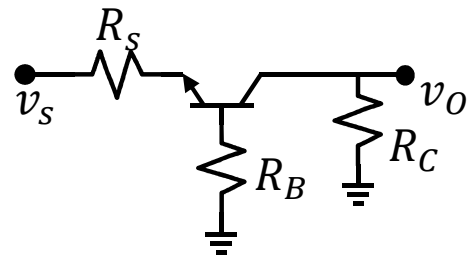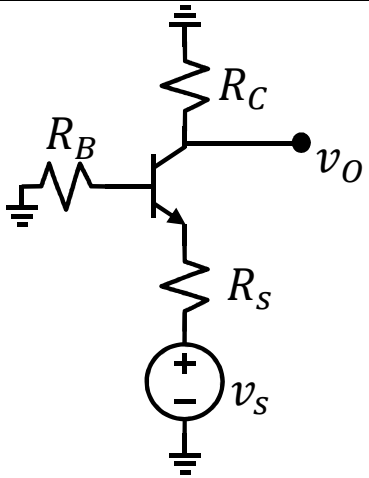

$$R_{in} = \frac{R_B + r_{\pi}}{\beta + 1}$$

$$R_o = R_C$$
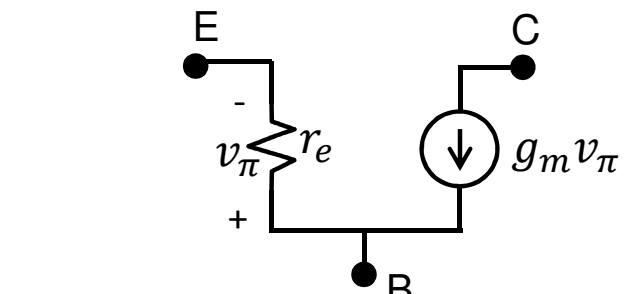
$$A_v = \frac{v_o}{v_s} = \frac{R_C}{\frac{R_B + r_{\pi}}{\beta + 1} + R_S}$$




$$r_e = r_m \parallel r_{\pi} = r_m \frac{\beta}{\beta + 1} \cong r_m$$

Cascode Amplifier, CE-CB


- 1.
- 2.
- 3.
- 4.
- 5.

neglecting
base
current

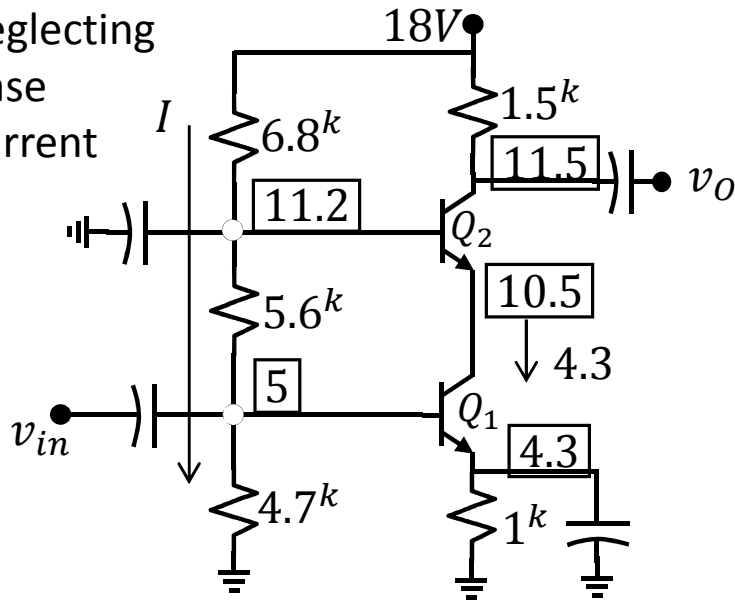

$$I = \frac{18}{6.8 + 5.6 + 4.7} = 1.1 \text{ mA}$$

AC circuit:

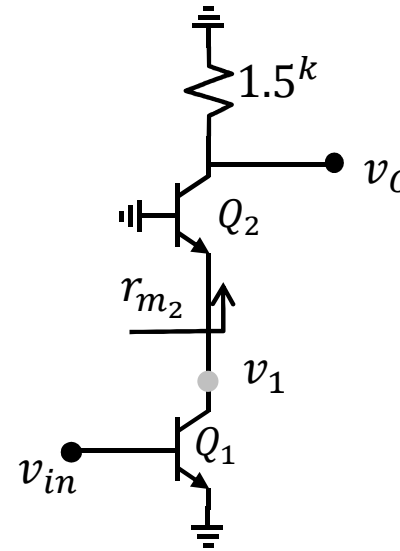






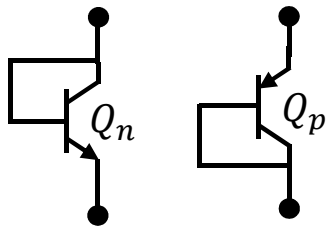
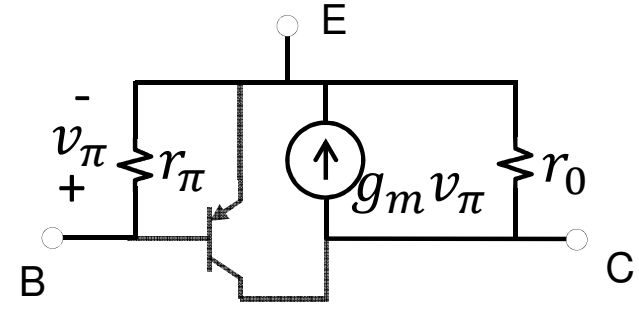
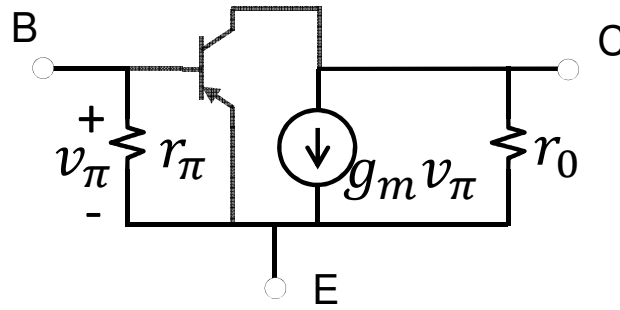
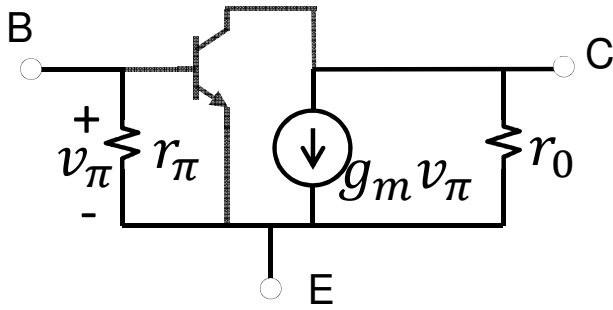
$$\frac{v_1}{v_{in}} = -g_{m_1}(r_{m_2}) = -1$$

$$\frac{v_o}{v_1} = \frac{1.5^k}{\frac{r_{\pi_2}}{\beta}} = 245$$


$$A_v = -245$$

Some Notes:


1. 
2. 
3. 
4. 
5. 



≡

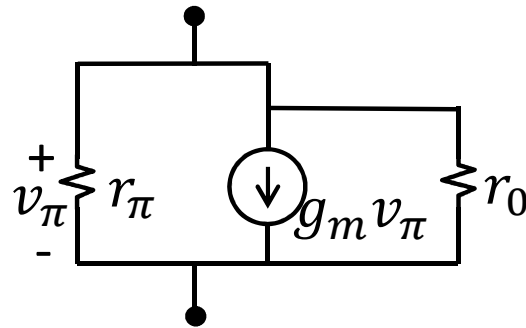


≡

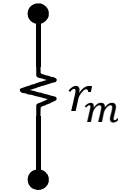

Summary


1.
2.
3.
4.
5.

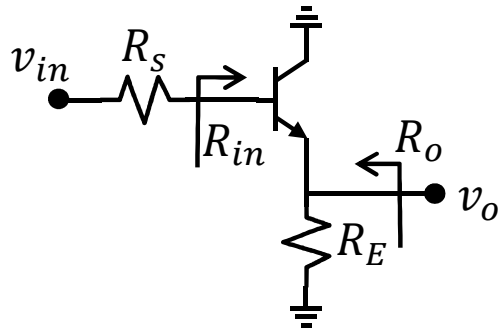

$$\frac{v_o}{v_{in}} = \frac{R_E}{\frac{R_S + r_{\pi}}{1 + \beta} + R_E}$$

$$R_{in} = r_{\pi} + R_E(1 + \beta)$$

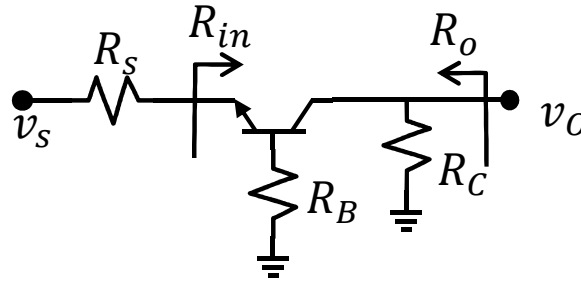
$$R_o = R_E \parallel \frac{R_S + r_{\pi}}{1 + \beta}$$



$$\frac{v_o}{v_s} = \frac{R_C}{\frac{R_B + r_{\pi}}{\beta + 1} + R_S}$$

$$R_{in} = \frac{R_B + r_{\pi}}{\beta + 1}$$

$$R_o = R_C$$

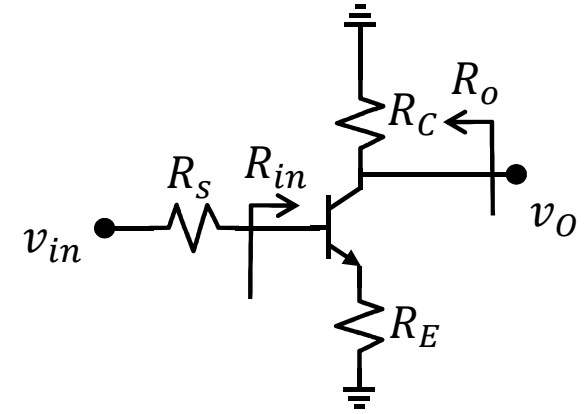


$$\frac{v_o}{v_s} = \frac{-R_C}{\frac{R_S + r_{\pi}}{\beta + 1} + R_E}$$

$$R_{in} = r_{\pi} + R_E(1 + \beta)$$

$$R_o = R_C$$

? V_A

- 1.
- 2.
- 3.
- 4.
- 5.

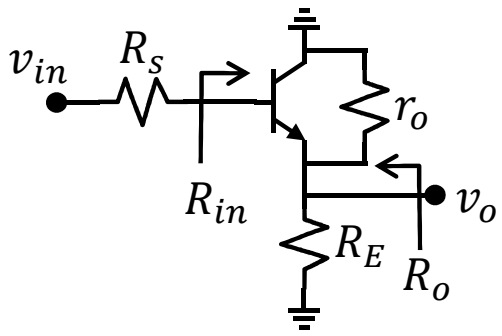


$$r_o = \infty$$

$$\frac{v_o}{v_{in}} = \frac{R_E}{\frac{R_S + r_{\pi}}{1 + \beta} + R_E}$$

$$R_{in} = r_{\pi} + R_E(1 + \beta)$$
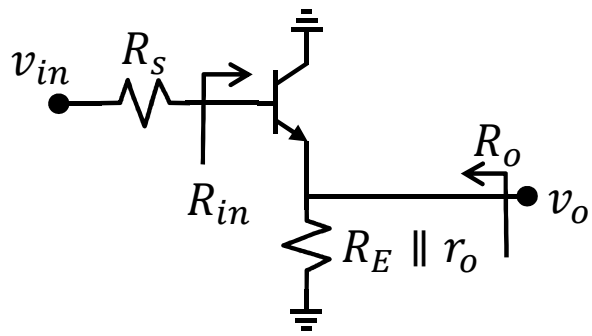
$$R_o = R_E \parallel \frac{R_S + r_{\pi}}{1 + \beta}$$






$$\frac{v_o}{v_{in}} = \frac{R_E \parallel r_o}{\frac{R_S + r_{\pi}}{1 + \beta} + R_E \parallel r_o}$$

$$R_{in} = r_{\pi} + (R_E \parallel r_o)(1 + \beta)$$


$$R_o = R_E \parallel r_o \parallel \frac{R_S + r_{\pi}}{1 + \beta}$$

Input / Output Impedances


- 1.
- 2.
- 3.
- 4.
- 5.

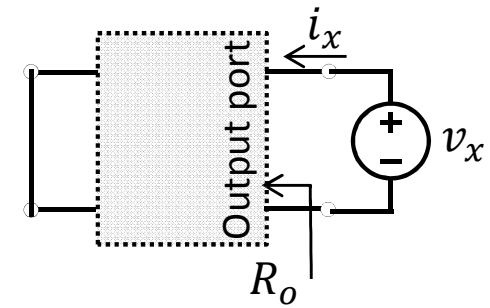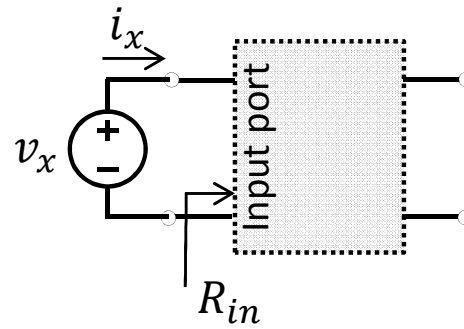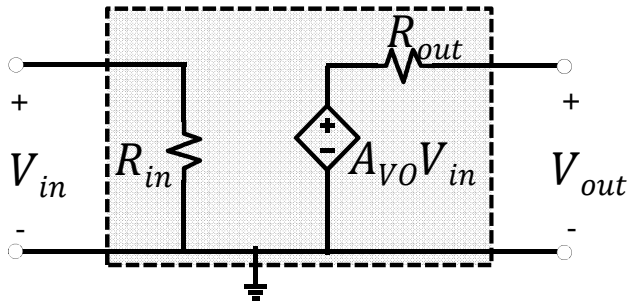

DC Analysis


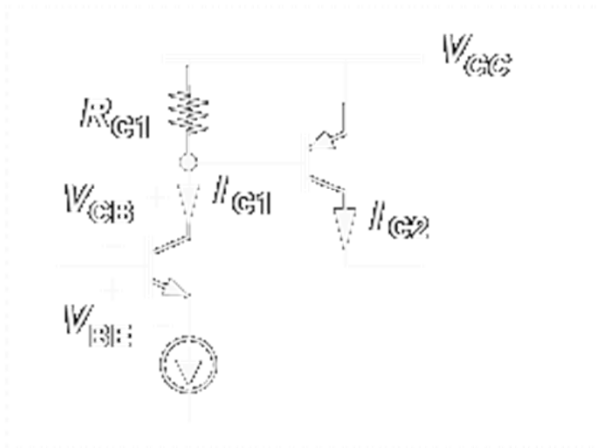


Small Signal Analysis

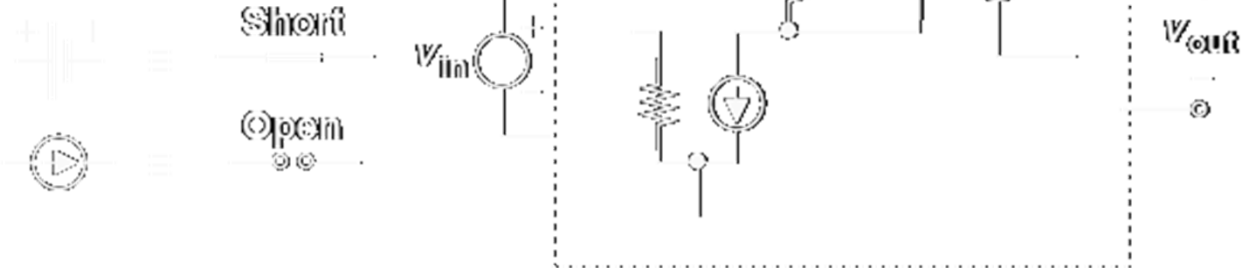


? V_A

1.
2.
3.
4.
5.

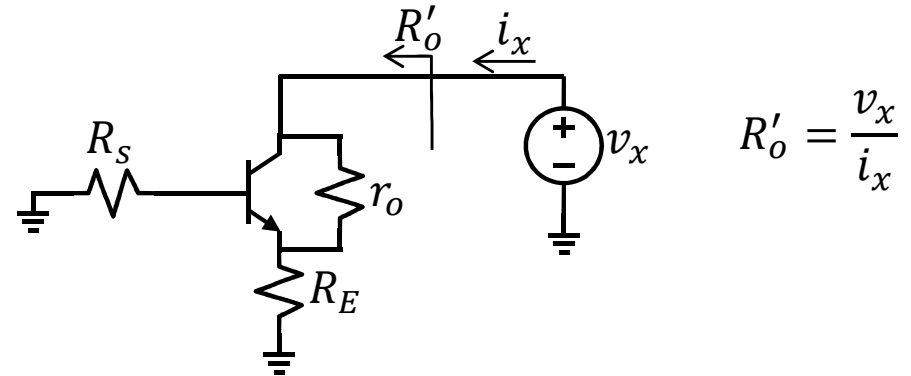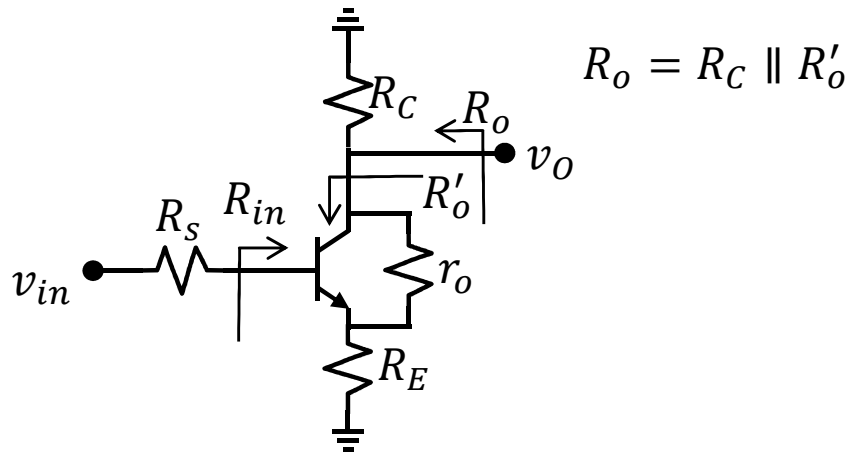
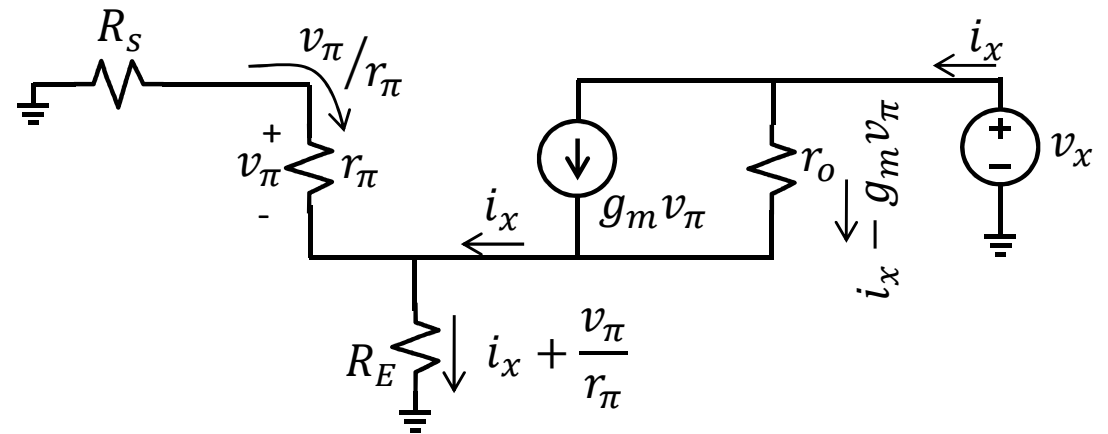
$$\begin{cases} R_s \frac{v_\pi}{r_\pi} + v_\pi + R_E \left(i_x + \frac{v_\pi}{r_\pi} \right) = 0 \\ v_x = r_o (i_x - g_m v_\pi) + R_E \left(i_x + \frac{v_\pi}{r_\pi} \right) \end{cases}$$








$$R'_o = \frac{v_x}{i_x} = r_o \left(1 + \frac{\beta R_E}{R_s + r_\pi + R_E} \right) + R_E \parallel (R_s + r_\pi)$$


$$\cong r_o \left(1 + \frac{\beta R_E}{R_s + r_\pi + R_E} \right)$$

$$R_s = 0 \rightarrow \begin{cases} R_E \ll r_\pi : R'_o = r_o (1 + g_m R_E) \\ R_E \gg r_\pi : R'_o = \beta r_o \end{cases}$$


Nonlinear Transfer Function

Biasing

1. 
2. 
3. 
4. 
5. 

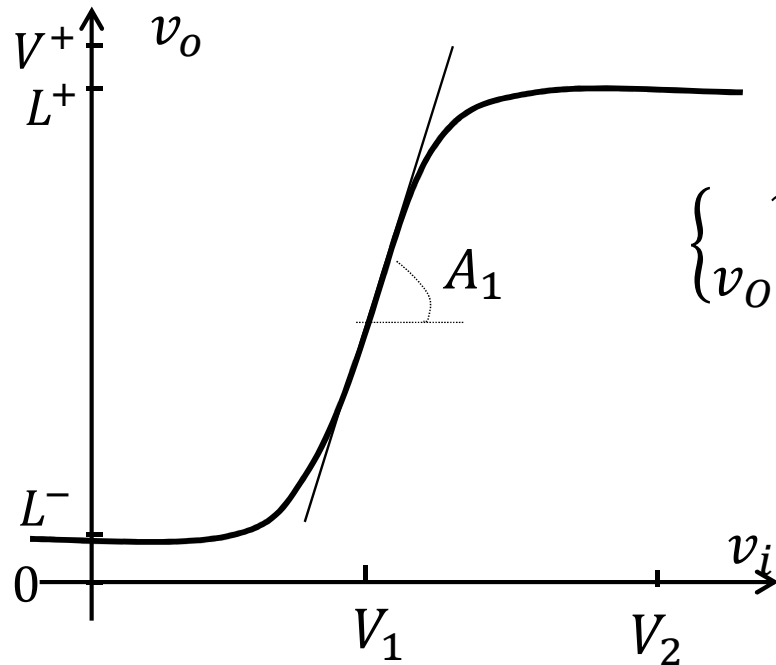

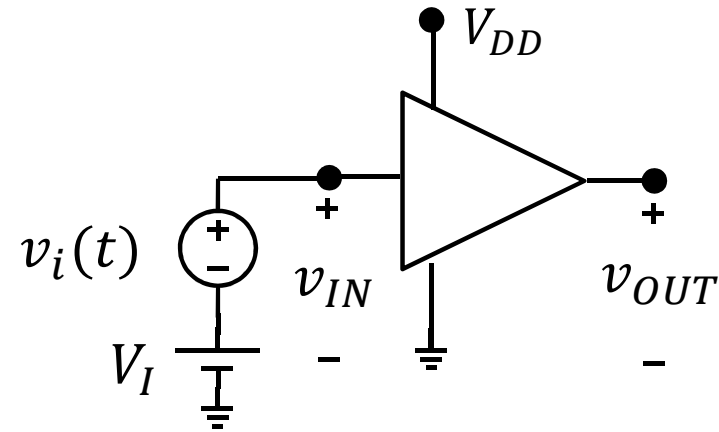
$$\begin{cases} v_{IN} = V_I + v_i(t) \\ v_{OUT} = V_O + A_v v_i(t) \end{cases}$$



$$V_I = 0 \rightarrow A_v = 0$$



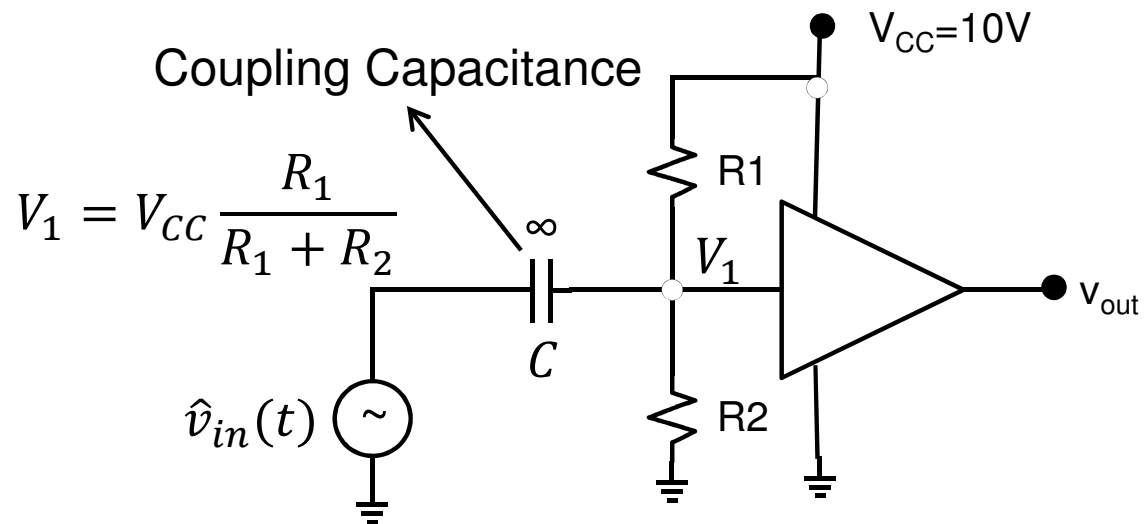


$$V_I = V_1 \rightarrow A_v = A_1$$


$$V_I = V_2 \rightarrow A_v = 0$$







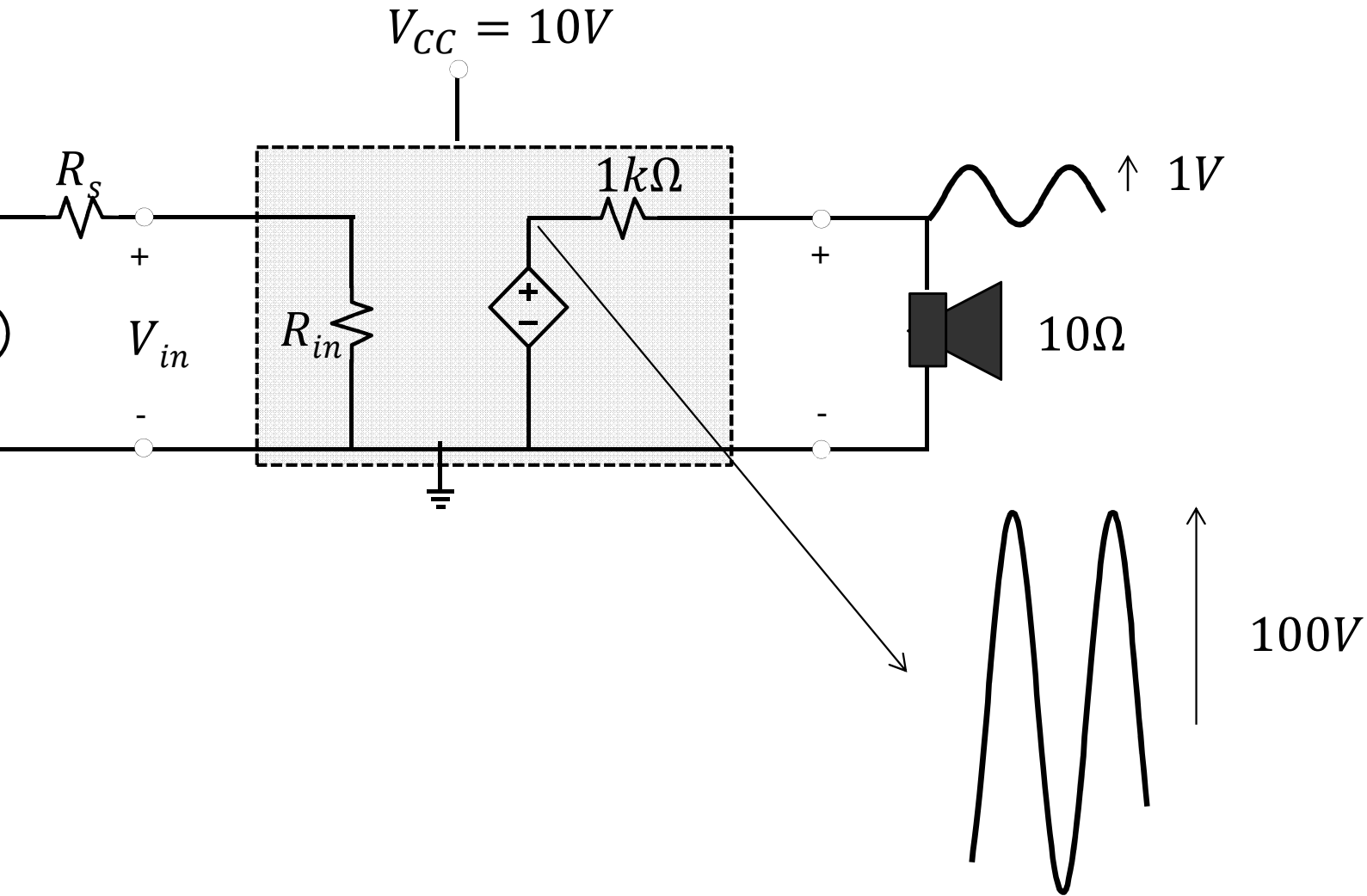

$$v_{out}(t) = V_{out} + A_v \hat{v}_{in}(t)$$


Practical Consideration

1. 
2. 
3. 
4. 
5. 



Practical Consideration: Input / Output Resistance

1.  
2. 
3. 
4. 
5. 


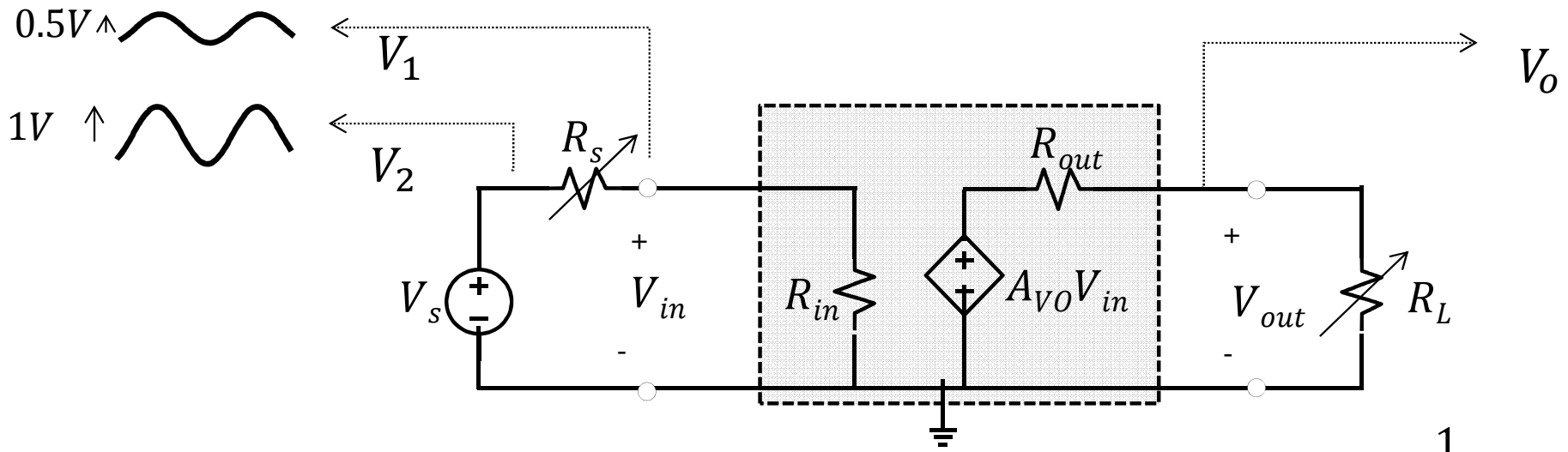


$$R_S = 1k\Omega \rightarrow \frac{V_1}{V_2} = \frac{R_{in}}{R_{in} + 1k}$$






$$R_{in} = 1k \times \frac{1}{\frac{V_2}{V_1} - 1}$$

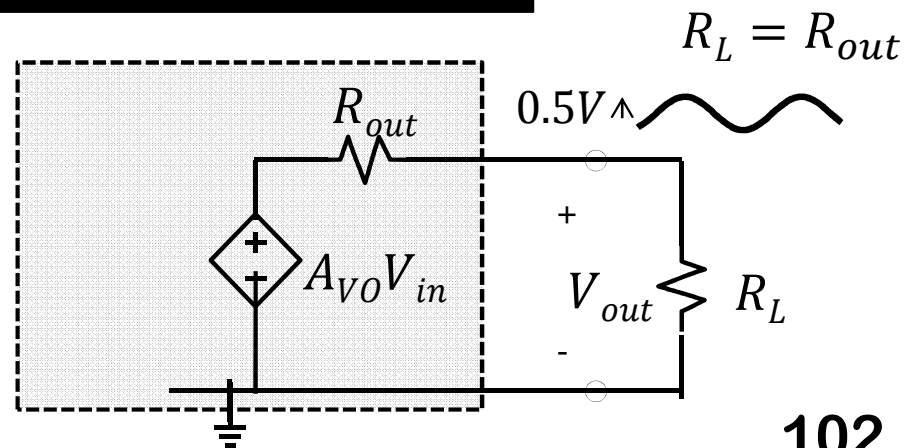
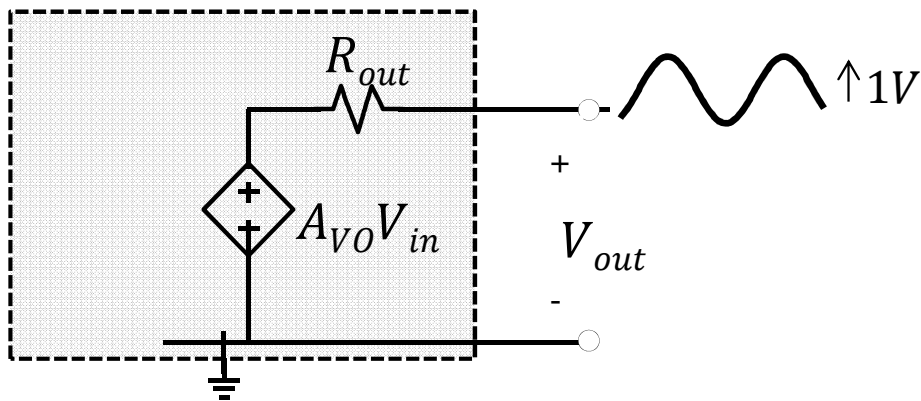
How about R_{out} ?

NOTE: You need to make sure circuit is in its linear operation regime



Amplifier Frequency Response

1. 
2. 
3. 
4. 
5. 

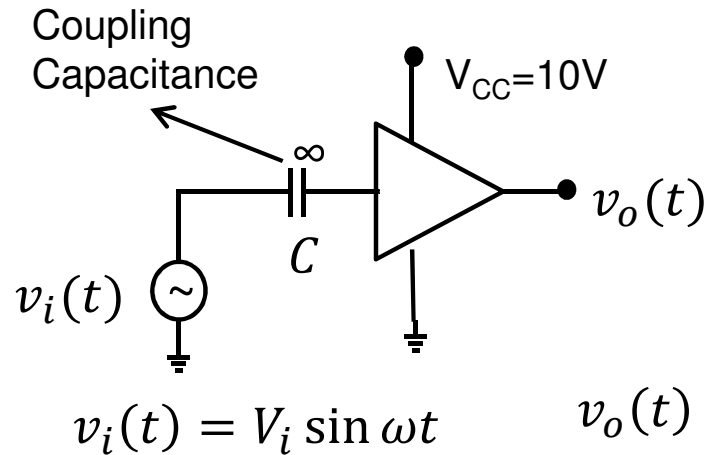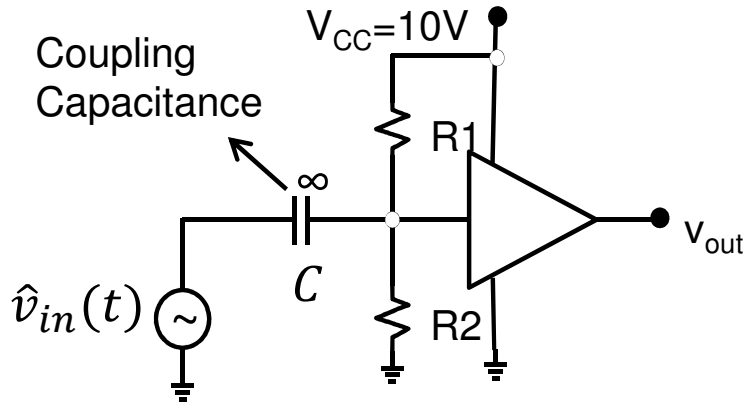


Transfer Function: $T(\omega) = \frac{v_o}{v_i}$






$|T(\omega)| = \frac{V_o}{V_i}$

Amplitude in dB

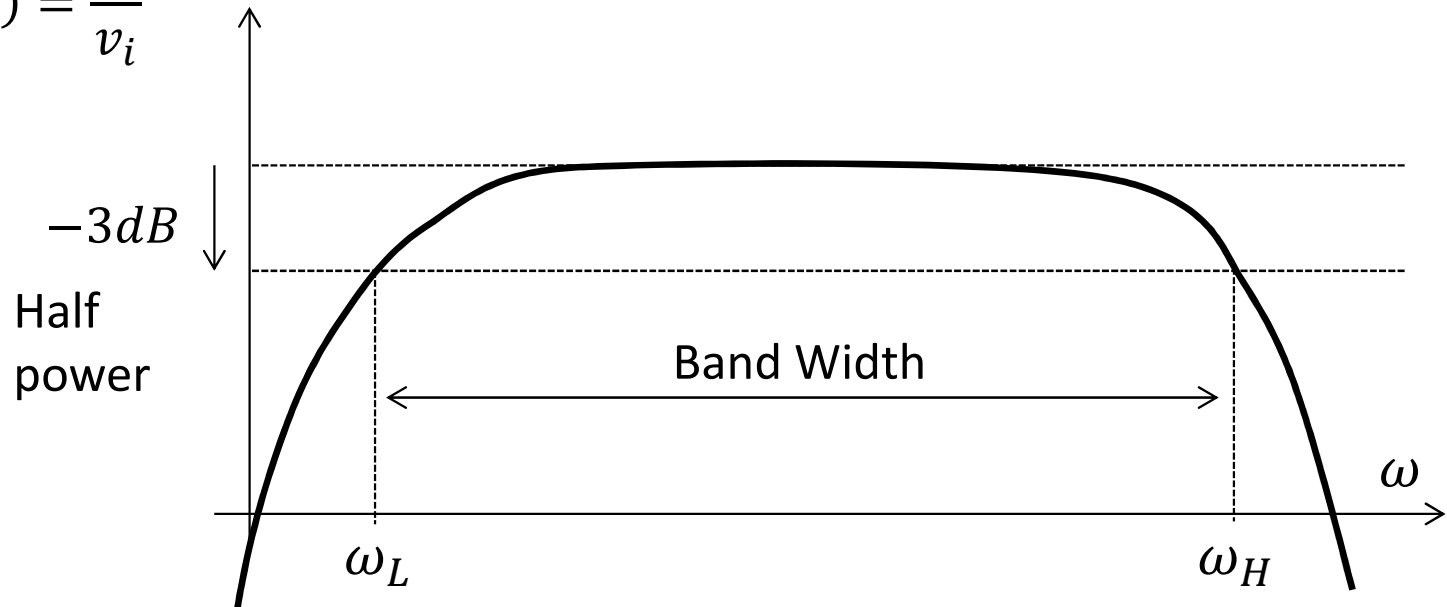$\angle T(\omega) = \varphi$

Phase



1. 
 2. 
 3. 
 4. 
 5. 
-

1.



2.



3.



4.



5.



- 1.
- 2.
- 3.
- 4.
- 5.

