
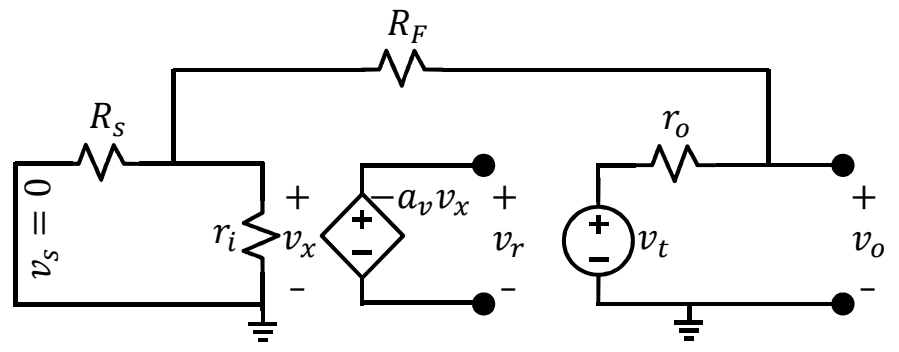


# Return Ratio!

1.	██████████
2.	██████████████
3.	██████████
4.	████
5.	████

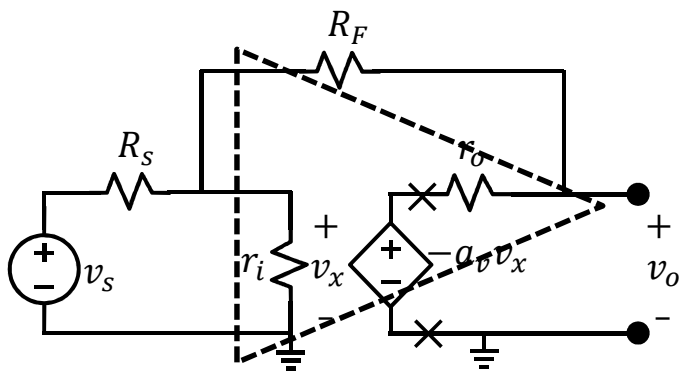1. Set all independent sources to zero
2. Break the feedback loop by disconnecting a dependent source
3. Call signal right after dependent source:  $s_t$
4. Call the return signal by dependent source:  $s_r$

Define return ratio of that dependent source as  $\mathcal{R} = -s_r/s_t$




$$v_x = \frac{r_i \parallel R_s}{r_i \parallel R_s + R_F + r_o} v_t \quad v_r = -a_v v_x$$

$$\mathcal{R} = -\frac{v_r}{v_t} = a_v \frac{r_i \parallel R_s}{r_i \parallel R_s + R_F + r_o}$$

# Return Ratio!

1.
2.
3.
4.
5.

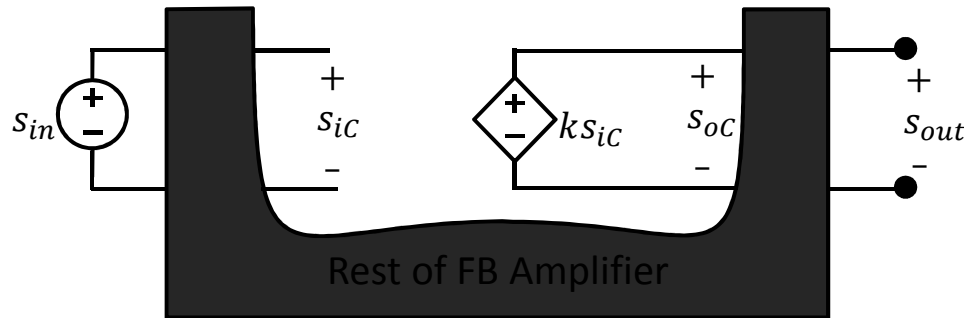

$$s_{ic} = \frac{B_1}{1 + kH} s_{in}$$

$$A = \frac{s_{out}}{s_{in}} = \frac{kB_1B_2}{1 + kH} + d$$

$$s_{in} = 0 \rightarrow s_{ic} = -Hs_{oc} \rightarrow \mathcal{R} = kH$$

$$A = \frac{s_{out}}{s_{in}} = \frac{g}{1 + \mathcal{R}} + d = \frac{\mathcal{R}(\frac{g}{\mathcal{R}} + d)}{1 + \mathcal{R}} + \frac{d}{1 + \mathcal{R}}$$

$$A_\infty = \frac{g}{\mathcal{R}} + d \quad A = \frac{\mathcal{R}}{1 + \mathcal{R}} A_\infty + \frac{d}{1 + \mathcal{R}}$$

$$s_{oc} = k s_{ic}$$

$$s_{ic} = B_1 s_{in} - H s_{oc}$$

$$s_{out} = d s_{in} + B_2 s_{oc}$$

$$B_1 = \left. \frac{s_{ic}}{s_{in}} \right|_{s_{oc}=0} = \left. \frac{s_{ic}}{s_{in}} \right|_{k=0}$$

$$B_2 = \left. \frac{s_{out}}{s_{oc}} \right|_{s_{in}=0}$$




$$H = - \left. \frac{s_{ic}}{s_{oc}} \right|_{s_{in}=0}$$

$$d = \left. \frac{s_{out}}{s_{in}} \right|_{s_{oc}=0} = \left. \frac{s_{out}}{s_{in}} \right|_{k=0}$$

# Return Ratio!

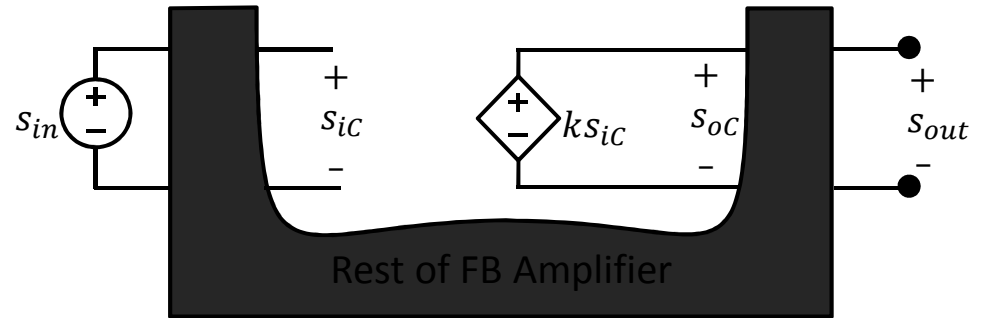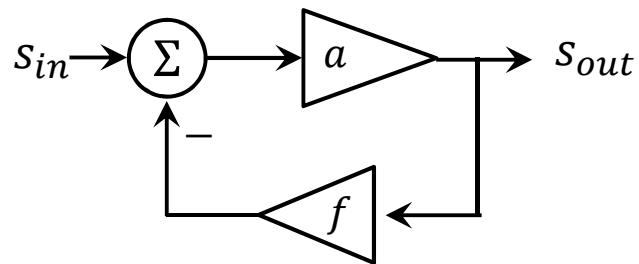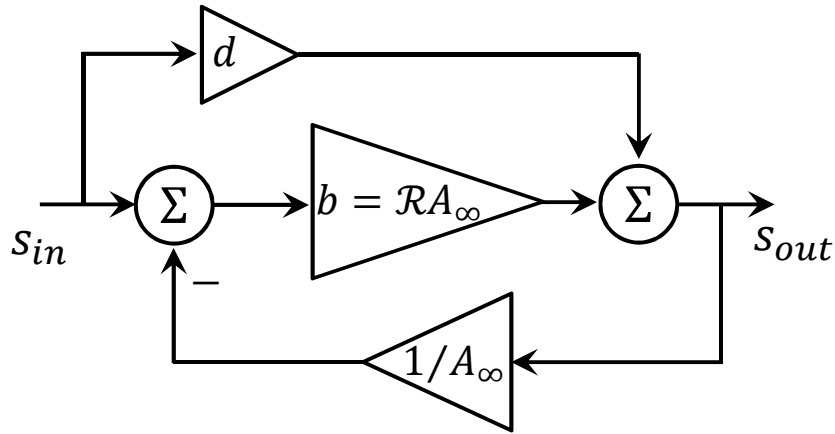
1.
2.
3.
4.
5.

$$A = \frac{\mathcal{R}}{1 + \mathcal{R}} A_{\infty} + \frac{d}{1 + \mathcal{R}}$$



# Return Ratio!

1.
2.
3.
4.
5.

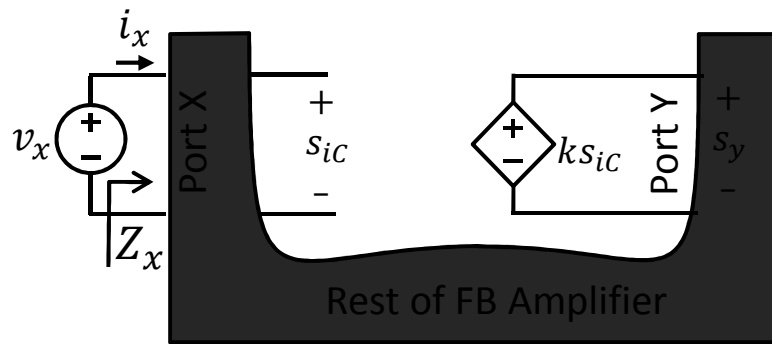

Linear circuit

$$v_x = a_1 i_x + a_2 s_y$$

$$s_{ic} = a_3 i_x + a_4 s_y$$

$$Z_{port} \Big|_{k=0} = \frac{v_x}{i_x} \Big|_{k=0} = \frac{v_x}{i_x} \Big|_{s_y=0} = a_1$$

$$Z_{port} = \frac{v_x}{i_x} = a_1 \frac{1 - k \left( a_4 - \frac{a_2 a_3}{a_1} \right)}{1 - k a_4}$$

Port Open:  $i_x = 0$        $s_{ic} = a_4 s_y$   
 $s_r = k s_{ic}$

$$\mathcal{R}(\text{open}) = -\frac{s_r}{s_t} = -k a_4$$

Port Short:  $v_x = 0$        $i_x = -\frac{a_2}{a_1} s_y$        $s_y = s_t$

$$s_{ic} = \left( a_4 - \frac{a_2 a_3}{a_1} \right) s_t$$




$$s_r = k s_{ic}$$

$$\mathcal{R}(\text{short}) = -\frac{s_r}{s_t} = -k \left( a_4 - \frac{a_2 a_3}{a_1} \right)$$

$$Z_{port} = Z_{port} \Big|_{k=0} \frac{1 + \mathcal{R}(\text{short})}{1 + \mathcal{R}(\text{open})}$$

Blackman's impedance formula

1.
2.
3.
4.
5.

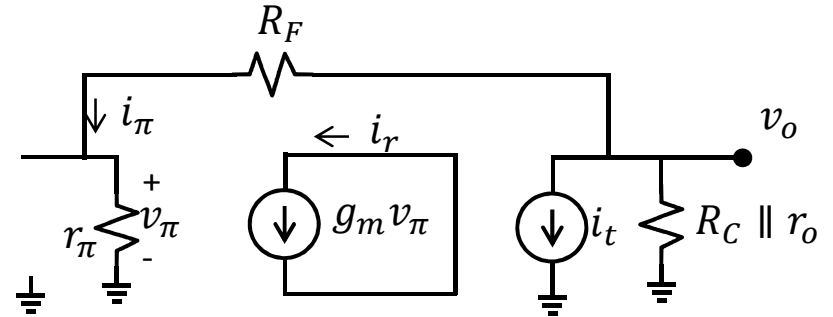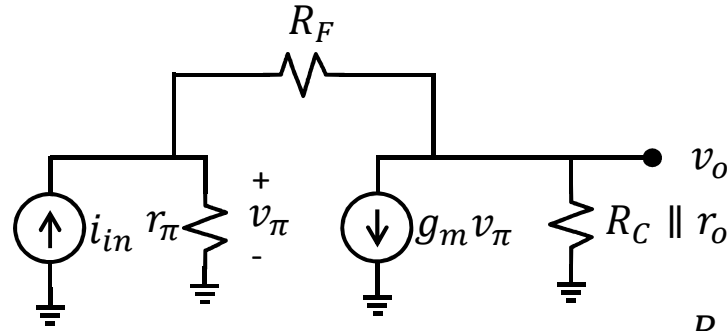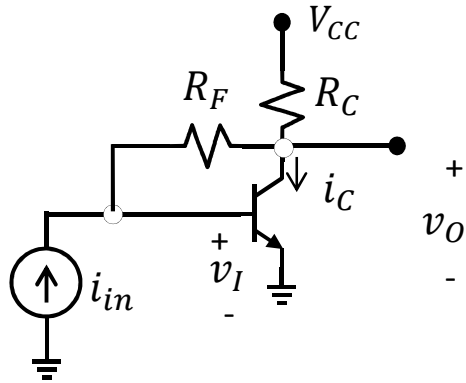

$$A_{\infty} = \left. \frac{v_o}{i_{in}} \right|_{g_m = \infty} = -R_F$$

$$d = \left. \frac{v_o}{i_{in}} \right|_{g_m = 0} = [r_{\pi} \parallel (R_F + R_C \parallel r_o)] \frac{R_C \parallel r_o}{R_F + R_C \parallel r_o}$$

$$i_{\pi} = -\frac{R_C \parallel r_o}{r_{\pi} + R_F + R_C \parallel r_o} i_t$$

$$i_r = g_m r_{\pi} i_t$$

$$\mathcal{R} = -\frac{i_r}{i_t} = \frac{g_m r_{\pi} (R_C \parallel r_o)}{r_{\pi} + R_F + R_C \parallel r_o}$$

$$A = \frac{\mathcal{R}}{1 + \mathcal{R}} A_{\infty} + \frac{d}{1 + \mathcal{R}}$$






$$R_{out} = Z_{out} \Big|_{g_m = 0} \frac{1 + \mathcal{R}(\text{short})}{1 + \mathcal{R}(\text{open})}$$

$$= [(r_{\pi} + R_F) \parallel R_C \parallel r_o] \frac{1 + 0}{1 + \mathcal{R}}$$

Session ?:  
Principles of Electronics


# Voltage Regulators

# Voltage Regulators

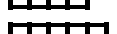1. 
2. 
3. 
4. 
5. 


---

## Power Supplies (Voltage Regulators)

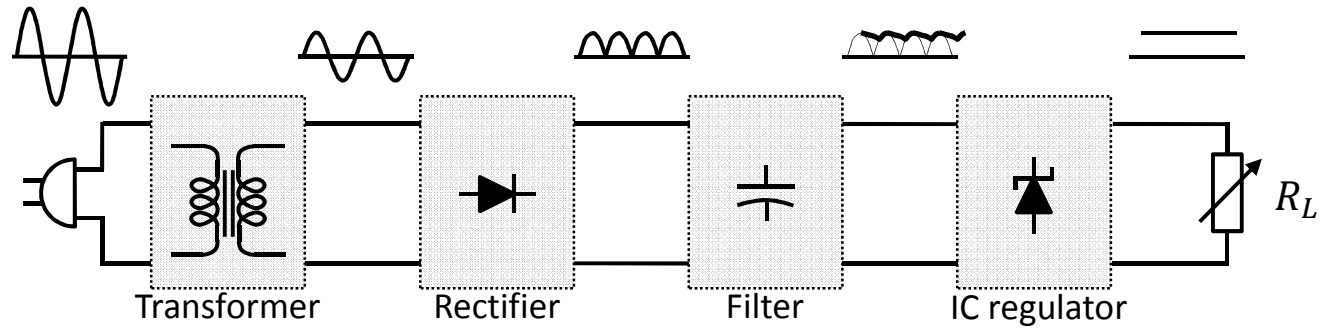

# Definitions

1.
2.
3.
4.
5.

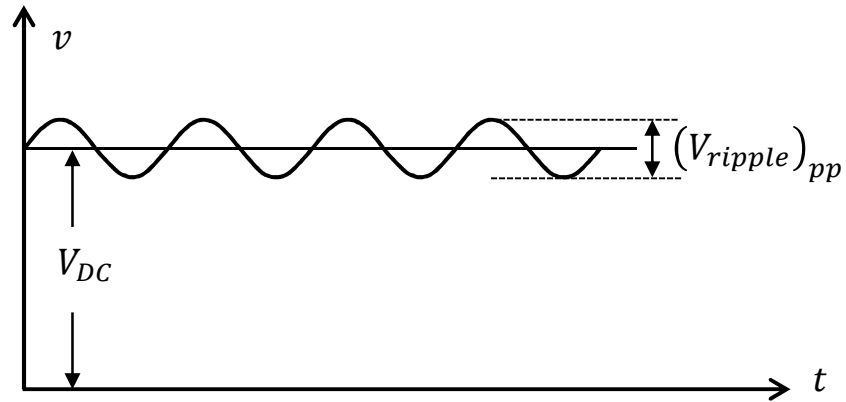

Ripple Voltage






$$r \equiv \frac{V_{r(rms)}}{V_{DC}} \times 100\%$$




Voltage Regulation

$$\%V.R. \equiv \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$




# Rectifier

1. 
2. 
3. 
4. 
5. 

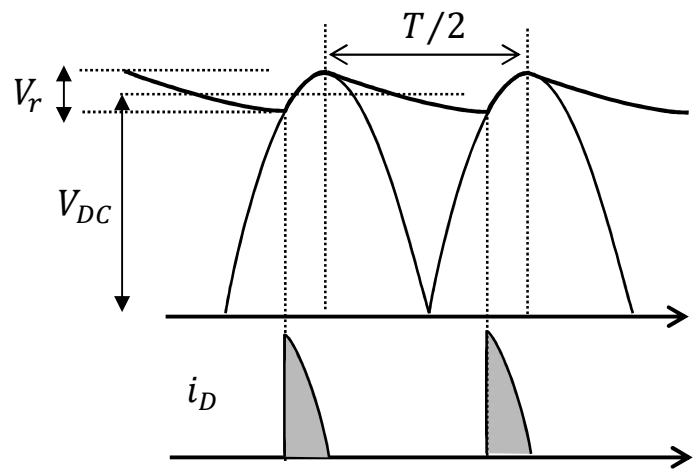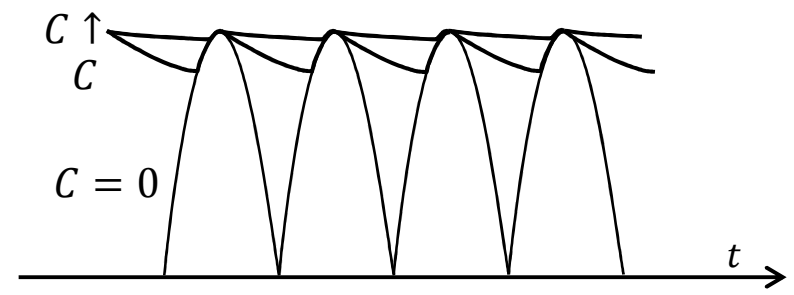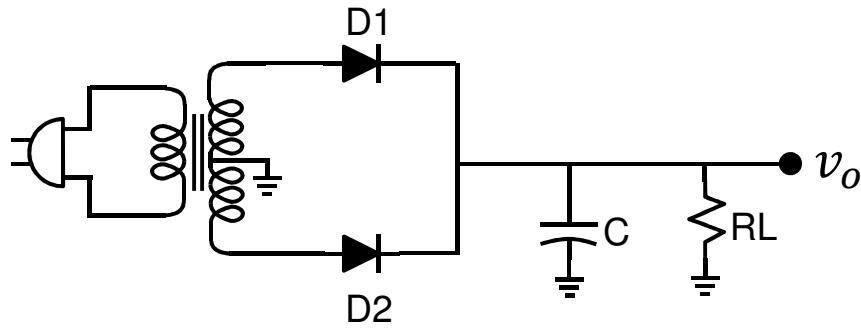

$$V_r = \frac{I_{DC}}{2fC}$$

$$V_{DC} = V_m - \frac{V_r}{2}$$

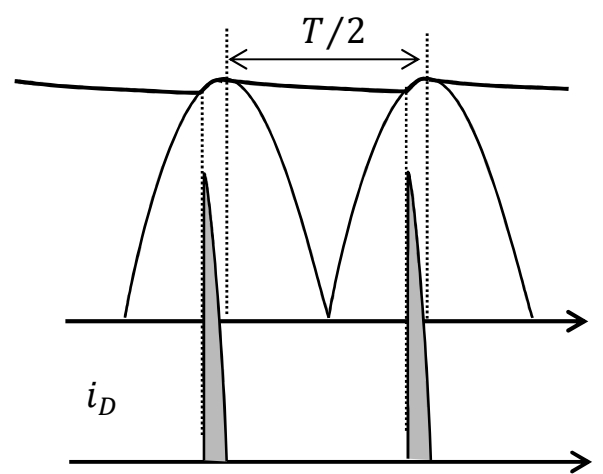


$$C \nearrow \Rightarrow \begin{matrix} V_r \searrow \\ i_{Dmax} \nearrow \end{matrix}$$



# Zener Diode

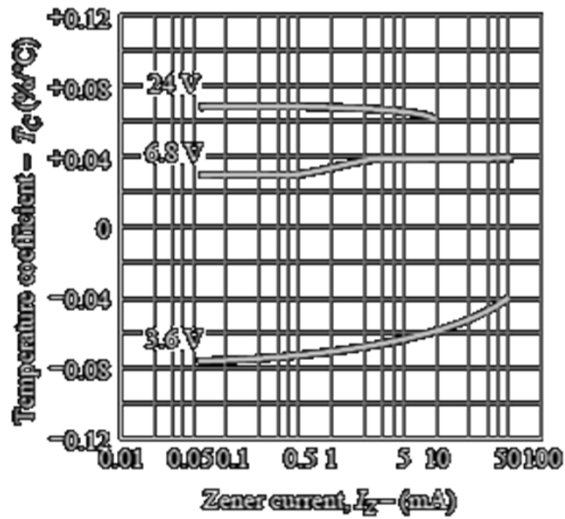1.
2.
3.
4.
5.


Temperature coefficient versus Zener current



Dynamic impedance versus Zener current

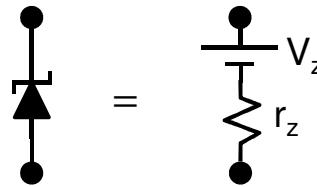
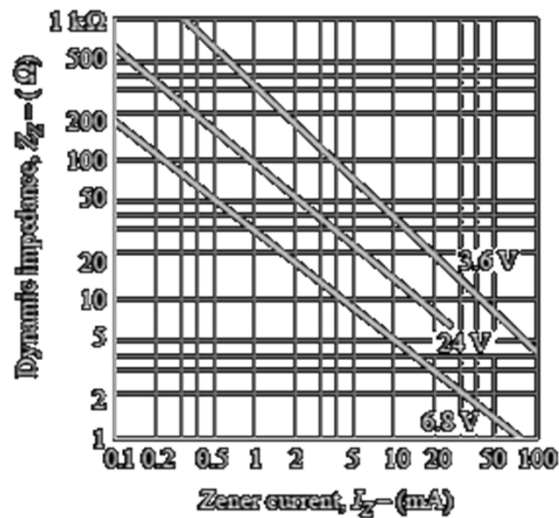

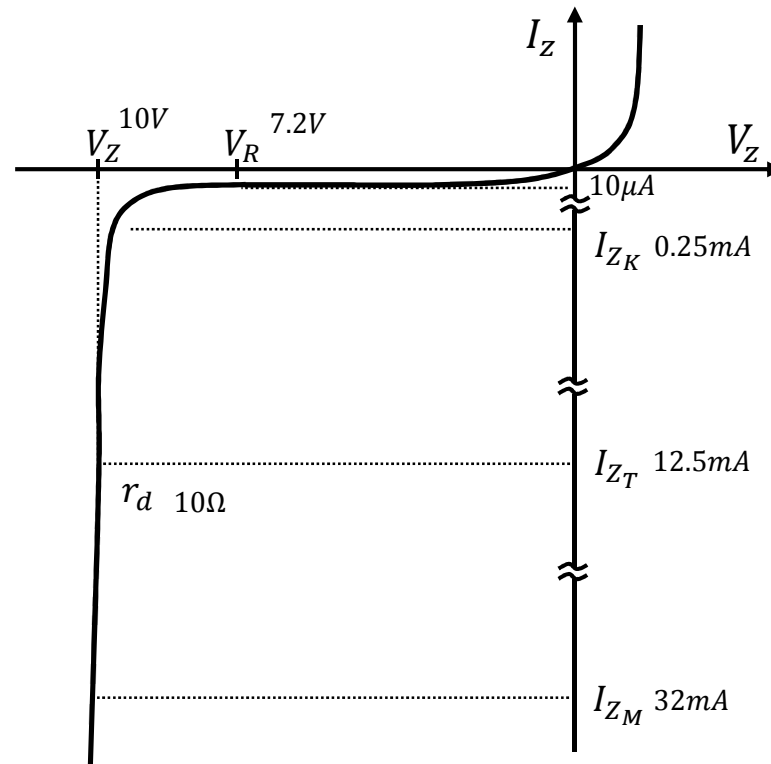
$$T_c = \frac{\Delta V_Z / V_Z}{T_1 - T_0} \times 100\% + 0.072(\%/^{\circ}\text{C})$$




# Zener Diode Regulator


1.
2.
3.
4.
5.

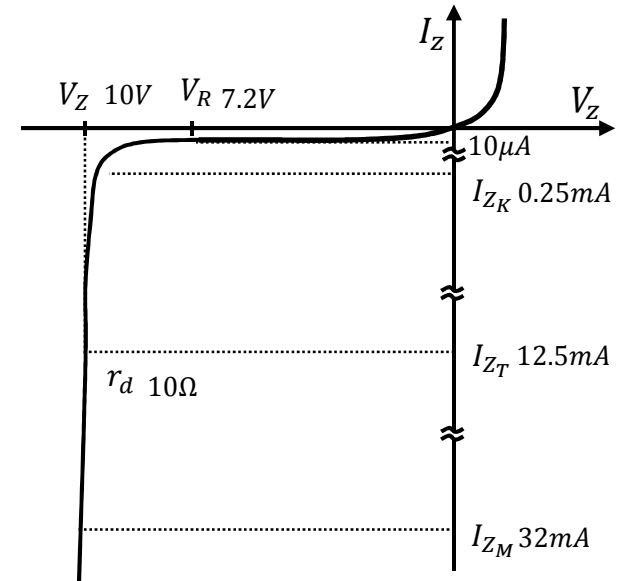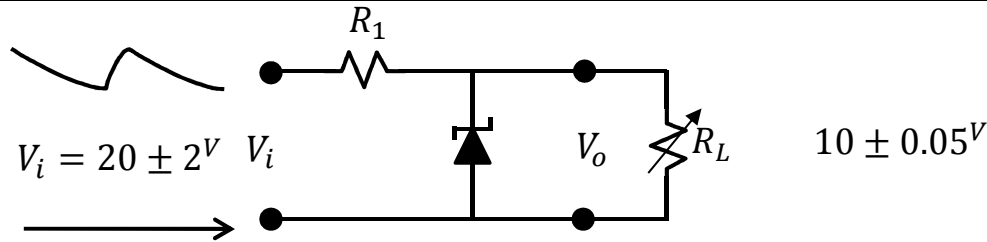

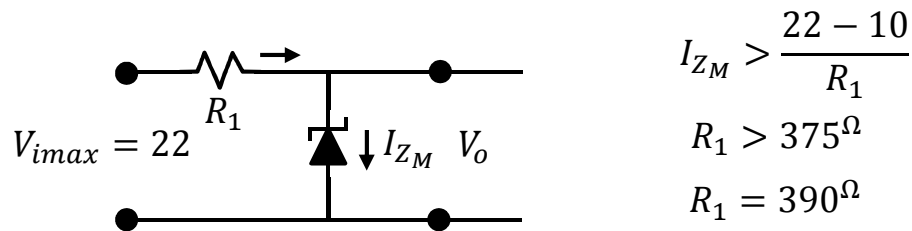1. Find  $R_1$  such that circuits work for no load



2. Find  $R_{Lmin}$

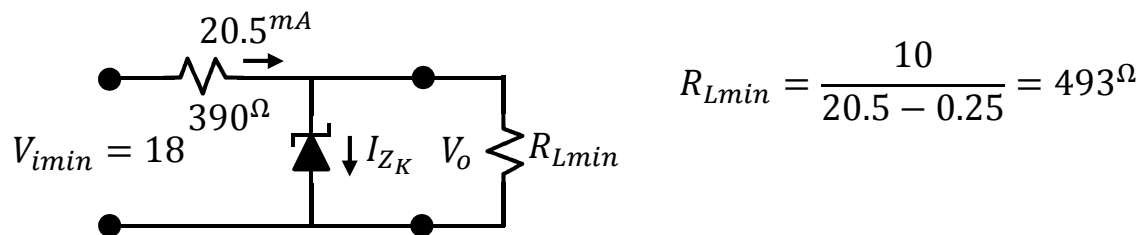


3. Find output ripple

$$V_{Or} = V_{ir} \frac{r_d}{r_d + R_1} = 0.1V$$

$$V_o = 10 \pm 0.05V$$

# Stability Measures

1.
2.
3.
4.
5.

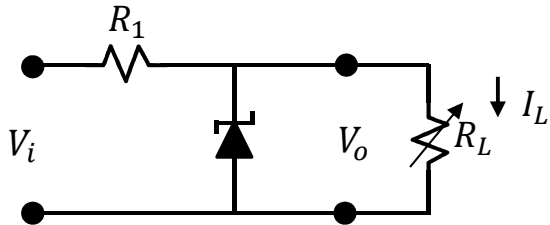

$$V_o = V_o(I_L, V_i, T)$$

Stability measures




$$S_I = \left. \frac{\partial V_o}{\partial I_L} \right|_{\substack{V_i = cte \\ T = cte}}$$

$$S_V = \left. \frac{\partial V_o}{\partial V_i} \right|_{\substack{I_L = cte \\ T = cte}}$$


$$S_T = \left. \frac{\partial V_o}{\partial T} \right|_{\substack{I_L = cte \\ V_i = cte}}$$

# Series Voltage Regulators

1.
2.
3.
4.
5.

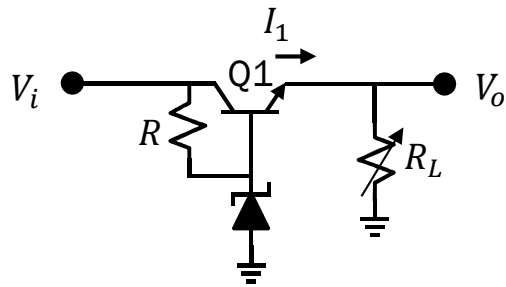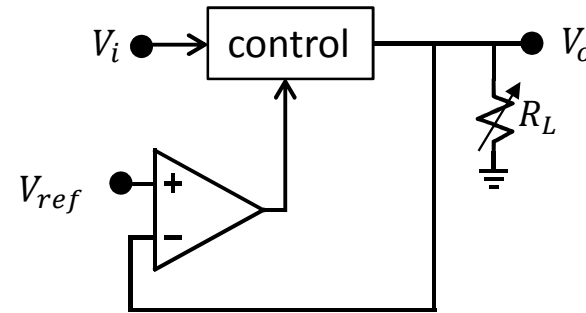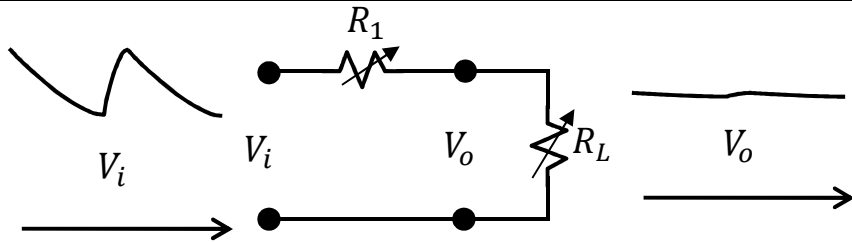


⊖ feedback

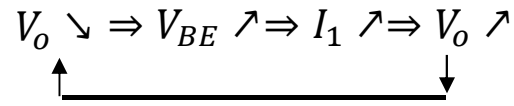


# Series Voltage Regulators

1.
2.
3.
4.
5.

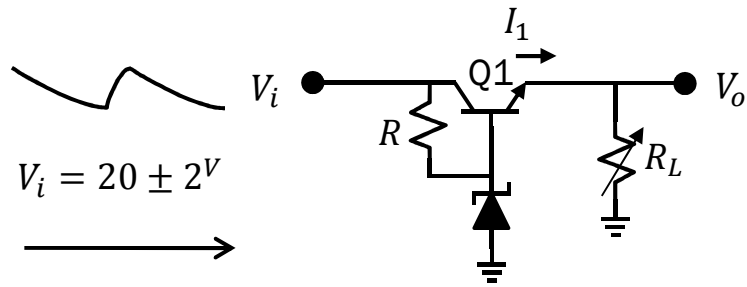

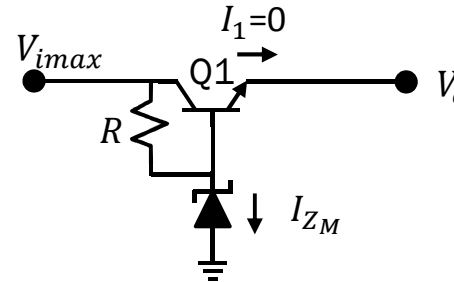1. Find  $R$  such that circuits work for no load




$$I_{ZM} > \frac{22 - 10}{R}$$

$$R > 375\Omega$$

$$R = 390\Omega$$


2. Find  $R_{Lmin}$

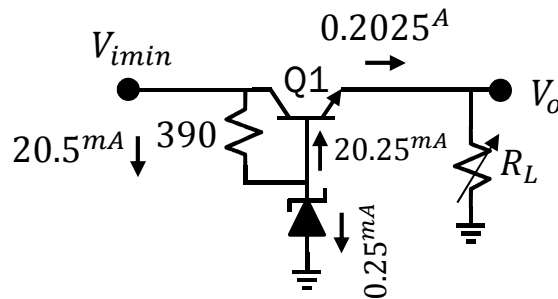

$$R_{Lmin} = \frac{9.3}{0.2025} = 4.6\Omega$$

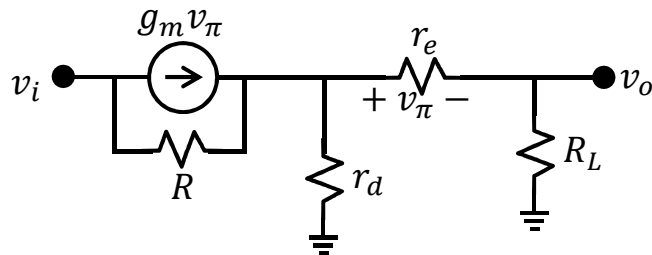3. Find output ripple

$$R_L = 100\Omega, I_C = 93mA, r_m = 0.26\Omega$$




$$V_{or} = V_{ir} \frac{r_d}{r_d + R} \frac{R_L}{R_L + r_m} \cong V_{ir} \frac{r_d}{r_d + R} = 0.1$$

$$V_o = 9.3 \pm 0.05V$$

# Series Voltage Regulators


1.
2.
3.
4.
5.

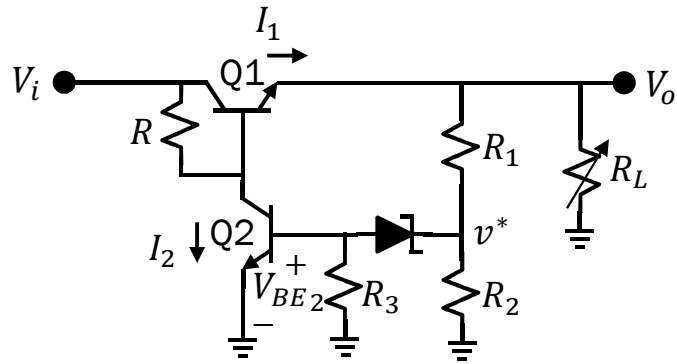


⊖ feedback

$V_o \nearrow \Rightarrow v^* \nearrow \Rightarrow V_{BE2} \nearrow \Rightarrow I_2 \nearrow \Rightarrow I_1 \searrow \Rightarrow V_o \searrow$
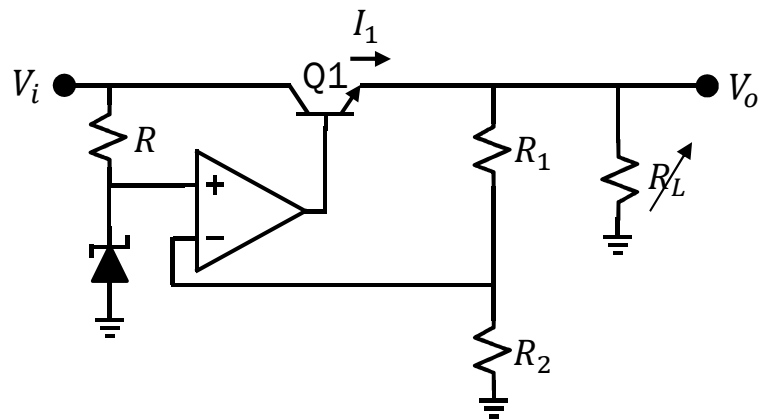
$$V_o \left( \frac{R_2}{R_1 + R_2} \right) = V_{BE2} + V_Z$$





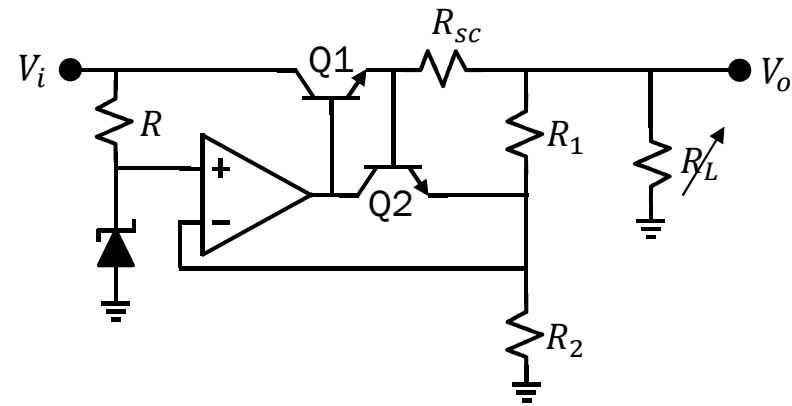
$$V_o \left( \frac{R_2}{R_1 + R_2} \right) = V_Z$$



$$I_{Lmax} R_{sc} = V_{BEon}$$



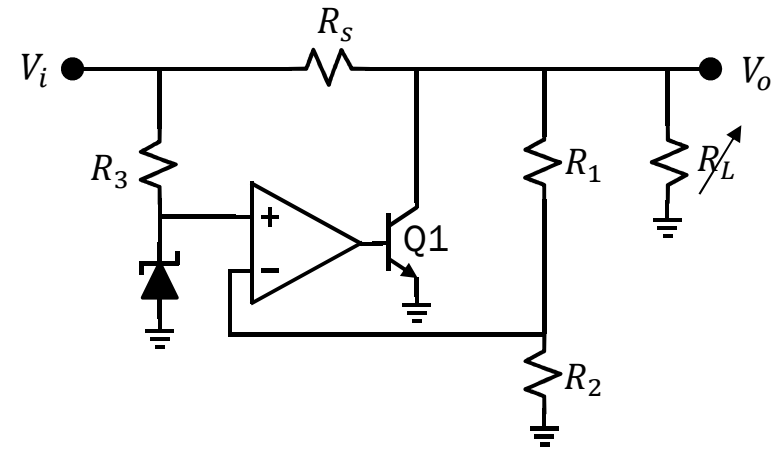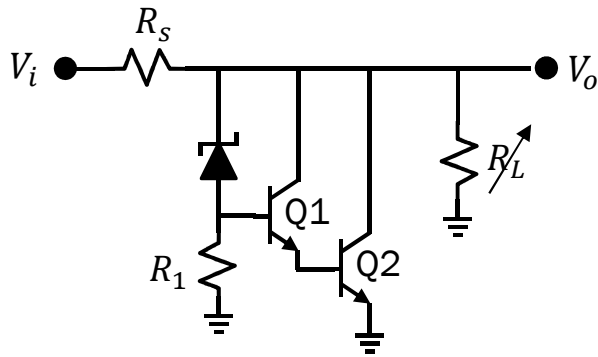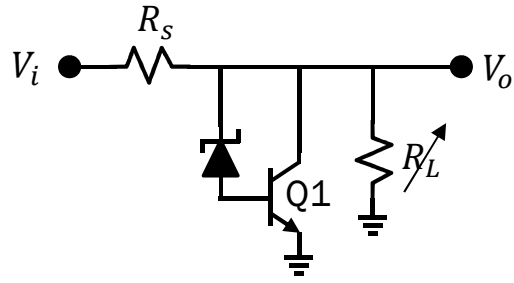


# Shunt Voltage Regulators


1.
2.
3.
4.
5.






# PN junctions , Forward Biased



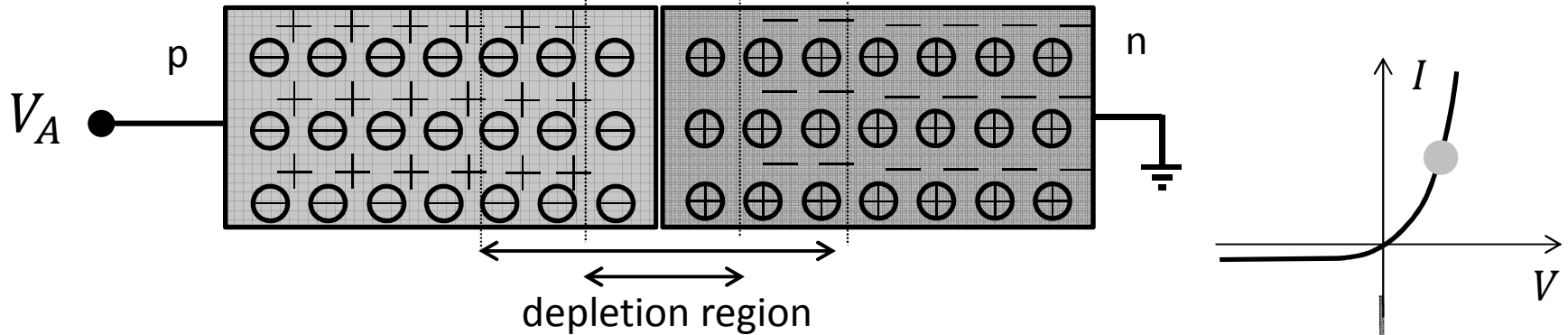


1. 
2. 
3. 
4. 
5. 

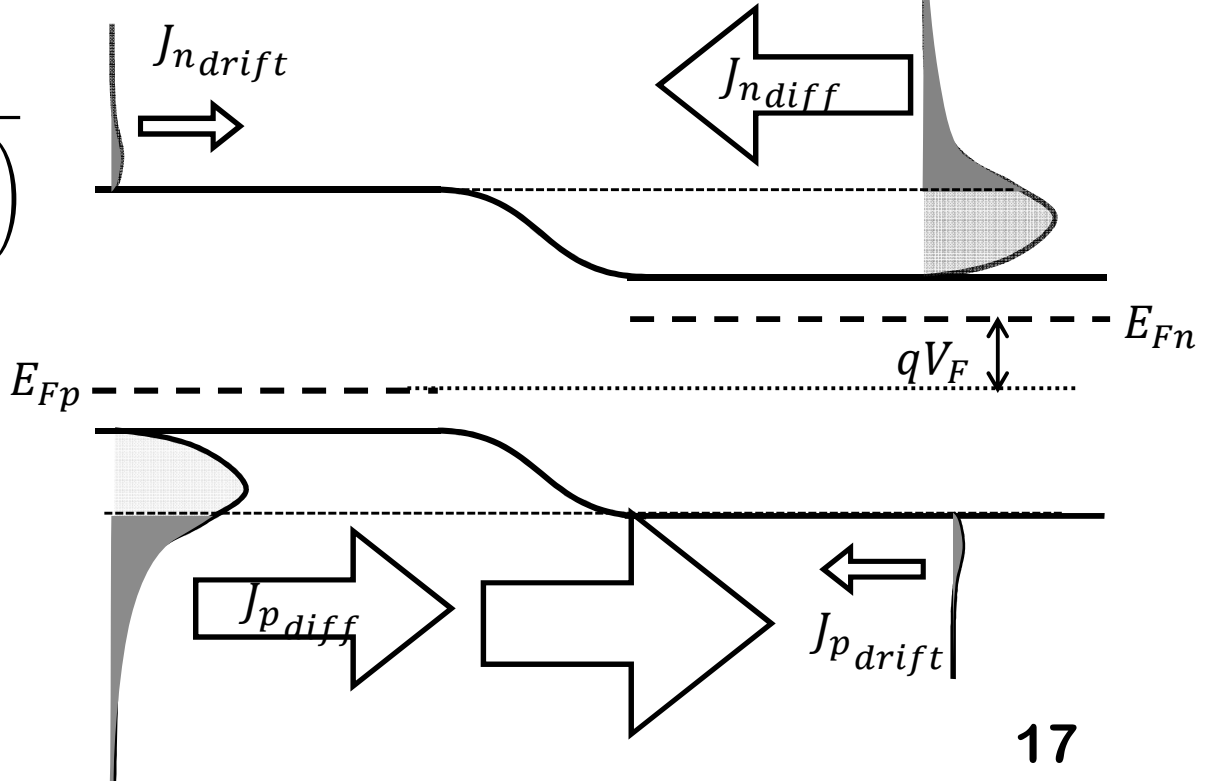


$$W = \sqrt{\frac{2\epsilon_s(V_{bi} - V_A)}{q} \left( \frac{1}{N_D} + \frac{1}{N_A} \right)}$$



# Reverse Bias Admittance


1. 
2. 
3. 
4. 
5. 

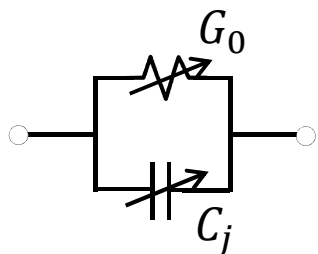

$$Y = G_0 + j\omega C_j$$

$C_j$  : Junction (depletion layer) capacitance  
 $G_0$ : Reverse bias conductance

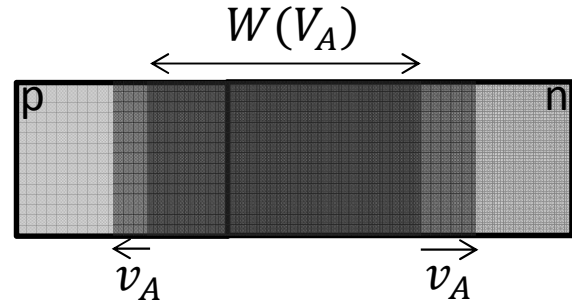A pn junction under reverse bias behaves like a capacitor.  
 Such capacitors are used in ICs as voltage-controlled capacitors.



$$W = \sqrt{\frac{2\epsilon_s(V_{bi} - V_A)}{q} \left( \frac{1}{N_D} + \frac{1}{N_A} \right)}$$


$$C_j = \frac{\epsilon_s A}{W} = \frac{C_{j0}}{\left(1 - \frac{V_A}{V_0}\right)^{1/2}}$$

where

$$C_{j0} = \epsilon_s A / \sqrt{\frac{2\epsilon_s V_{bi}}{q} \left( \frac{1}{N_D} + \frac{1}{N_A} \right)}$$


$$C_j = \frac{C_{j0}}{\left(1 - \frac{V_A}{V_0}\right)^m} \quad \begin{cases} m = 1/2 & \text{step junction} \\ m = 1/3 & \text{linear junction} \end{cases}$$

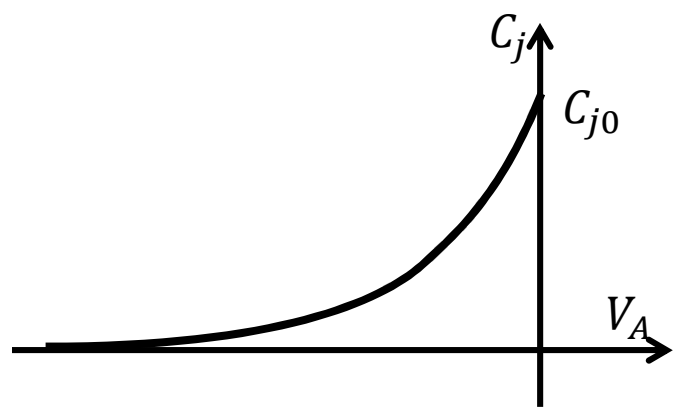C-V curve is very useful for characterization of the devices





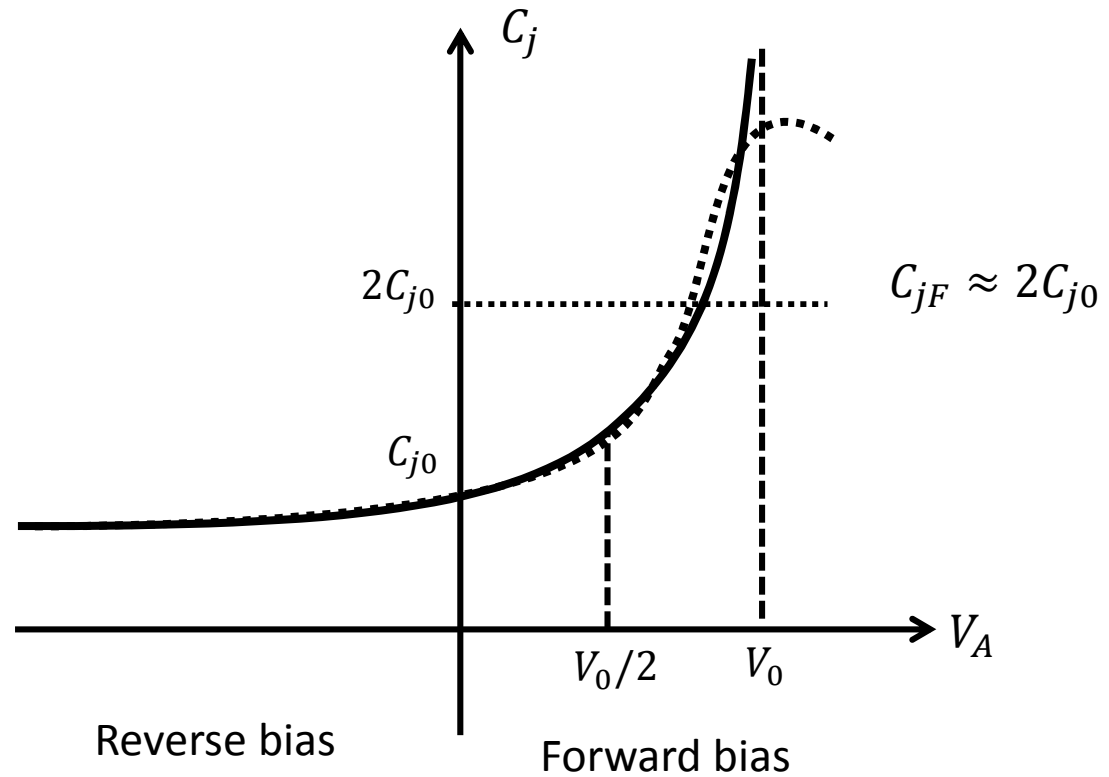


# Reverse Bias Admittance

1.
2.
3.
4.
5.




$$C_j = \frac{C_{j0}}{\left(1 - \frac{V_A}{V_0}\right)^m} \quad \begin{cases} m = 1/2 & \text{step junction} \\ m = 1/3 & \text{linear junction} \end{cases}$$


# pn Junction: I-V Characteristic

1. 
2. 
3. 
4. 
5. 



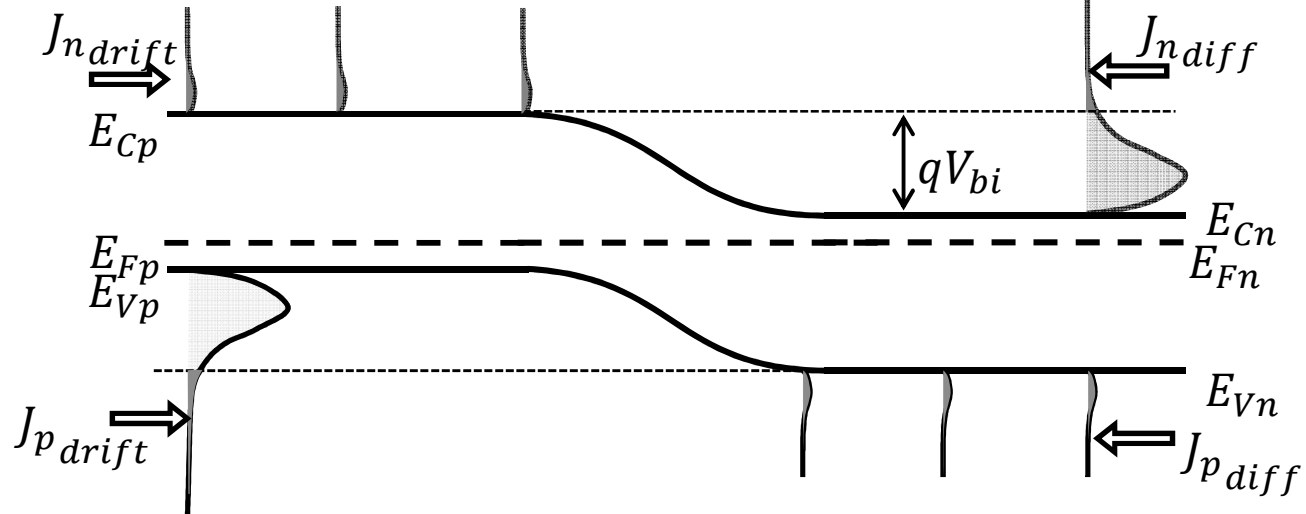


$V=0$

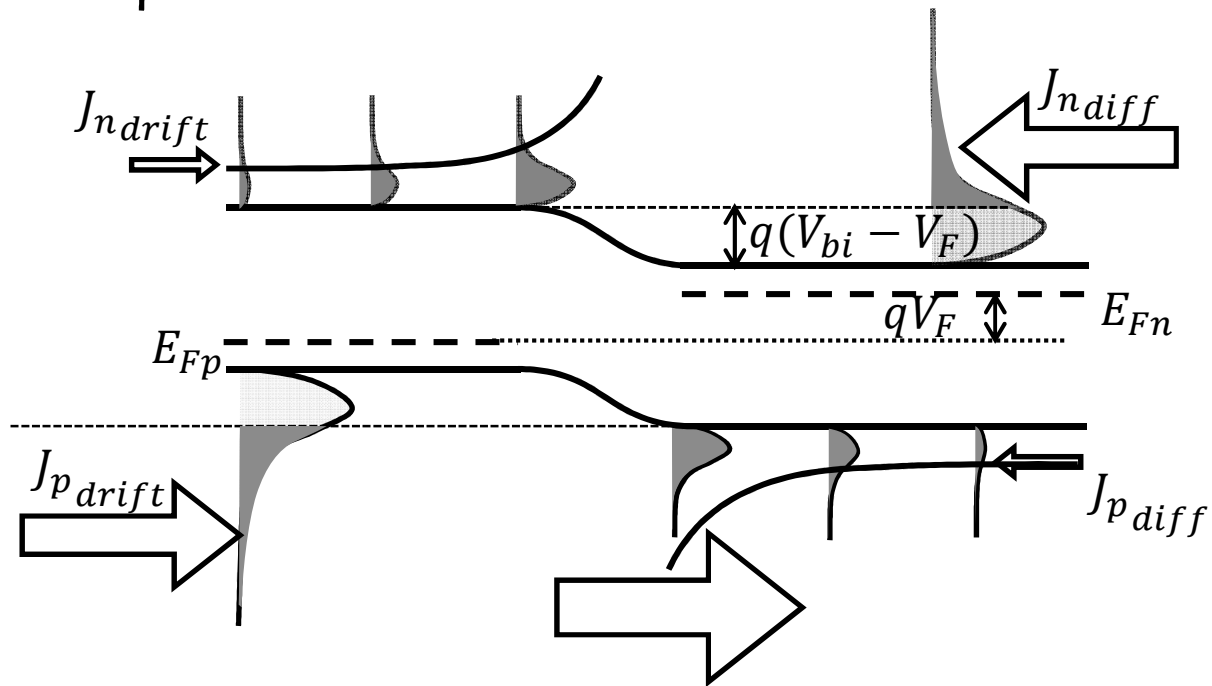


$V>0$



# pn Junction: I-V Characteristic

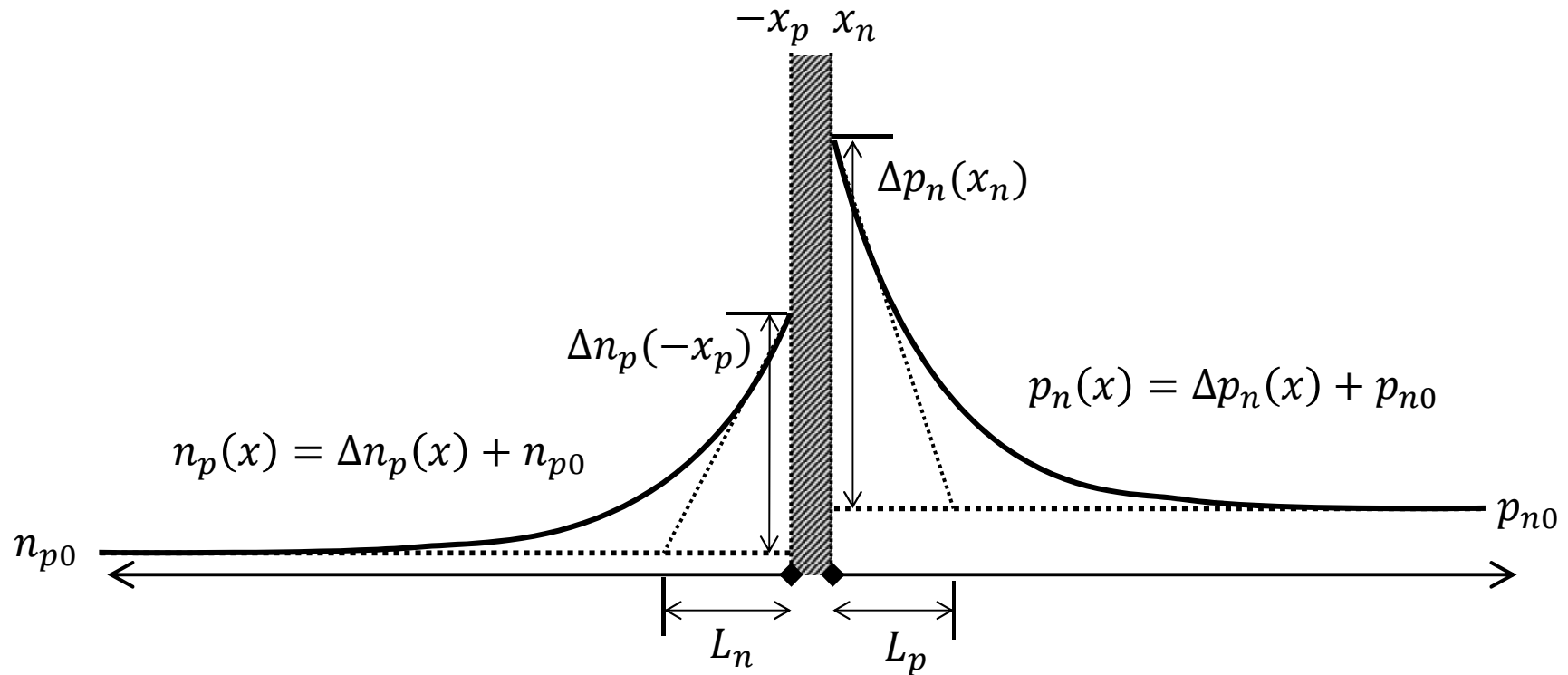1. 
2. 
3. 
4. 
5. 


The minority carrier concentrations on either side of the junction under forward bias



$$C_D = \tau_F \frac{i}{v} = \tau_F g_m$$


# BJT Small Signal Model (h- $\pi$ )

1.
2.
3.
4.
5.

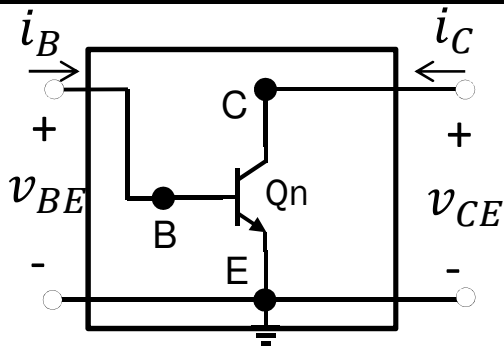

$$i_C = I_S \left( e^{\frac{v_{EB}}{V_T}} - 1 \right) \left( 1 + \frac{v_{CE}}{V_A} \right)$$
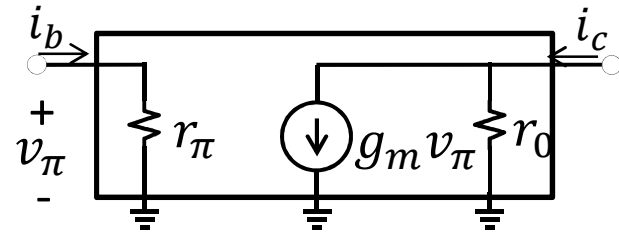
$$\cong \underbrace{I_S e^{\frac{v_{EB}}{V_T}}}_{I_C} \left( 1 + \frac{v_{CE}}{V_A} \right)$$



Input resistance:

$$r_\pi \equiv \frac{\partial v_{BE}}{\partial i_B} = \left( \frac{\partial i_B}{\partial v_{BE}} \right)^{-1} = \beta \left( \frac{\partial i_C}{\partial v_{BE}} \right)^{-1} = \beta \left( \frac{I_S}{V_T} e^{\frac{v_{EB}}{V_T}} \right)^{-1} = \beta \frac{V_T}{I_C} = \frac{\beta}{g_m} = \beta r_m$$

Output resistance:



$$r_o \equiv \frac{\partial v_{CE}}{\partial i_C} = \left( \frac{\partial i_C}{\partial v_{CE}} \right)^{-1} = \left( \frac{I_C}{V_A} \right)^{-1} = \frac{V_A}{I_C}$$

Trance-Conductance:

$$g_m \equiv \frac{\partial i_C}{\partial v_{BE}} = \frac{I_S}{V_T} e^{\frac{v_{EB}}{V_T}} = \frac{I_C}{V_T} = \frac{1}{r_m}$$

# BJT Small Signal Model (h- $\pi$ )

1.
2.
3.
4.
5.

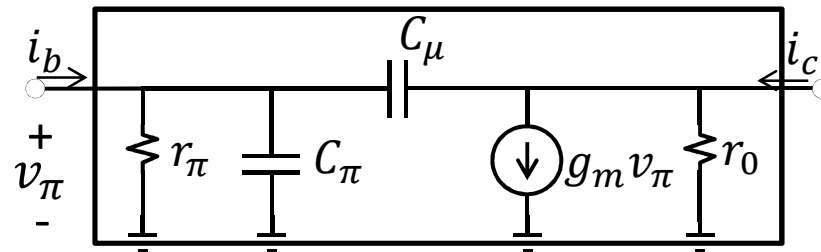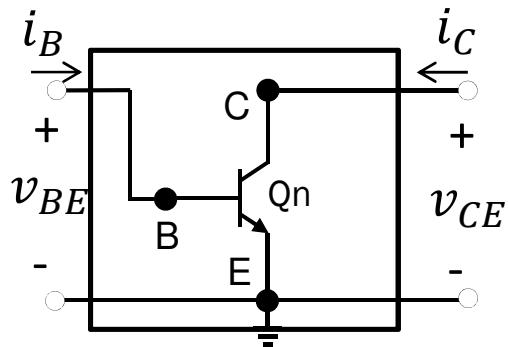

$$r_{\pi} \equiv \frac{\partial v_{BE}}{\partial i_B} = \frac{\beta}{g_m} = \beta r_m$$

$$r_o \equiv \frac{\partial v_{CE}}{\partial i_C} = \frac{V_A}{I_C}$$




$$g_m \equiv \frac{\partial i_C}{\partial v_{BE}} = \frac{I_C}{V_T}$$

$$C_{\pi} = C_{je} + C_{De} \approx 2C_{je0} + \tau_F g_m$$

$$C_{\mu} = C_{jc} = \frac{C_{\mu 0}}{\left(1 - \frac{V_{CB}}{V_{OC}}\right)^m}$$

# BJT Small Signal Model (h- $\pi$ )


- 1.
- 2.
- 3.
- 4.
- 5.

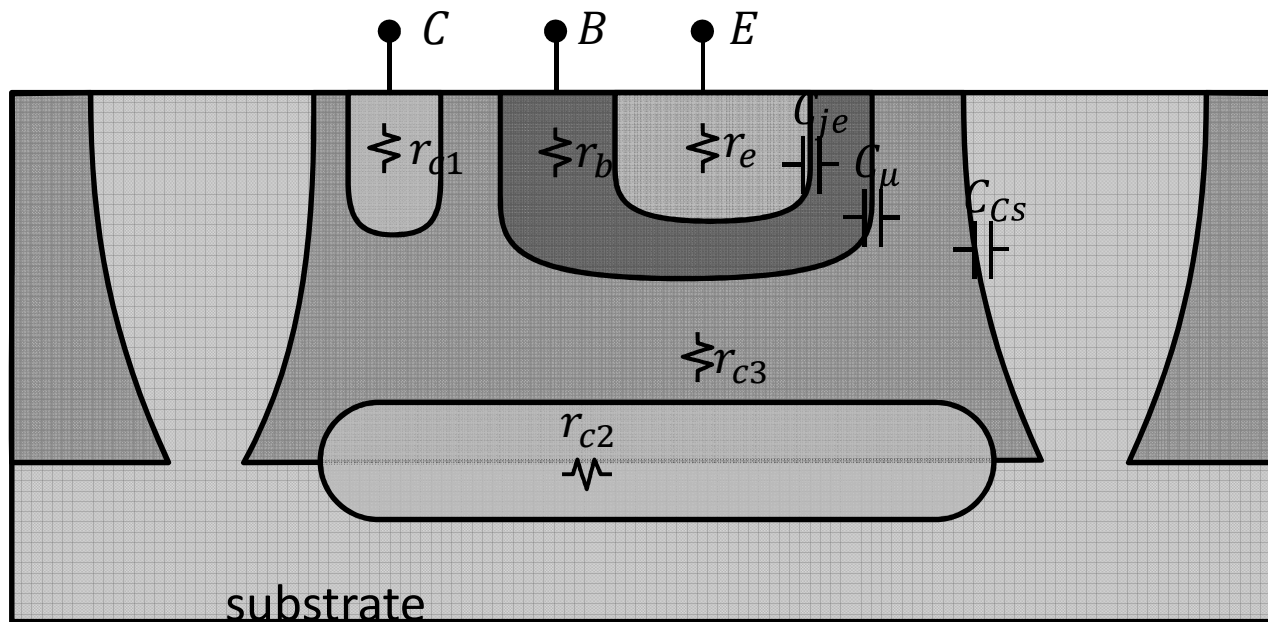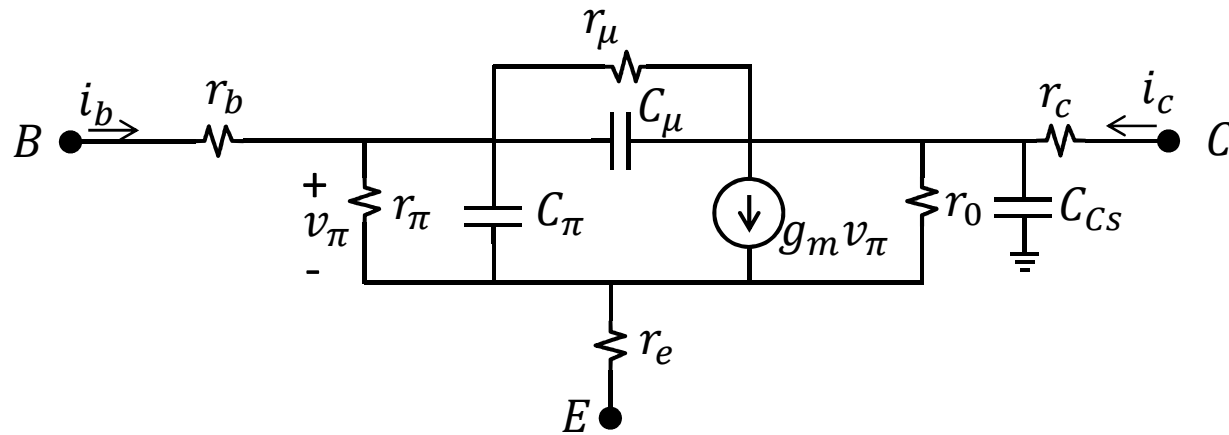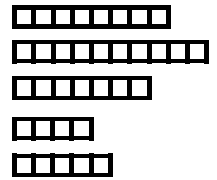



# BJT Small Signal Model (h- $\pi$ )

1.
2.
3.
4.
5.

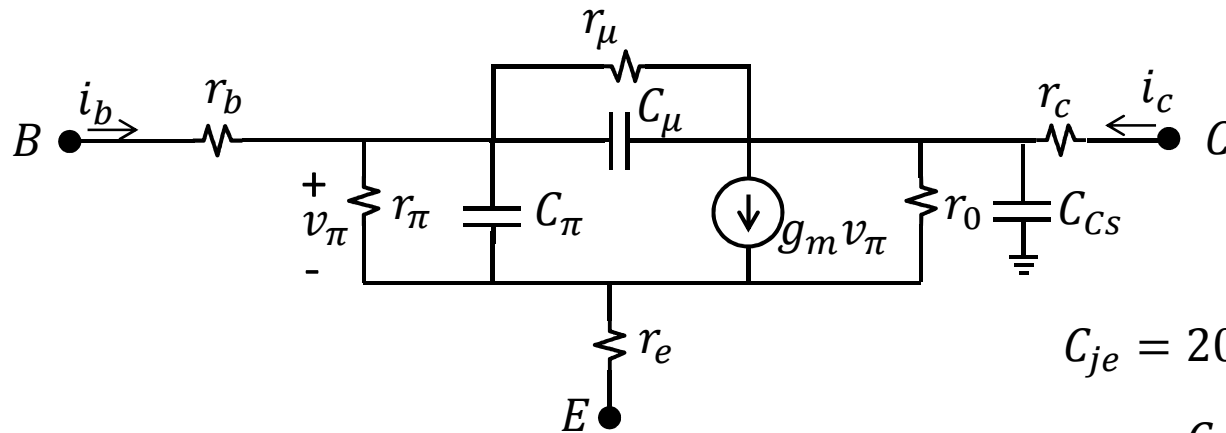

$$g_m = 38 \text{ mmho}$$

$$C_{je} = 20 \text{ fF} \quad C_b = \tau_F g_m = 0.38 \text{ pF}$$

$$C_\mu = \frac{C_{\mu 0}}{\left(1 - \frac{V_{CB}}{V_{0C}}\right)^{m_c}} = 5.6 \text{ fF}$$

$$C_{Cs} = \frac{C_{Cs0}}{\left(1 - \frac{V_{CB}}{V_{0s}}\right)^{m_s}} = 10.5 \text{ fF}$$

$$C_\pi = 0.02 \text{ pF} + 0.38 \text{ pF} = 0.4 \text{ pF}$$

$$r_\pi = 2.6 \text{ k}\Omega \quad r_o = 20 \text{ k}\Omega \quad r_\mu = 20 \text{ M}\Omega$$

$$I_C = 1 \text{ mA} \quad V_{CB} = 3 \text{ V} \quad V_{Cs} = 5 \text{ V}$$

$$\beta = 100 \quad \tau_F = 10 \text{ ps} \quad V_A = 20 \text{ V}$$

$$r_b = 300 \Omega \quad r_c = 50 \Omega \quad r_e = 5 \Omega$$

$$r_\mu = 10\beta r_o$$


$$C_{je0} = 10 \text{ fF}, m_e = 0.5, V_{0e} = 0.9 \text{ V}$$

$$C_{\mu 0} = 10 \text{ fF}, m_c = 0.3, V_{0c} = 0.5 \text{ V}$$

$$C_{Cs0} = 20 \text{ fF}, m_s = 0.3, V_{0s} = 0.65 \text{ V}$$

# BJT Small Signal Model (h- $\pi$ )

1.
2.
3.
4.
5.

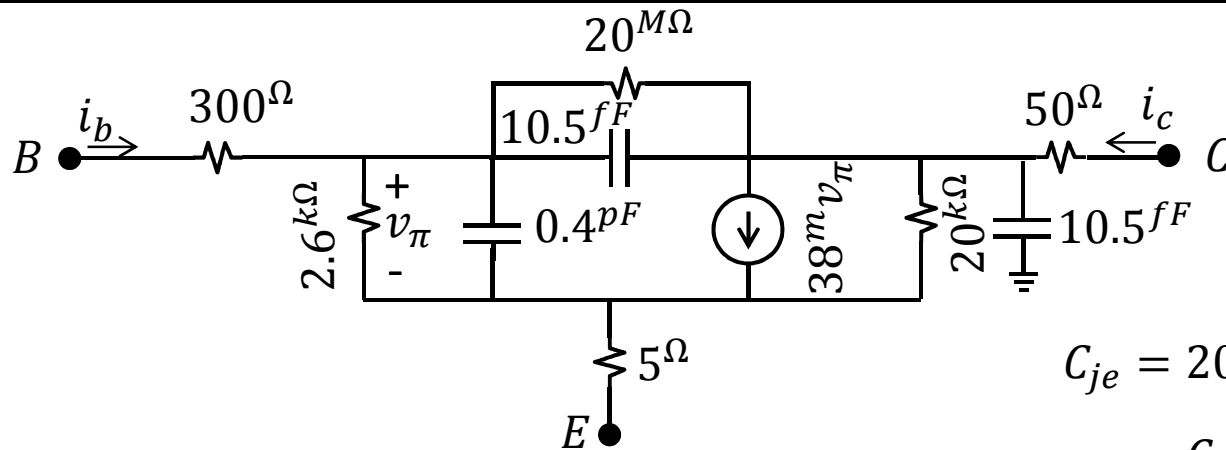

$$g_m = 38 \text{ mmho}$$

$$C_{je} = 20 \text{ fF} \quad C_b = \tau_F g_m = 0.38 \text{ pF}$$

$$C_{\mu} = \frac{C_{\mu 0}}{\left(1 - \frac{V_{CB}}{V_{0C}}\right)^{m_c}} = 5.6 \text{ fF}$$

$$C_{Cs} = \frac{C_{Cs0}}{\left(1 - \frac{V_{CB}}{V_{0s}}\right)^{m_s}} = 10.5 \text{ fF}$$

$$C_{\pi} = 0.02 \text{ pF} + 0.38 \text{ pF} = 0.4 \text{ pF}$$

$$r_{\pi} = 2.6 \text{ k}\Omega \quad r_o = 20 \text{ k}\Omega \quad r_{\mu} = 20 \text{ M}\Omega$$

$$I_C = 1 \text{ mA} \quad V_{CB} = 3 \text{ V} \quad V_{Cs} = 5 \text{ V}$$

$$\beta = 100 \quad \tau_F = 10 \text{ ps} \quad V_A = 20 \text{ V}$$

$$r_b = 300 \Omega \quad r_c = 50 \Omega \quad r_e = 5 \Omega$$

$$r_{\mu} = 10\beta r_o$$




$$C_{je0} = 10 \text{ fF}, m_e = 0.5, V_{0e} = 0.9 \text{ V}$$

$$C_{\mu 0} = 10 \text{ fF}, m_c = 0.3, V_{0c} = 0.5 \text{ V}$$

$$C_{Cs0} = 20 \text{ fF}, m_s = 0.3, V_{0s} = 0.65 \text{ V}$$

# Frequency Response

1.
2.
3.
4.
5.

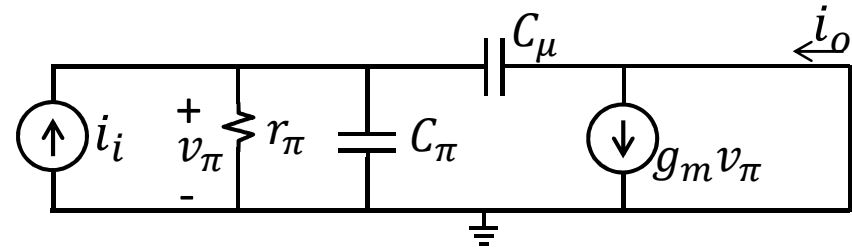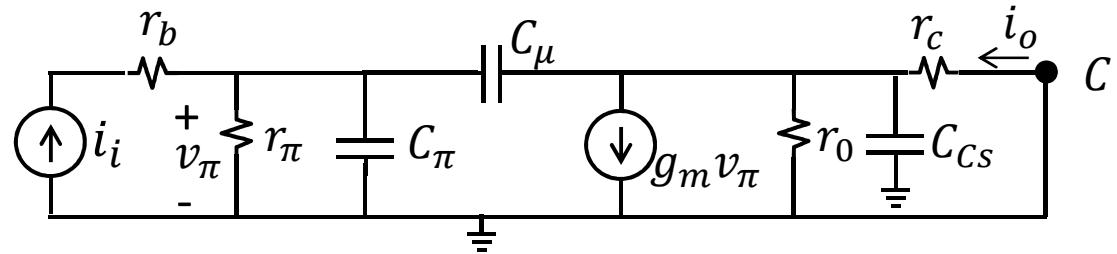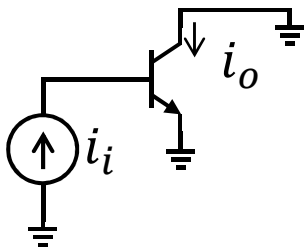


$$\frac{i_o}{i_{in}}(s) = \frac{g_m r_\pi}{1 + r_\pi (C_\pi + C_\mu) s}$$

$$\beta(j\omega) = \frac{\beta_0}{1 + \beta_0 \frac{C_\pi + C_\mu}{g_m} j\omega}$$


$$\omega_T = \frac{g_m}{C_\pi + C_\mu}$$
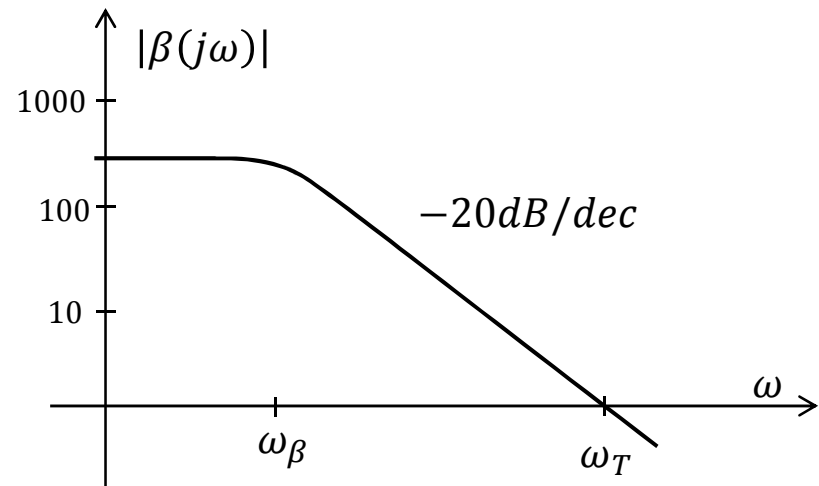
$$\omega_\beta = \frac{\omega_T}{\beta_0}$$




# Frequency Response

1.
2.
3.
4.
5.

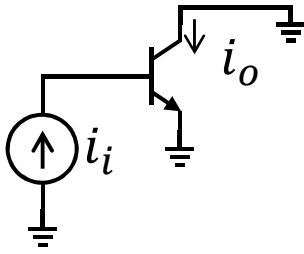



$$\omega_T = \frac{g_m}{C_\pi + C_\mu}$$
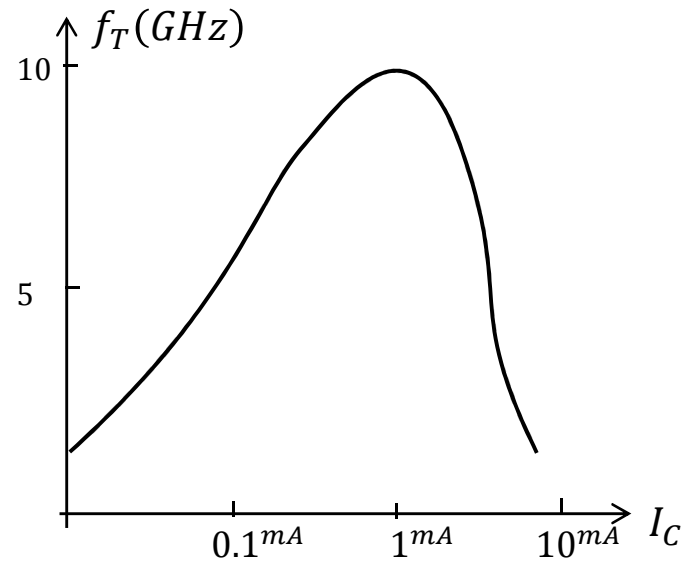
$$\begin{aligned} \tau_T &= \frac{C_\pi + C_\mu}{g_m} = \frac{C_b}{g_m} + \frac{C_\pi}{g_m} + \frac{C_\mu}{g_m} \\ &= \tau_F + \frac{C_\pi}{g_m} + \frac{C_\mu}{g_m} \end{aligned}$$





# Frequency Response

1.
2.
3.
4.
5.

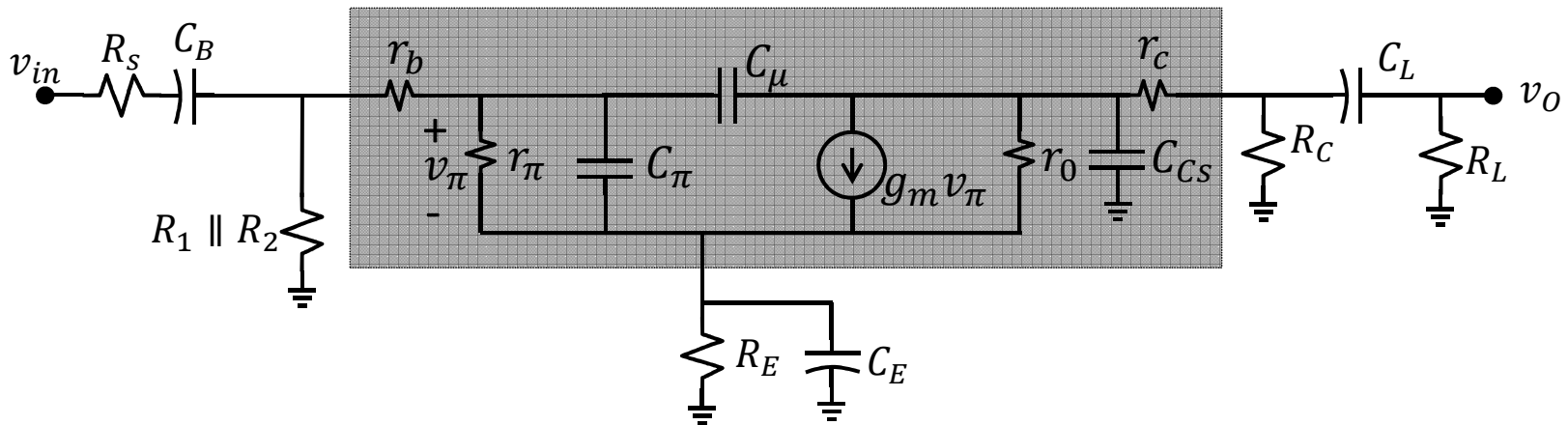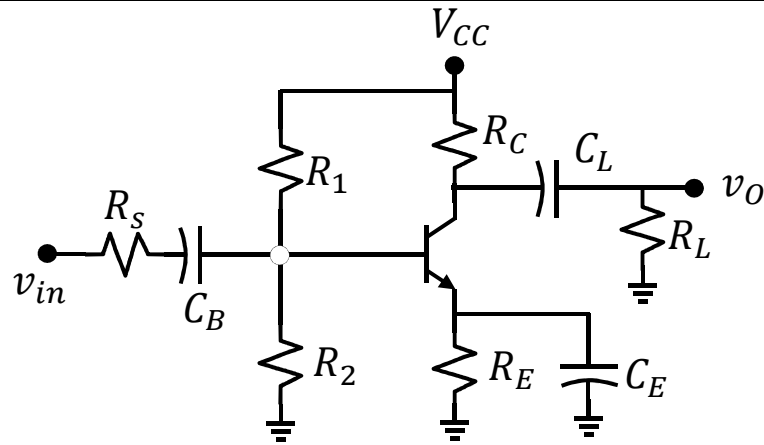

# Amplifier Frequency Response

1.
2.
3.
4.
5.

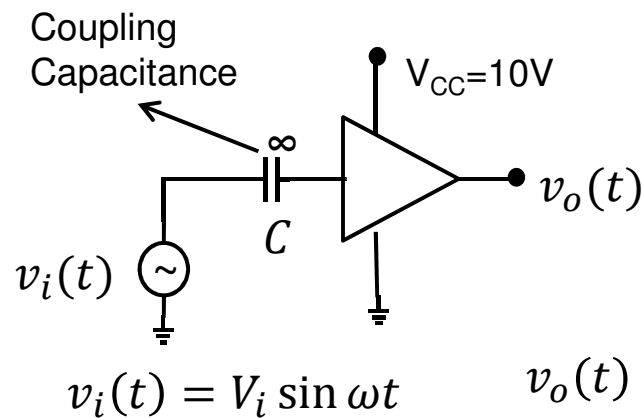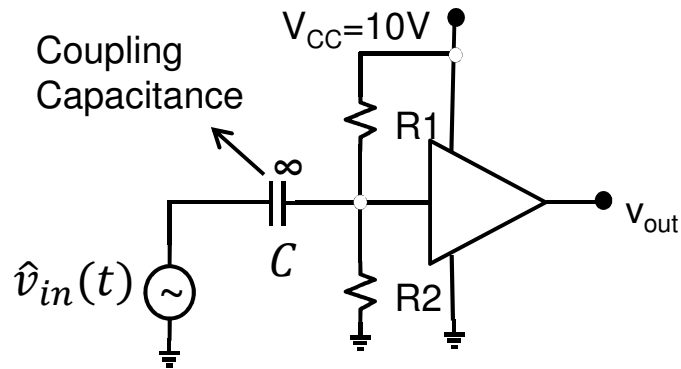


Transfer Function:  $T(\omega) = \frac{v_o}{v_i}$

$|T(\omega)| = \frac{V_o}{V_i}$

Amplitude in dB

$\angle T(\omega) = \varphi$

Phase

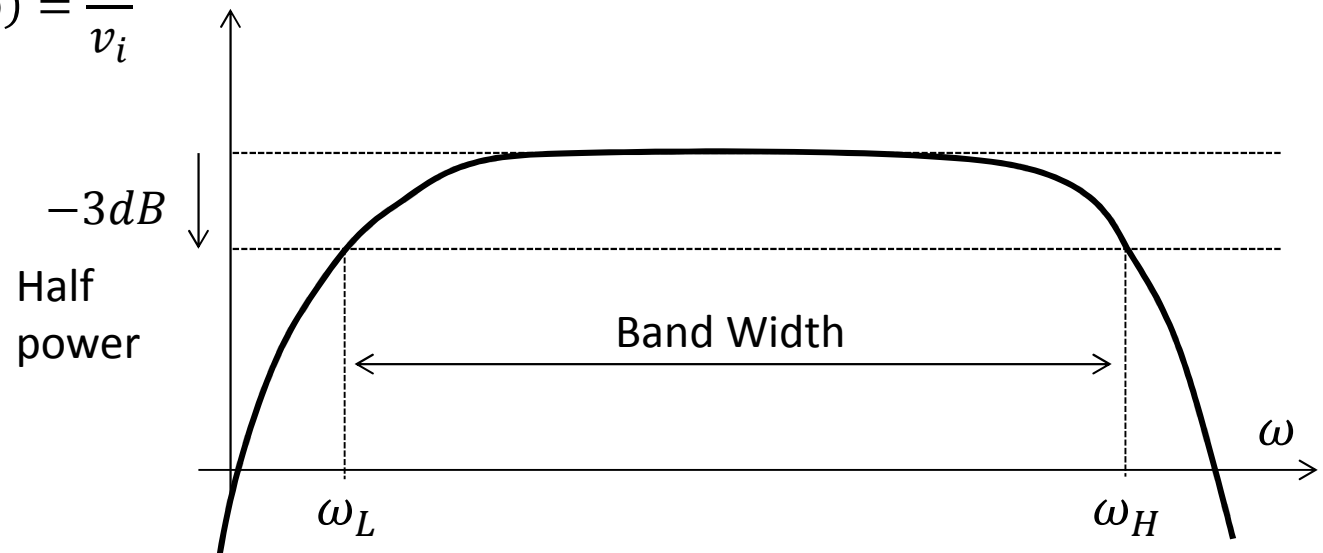

# Amplifier Frequency Response


1.
2.
3.
4.
5.

$$A_v(s) = \frac{a_0 + a_1s + a_2s^2 + \dots + a_ms^m}{b_0 + b_1s + b_2s^2 + \dots + b_ns^n}$$

$$= A_{mid}F_L(s)F_H(s)$$

$$F_L(s) = \frac{(s + \omega_{Z_1}^L)(s + \omega_{Z_2}^L) \dots (s + \omega_{Z_k}^L)}{(s + \omega_{P_1}^L)(s + \omega_{P_2}^L) \dots (s + \omega_{P_k}^L)}$$
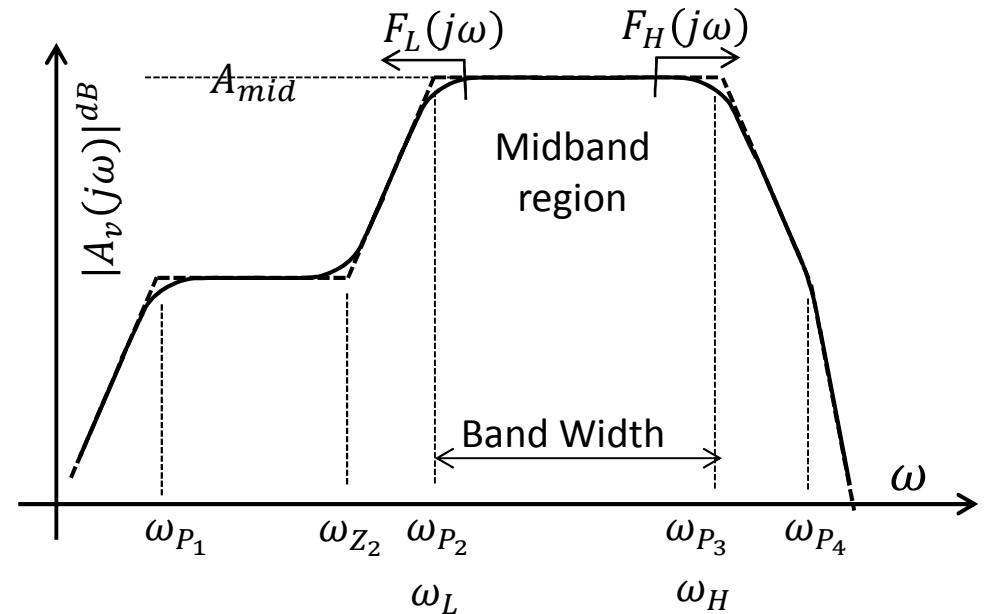
$$F_H(s) = \frac{\left(1 + \frac{s}{\omega_{Z_1}^H}\right) \left(1 + \frac{s}{\omega_{Z_2}^H}\right) \dots \left(1 + \frac{s}{\omega_{Z_l}^H}\right)}{\left(1 + \frac{s}{\omega_{P_1}^H}\right) \left(1 + \frac{s}{\omega_{P_2}^H}\right) \dots \left(1 + \frac{s}{\omega_{P_l}^H}\right)}$$



$$A_v(s) \cong A_{mid}F_L(s) \quad A_{mid}F_H(s)$$

Dominant pole

$$\omega_{P_2} \gg \omega_{Z_2}, \omega_{P_1}, \omega_{Z_1} \quad F_L(s) \cong \frac{s}{(s + \omega_{P_2})} \quad \omega_L \cong \omega_{P_2}$$

# Amplifier Frequency Response

1.	██████████
2.	██████████████
3.	██████████
4.	████
5.	████

Absence of Dominant pole  $\omega_{P_2} \sim \omega_{Z_2}, \omega_{P_1}, \omega_{Z_1}$

$$A_L(s) = A_{mid} \frac{(s + \omega_{Z_1})(s + \omega_{Z_2})}{(s + \omega_{P_1})(s + \omega_{P_2})} \rightarrow |A_L(j\omega)| = A_{mid} \sqrt{\frac{(\omega^2 + \omega_{Z_1}^2)(\omega^2 + \omega_{Z_2}^2)}{(\omega^2 + \omega_{P_1}^2)(\omega^2 + \omega_{P_2}^2)}}$$

$$|A_L(j\omega_L)| = \frac{A_{mid}}{\sqrt{2}} = A_{mid} \sqrt{\frac{(\omega_L^2 + \omega_{Z_1}^2)(\omega_L^2 + \omega_{Z_2}^2)}{(\omega_L^2 + \omega_{P_1}^2)(\omega_L^2 + \omega_{P_2}^2)}}$$

$$\omega_L \cong \sqrt{\omega_{P_1}^2 + \omega_{P_2}^2 - 2\omega_{Z_1}^2 - 2\omega_{Z_2}^2}$$



# Amplifier Frequency Response

1.	██████████
2.	██████████████
3.	██████████
4.	████
5.	██████

$$A_v(s) \cong A_{mid} F_H(s)$$

Dominant pole

$$F_H(s) \cong \frac{1}{\left(1 + \frac{s}{\omega_{P_3}}\right)} \quad \omega_H \cong \omega_{P_3}$$



Absence of Dominant pole

$$A_H(s) = A_{mid} \frac{\left(1 + \frac{s}{\omega_{Z_1}}\right) \left(1 + \frac{s}{\omega_{Z_2}}\right)}{\left(1 + \frac{s}{\omega_{P_1}}\right) \left(1 + \frac{s}{\omega_{P_2}}\right)} \rightarrow |A_L(j\omega_H)| = \frac{A_{mid}}{\sqrt{2}} = A_{mid} \sqrt{\frac{\left(1 + \frac{\omega^2}{\omega_{Z_1}^2}\right) \left(1 + \frac{\omega^2}{\omega_{Z_2}^2}\right)}{\left(1 + \frac{\omega^2}{\omega_{P_1}^2}\right) \left(1 + \frac{\omega^2}{\omega_{P_2}^2}\right)}}$$

$$\omega_H \cong \frac{1}{\sqrt{\omega_{P_1}^{-2} + \omega_{P_2}^{-2} - 2\omega_{Z_1}^{-2} - 2\omega_{Z_2}^{-2}}}$$

# Miller's Theorem



1.
2.
3.
4.
5.

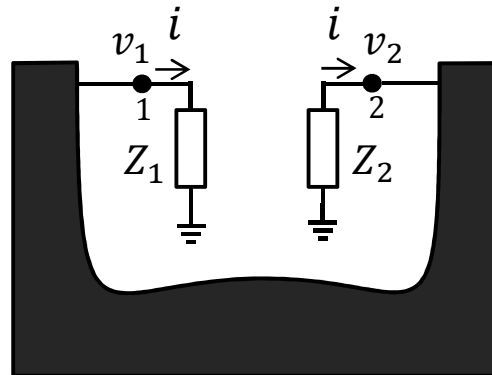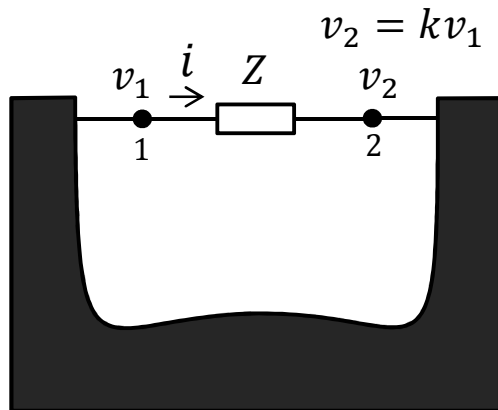

$$i = \frac{v_1 - v_2}{Z}$$

$$i = \frac{v_1}{Z_1} \quad Z_1 = \frac{Z}{1 - k}$$
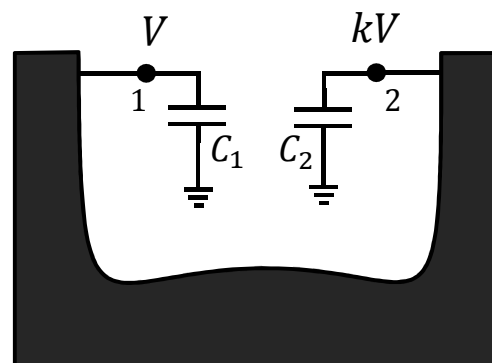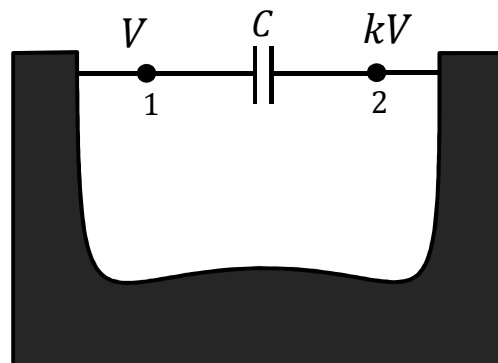
$$i = \frac{-v_2}{Z_2} \quad Z_2 = \frac{Z}{1 - \frac{1}{k}}$$






$$C_1 = C(1 - k)$$

$$C_2 = C\left(1 - \frac{1}{k}\right)$$

# Frequency Response


1.
2.
3.
4.
5.

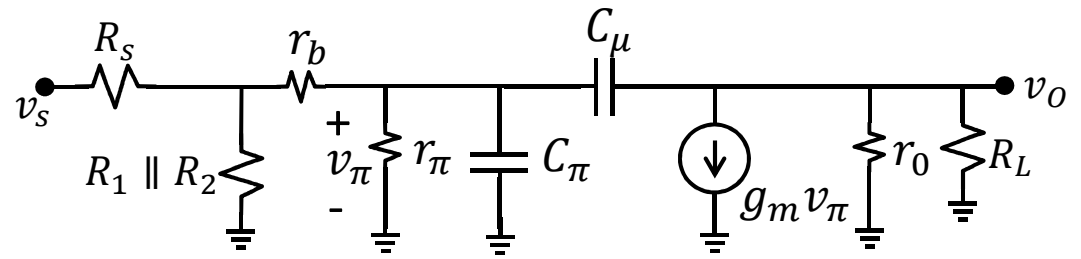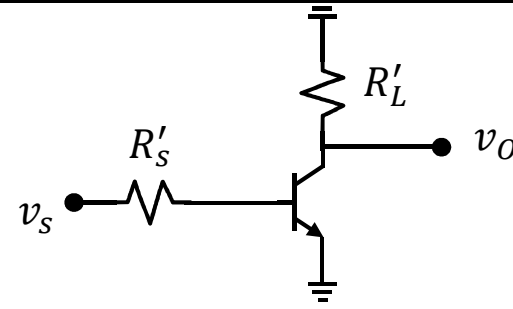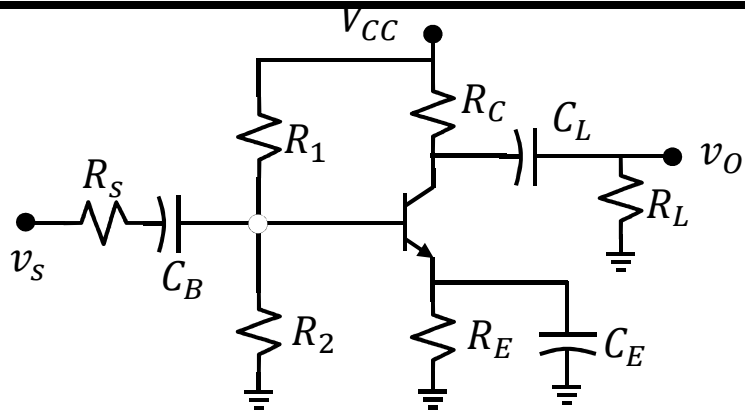

$$R_1 = r_\pi \parallel (r_b + R_1 \parallel R_2 \parallel R_S)$$



$$v_1 = v_{in} \frac{R_1 \parallel R_2 \parallel (r_b + r_\pi)}{R_s + R_1 \parallel R_2 \parallel (r_b + r_\pi)} \frac{r_\pi}{r_b + r_\pi}$$

$$R_o = R_L \parallel r_o$$

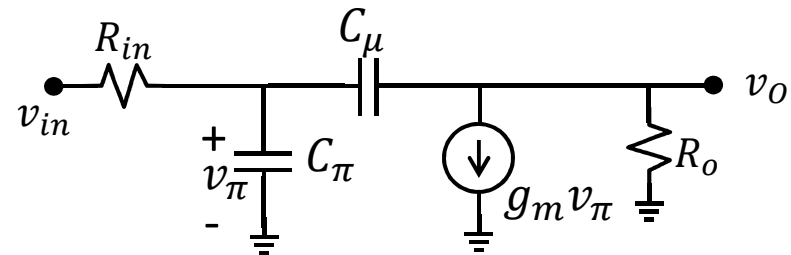

# Frequency Response

1.
2.
3.
4.
5.

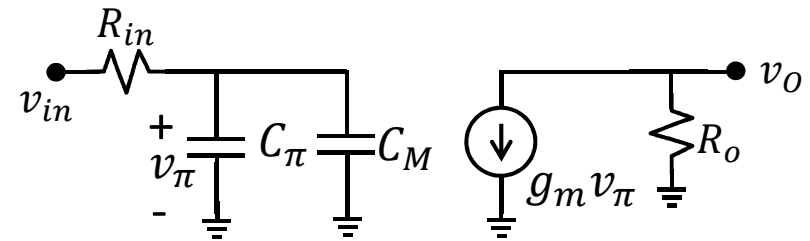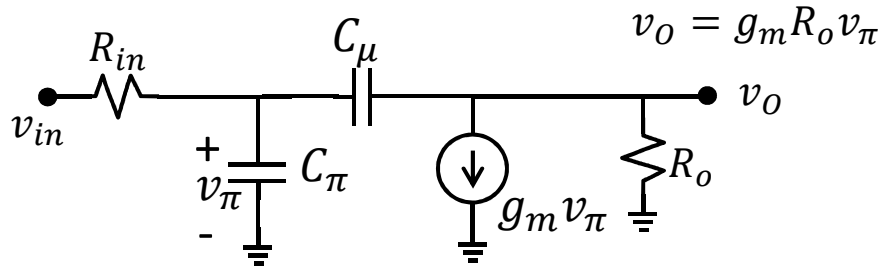

$$C_M = C_\mu(1 + g_m R_o)$$

$$p_{in} = 1/(R_{in}[C_\pi + C_\mu(1 + g_m R_o)])$$

KVL-KCL!

$$\frac{v_o}{v_{in}} = -g_m R_o \frac{1 - s \frac{C_\mu}{g_m}}{1 + s(C_\mu R_o + C_\pi R_{in} + C_\mu R_{in} + g_m R_o R_{in} C_\mu) + s^2 R_o R_{in} C_\mu C_\pi}$$

$$p_1 = \frac{1}{R_{in} \left( C_\pi + C_\mu \left( 1 + g_m R_o + \frac{R_o}{R_{in}} \right) \right)}$$