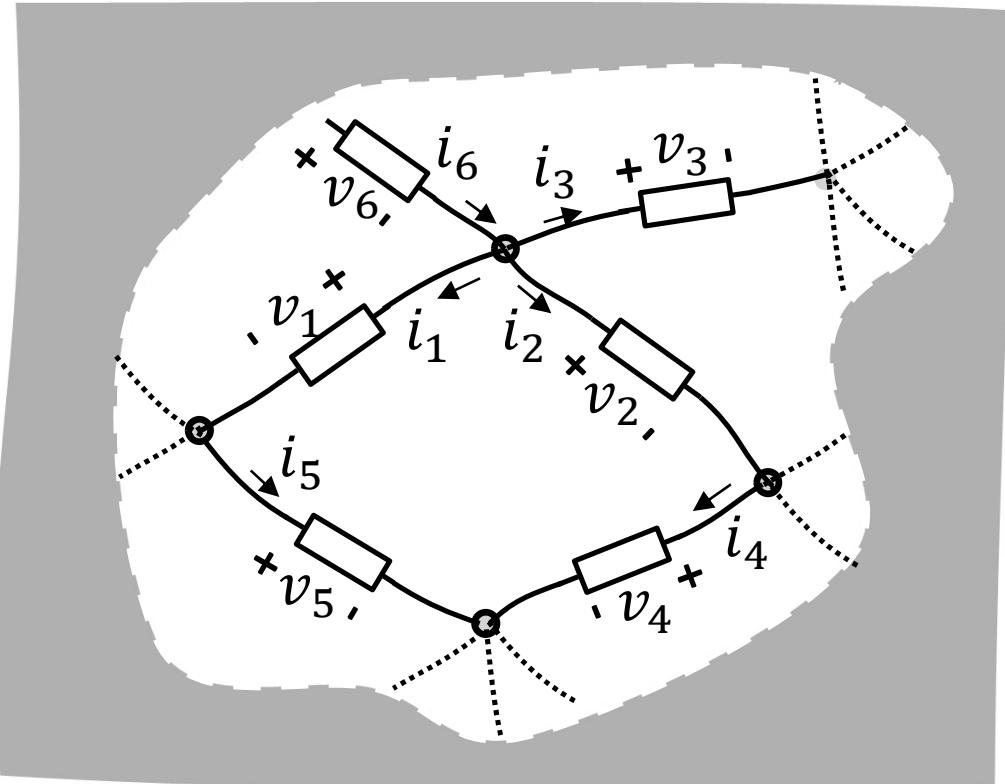


Week2 Electronics1

Reminders, Amplifiers




KVL, KCL



$$-\mathbb{V}_1 + \mathbb{V}_2 + \mathbb{V}_4 - \mathbb{V}_5 = 0$$

KVL

$$\sum_{i=1}^n \mathbb{V}_i = 0$$

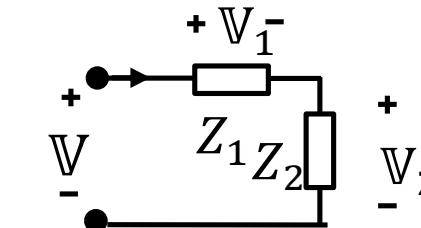


$$\mathbb{V}_2 = \frac{Z_2}{Z_1 + Z_2} \mathbb{V}$$

$$\mathbb{I}_1 + \mathbb{I}_2 + \mathbb{I}_3 - \mathbb{I}_6 = 0$$


KCL

$$\sum_{i=1}^m \mathbb{I}_i = 0$$

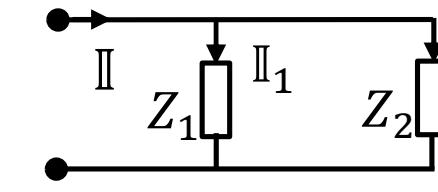

$$\mathbb{I}_2 = \frac{Y_2}{Y_1 + Y_2} \mathbb{I}$$




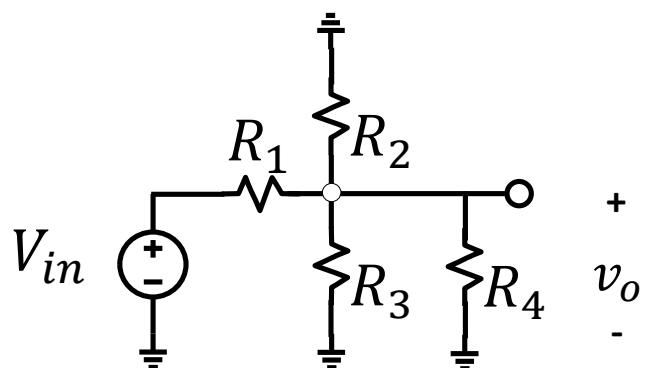
$$\mathbb{I}_2 = \frac{Z_1}{Z_1 + Z_2} \mathbb{I}$$






$$v_o = \frac{R_2 \parallel R_3 \parallel R_4}{R_1 + (R_2 \parallel R_3 \parallel R_4)} V_{in}$$



Source Transformation

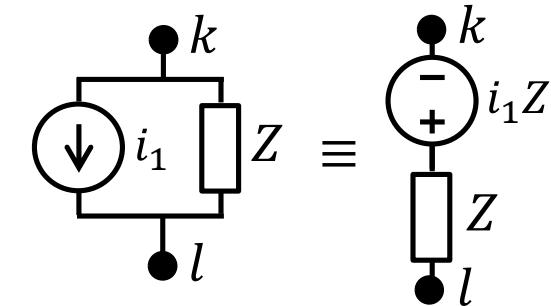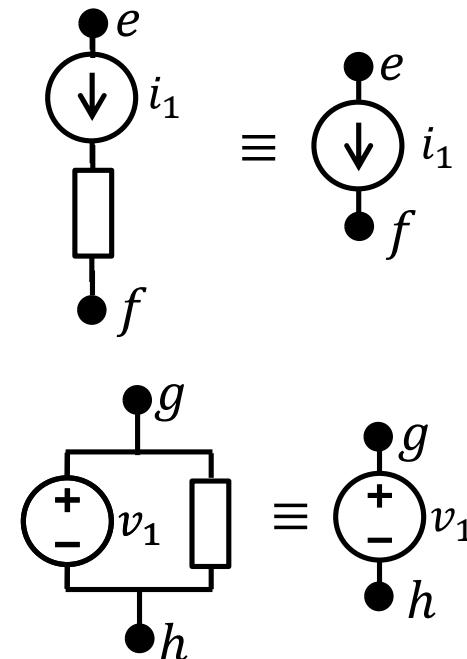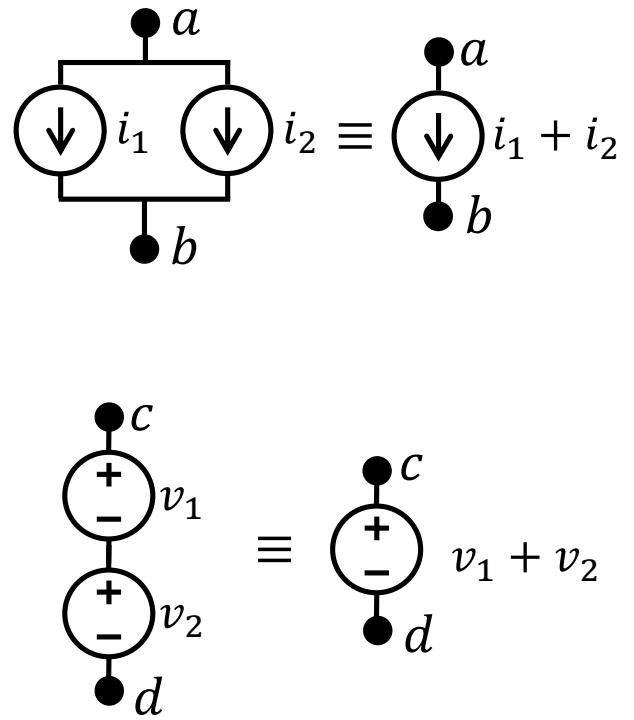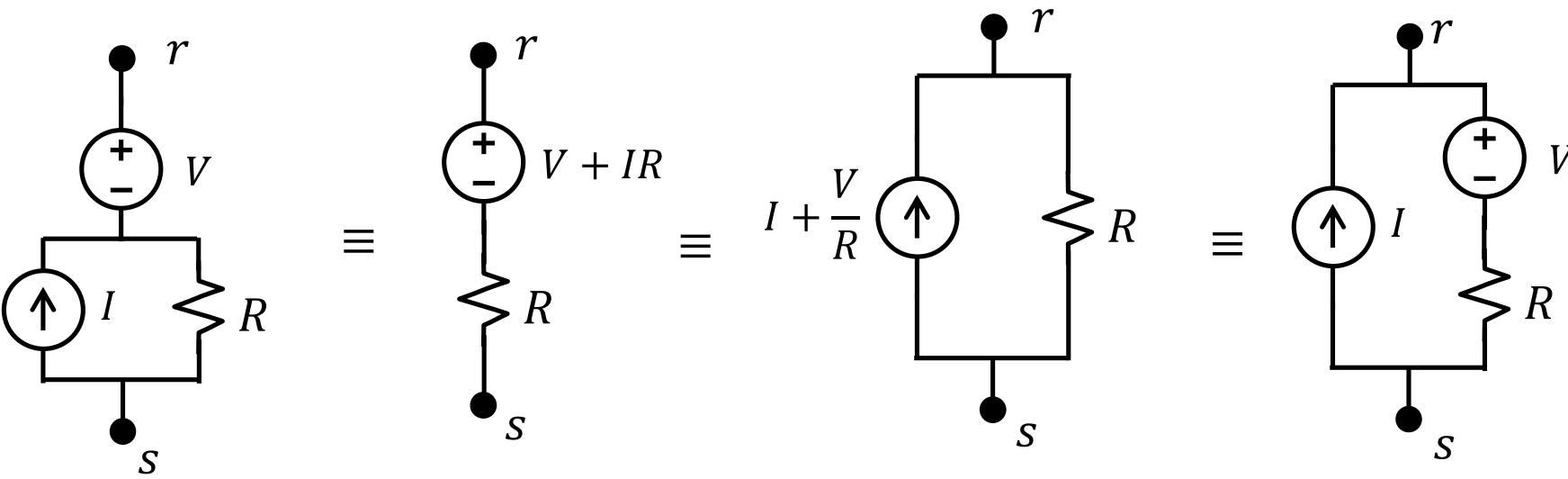

Replacement Theorem

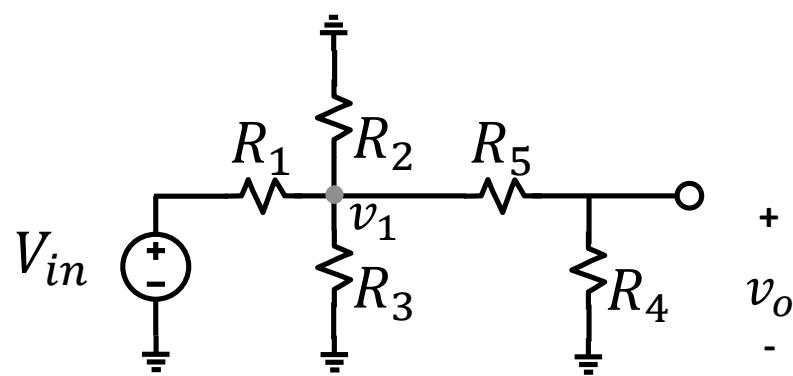
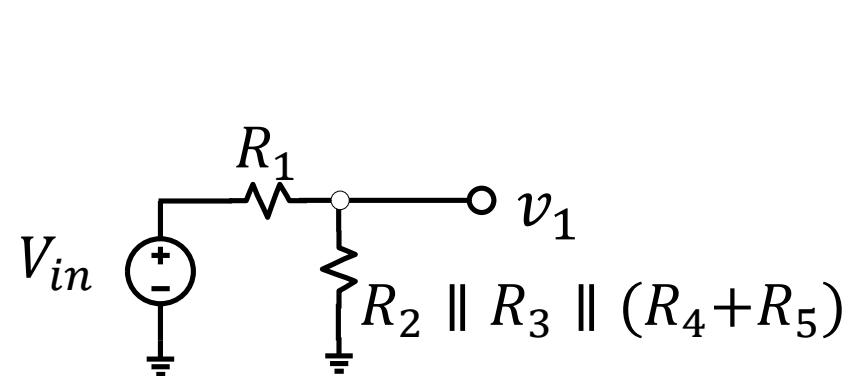
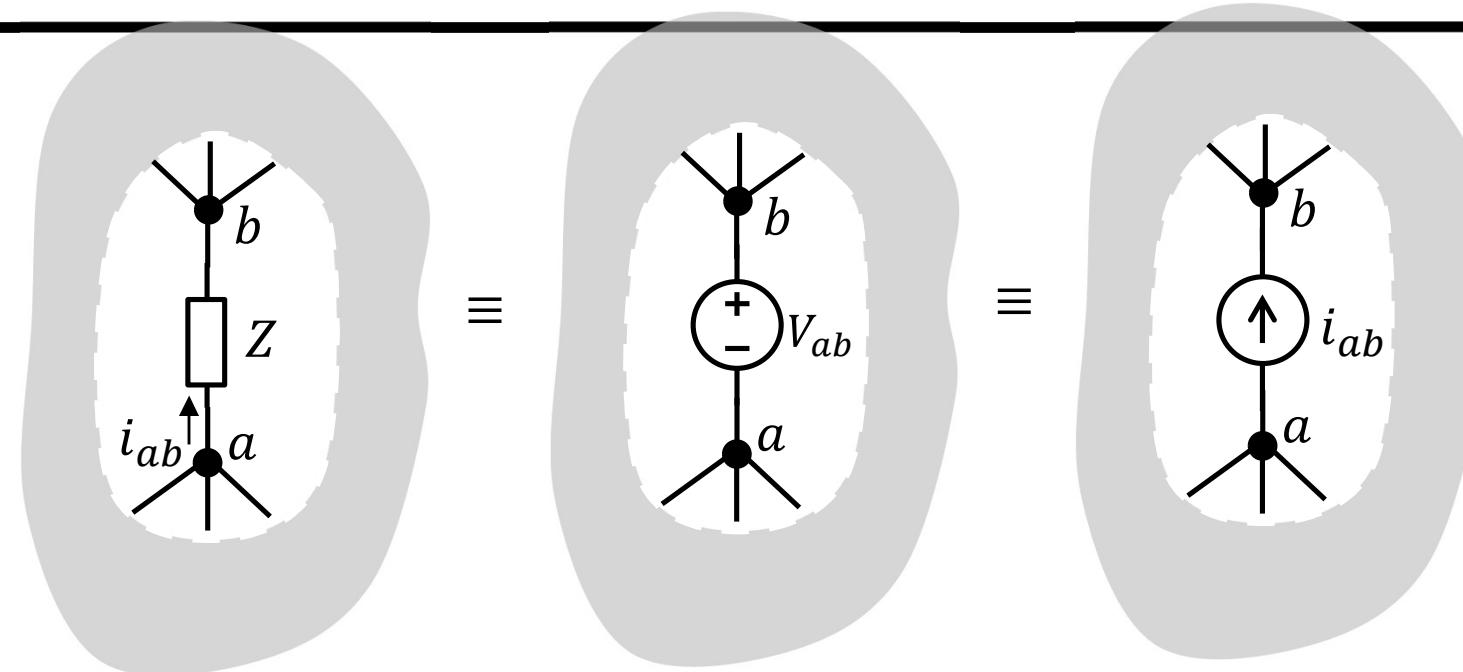


$$v_1 = \frac{R_2 \parallel R_3 \parallel (R_4 + R_5)}{R_1 + (R_2 \parallel R_3 \parallel (R_4 + R_5))} V_{in}$$

$$v_o = \frac{R_4}{R_4 + R_5} \frac{R_2 \parallel R_3 \parallel (R_4 + R_5) V_{in}}{R_1 + (R_2 \parallel R_3 \parallel (R_4 + R_5))}$$



Thevenin / Norton Equivalent

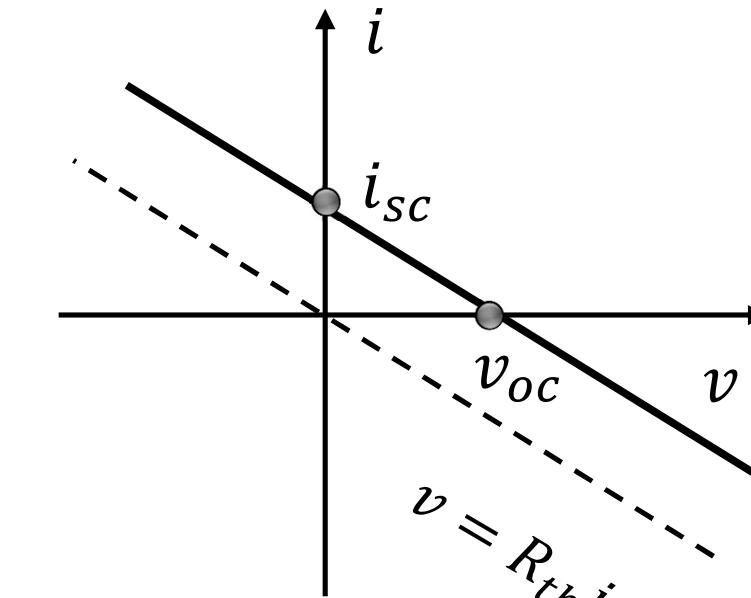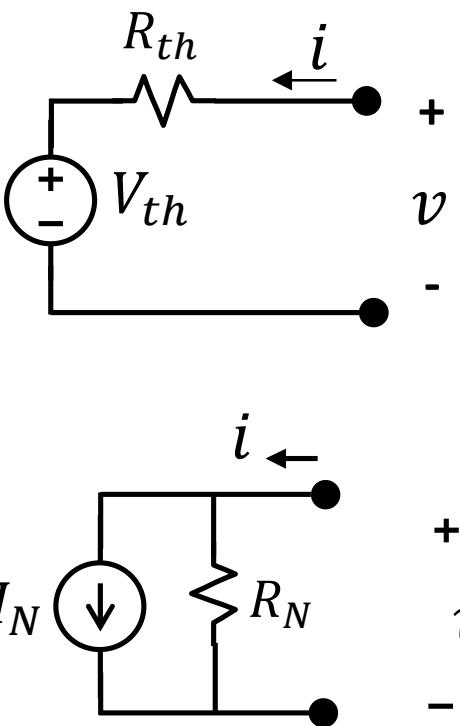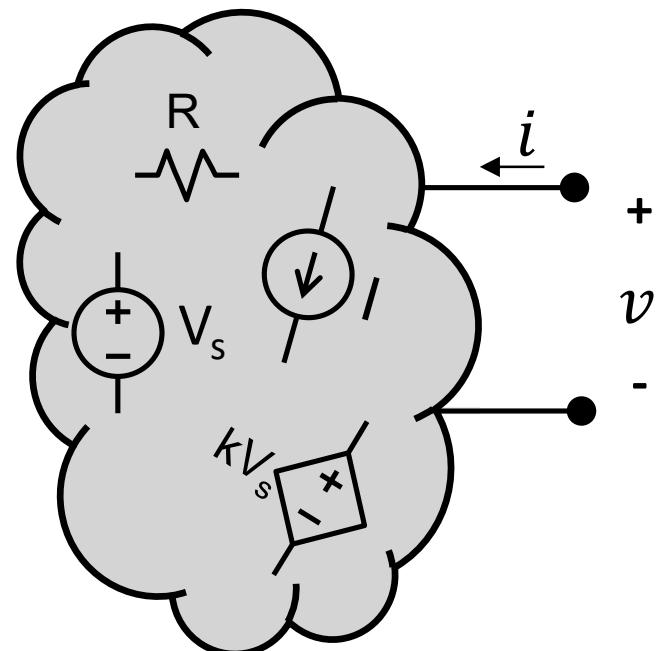


$$v_{oc} = V_{th}$$

$$i_{sc} = I_N \\ = V_{th}/R_{th}$$




Thevenin / Norton Equivalent

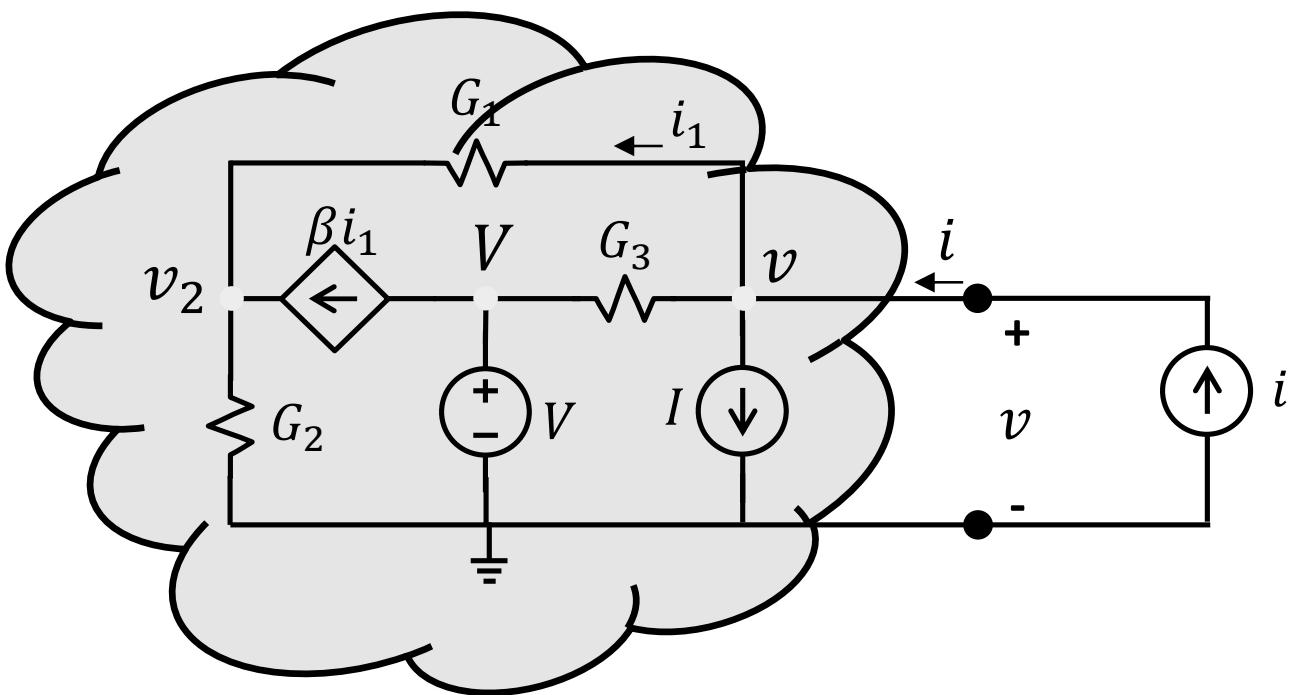


$$\begin{cases} \boxed{v}: & G_1(v - v_2) + G_3(v - V) + I - i = 0 \\ \boxed{v_2}: & G_1(v_2 - v) + G_2 v_2 - \beta G_1(v - v_2) = 0 \end{cases}$$

$$\begin{pmatrix} G_1 + G_3 & -G_1 \\ -G_1 - \beta G_1 & G_1 + G_2 + \beta G_1 \end{pmatrix} \begin{pmatrix} v \\ v_2 \end{pmatrix} = \begin{pmatrix} i - I + G_3 V \\ 0 \end{pmatrix}$$
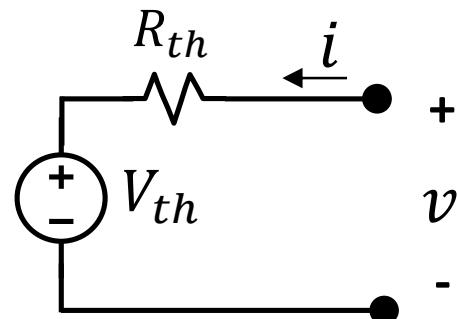
$$\begin{pmatrix} v \\ v_2 \end{pmatrix} = [G]^{-1} \begin{pmatrix} i \\ 0 \end{pmatrix} + [G]^{-1} \begin{pmatrix} G_3 V - I \\ 0 \end{pmatrix}$$



$$v = R_{th}i + V_{th}$$

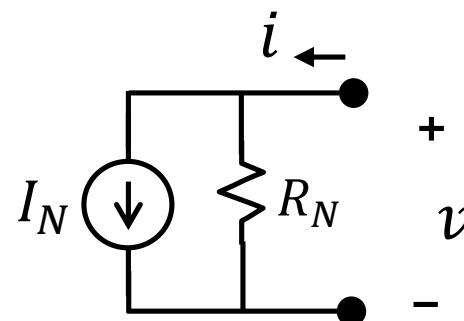





$$v_{oc} = V_{th}$$

$$\begin{aligned} i_{sc} &= I_N \\ &= V_{th}/R_{th} \end{aligned}$$




Amplifier

Audio Amplifier:

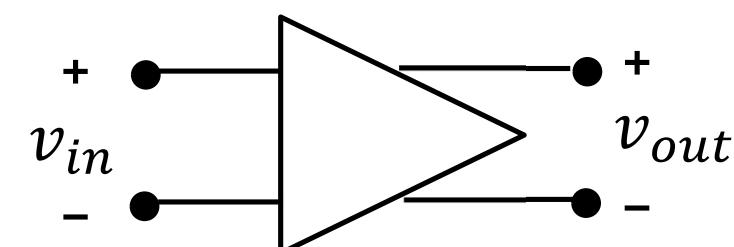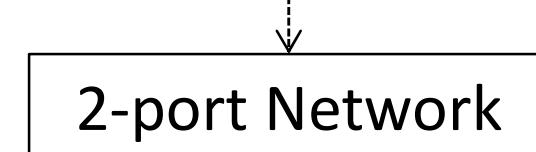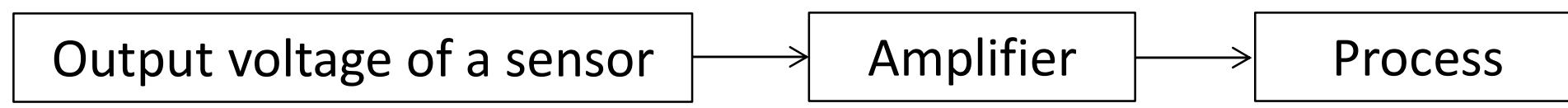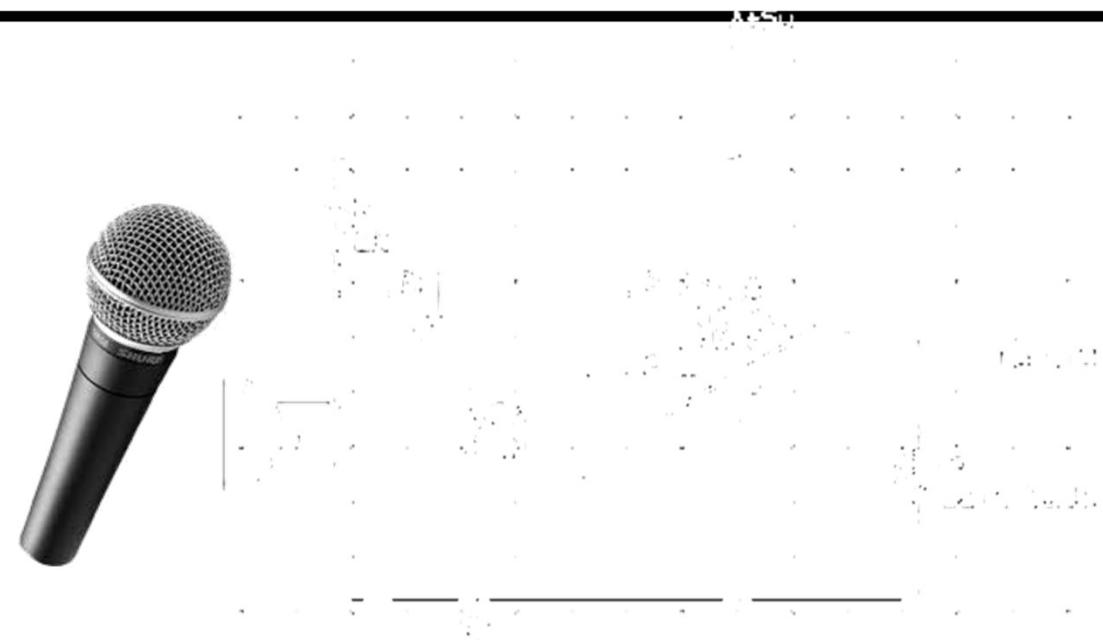

Amplifier

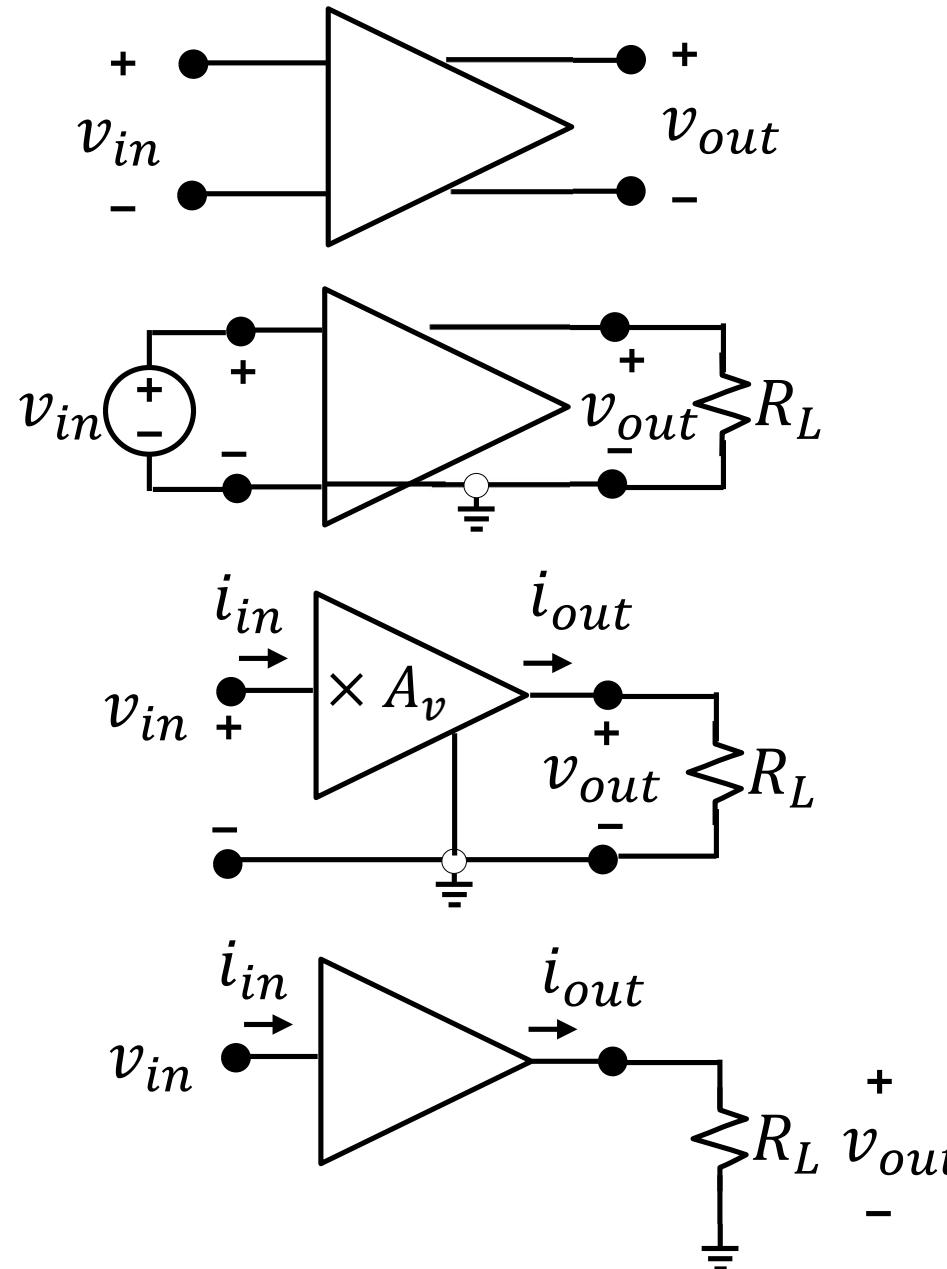


Note: There is a difference between Amplifier and Transformer

? Where is the source of this extra power?

Ideal amplifier

$$v_{out} = A_v v_{in}$$

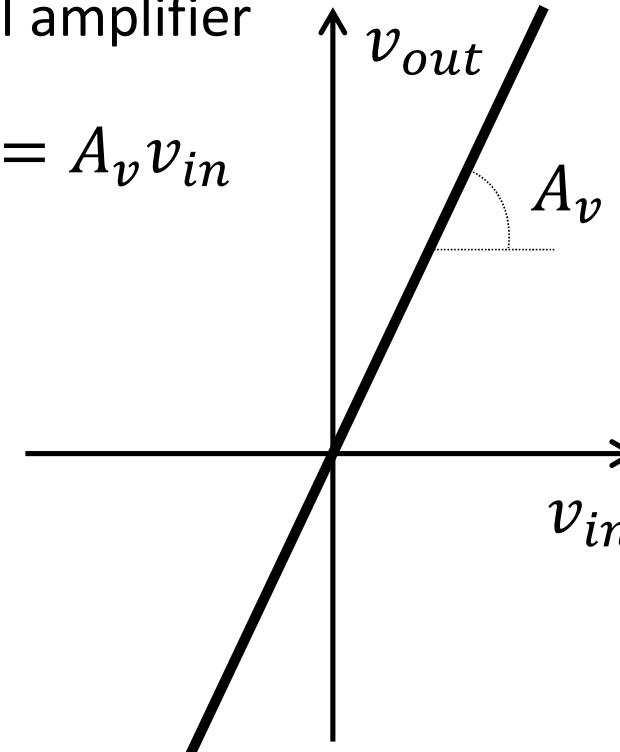

$$A_v = 10 = 20dB$$

$$A_v = 100 = 40dB$$

$$A_v = 1 = 0dB$$

$$A_v = \frac{1}{\sqrt{2}} = -3dB$$

$$A_P = \frac{1}{2} = -3dB$$



$$A_P \triangleq \frac{P_{out}}{P_{in}} \rightarrow 10 \log_{10} A_P \text{ in } dB$$

$$A_v \triangleq \frac{v_{out}}{v_{in}} \rightarrow 20 \log_{10} A_v \text{ in } dB$$

$$A_i \triangleq \frac{i_{out}}{i_{in}} \rightarrow 20 \log_{10} A_i \text{ in } dB$$



Amplifier - Efficiency

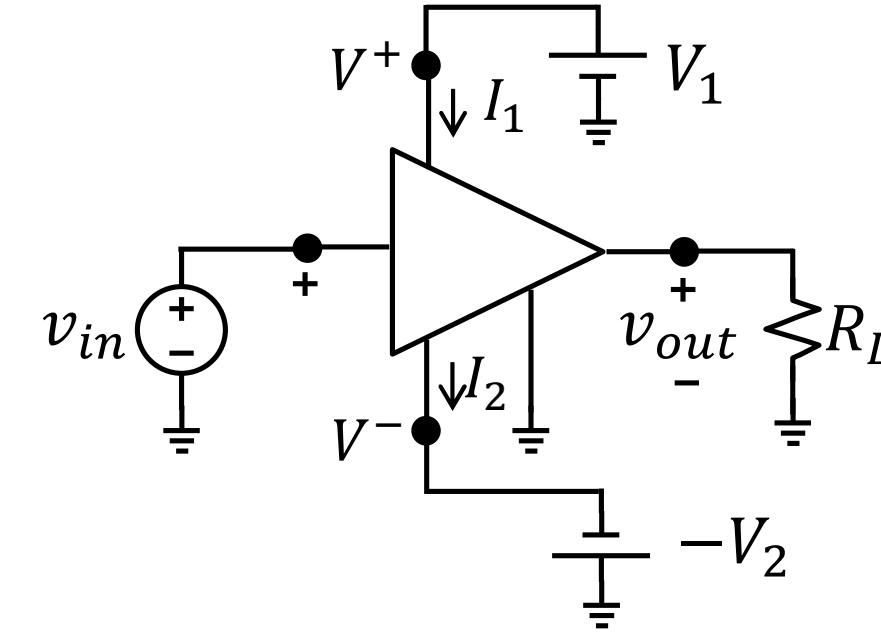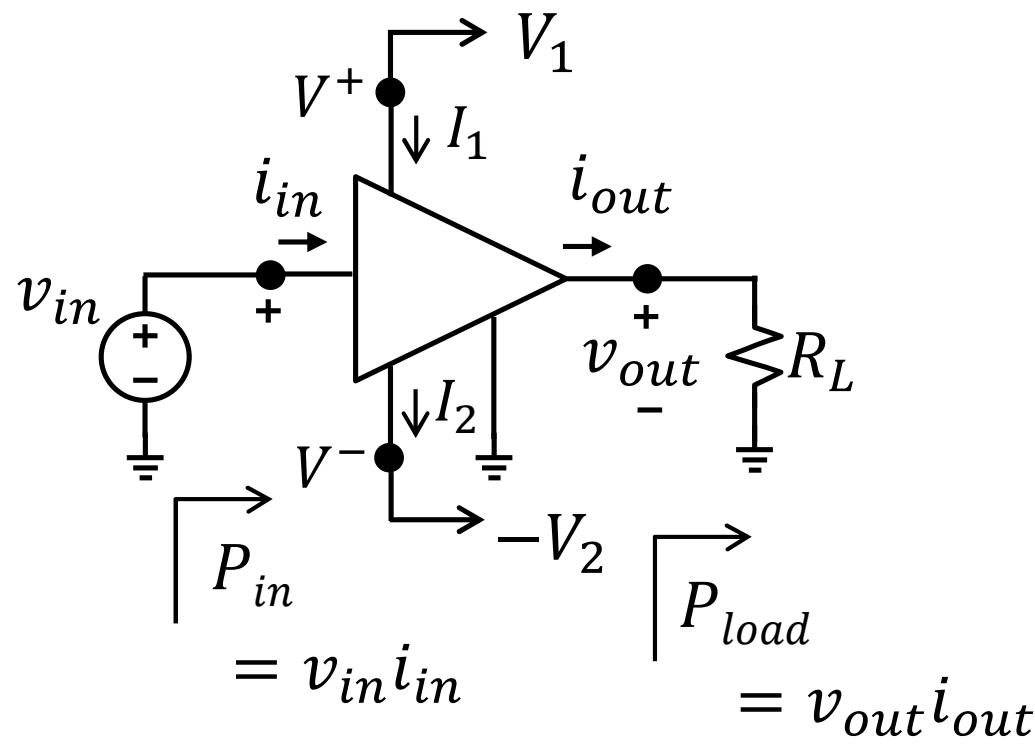

$$P_{dc} = P_{supply} = V^+ I_1 - V^- I_2$$

$$= V_1 I_1 + V_2 I_2$$

Conservation of energy:


$$P_{in} + P_{dc} = P_{load} + P_{dissipated}$$

$$\eta \equiv \frac{P_{load}}{P_{dc}} \quad \text{Efficiency}$$

$$= \frac{P_{load}}{P_{dc}} \times 100\%$$



Efficiency : Example

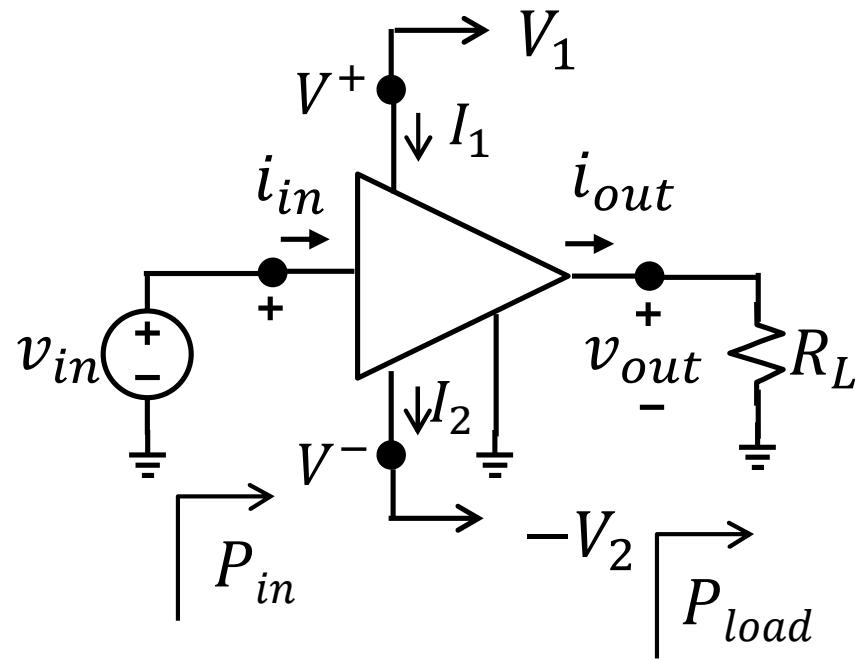

$$\left\{ \begin{array}{l} V_{1,2} = \pm 10V \\ I_1 = 9.5mA \quad I_2 = 9.5mA \\ v_{in} = 1^V \sin \omega t \quad v_{out} = 9^V \sin \omega t \\ i_{in} = 0.1^{mA} \sin \omega t \quad R_L = 1^{k\Omega} \end{array} \right.$$

$$A_v = 9 = 19.1 \text{ dB}$$

$$i_{out} = \frac{v_{out}}{R_L} = 9^{mA} \sin \omega t \quad A_i = \frac{i_{out}}{i_{in}} = 90 = 39.1 \text{ dB}$$

$$P_{load} = v_{orms} i_{orms} = \frac{9 \times 9^m}{\sqrt{2}\sqrt{2}} = 40.5^{\text{mW}}$$

$$A_P = 810 = 29.1 \text{ dB}$$

$$P_{in} = v_{irms} i_{irms} = \frac{1 \times 0.1^m}{\sqrt{2}\sqrt{2}} = 0.05^{\text{mW}}$$


$$P_{dc} = 10 \times 9.5 \times 2 = 190^{\text{mW}}$$

$$\eta = \frac{P_{load}}{P_{dc}} \times 100\% = 21.3\%$$


$$P_{diss} = P_{dc} + P_{in} - P_{load} = 149.6^{\text{mW}}$$




Non-ideal Amplifier

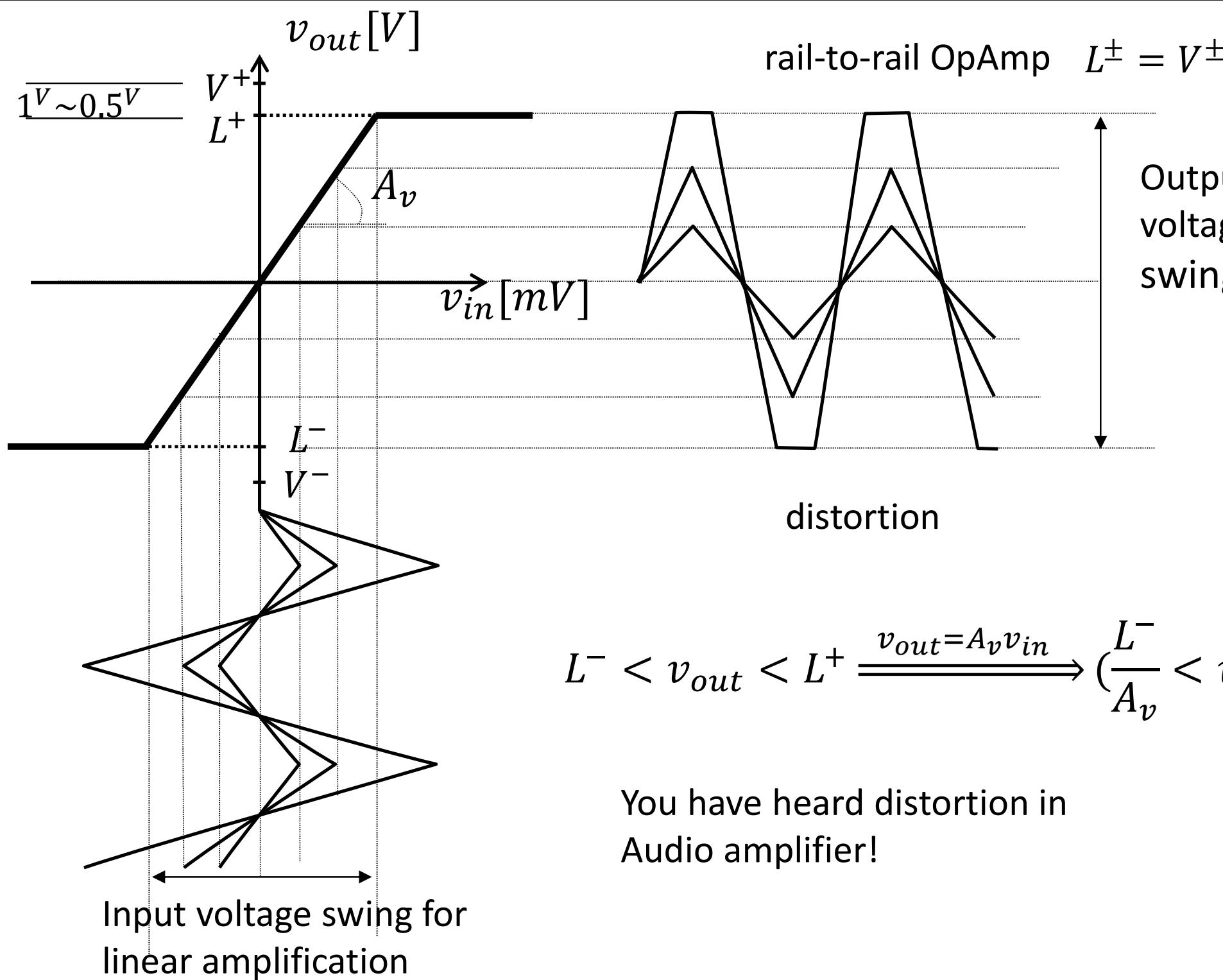


Nonlinear Transfer Function Biasing

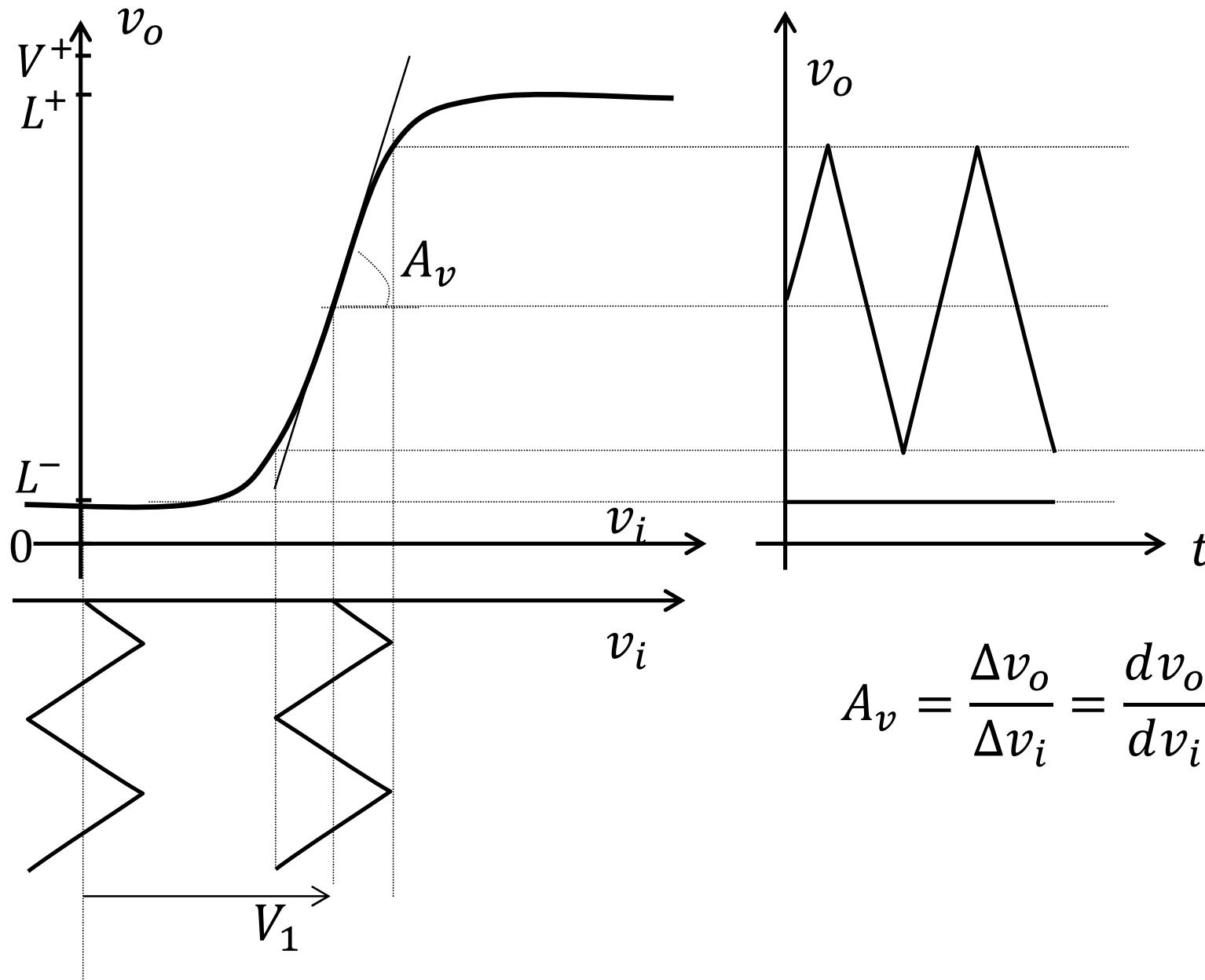


$$A_v = \frac{\Delta v_o}{\Delta v_i} = \left. \frac{dv_o}{dv_i} \right|_Q \quad \text{bias point}$$

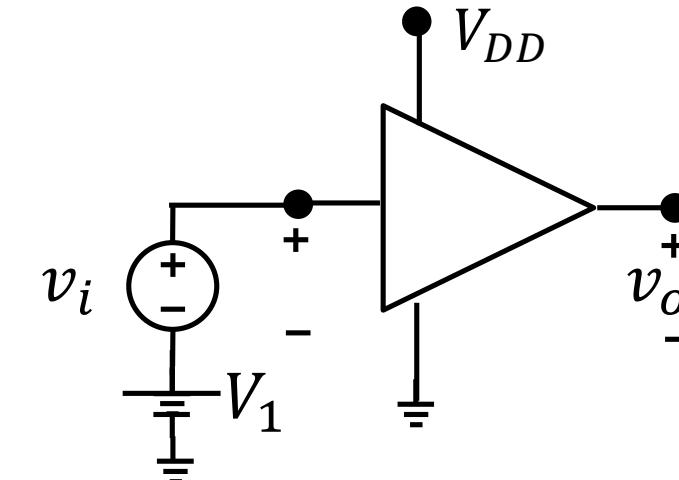

Nonlinear Transfer Function Biasing

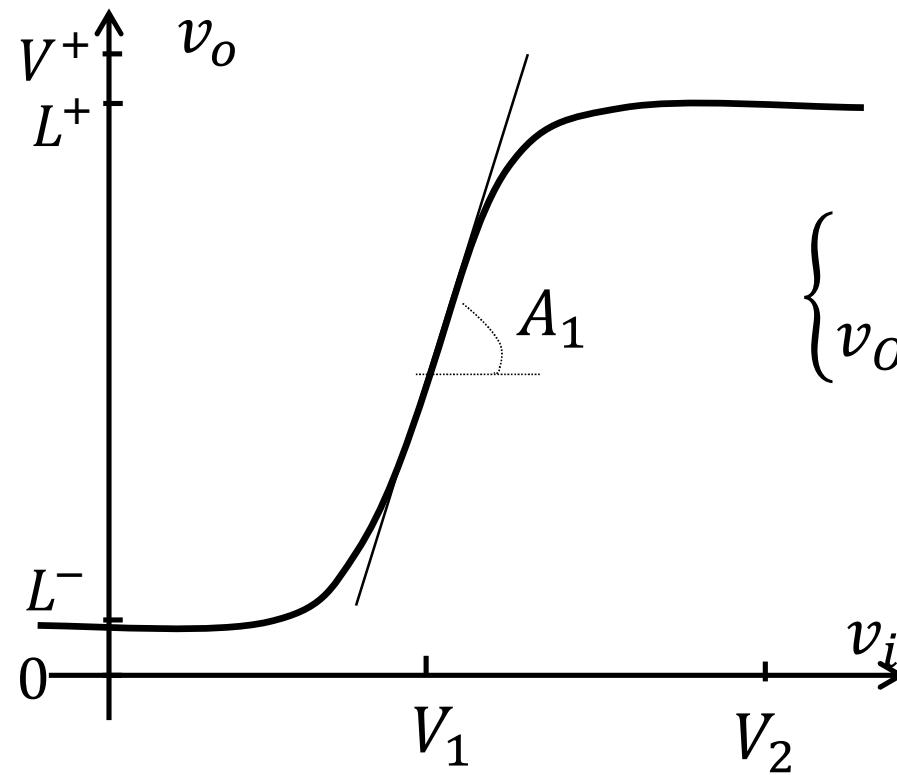

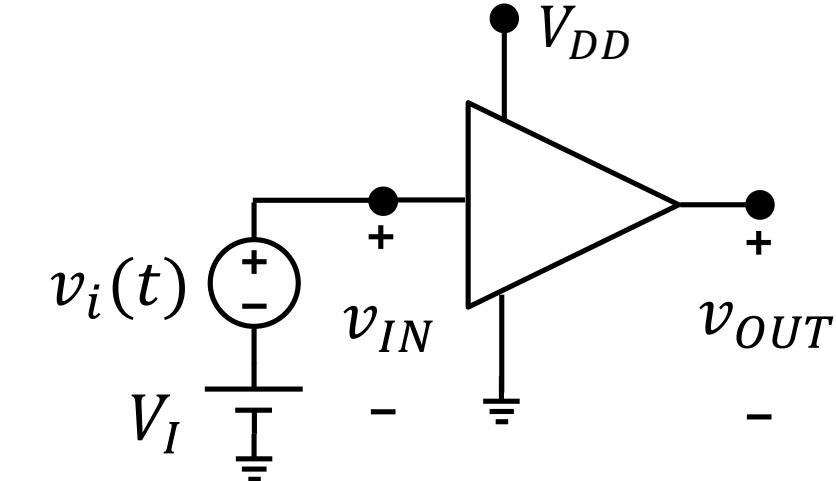
$$\begin{cases} v_{IN} = V_I + v_i(t) \\ v_{OUT} = V_O + A_v v_i(t) \end{cases}$$



$$V_I = 0 \rightarrow A_v = 0$$

$$V_I = V_1 \rightarrow A_v = A_1$$

$$V_I = V_2 \rightarrow A_v = 0$$

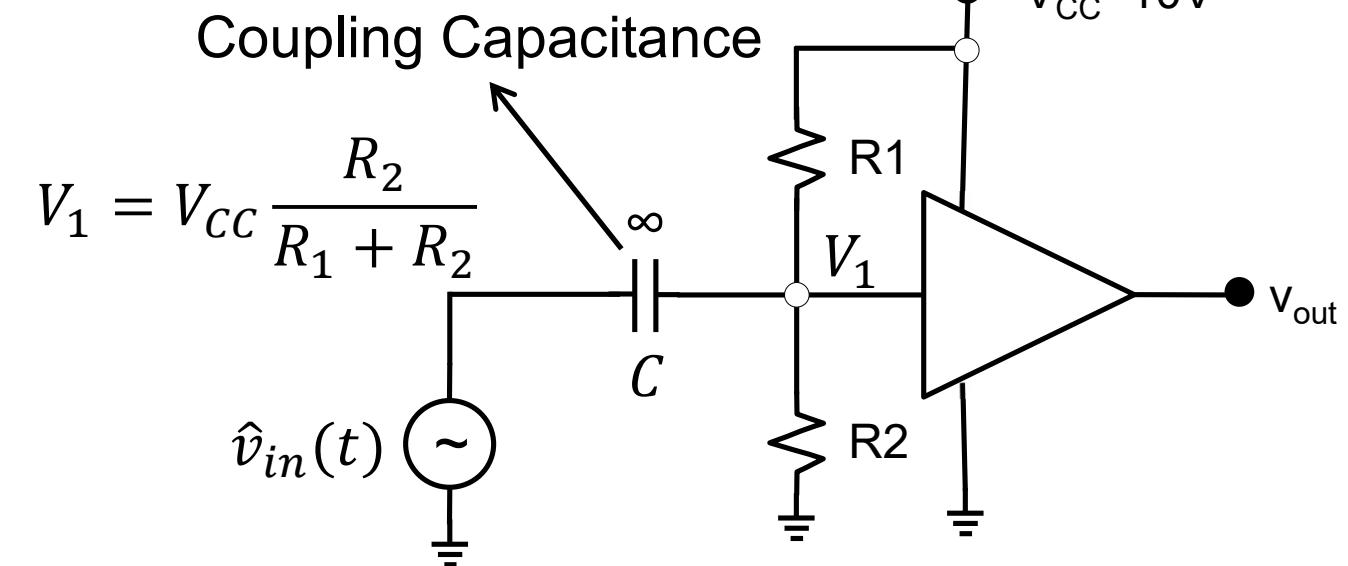

$$v_{out}(t) = V_{out} + A_v \hat{v}_{in}(t)$$



Summary

KVL, KCL: voltage division

Source Transformation

Replacement Theorem

Thevenin / Norton Equivalent

Amplifier, ideal / non-ideal

Amplifier - Efficiency

Output voltage swing

Nonlinear Transfer Function

Biasing

