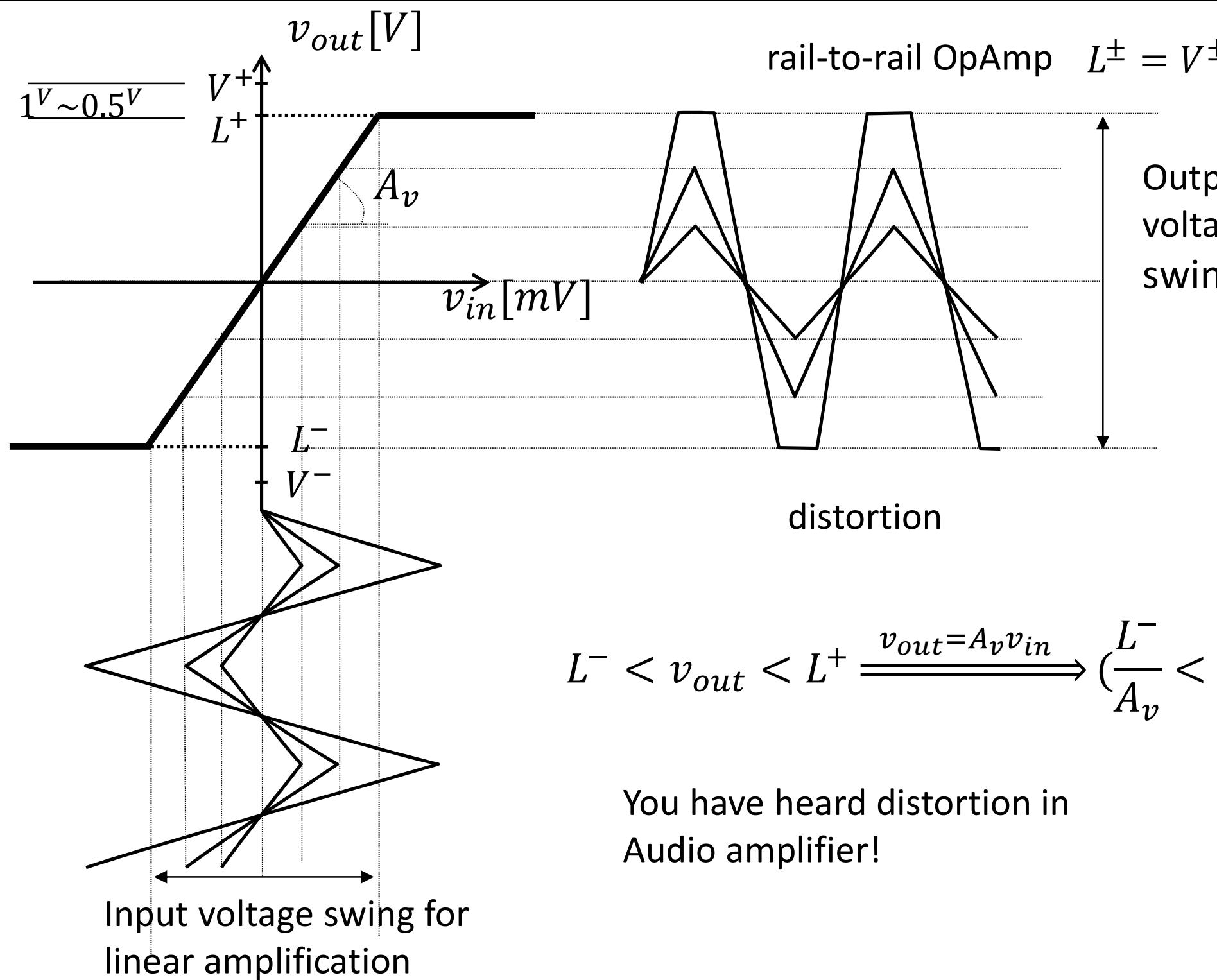


Week2 Electronics1


# Amplifiers 2




# Non-ideal Amplifier




# Nonlinear Transfer Function Biasing

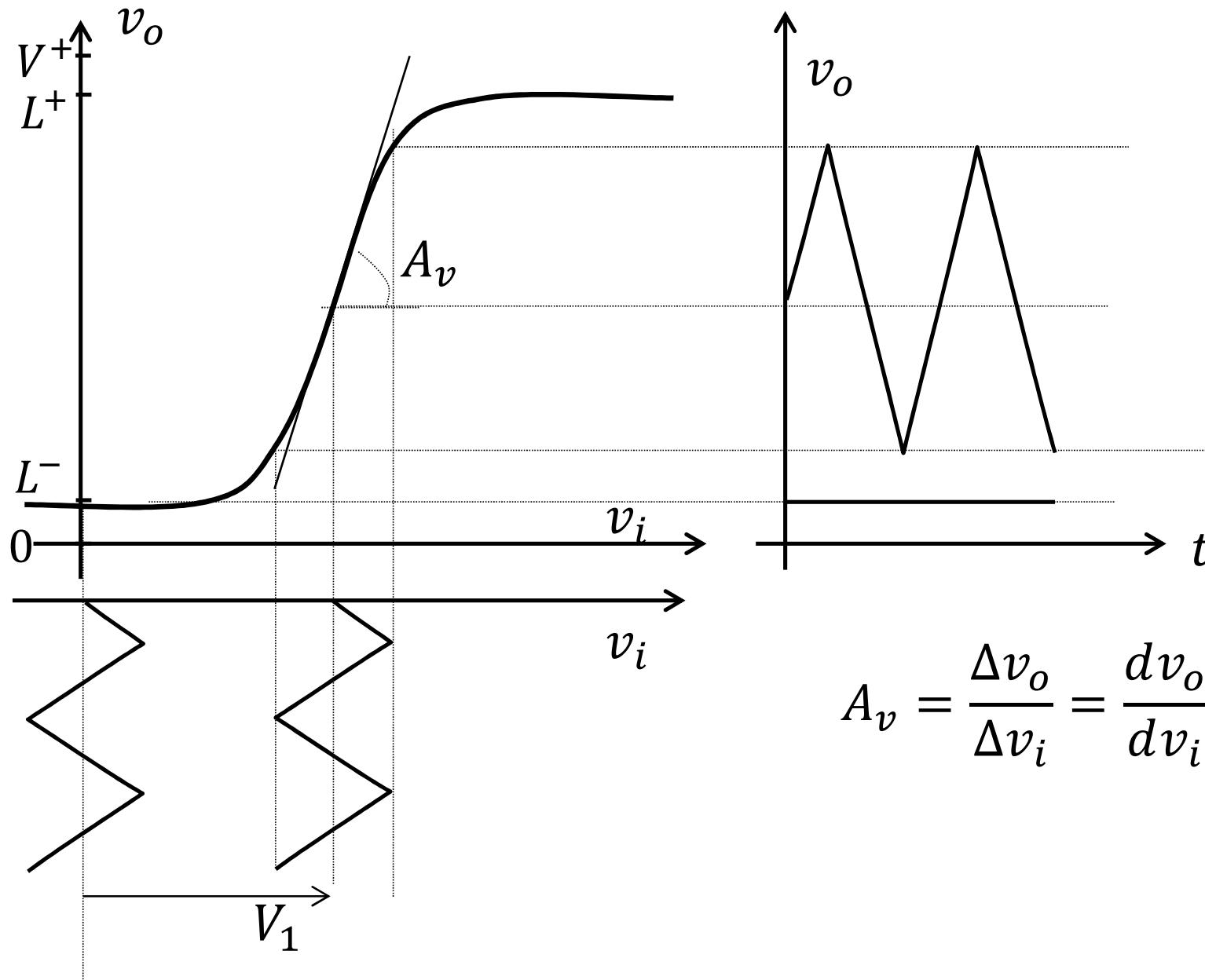


$$A_v = \frac{\Delta v_o}{\Delta v_i} = \left. \frac{dv_o}{dv_i} \right|_{Q \text{ bias point}}$$

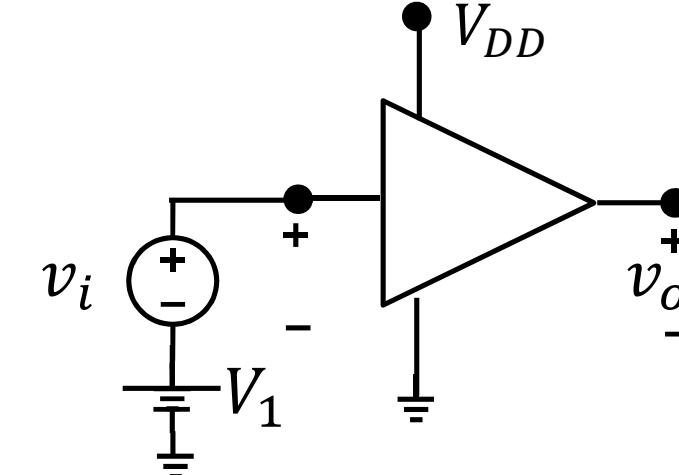

# Nonlinear Transfer Function Biasing

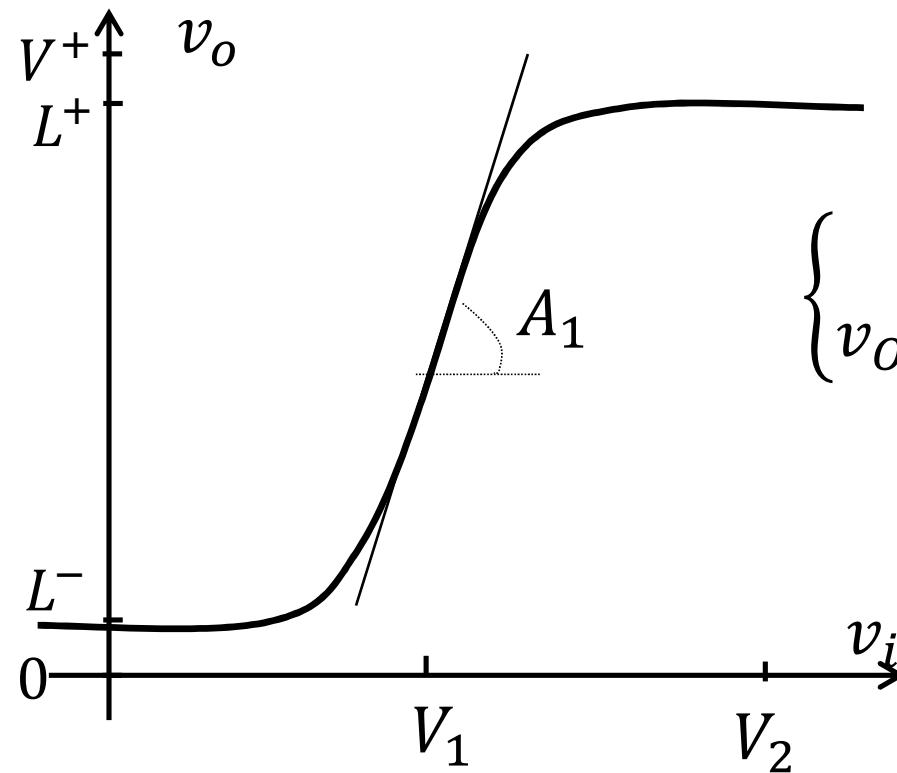

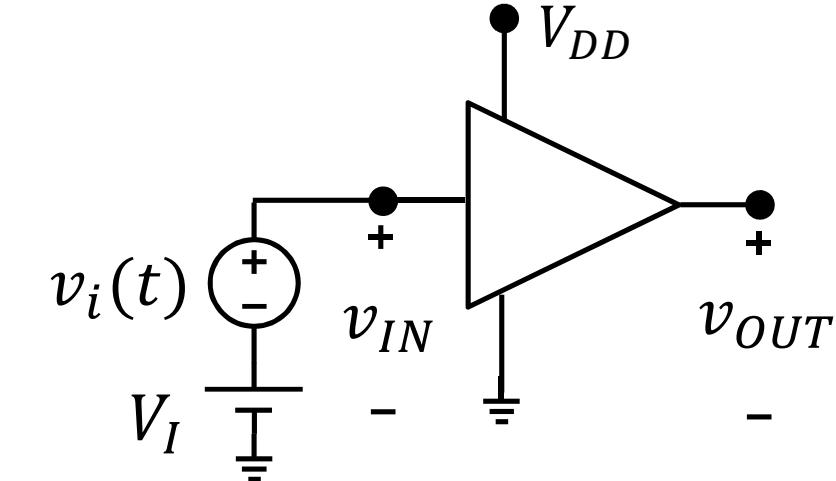
$$\begin{cases} v_{IN} = V_I + v_i(t) \\ v_{OUT} = V_O + A_v v_i(t) \end{cases}$$



$$V_I = 0 \rightarrow A_v = 0$$

$$V_I = V_1 \rightarrow A_v = A_1$$



$$V_I = V_2 \rightarrow A_v = 0$$

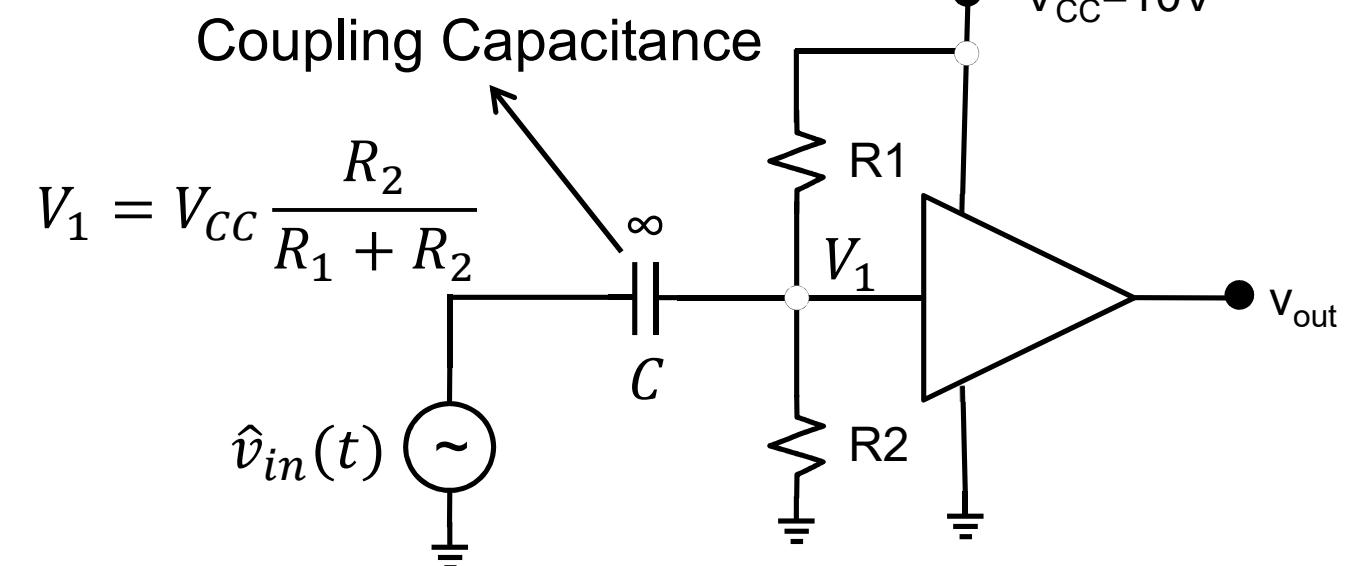

$$v_{out}(t) = V_{out} + A_v \hat{v}_{in}(t)$$



# Voltage Amplifier

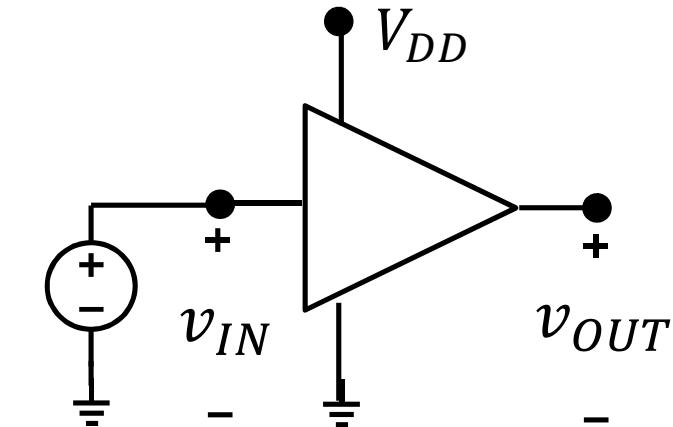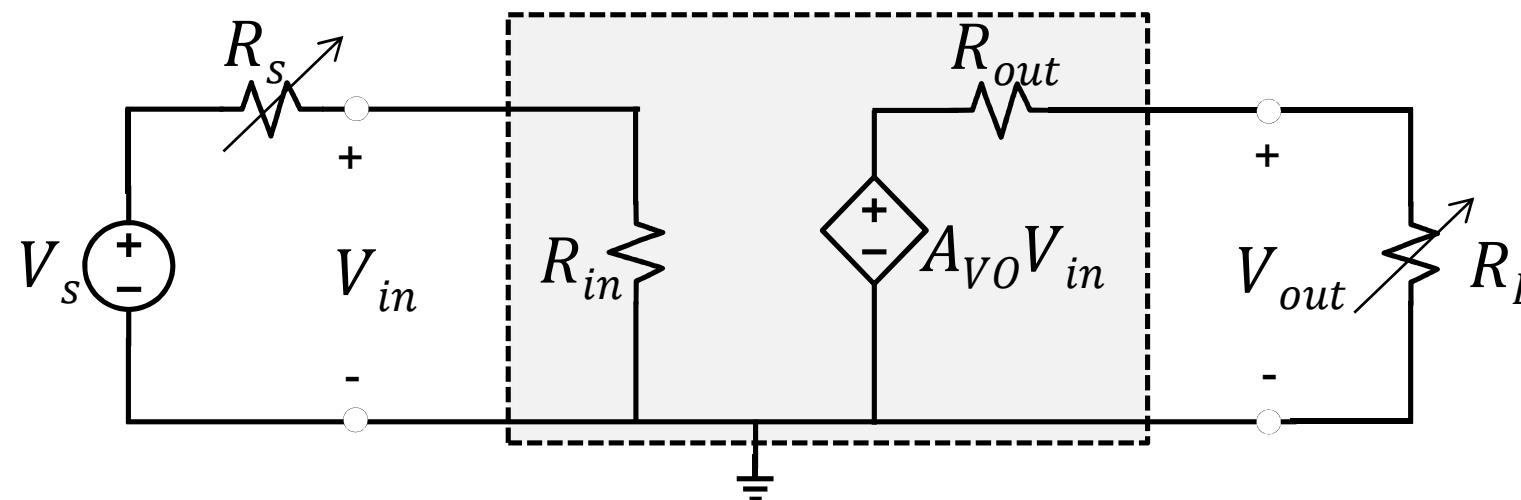

Open circuit:  $R_L = \infty \rightarrow \frac{V_{out}}{V_{in}} = A_{VO} \quad \left[ \frac{V}{V} \right]$  open circuit voltage gain

$$V_{in} = \frac{R_{in}}{R_{in} + R_s} \cdot V_s \quad V_{in} = V_s \quad \forall R_s \quad \text{if } R_{in} = \infty \quad \text{Ideal case}$$

$$V_{out} = A_{VO} V_{in} \frac{R_L}{R_L + R_{out}} \quad V_{out} = A_{VO} V_{in} \quad \forall R_L \quad \text{if } R_{out} = 0 \quad \text{Ideal case}$$

Generally:


$$\frac{V_{out}}{V_s} = A_{VO} \left( \frac{R_L}{R_L + R_{out}} \right) \left( \frac{R_{in}}{R_{in} + R_s} \right)$$

Ideal case:

$$\frac{V_{out}}{V_s} = A_{VO}$$



# Current Amplifier

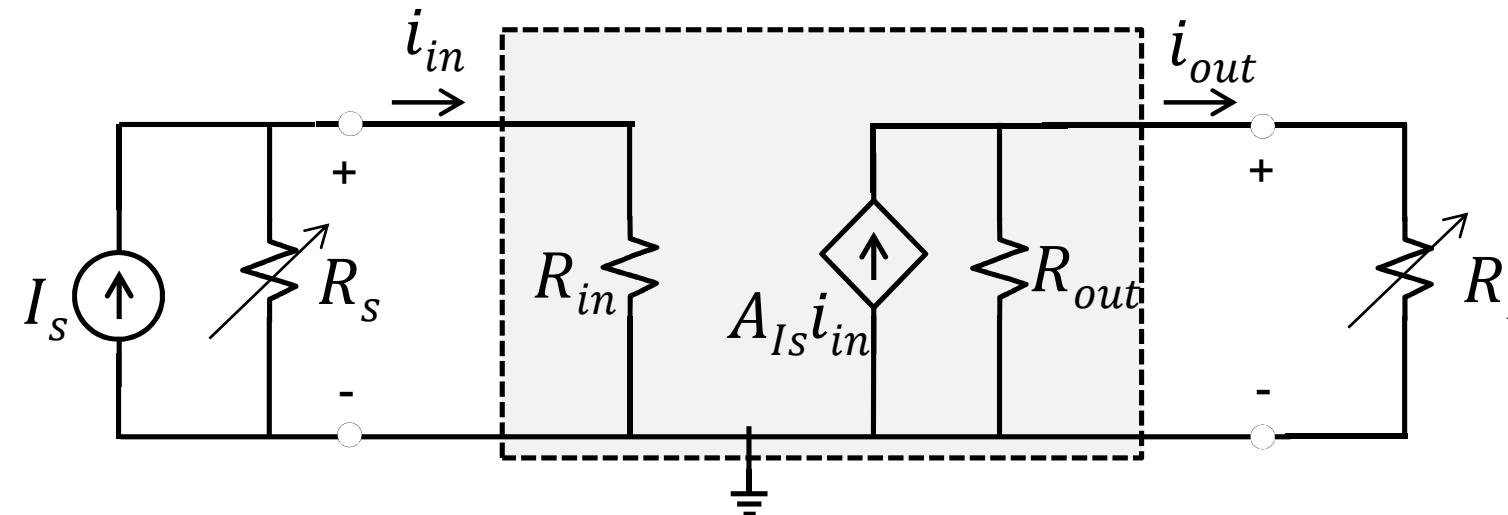

Short circuit:  $R_L = 0 \rightarrow \frac{i_{out}}{i_{in}} = A_{Is} \quad \left[ \frac{A}{A} \right]$  short circuit current gain

$$i_{in} = \frac{R_s}{R_{in} + R_s} \cdot I_s \quad i_{in} = I_s \quad \forall R_s \quad \text{if } R_{in} = 0 \quad \text{Ideal case}$$

$$i_{out} = A_{Is} i_{in} \frac{R_{out}}{R_L + R_{out}} \quad i_{out} = A_{Is} i_{in} \quad \forall R_L \quad \text{if } R_{out} = \infty \quad \text{Ideal case}$$

Generally:

$$\frac{i_{out}}{I_s} = A_{Is} \left( \frac{R_{out}}{R_L + R_{out}} \right) \left( \frac{R_s}{R_{in} + R_s} \right)$$


Ideal case:

$$\frac{i_{out}}{I_s} = A_{Is}$$



# TransConductance Amplifier

---

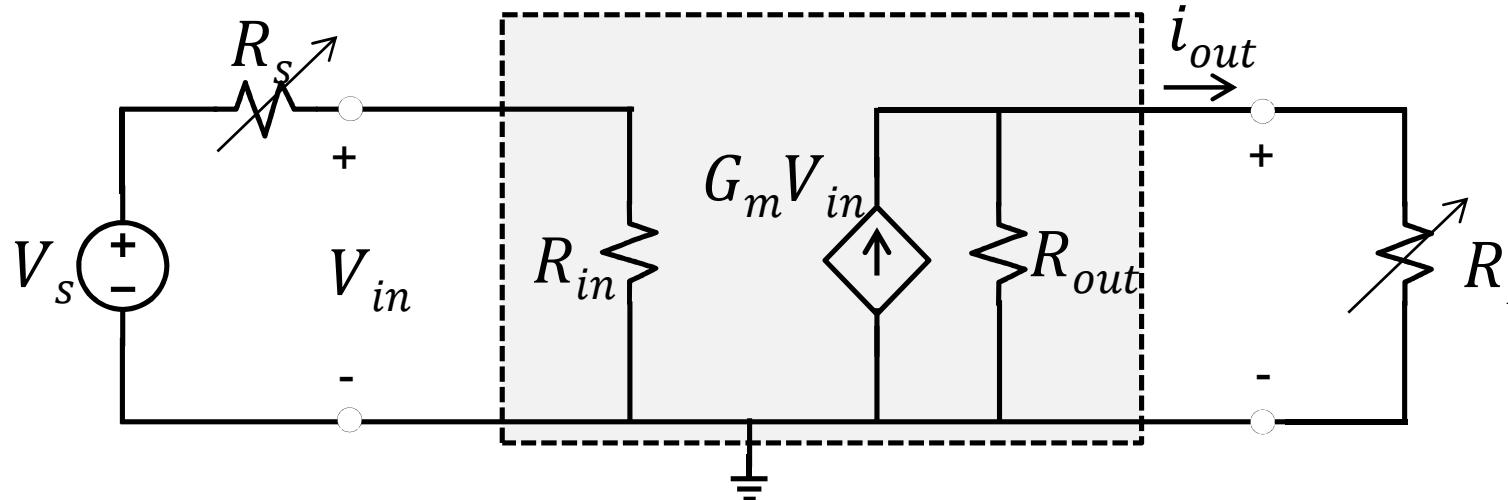

Short circuit:  $R_L = 0 \rightarrow \frac{i_{out}}{V_{in}} = G_m \quad \left[ \frac{A}{V} = \Omega^{-1} \right]$  short circuit Trans-conductance

$$V_{in} = \frac{R_{in}}{R_{in} + R_s} \cdot V_s \quad V_{in} = V_s \quad \forall R_s \quad \text{if } R_{in} = \infty \quad \text{Ideal case}$$

$$i_{out} = G_m V_{in} \frac{R_{out}}{R_L + R_{out}} \quad i_{out} = G_m V_{in} \quad \forall R_L \quad \text{if } R_{out} = \infty \quad \text{Ideal case}$$

Generally:


$$\frac{i_{out}}{V_s} = G_m \left( \frac{R_{out}}{R_L + R_{out}} \right) \left( \frac{R_{in}}{R_{in} + R_s} \right)$$

Ideal case:

$$\frac{i_{out}}{V_s} = G_m$$



# TransResistance Amplifier

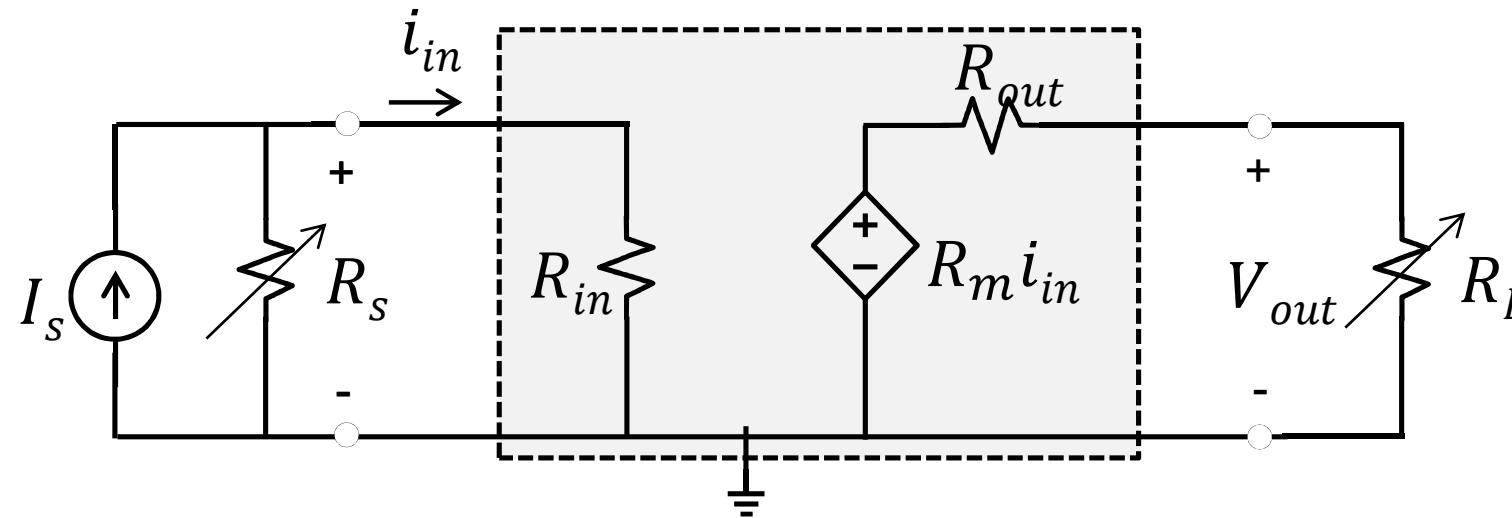

Short circuit:  $R_L = \infty \rightarrow \frac{V_{out}}{i_{in}} = R_m \quad \left[ \frac{V}{A} = \Omega \right]$  open circuit Trans-resistance

$$i_{in} = \frac{R_s}{R_{in} + R_s} \cdot I_s \quad i_{in} = I_s \quad \forall R_s \quad \text{if } R_{in} = 0 \quad \text{Ideal case}$$

$$V_{out} = R_m i_{in} \frac{R_L}{R_L + R_{out}} \quad V_{out} = R_m i_{in} \quad \forall R_L \quad \text{if } R_{out} = 0 \quad \text{Ideal case}$$

Generally:

$$\frac{V_{out}}{I_s} = R_m \left( \frac{R_L}{R_L + R_{out}} \right) \left( \frac{R_s}{R_{in} + R_s} \right)$$


Ideal case:

$$\frac{V_{out}}{I_s} = R_m$$



# Amplifiers

Voltage Amplifier

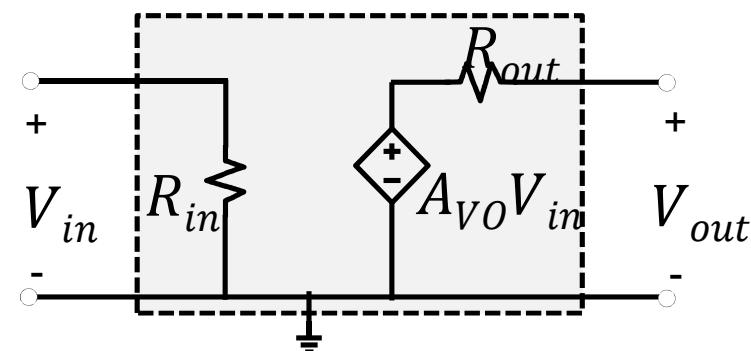


$$A_{VO} = \frac{V_{out}}{V_{in}} \Big|_{i_{out}=0}$$

open circuit voltage gain

Ideal:

$$\begin{aligned}R_{in} &= \infty \\R_{out} &= 0\end{aligned}$$

Current Amplifier

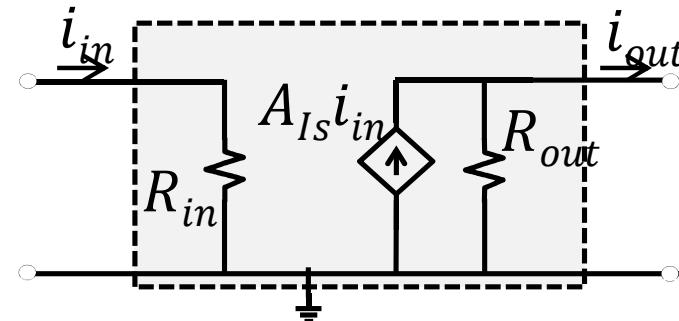


$$A_{IS} = \frac{i_{out}}{i_{in}} \Big|_{V_{out}=0}$$

short circuit current gain

$$\begin{aligned}R_{in} &= 0 \\R_{out} &= \infty\end{aligned}$$

Trans-Conductance Amplifier

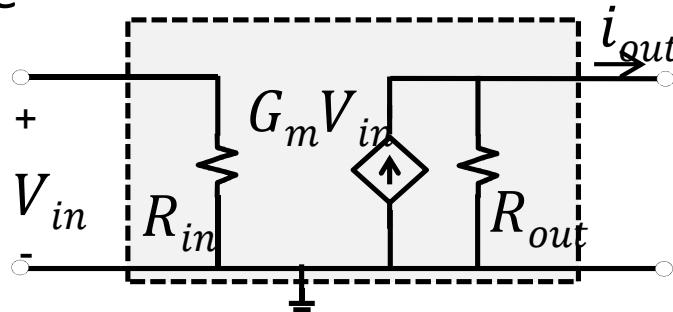


$$G_m = \frac{i_{out}}{V_{in}} \Big|_{V_{out}=0}$$

short circuit Trans-conductance

$$\begin{aligned}R_{in} &= \infty \\R_{out} &= \infty\end{aligned}$$

Trans-Resistance Amplifier

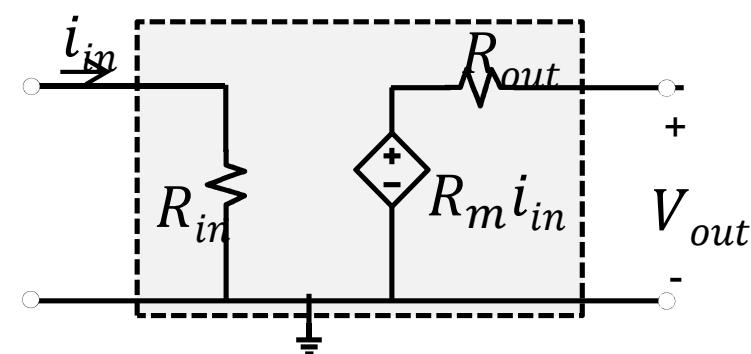

$$R_m = \frac{V_{out}}{i_{in}} \Big|_{i_{out}=0}$$



open circuit Trans-resistance

$$\begin{aligned}R_{in} &= 0 \\R_{out} &= 0\end{aligned}$$



# Amplifiers

Voltage  
Amplifier

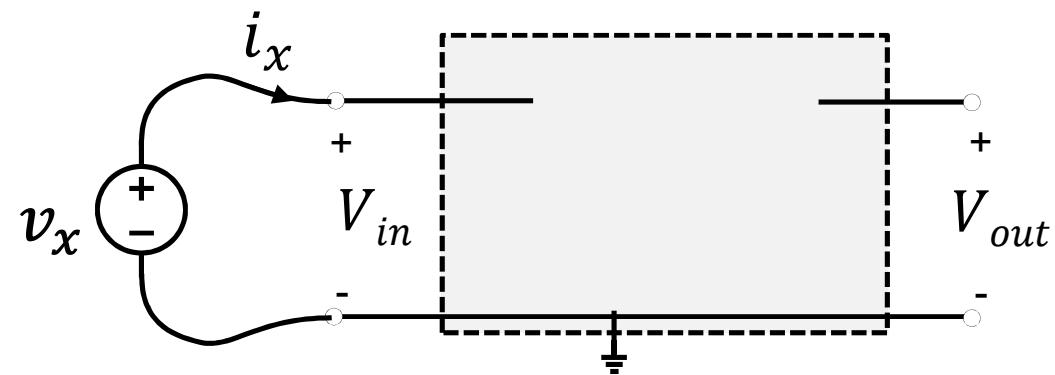
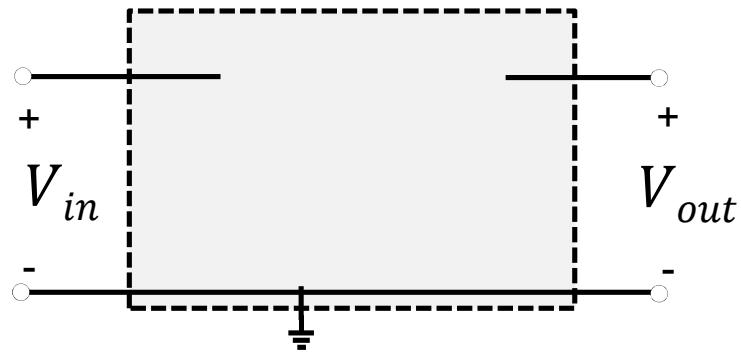


$$R_{in} = \frac{v_x}{i_x}$$

$$V_{in} = v_x$$

$$A_{VO} = \left. \frac{V_{out}}{v_x} \right|_{I_{out}=0}$$

Open Output

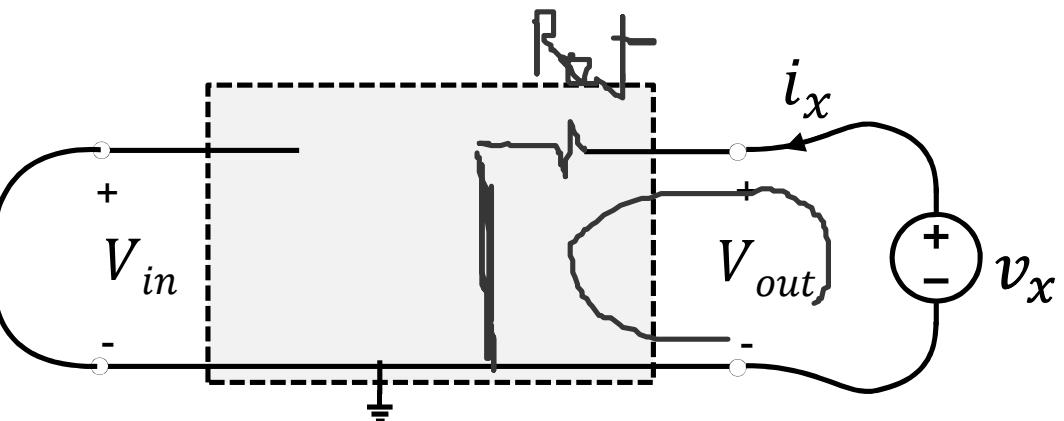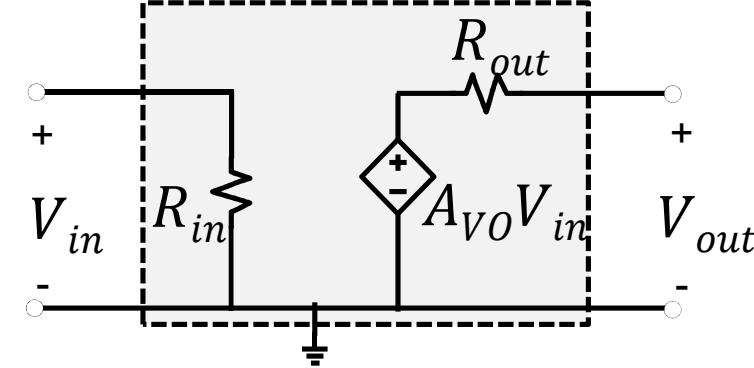


$$R_{out} = \left. \frac{v_x}{i_x} \right|_{V_{in}=0}$$




# Practical Consideration

---

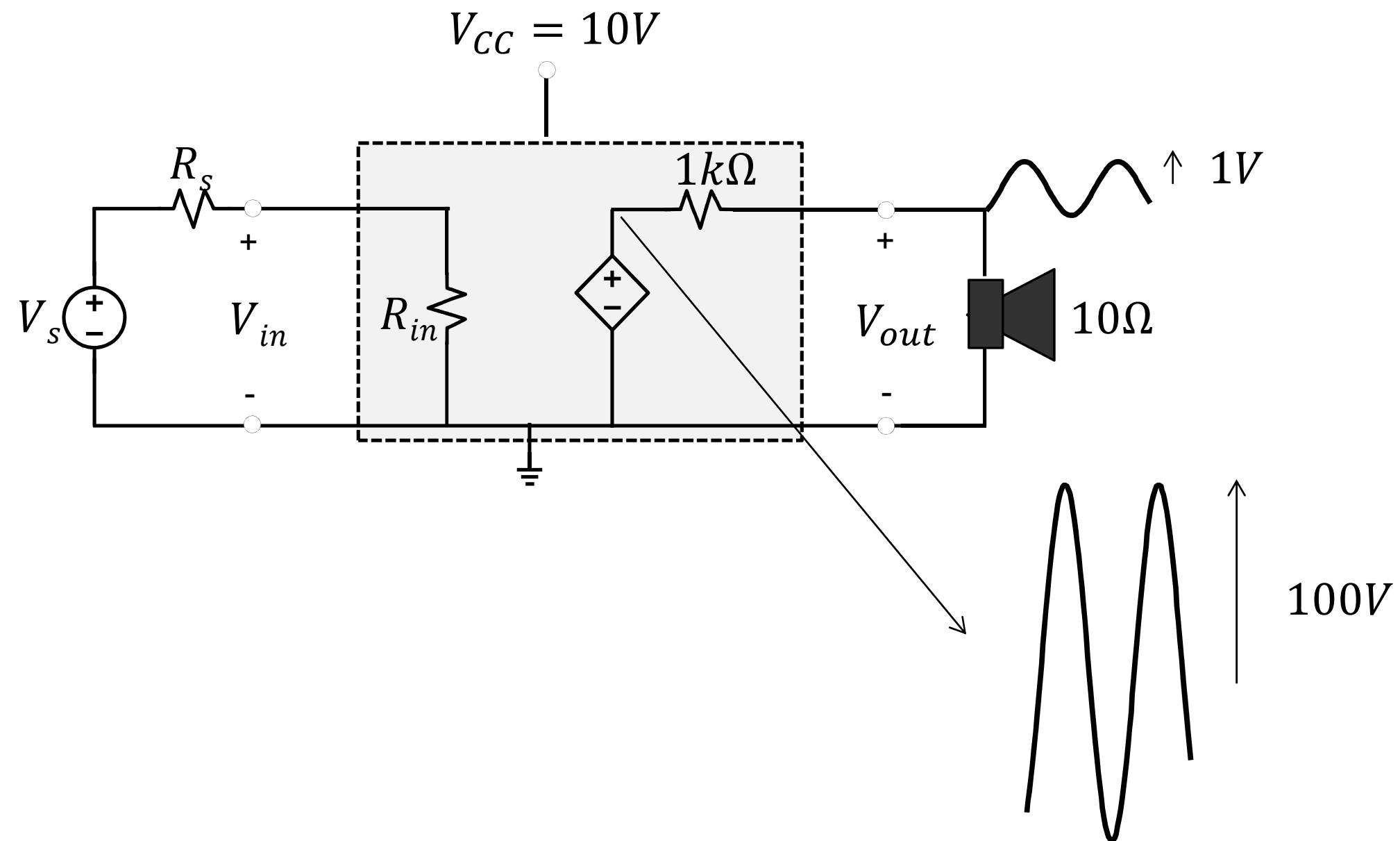
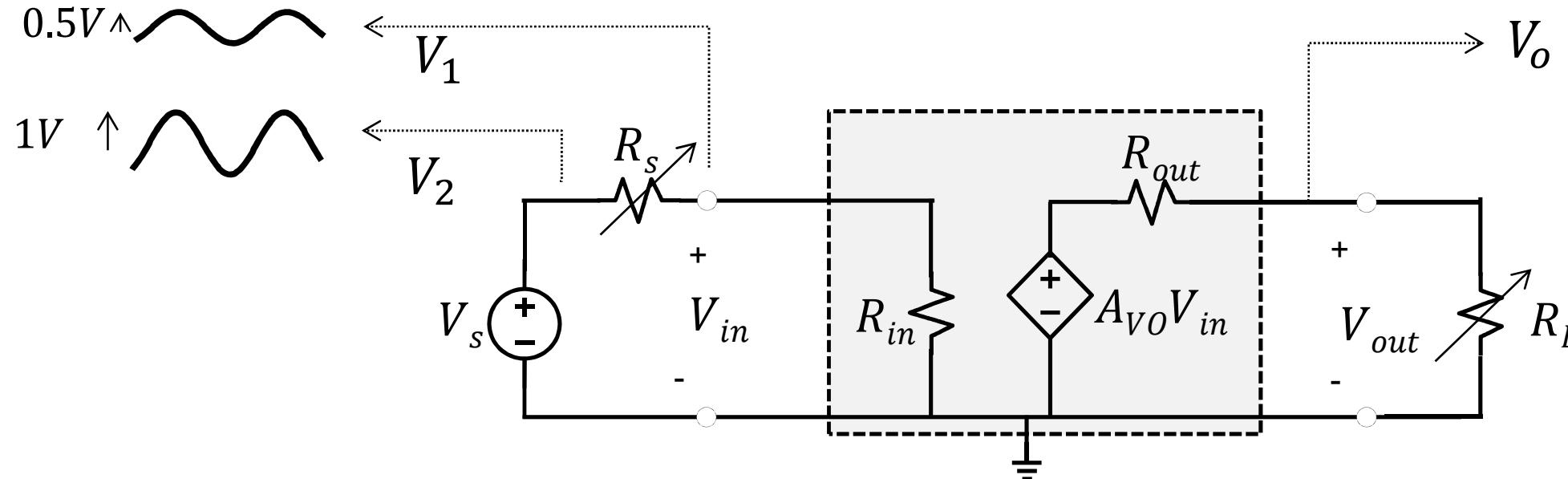
# Practical Consideration: Input / Output Resistance





$$R_s = 1k\Omega \rightarrow \frac{V_1}{V_2} = \frac{R_{in}}{R_{in} + 1k}$$



$$R_{in} = 1k \times \frac{1}{\frac{V_2}{V_1} - 1}$$

Point: You need to make sure circuit is in its linear operation regime (desired bias point)

How about  $R_{out}$ ?

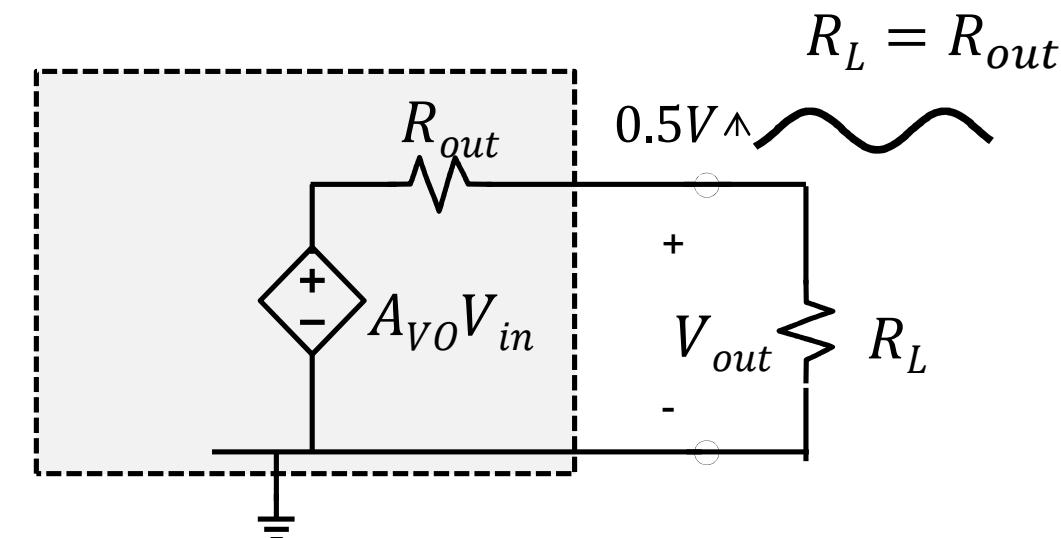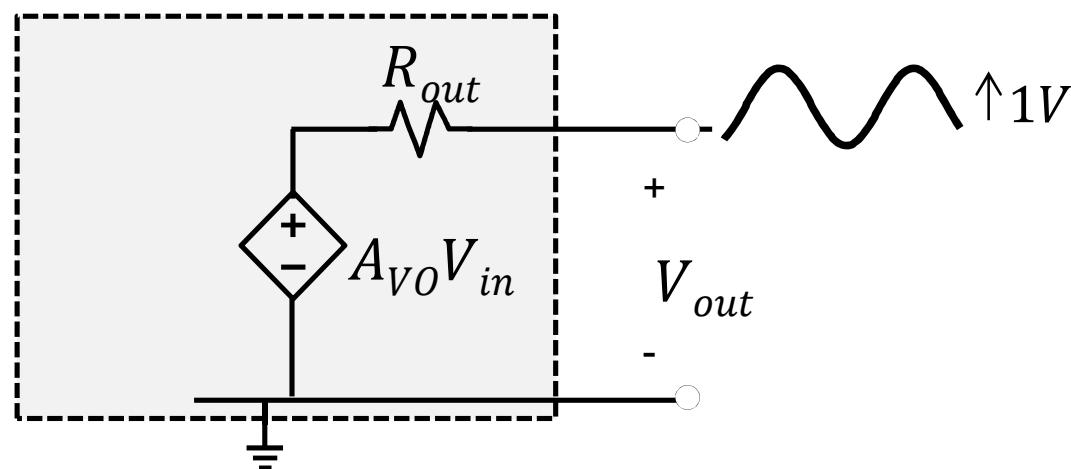

# Amplifier Frequency Response

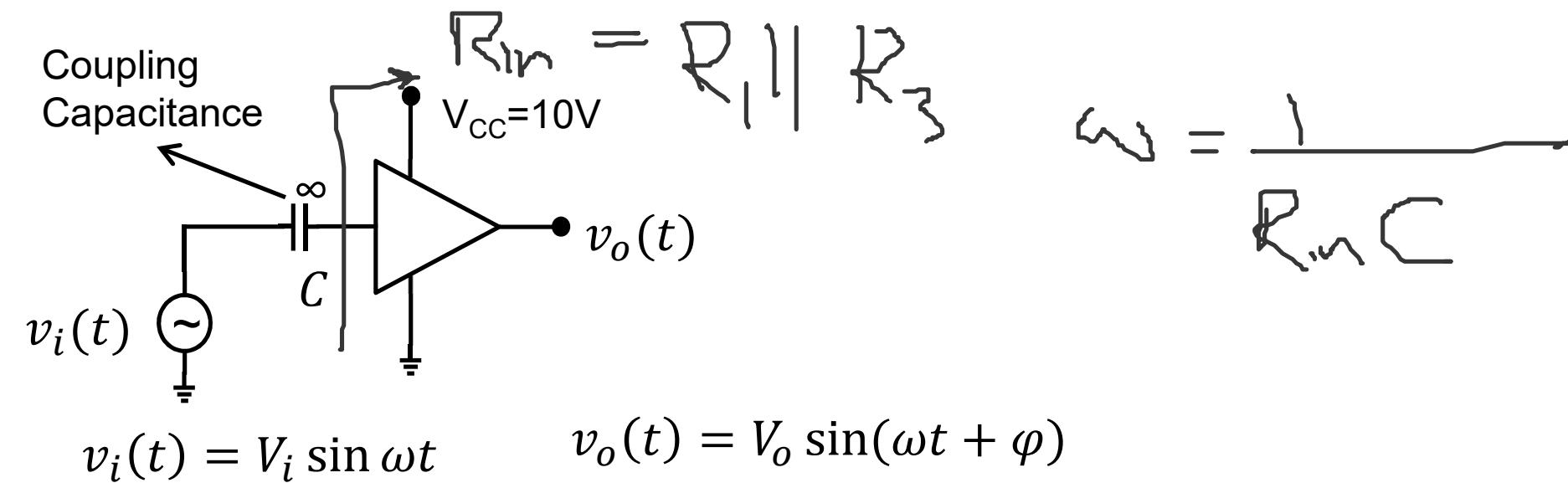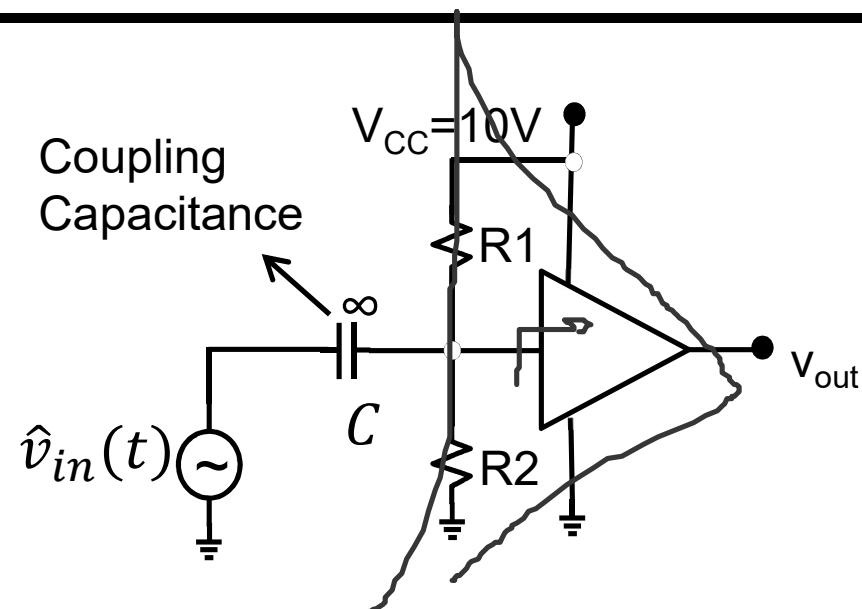


Transfer Function:  $T(\omega) = \frac{v_o}{v_i}$

$$|T(\omega)| = \frac{V_o}{V_i}$$

Amplitude in dB

$$\angle T(\omega) = \varphi$$

Phase

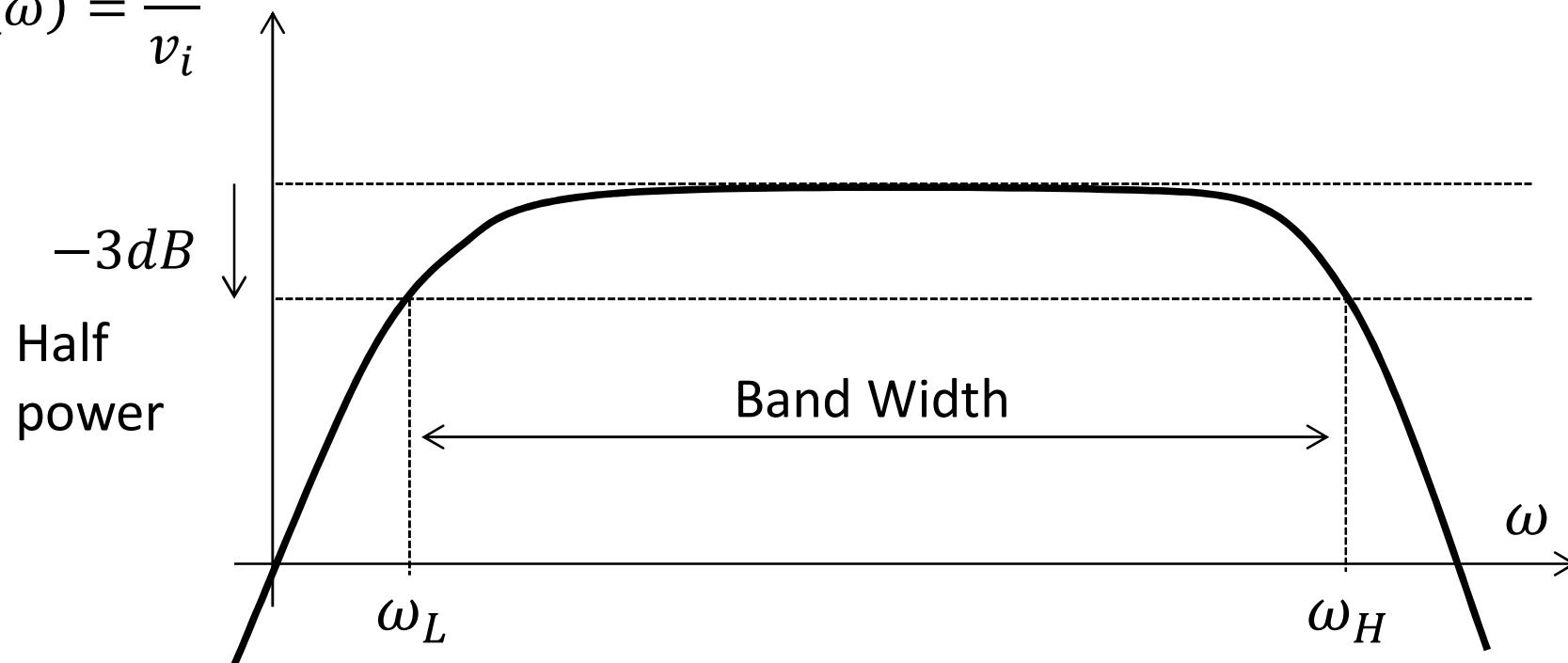

**end**

---

