

$$R_{in} = \frac{v_{in}}{\frac{v_{in} - v_i}{R_1}}$$

$|a| \gg 1$

$$r_i \gg R_1, R_2 \gg r_o$$

(\*)

$$\frac{v_i}{r_i} + \frac{v_i - v_{out}}{R_2} + \frac{v_i - v_{in}}{R_1} = 0$$

$$\frac{v_{out} - av_i}{r_o} + \frac{v_{out} - v_i}{R_2} = 0 \rightarrow v_{out} \left( \frac{1}{r_o} + \frac{1}{R_2} \right) = v_i \left( \frac{1}{R_2} + \frac{a}{r_o} \right)$$


$$v_{out} = v_i \frac{r_o \parallel R_2}{\frac{r_o}{a} \parallel R_2} \approx av_i$$

$$v_i = \frac{1}{a} v_{out}$$

$$\frac{-v_{in}}{R_1} + v_{out} \left( \frac{\frac{r_o \parallel R_2}{a}}{r_o \parallel R_2} \frac{r_o}{a R_2 + a} \frac{1}{R_1 \parallel r_i \parallel R_2} - \frac{1}{R_2} \right) = 0 \approx \frac{v_{out}}{v_{in}} = -\frac{R_2}{R_1}$$

$\frac{1}{a}$        $\frac{1}{a(R_1 \parallel R_2 \parallel r_i)}$        $r_o \ll R_2$
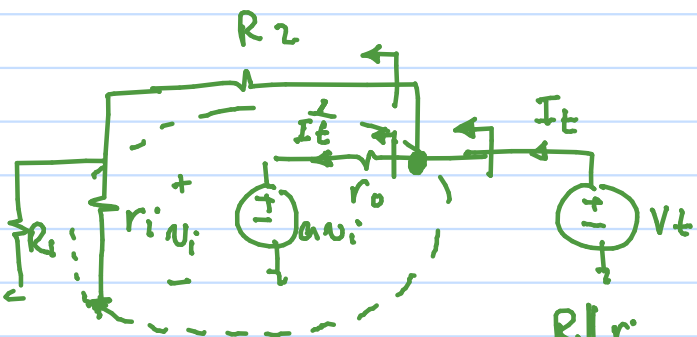
$$R_{in} = R_1 \frac{v_{in}}{v_{in} - v_i} = \frac{R_1}{1 + \frac{R_2}{a R_1}} \approx R_1$$






$$R_{out} = (R_2 + r_i \parallel R_1) \parallel \frac{V_t}{I_t}$$

$$I_t = \frac{V_t - av_i}{r_o}$$

$$v_i = \frac{R_1 \parallel r_i}{R_1 \parallel r_i + R_2} V_t$$

$$= V_t \left( 1 - a \frac{R_1 \parallel r_i}{R_1 \parallel r_i + R_2} \right) \frac{1}{r_o}$$

$$R_{out} = (R_2 + R_1 \parallel r_i) \parallel \frac{r_o}{-a \left( 1 + \frac{R_2}{R_1} \right)} \approx \frac{r_o}{|a| \left( 1 + \frac{R_2}{R_1} \right)} \approx 0$$

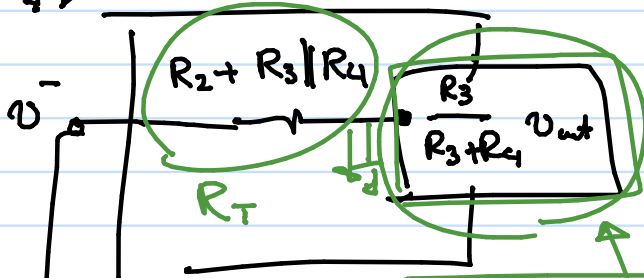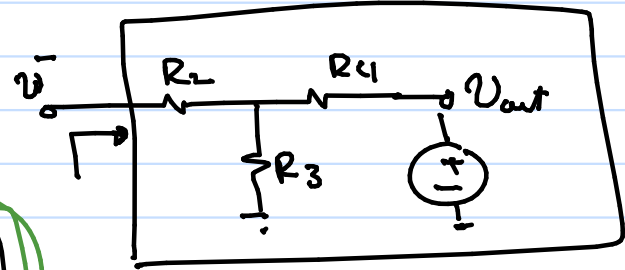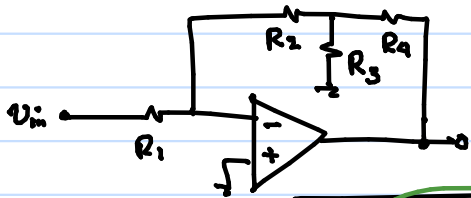

$$0 = V^- = \frac{R_3 V_{out}}{R_3 + R_4} + \frac{R_1}{R_1 + R_2 + R_3 || R_4} V_{in}$$










$$V^- = V_{in} \frac{R_2 + R_3 || R_4}{R_2 + R_3 || R_4 + R_1}$$

$$\frac{V_{out}}{V_{in}} = - \frac{R_2 + R_3 || R_4}{R_1} \times \frac{R_3 + R_4}{R_3}$$

if  $R_3 = \infty$   $A_v = - \frac{R_2 + R_4}{R_1}$

11/18

4

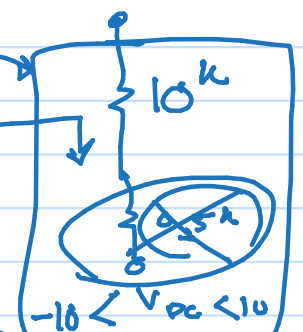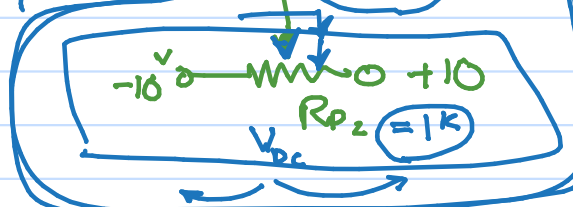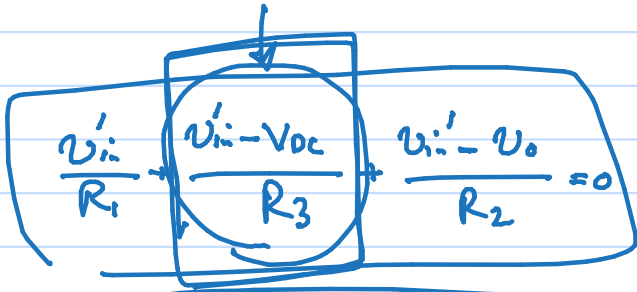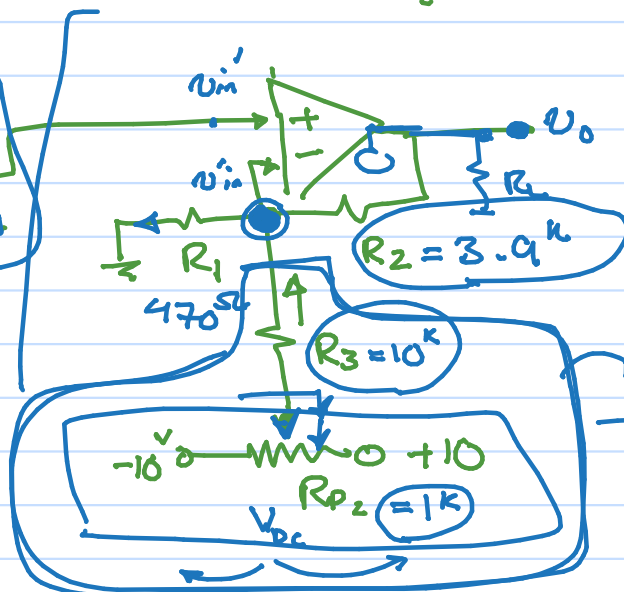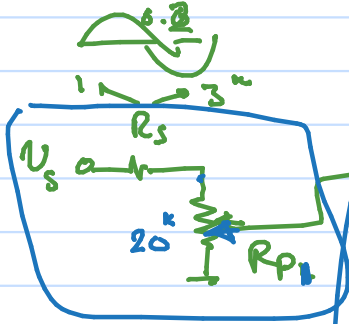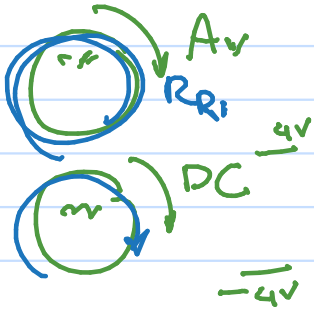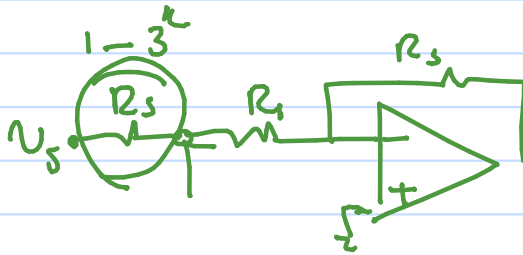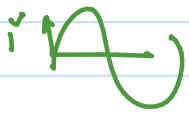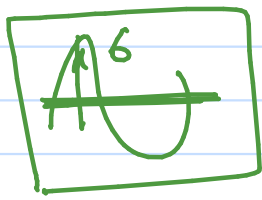

$$V_o = v_{in}' \left( 1 + \frac{R_2}{R_1} + \frac{R_2}{R_3} \right) - V_{DC} \frac{R_2}{R_3}$$

$$\frac{R_2}{R_3} = \frac{4}{10}$$


$$10 \rightarrow R_1 = 465 \Omega \rightarrow 470 \Omega$$

$$0.2 < \frac{R_{R1}}{R_{R1} + R_s} \times 10 < 6$$

$$0.2 < \frac{R_s}{R_p} < 1.5$$

$$0.2^k < R_p < 15^k$$


تصميم

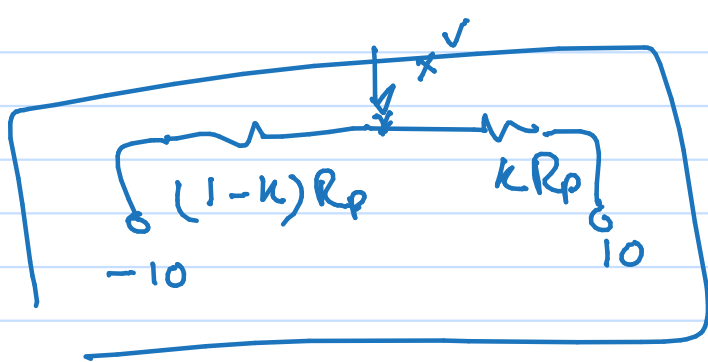




$$X = 10 \frac{k}{R_R} + \frac{-10(1-k)}{R_p}$$



$$R_L \gg R_T$$

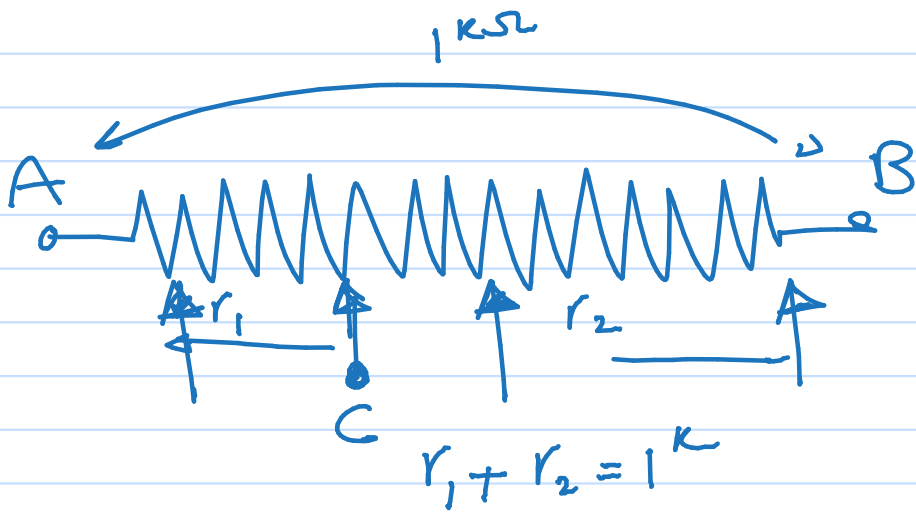



5

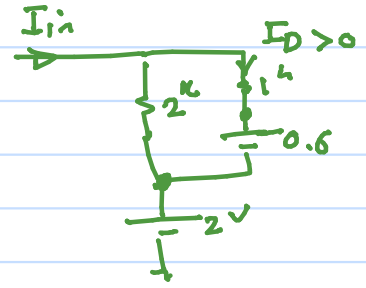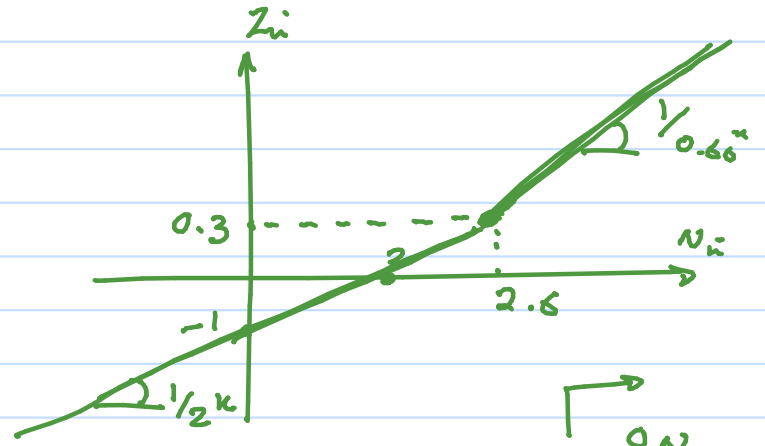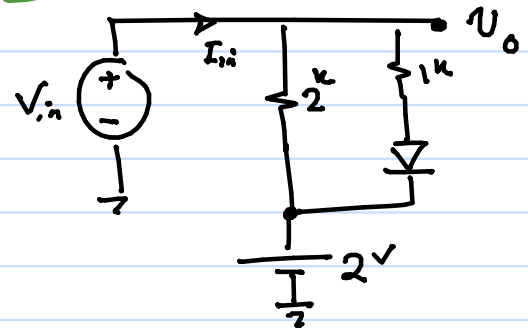

$$I_{in} = \frac{V_{in} - 2}{2k} + \frac{V_{in} - 2.6}{1k}$$
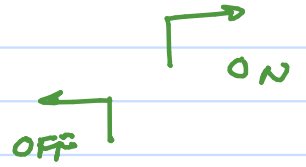
$$= \frac{V_{in}}{2k \parallel 1k} - 3.6$$




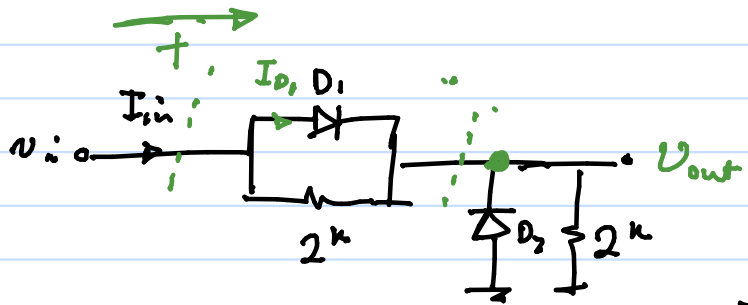




$$I_{i1} = I_{2k} = \frac{v_o}{2k} = \frac{v_{in} - 0.6}{2k}$$



$$I_{D1} = I_{i1} - \frac{0.6}{2k} > 0$$

$$I_{i1} > \frac{0.6}{2k}$$

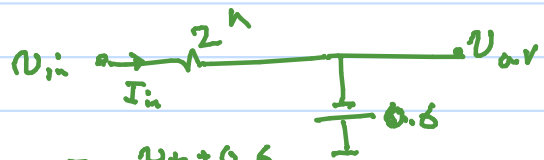

$$I_{in} = \frac{v_{in} + 0.6}{2k}$$

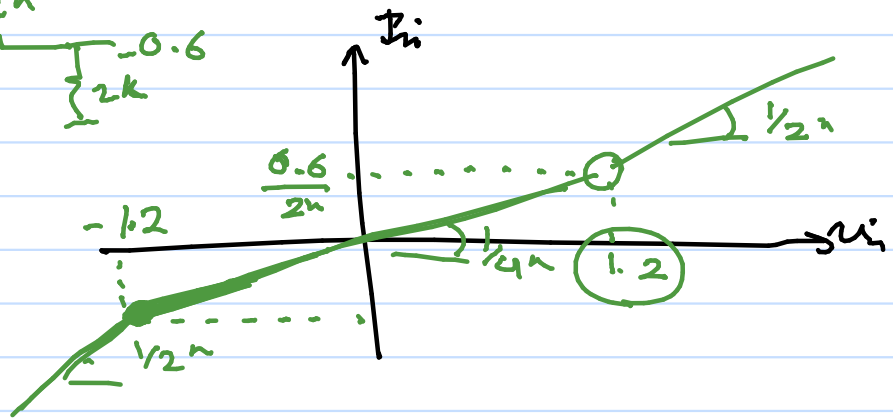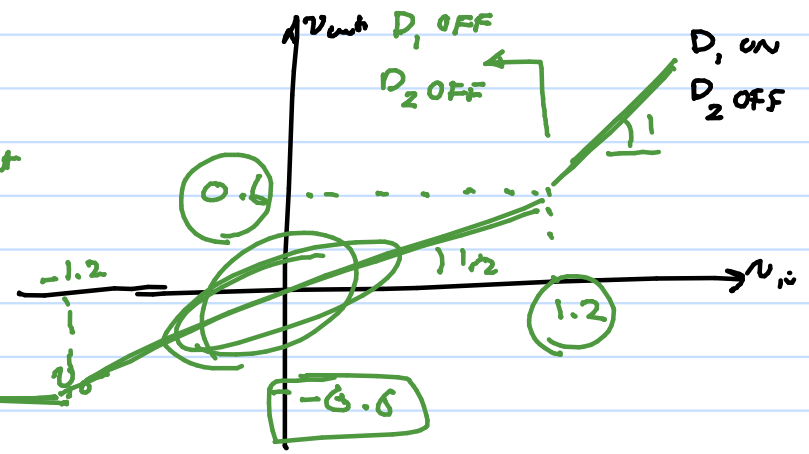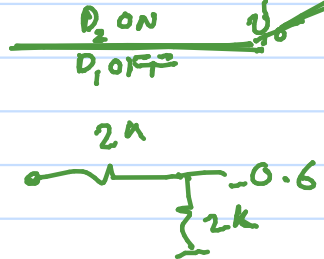

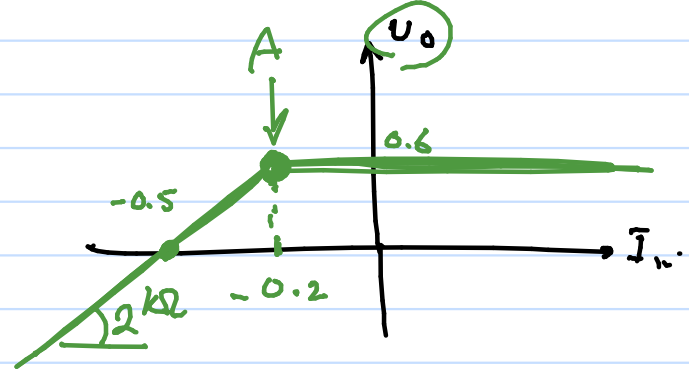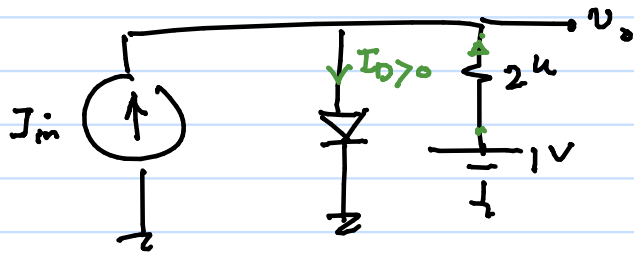

D: ON

$$v_o = 0.6$$

$$I_D = I_{in} + \frac{0.4}{2k} > 0$$

$$I_{in} > -0.2$$

D: OFF

$$v_o < 0$$

$$v_o = 1 + 2k \cdot I_{in}$$

