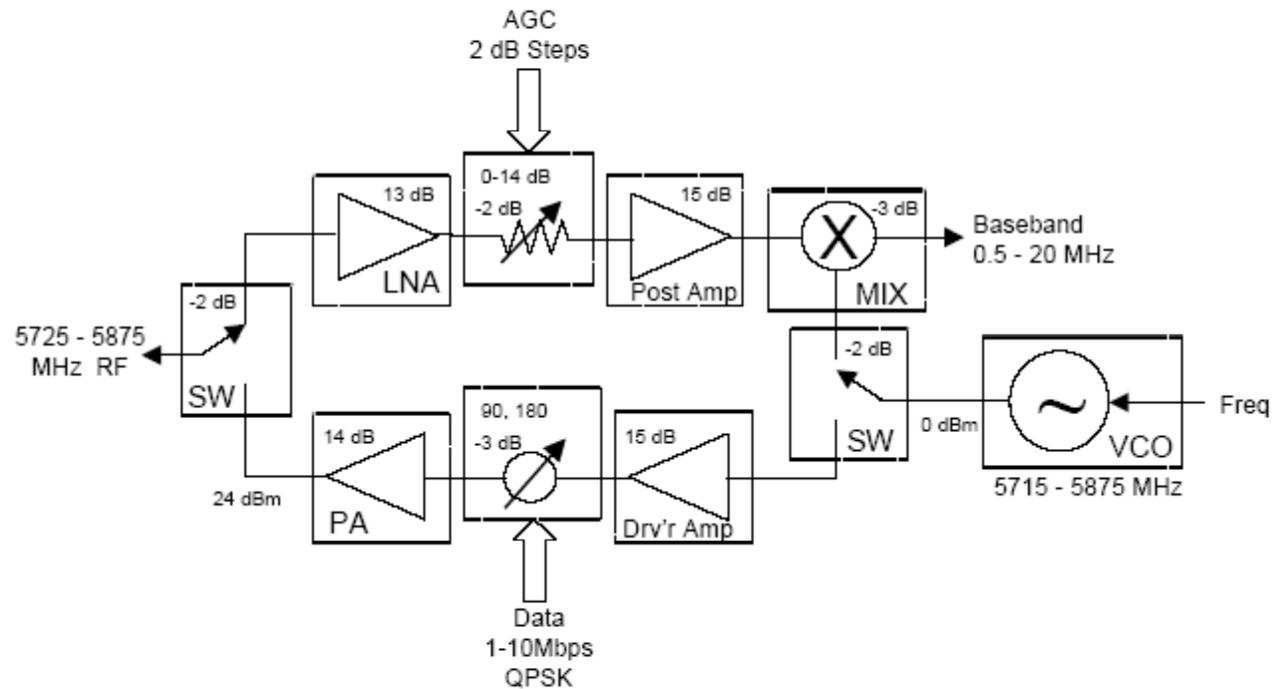


MMIC Design and Technology

Oscillator Design


Instructor Dr. Ali Medi

Transceiver Example



We now know amplifier design
And techniques for low noise amplifier design

Oscillator

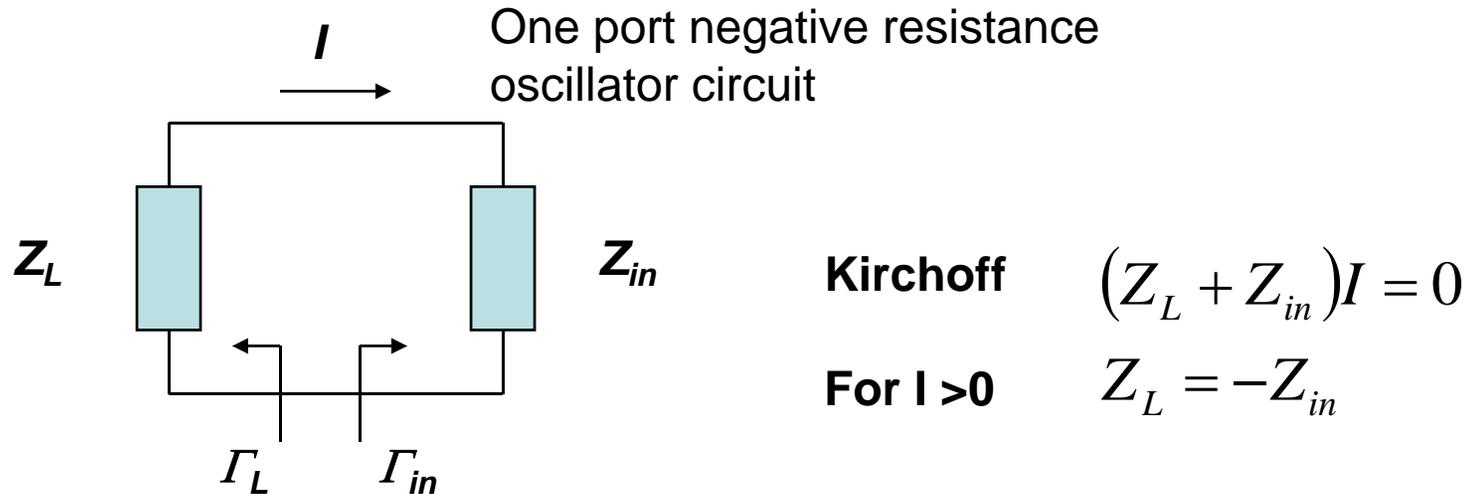

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{-Z_{in} - Z_0}{-Z_{in} + Z_0} = \frac{Z_{in} + Z_0}{Z_{in} - Z_0} = \frac{1}{\Gamma_{in}}$$

$$\Gamma_L \Gamma_{in} = 1$$

$$\Gamma_{in} > 1$$

Oscillation

$$Z_L = -Z_{in}$$

$$Z_L = R_L + jX_L \quad R_L + R_{in} = 0$$

$$Z_{in} = R_{in} + jX_{in} \quad X_L + X_{in} = 0$$

$$X_L(j\omega_0) = -X_{in}(I, j\omega_0)$$

ω_0 Is the oscillation frequency

Oscillator Stability

For stability the circuit should resist small changes in I or ω and return to its original state.


Detailed perturbation analysis results in :

$$\frac{\partial(X_L + X_{in})}{\partial\omega} \gg 0$$


High Q circuit results in maximum oscillator stability

Oscillator Design

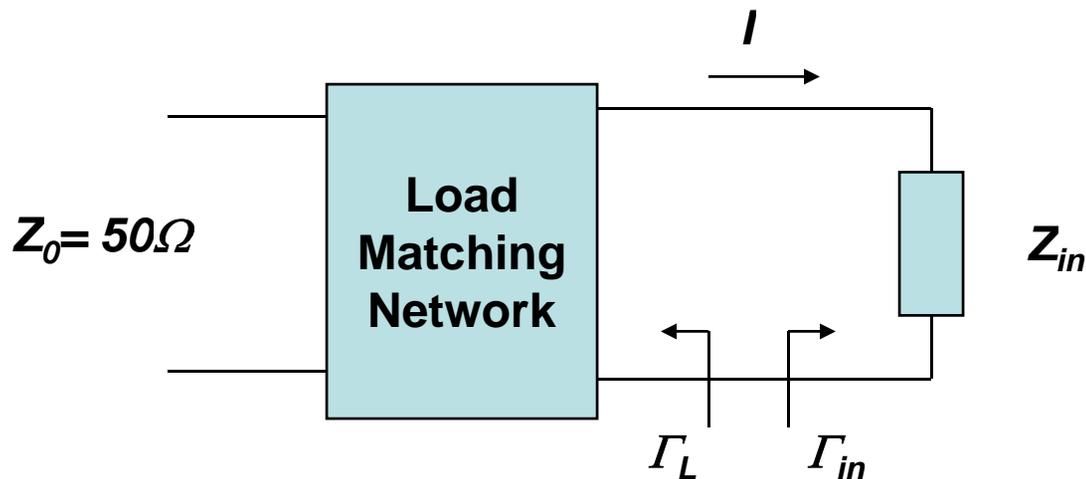- For a given Γ_{in} transform a 50 ohm output to present Γ_L to the oscillator.



Example

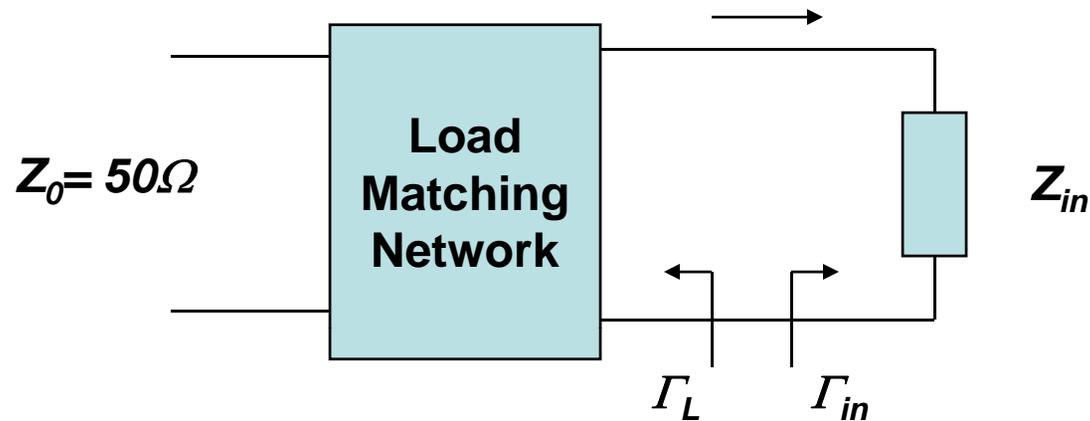

Given:

$\Gamma_{in} = 1.25 / 40$ degrees when measured at 50Ω

$$|\Gamma_{in}| > 1$$

$$\Gamma_L = \frac{1}{\Gamma_{in}} = \frac{\text{Re}[\Gamma_{in}] - j \text{Im}[\Gamma_{in}]}{|\Gamma_{in}|^2}$$


Plot on smith chart
Then transform \mathbf{Z}_0 to \mathbf{Z}_L

Calculation of example

$\Gamma_{in} = 1.25 / 40 \text{ degrees}$ when measured at 50Ω

$\Gamma_L = 1.25^{-1} / -40 \text{ degrees}$
 $= 0.8 / -40 \text{ degrees}$

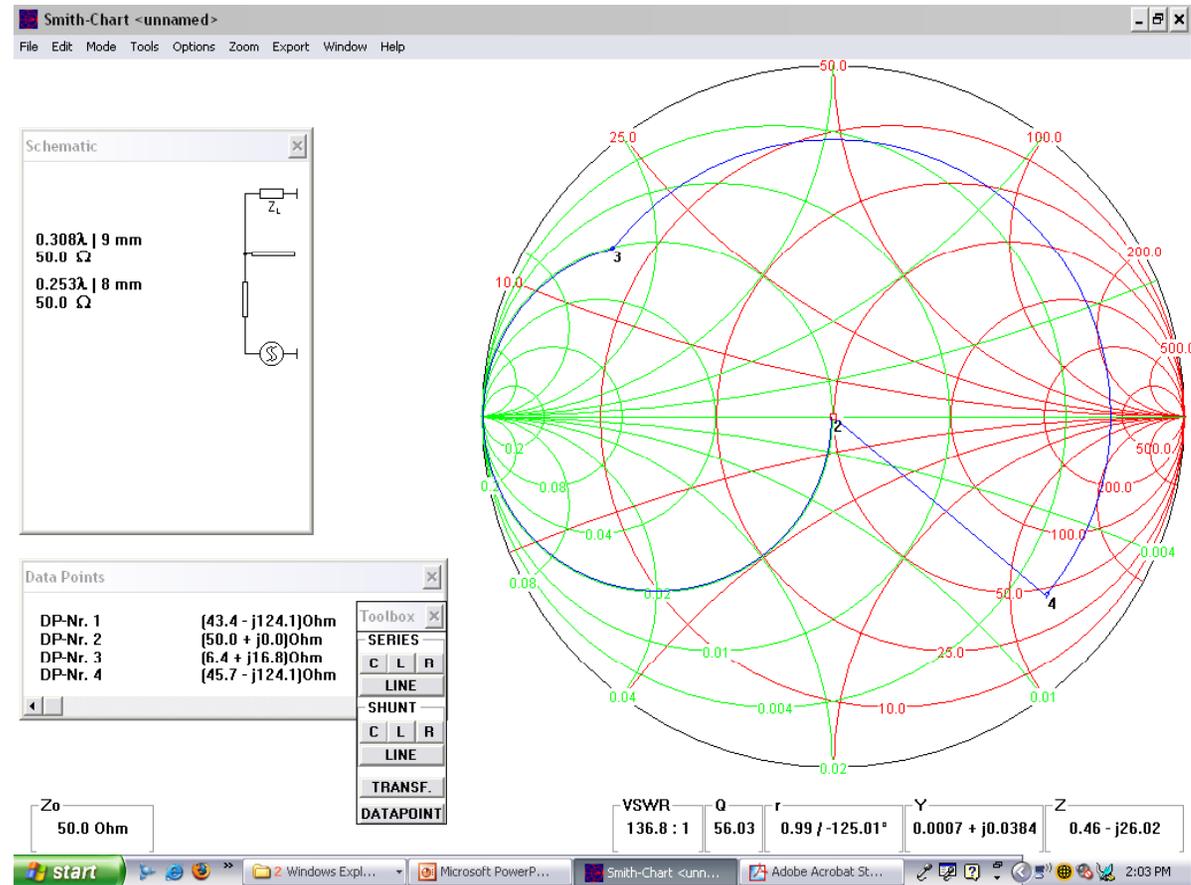
Plot on smith chart
and
transform 50Ω to give Γ_L



Oscillation Stability

- Analysis is done at small signal
- R_{in} is an increasing function of I
 - R_{in} becomes less negative as power increases
- If at small signal $R_L + R_{in} = 0$
 - When power increases $R_L + R_{in} > 0$ and oscillation will stop
- In practice choose $R_L = -R_{in} / 3$
- X_L is chosen to resonate so $X_L = -X_{in}$

Transistor Oscillators

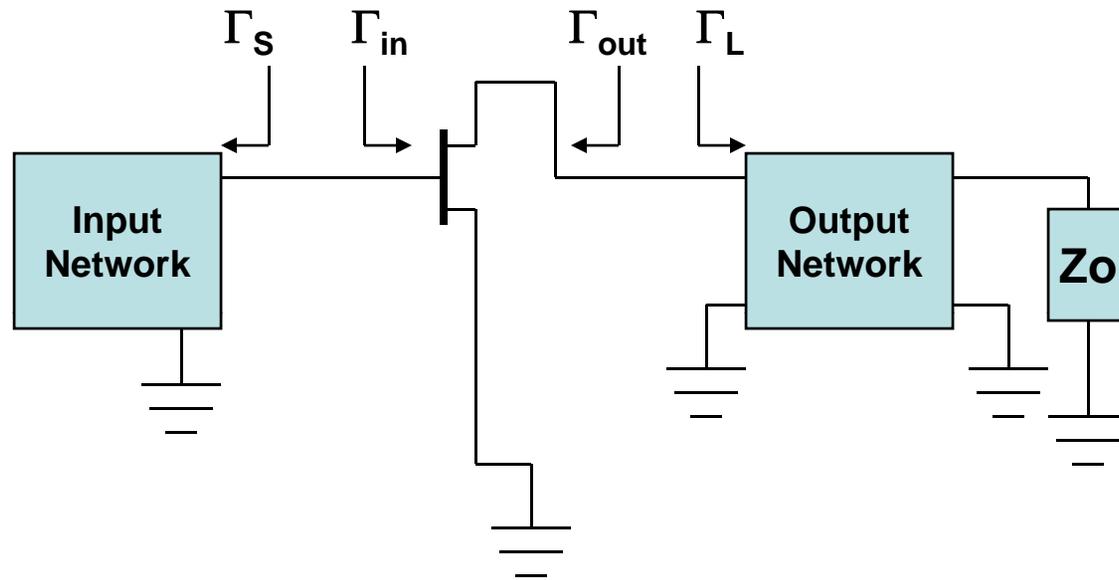

Choose Γ_L such that $\Gamma_{in} > 1$

Or


Choose Γ_s such that $\Gamma_{out} > 1$

Stability

- Transistor is unstable when $|\Gamma_{in}| > 1$

$$\Gamma_{in} = S_{11} + \frac{S_{21}S_{12}\Gamma_L}{1 - S_{22}\Gamma_L}$$

Transistor Oscillator Design

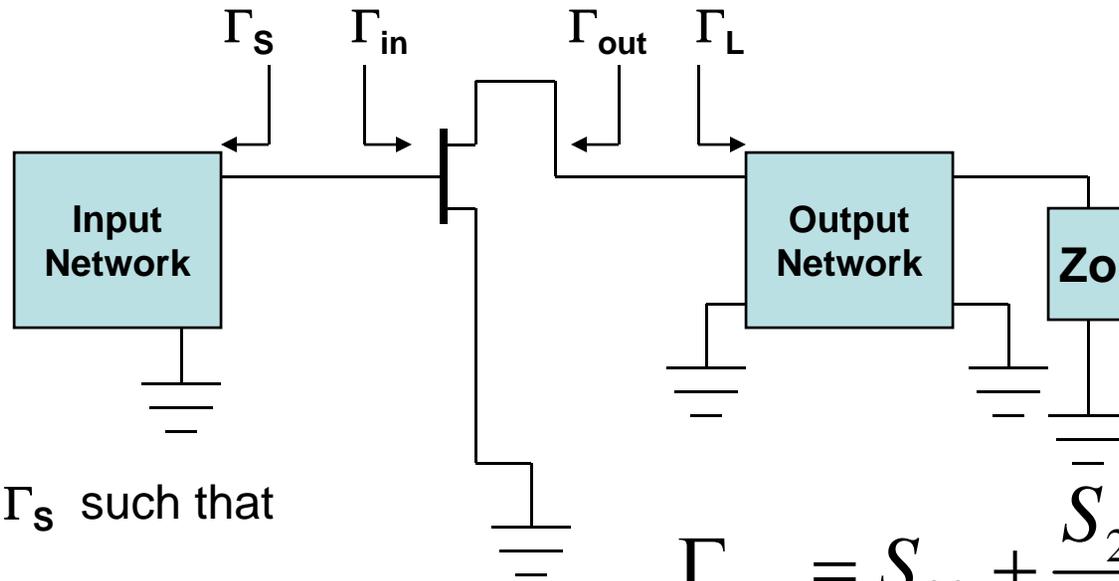

Choose Γ_s such that $\Gamma_{out} > 1$


Develop network to provide Z_s

$$\Gamma_{out} = S_{22} + \frac{S_{21}S_{12}\Gamma_s}{1 - S_{11}\Gamma_s} > 1$$

$$\Gamma_L = \frac{1}{\Gamma_{out}} = \frac{\text{Re}[\Gamma_{out}] - j \text{Im}[\Gamma_{out}]}{|\Gamma_{out}|^2}$$

Develop network to transform Z_o to Γ_L

FET Oscillator Circuits

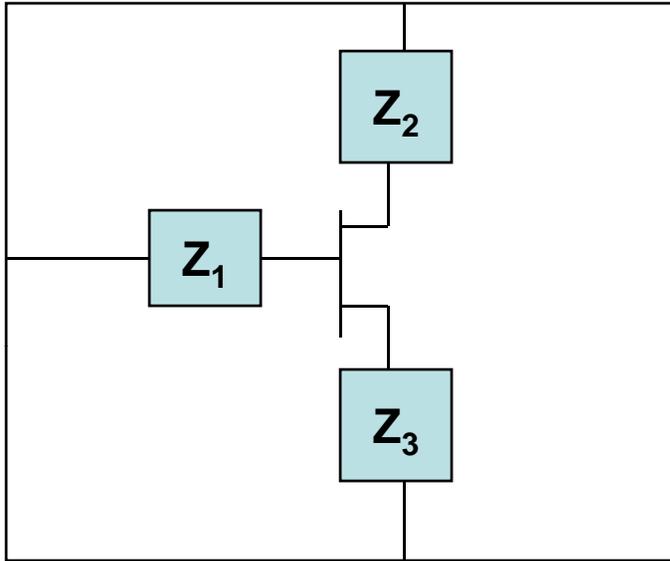

Use 3 port S parameters for the FET

3 port parameters can be developed from 2 port

Choose one of the Z_i to give a 2 port
With instability.

$$S_{ii}^T > 1$$


With $Z_1 = Z_2 = Z_0$

And

$$\Gamma_3 = \frac{Z_3 - Z_0}{Z_3 + Z_0}$$

$$[S^T] = \begin{bmatrix} S_{11} + \frac{S_{31}S_{13}\Gamma_3}{1 - S_{33}\Gamma_3} & S_{12} + \frac{S_{13}S_{32}\Gamma_3}{1 - S_{33}\Gamma_3} \\ S_{21} + \frac{S_{31}S_{23}\Gamma_3}{1 - S_{33}\Gamma_3} & S_{22} + \frac{S_{23}S_{32}\Gamma_3}{1 - S_{33}\Gamma_3} \end{bmatrix}$$


Example

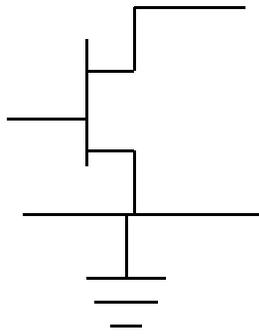

For a particular FET the Common source
 50Ω measured S parameters at 4GHz are

$$[S] = \begin{bmatrix} .72 / -116^\circ & .03 / 57^\circ \\ 2.60 / 76^\circ & .73 / -54^\circ \end{bmatrix}$$

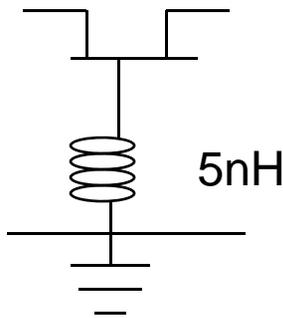The same FET in Common gate with 5nH
Has S' parameters



$$[S'] = \begin{bmatrix} 2.18 / -35^\circ & 1.26 / 18^\circ \\ 2.75 / 96^\circ & .52 / 155^\circ \end{bmatrix}$$

More unstable than Common source
 $S'_{11} > 1$ and S'_{12} is large

Example

- Design a 10GHz Oscillator using the FET data.

Example continued

$$\Gamma_{in} = S'_{11} + \frac{S'_{12} S'_{21} \Gamma_T}{1 - S'_{22} \Gamma_T}$$

Choose $\Gamma_T = 0.59 / -104\text{deg}$

$$\Gamma_{in} = 3.96 / -2.4 \text{ deg}$$

$$Z_{in} = -84 - j1.9\Omega$$

$$Z_L = \frac{-R_{in}}{3} - jX_{in} = 28 + j1.9\Omega$$

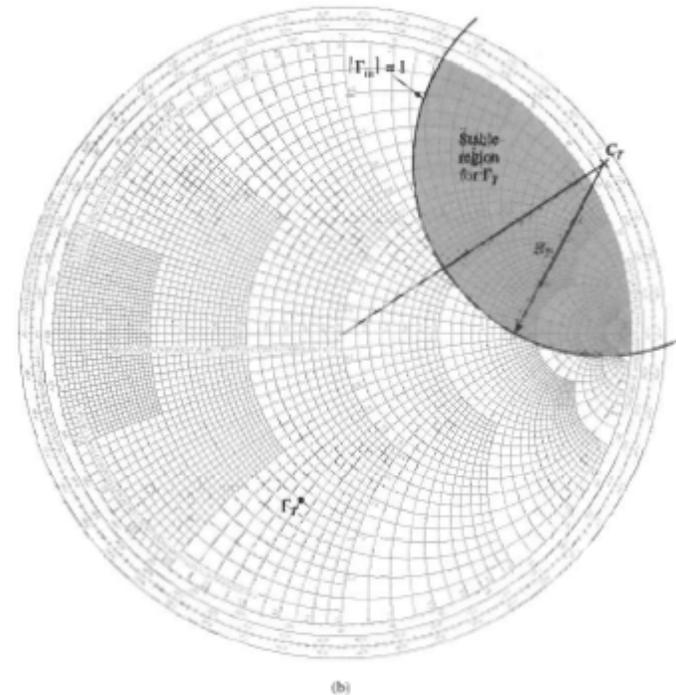
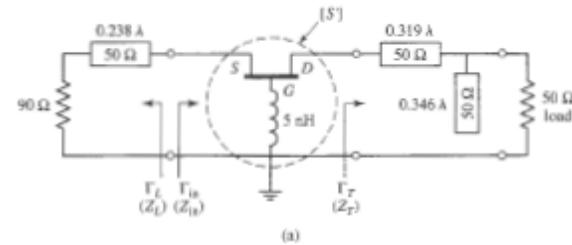


FIGURE 11.25 Circuit design for the transistor oscillator of Example 11.9. (a) Oscillator circuit. (b) Smith chart for determining Γ_T .

Tunable Oscillators

- Choice of Γ s determines Γ_{out} and therefore determines oscillation frequency
- An adjustable impedance would allow for adjusting the oscillation frequency

Voltage Controlled Oscillator

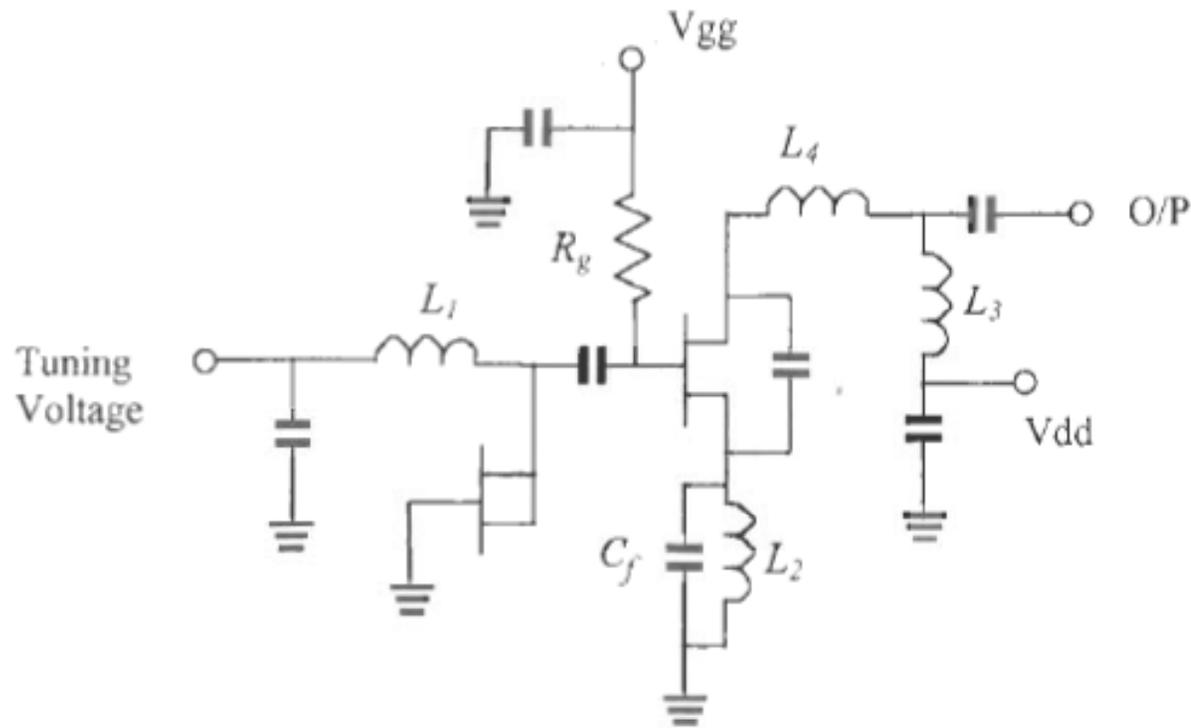


Figure 6.8 VCO circuit diagram