

# Sharif University of Technology

## Communication Circuits

### Problem set 1

Due Date: Tuesday, 25 mehr

You may submit your solutions in class or in the box.

1. Consider the 11g sliding-IF receiver shown in figure1: (the input RF range:[f1,f2]).

- Determine the required LO frequency range.
- Determine the image frequency range.
- Is this architecture preferable to that in figure 2? Why?
- Determine some of the mixing spurs in the architecture of figure 1.

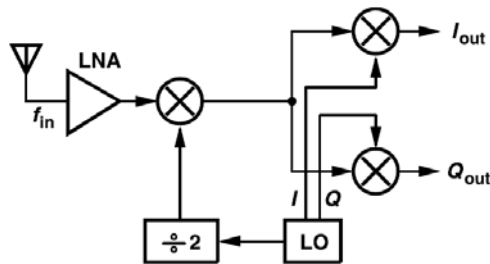


Figure 1 sliding IF receiver for 11g

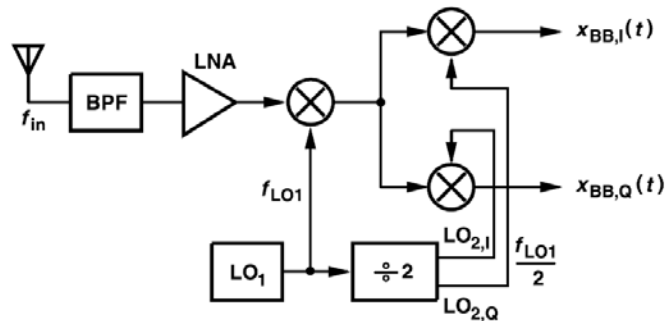


Figure 2 sliding IF heterodyne receiver

2. A 1GHz receiver with 1MHz channel spacing must tolerate an alternate adjacent channel blocker 15dB higher than desired signal. Calculate the Q of second-order LC filter required to suppress this interferer by 33dB.
3. Downconversion to what minimum intermediate frequency avoids self-corruption of asymmetric signals.
4. Calculate the input-referred gain, NF, and IIP3 of the following receiver. Assume the input LNA is matched to  $50\Omega$ , while the LNA/mixer interface is  $300\Omega$ , and the mixer load is  $1k\Omega$  differential. The filter input impedance is capacitive (high-Z), and VGA drives a  $10k\Omega//5pF$  differential load.

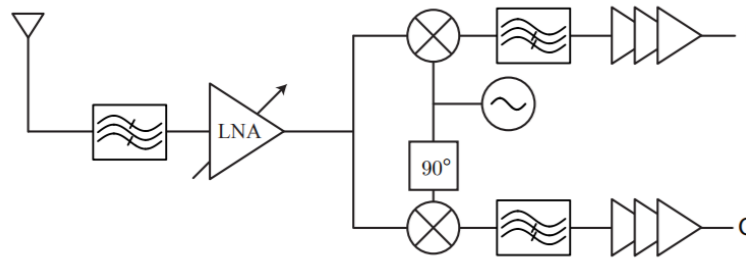


Figure 3 simple receiver

Block	Gain	NF	IIP3
RF Filter	-1dB	1dB	+100dBm
LNA	15dB	1.5dB	+0dBm
mixer	10dB	8dB	+16dBm
IF filter	-5dB	5dB	+100dBm(referred to $50\Omega$ )
VGA	+65dB	15dB	+20dBm(referred to $50\Omega$ )

Figure 4 spec for each block

Voltage Gain	91.78dB
NF	2.74dB
IIP3	-9.71dBm

Figure 5 overall performance