
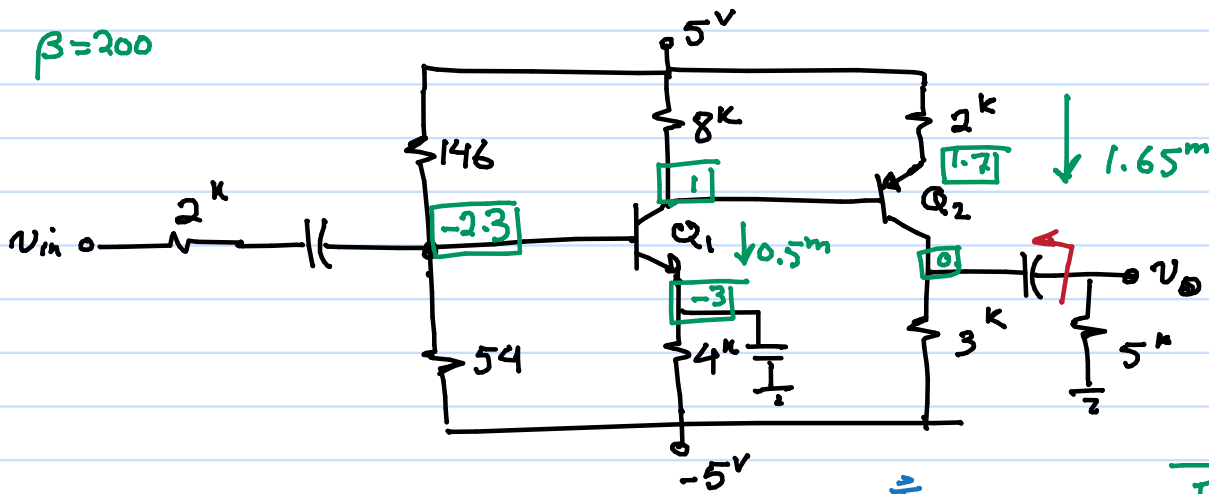


$\beta = 200$

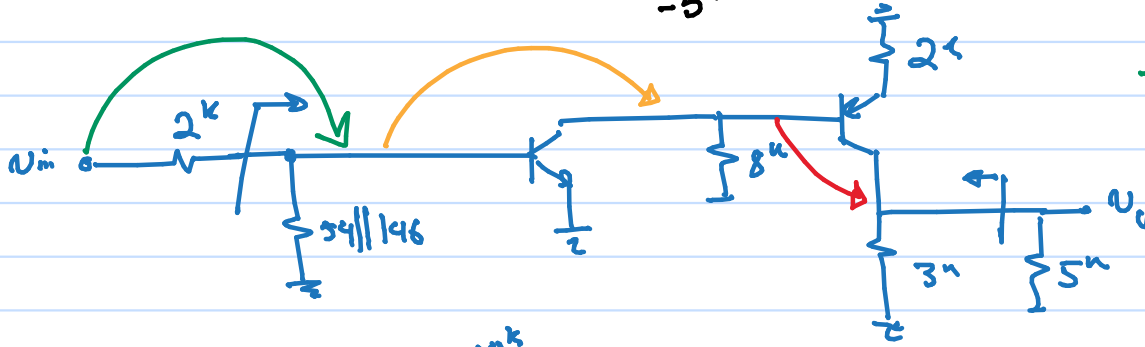

	Q_1	Q_2
I_C mA	0.5	1.65
V_{CE} V	4	-1.75




$$R_{i1} = 54 \parallel 146 \parallel r_{m1} = 8^k$$

$$R_{out} = 3^k \parallel \infty = 3^k$$

$$\begin{cases} g_{m1} = 20^m \\ g_{m2} = 66^m \\ r_{m1} = 0^i \\ r_{m2} = 3^i \end{cases}$$

$$\frac{v_o}{v_{in}} = \underbrace{\frac{R_{in}}{R_{in} + 2^k}}_{\frac{8}{10}} \times \left(-g_{m1} \times \left(8^k \parallel \left(r_{m2} + 200 \times 2^k \right) \right) \right) \times \underbrace{\frac{-3^k \parallel 5^k}{2^k + r_{m2}}}_{-\frac{15}{16}} = 120$$

4320

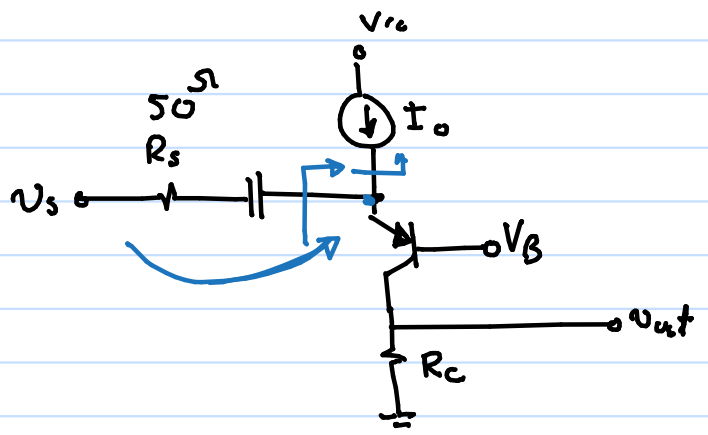





$$r_m = 50 = \frac{V_T}{I_0} \rightarrow I_0 = \frac{25\text{m}}{50} = 0.5\text{m}$$

$$A_v = \frac{1}{2} \times g_m R_c = \frac{R_c}{2r_m} = \frac{10^4}{100} = 100$$



$$R_c = 10^4$$

$$R_{in} = r_m \parallel \infty =$$

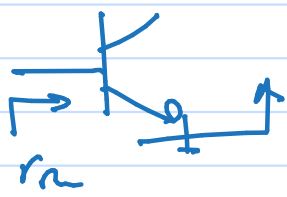

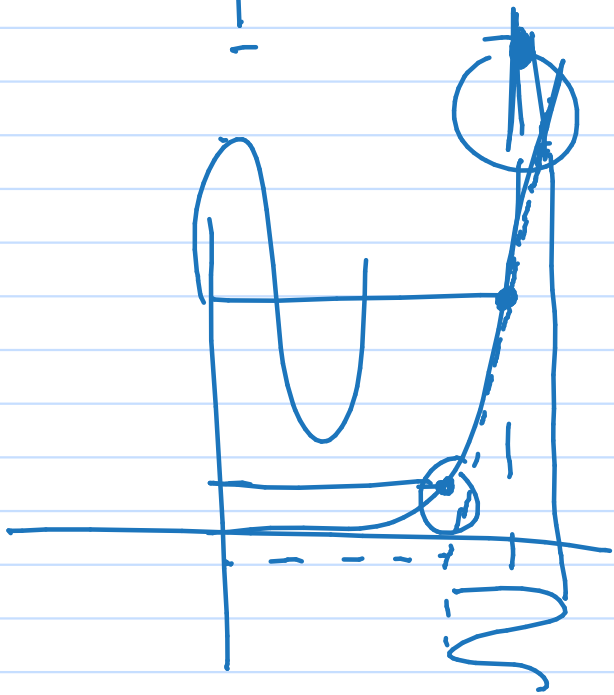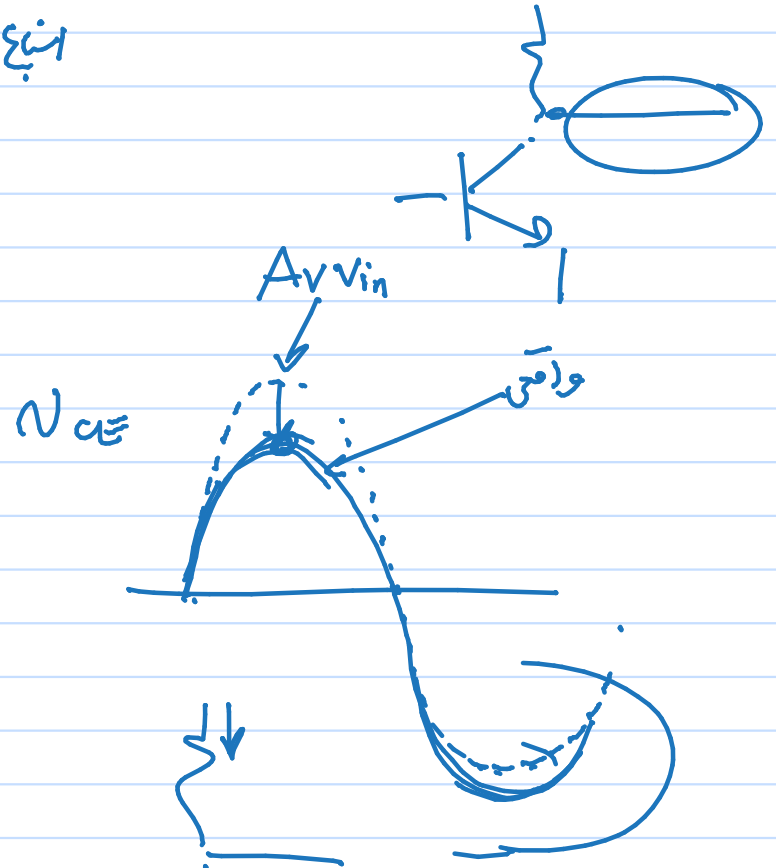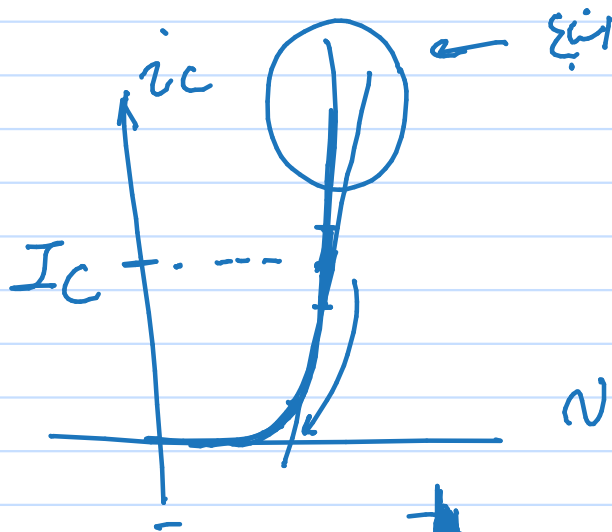

$$\frac{g_m R_c}{g_m(I_C) R_c} = A_v$$

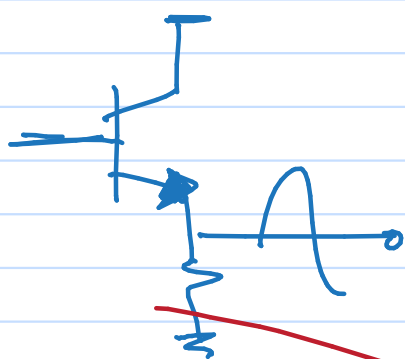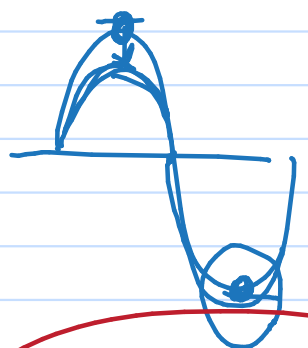

$$\frac{R_E}{R_E + r_m(I_C)} \approx 1$$

