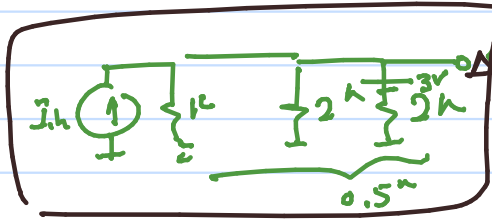


$-3 < V_{out} < 3$

$V_{out} = \frac{2}{3} I_{in}$



~~$3 < V_{out} < 4$~~




$V_{out} = 0.5 I_{in}$
 $V_{out} = 0.5 I_{in} + 3$



$V_{out} = 4$

$V_{out} = 4V$

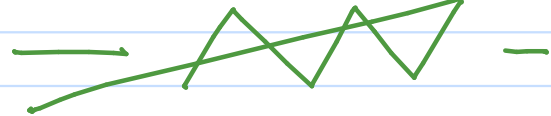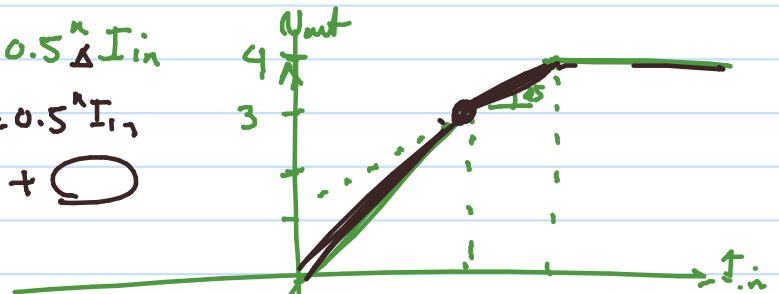

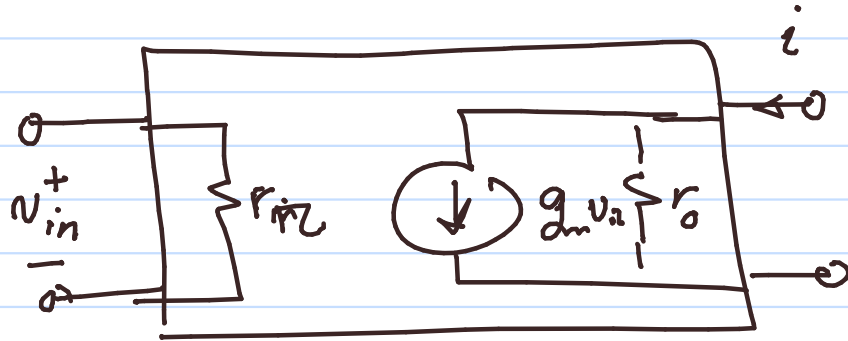


npn	pnp
V_{BE}	V_{EB}
V_{CE}	V_{EC}

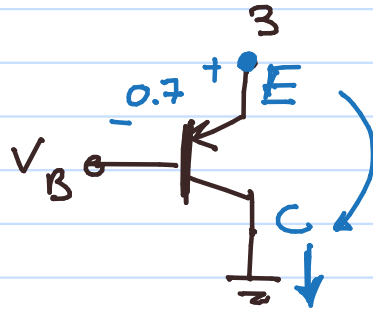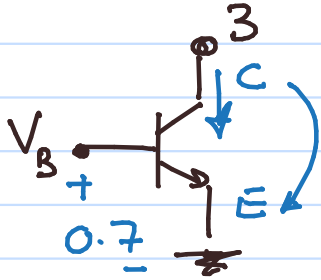

$$I_c = I_s e^{\frac{V_{BE}}{V_T}} \left(1 + \frac{V_{CE}}{V_A} \right)$$




$$I_c = \dots \frac{V_{EB}}{V_{EC}}$$

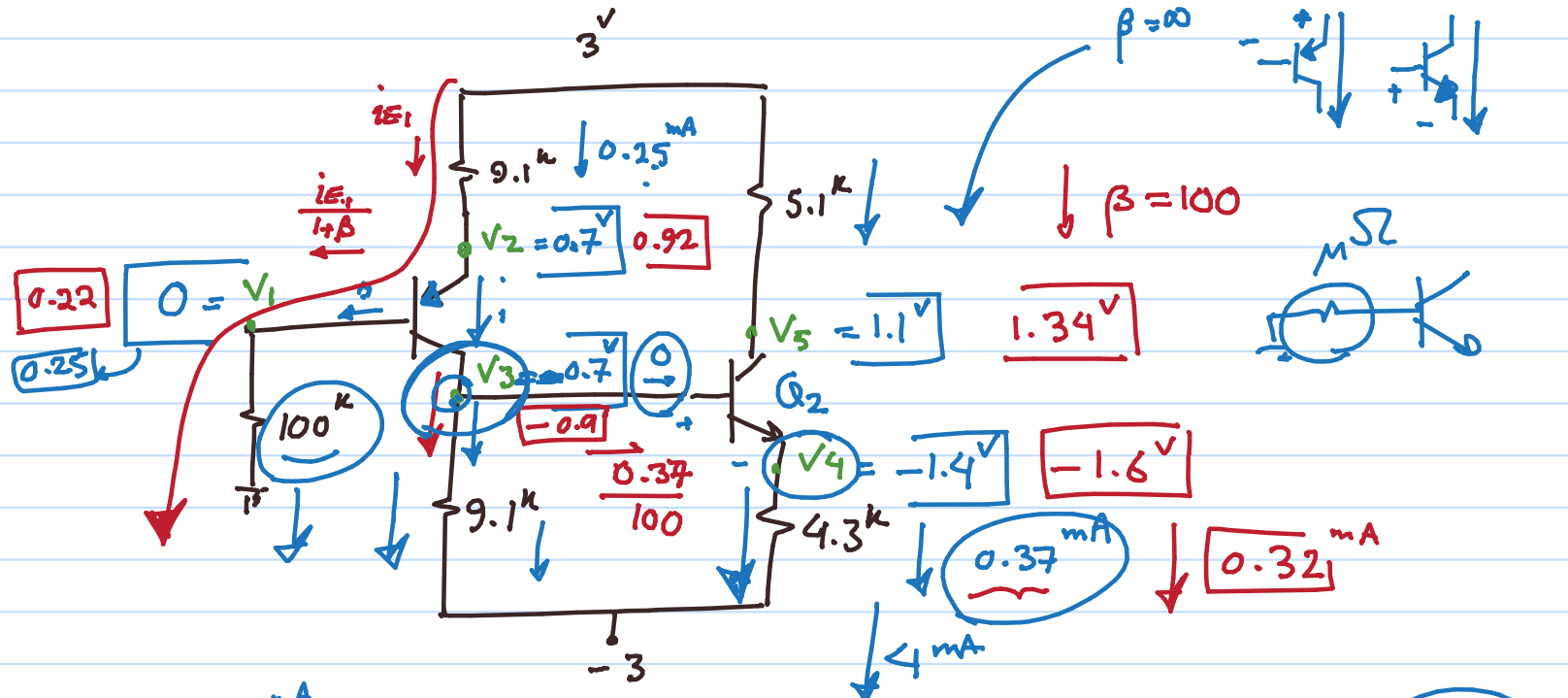

0.22
 $0 = V_1$
 $0.25k$

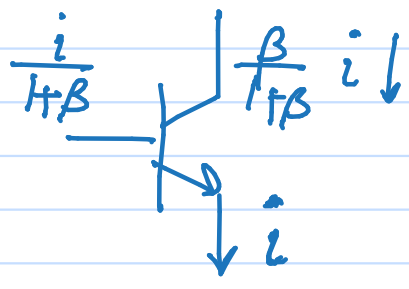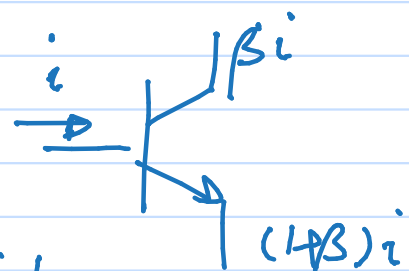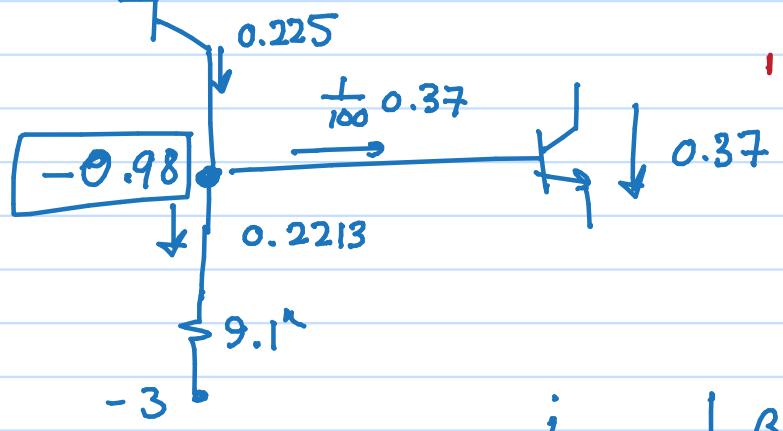
0.25 mA
 $\frac{1}{100} 0.25 \times 100k = V_1$

$i_{E1} = \frac{2.3}{9.1k + \frac{100k}{101}} = 0.228 \text{ mA}$



$$I_C = \alpha I_B^2$$

$$I_C = I_S e^{V_{BE}/V_T}$$

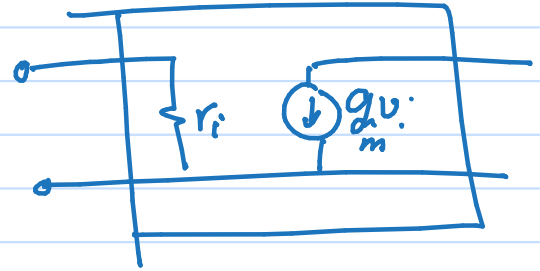

$$g_m \triangleq \frac{\Delta I_{out}}{\Delta V_{in}} = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_C}{V_T}$$


$$r_i \triangleq \frac{\Delta V_{in}}{\Delta I_{in}} = \frac{\partial V_{BE}}{\partial I_B} = \left(\frac{\partial I_B}{\partial V_{BE}} \right)^{-1}$$

$$= \left(\frac{\partial I_C}{\partial V_{BE}} \times \frac{\partial I_B}{\partial I_C} \right)^{-1}$$



$$= \frac{2\alpha}{I_C} \sqrt{\frac{I_C}{\alpha}} V_T$$

$$I_C = \alpha I_B^2$$
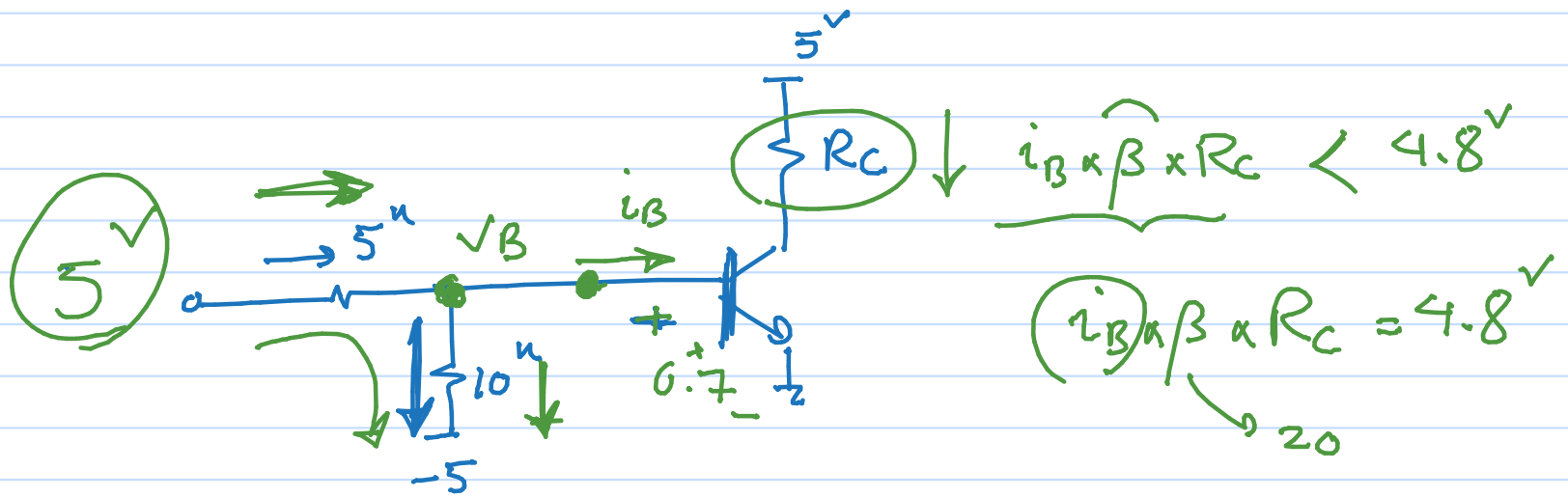
$$\frac{\partial I_C}{\partial I_B} = 2\alpha I_B =$$


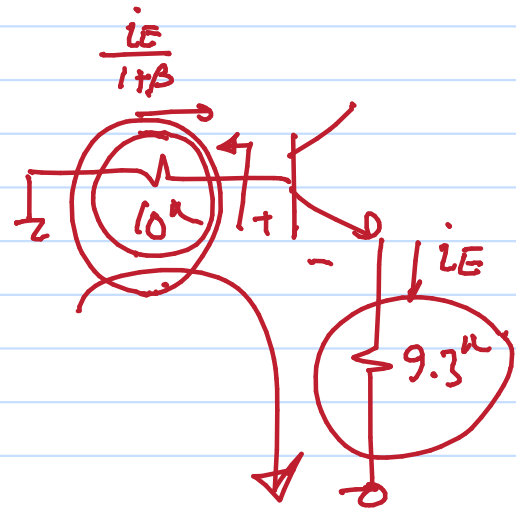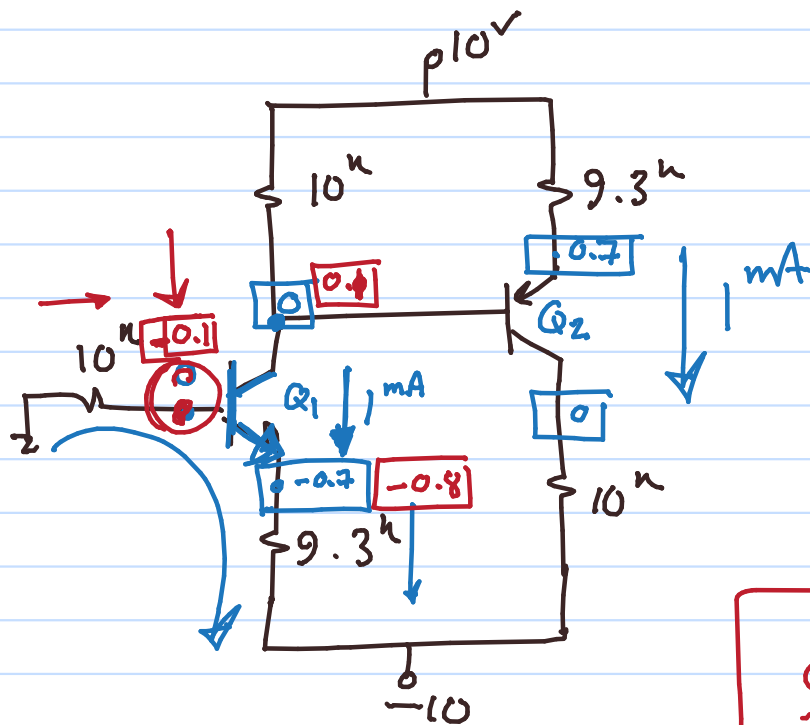
$$i_B = \frac{5 - 0.7}{5k} = \frac{0.7 + 5}{10k} =$$



$$9.3^V = i_E \left(9.3k + \frac{10k}{1+\beta} \right)$$

$$9.3^V \Rightarrow \frac{10k}{1+\beta}$$