

Session 3: Analog Circuits

Ideal Amplifiers
voltage/current/power
amplification
non-ideal amplifiers
biasing
types of amplifiers

1

Outline

1. Lab	□□□□
2. Power	□□□□
3. Ser/Parl	□□□□□□□□
4. Small sig.	□□□□□□□□□□
5. Applic	□□□□□□□□

◎ Amplifier

2

Amplifier

1. Lab

2. Power

3. Ser/Parl

4. Small sig.

5. Applic

Audio Amplifier:

Output voltage of a sensor → Amplifier → Process

↓

2-port Network

3

Amplifier

1. Lab

2. Power

3. Ser/Parl

4. Small sig.

5. Applic

Ideal amplifier

$A_v = 10 = 20dB$

$A_v = 100 = 40dB$

$A_v = 1 = 0dB$

$A_v = \frac{1}{\sqrt{2}} = -3dB$

$A_p = \frac{1}{2} = -3dB$

$v_{out} = A_v v_{in}$

$A_p \triangleq \frac{P_{out}}{P_{in}} \rightarrow 10 \log_{10} A_p \text{ in dB}$

$A_v \triangleq \frac{v_{out}}{v_{in}} \rightarrow 20 \log_{10} A_v \text{ in dB}$

$A_i \triangleq \frac{i_{out}}{i_{in}} \rightarrow 20 \log_{10} A_i \text{ in dB}$


Note: There is a difference between Amplifier and Transformer

? Where is the source of this extra power?

4

Amplifier - Efficiency

1. Lab	□□□□
2. Power	□□□□
3. Ser/Parl	□□□□□□□□
4. Small sig.	□□□□□□□□
5. Applic	□□□□□□□□

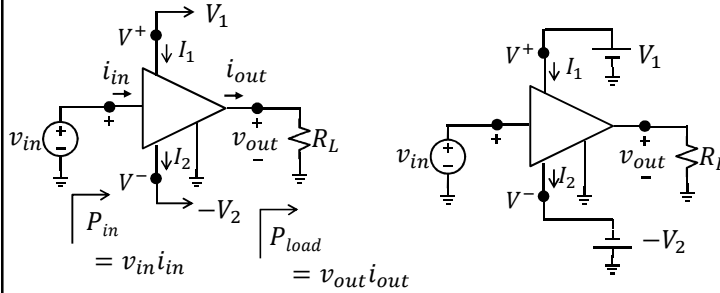

$$P_{dc} = P_{supply} = V^+ I_1 - V^- I_2 = V_1 I_1 + V_2 I_2$$

Conservation of energy:

$$P_{in} + P_{dc} = P_{load} + P_{dissipated}$$


$$\eta \equiv \frac{P_{load}}{P_{dc}} \quad \text{Efficiency}$$

$$= \frac{P_{load}}{P_{dc}} \times 100\%$$

5

Efficiency : Example

1. Lab	□□□□
2. Power	□□□□
3. Ser/Parl	□□□□□□□□
4. Small sig.	□□□□□□□□
5. Applic	□□□□□□□□

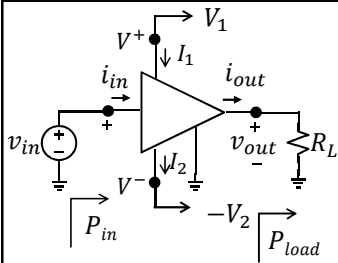

$$\begin{cases} V_{1,2} = \pm 10V \\ I_1 = 9.5mA & I_2 = 9.5mA \\ v_{in} = 1^V \sin \omega t & v_{out} = 9^V \sin \omega t \\ i_{in} = 0.1mA \sin \omega t & R_L = 1^k\Omega \end{cases}$$

$$A_v = 9 = 19.1^{dB}$$

$$i_{out} = \frac{v_{out}}{R_L} = 9mA \sin \omega t \quad A_i = \frac{i_{out}}{i_{in}} = 90 = 39.1^{dB}$$

$$P_{load} = v_{orms} i_{orms} = \frac{9 \times 9m}{\sqrt{2}\sqrt{2}} = 40.5^{mW}$$

$$P_{in} = v_{irms} i_{irms} = \frac{1 \times 0.1m}{\sqrt{2}\sqrt{2}} = 0.05^{mW}$$

$$P_{dc} = 10 \times 9.5 \times 2 = 0.05^{mW}$$

$$P_{diss} = P_{dc} + P_{in} - P_{load} = 149.6^{mW}$$

$$A_p = 810 = 29.1^{dB}$$

$$\eta = \frac{P_{load}}{P_{dc}} \times 100\% = 21.3\%$$

6

Non-ideal Amplifier

1. Lab	▢▢▢▢
2. Power	▢▢▢▢
3. Ser/Parl	▢▢▢▢▢▢▢▢
4. Small sig.	▢▢▢▢▢▢▢▢▢▢
5. Applic	▢▢▢▢▢▢▢▢

rail-to-rail OpAmp $L^\pm = V^\pm$

$L^- < v_{out} < L^+ \xrightarrow{v_{out} = A_v v_{in}} \left(\frac{L^-}{A_v} < v_{in} < \frac{L^+}{A_v} \right)$

You have heard distortion in Audio amplifier!

7

Nonlinear Transfer Function Biasing

1. Lab	▢▢▢▢
2. Power	▢▢▢▢
3. Ser/Parl	▢▢▢▢▢▢▢▢
4. Small sig.	▢▢▢▢▢▢▢▢▢▢
5. Applic	▢▢▢▢▢▢▢▢

$A_v = \frac{\Delta v_o}{\Delta v_i} = \left. \frac{dv_o}{dv_i} \right|_Q \rightarrow$ bias point

8

Nonlinear Transfer Function Biasing

1. Lab	▢▢▢▢
2. Power	▢▢▢▢
3. Ser/Parl	▢▢▢▢▢▢▢▢
4. Small sig.	▢▢▢▢▢▢▢▢▢▢
5. Applic	▢▢▢▢▢▢▢▢

$V_I = 0 \rightarrow A_v = 0$
 $V_I = V_1 \rightarrow A_v = A_1$
 $V_I = V_2 \rightarrow A_v = 0$

$v_{IN} = V_I + v_i(t)$
 $v_{OUT} = V_O + A_v v_i(t)$

$V_1 = V_{CC} \frac{R_1}{R_1 + R_2}$
 $v_{out}(t) = V_{out} + A_v \hat{v}_{in}(t)$

9

Voltage Amplifier

1. Lab	▢▢▢▢
2. Power	▢▢▢▢
3. Ser/Parl	▢▢▢▢▢▢▢▢
4. Small sig.	▢▢▢▢▢▢▢▢▢▢
5. Applic	▢▢▢▢▢▢▢▢

Open circuit: $R_L = \infty \rightarrow \frac{V_{out}}{V_{in}} = A_{VO} \left[\frac{V}{V} \right]$ open circuit voltage gain

$V_{in} = \frac{R_{in}}{R_{in} + R_s} \cdot V_s$ $V_{in} = V_s \quad \forall R_s$ if $R_{in} = \infty$ Ideal case

$V_{out} = A_{VO} V_{in} \frac{R_L}{R_L + R_{out}}$ $V_{out} = A_{VO} V_{in} \quad \forall R_L$ if $R_{out} = 0$ Ideal case


Generally: $\frac{V_{out}}{V_s} = A_{VO} \left(\frac{R_L}{R_L + R_{out}} \right) \left(\frac{R_{in}}{R_{in} + R_s} \right)$

Ideal case: $\frac{V_{out}}{V_s} = A_{VO}$

10

Current Amplifier

1. Lab	□□□□
2. Power	□□□□
3. Ser/Parl	□□□□□□□□
4. Small sig.	□□□□□□□□
5. Applic	□□□□□□□□

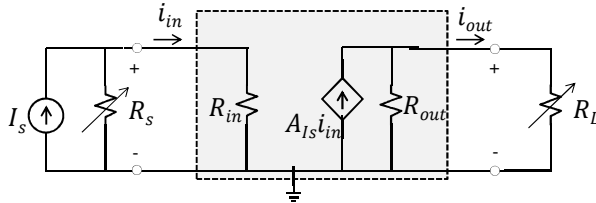

Short circuit: $R_L = 0 \rightarrow \frac{i_{out}}{i_{in}} = A_{I_s} \left[\frac{A}{A} \right]$ short circuit current gain

$$i_{in} = \frac{R_s}{R_{in} + R_s} \cdot I_s \quad i_{in} = I_s \quad \forall R_s \quad \text{if } R_{in} = 0 \quad \text{Ideal case}$$

$$i_{out} = A_{I_s} i_{in} \frac{R_{out}}{R_L + R_{out}} \quad i_{out} = A_{I_s} i_{in} \quad \forall R_L \quad \text{if } R_{out} = \infty \quad \text{Ideal case}$$


$$\text{Generally: } \frac{i_{out}}{I_s} = A_{I_s} \left(\frac{R_{out}}{R_L + R_{out}} \right) \left(\frac{R_s}{R_{in} + R_s} \right)$$

$$\text{Ideal case: } \frac{i_{out}}{I_s} = A_{I_s}$$

11

Trance-Conductance Amplifier

1. Lab	□□□□
2. Power	□□□□
3. Ser/Parl	□□□□□□□□
4. Small sig.	□□□□□□□□
5. Applic	□□□□□□□□

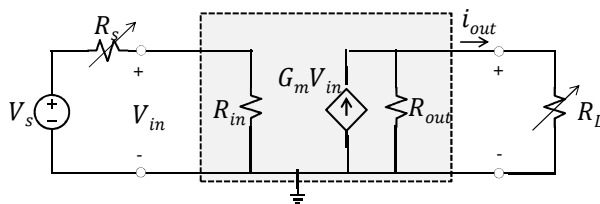

Short circuit: $R_L = 0 \rightarrow \frac{i_{out}}{V_{in}} = G_m \left[\frac{A}{V} = \Omega^{-1} \right]$ short circuit Trance-conductance

$$V_{in} = \frac{R_{in}}{R_{in} + R_s} \cdot V_s \quad V_{in} = V_s \quad \forall R_s \quad \text{if } R_{in} = \infty \quad \text{Ideal case}$$

$$i_{out} = G_m V_{in} \frac{R_{out}}{R_L + R_{out}} \quad i_{out} = G_m V_{in} \quad \forall R_L \quad \text{if } R_{out} = \infty \quad \text{Ideal case}$$


$$\text{Generally: } \frac{i_{out}}{V_s} = G_m \left(\frac{R_{out}}{R_L + R_{out}} \right) \left(\frac{R_{in}}{R_{in} + R_s} \right)$$

$$\text{Ideal case: } \frac{i_{out}}{V_s} = G_m$$

12

Trance-Resistance Amplifier

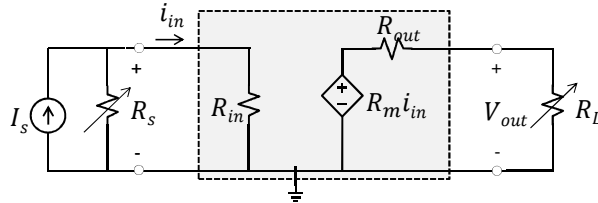- 1. Lab
- 2. Power
- 3. Ser/Parl
- 4. Small sig.
- 5. Applic



Short circuit: $R_L = \infty \rightarrow \frac{V_{out}}{i_{in}} = R_m \quad \left[\frac{V}{A} = \Omega \right]$ open circuit Trans-resistance

$$i_{in} = \frac{R_s}{R_{in} + R_s} \cdot I_s \quad i_{in} = I_s \quad \forall R_s \quad \text{if } R_{in} = 0 \quad \text{Ideal case}$$

$$V_{out} = R_m i_{in} \frac{R_L}{R_L + R_{out}} \quad V_{out} = R_m i_{in} \quad \forall R_L \quad \text{if } R_{out} = 0 \quad \text{Ideal case}$$

Generally:
$$\frac{V_{out}}{I_s} = R_m \left(\frac{R_L}{R_L + R_{out}} \right) \left(\frac{R_s}{R_{in} + R_s} \right)$$


Ideal case:
$$\frac{V_{out}}{I_s} = R_m$$

13

Amplifiers

- 1. Lab
- 2. Power
- 3. Ser/Parl
- 4. Small sig.
- 5. Applic

Voltage Amplifier

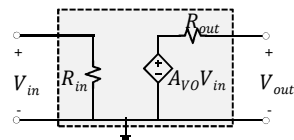


$$A_{vo} = \frac{V_{out}}{V_{in}} \Big|_{i_{out}=0}$$

open circuit voltage gain

Ideal:
 $R_{in} = \infty$
 $R_{out} = 0$

Current Amplifier

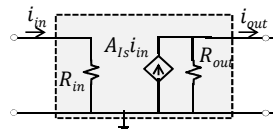


$$A_{is} = \frac{i_{out}}{i_{in}} \Big|_{v_{out}=0}$$

short circuit current gain

Ideal:
 $R_{in} = 0$
 $R_{out} = \infty$

Trance-Conductance Amplifier

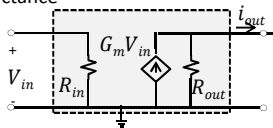


$$G_m = \frac{i_{out}}{V_{in}} \Big|_{v_{out}=0}$$

short circuit Trans-conductance

Ideal:
 $R_{in} = \infty$
 $R_{out} = \infty$

Trance-Resistance Amplifier

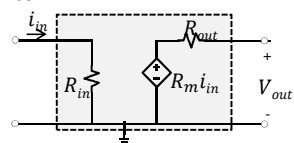

$$R_m = \frac{V_{out}}{i_{in}} \Big|_{i_{out}=0}$$

open circuit Trans-resistance

Ideal:
 $R_{in} = 0$
 $R_{out} = 0$

14

Practical Consideration

1. Lab	▢▢▢▢
2. Power	▢▢▢▢
3. Ser/Parl	▢▢▢▢▢▢▢▢
4. Small sig.	▢▢▢▢▢▢▢▢▢▢
5. Applic	▢▢▢▢▢▢▢▢

15

Practical Consideration: Input / Output Resistance

1. Lab	▢▢▢▢
2. Power	▢▢▢▢
3. Ser/Parl	▢▢▢▢▢▢▢▢
4. Small sig.	▢▢▢▢▢▢▢▢▢▢
5. Applic	▢▢▢▢▢▢▢▢



$R_S = 1k\Omega \rightarrow \frac{V_1}{V_2} = \frac{R_{in}}{R_{in} + 1k}$
 $R_{in} = 1k \times \frac{1}{\frac{V_2}{V_1} - 1}$

Point: You need to make sure circuit is in its linear operation regime

16

Amplifier Frequency Response

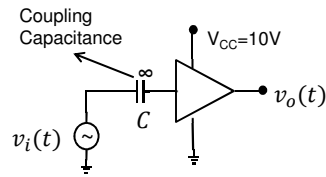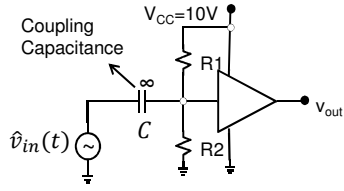- 1. Lab
- 2. Power
- 3. Ser/Parl
- 4. Small sig.
- 5. Applic



$$v_i(t) = V_i \sin \omega t \quad v_o(t) = V_o \sin(\omega t + \varphi)$$

Transfer Function: $T(\omega) = \frac{v_o}{v_i}$

$$|T(\omega)| = \frac{V_o}{V_i}$$

Amplitude in dB

$$\angle T(\omega) = \varphi$$

Phase

